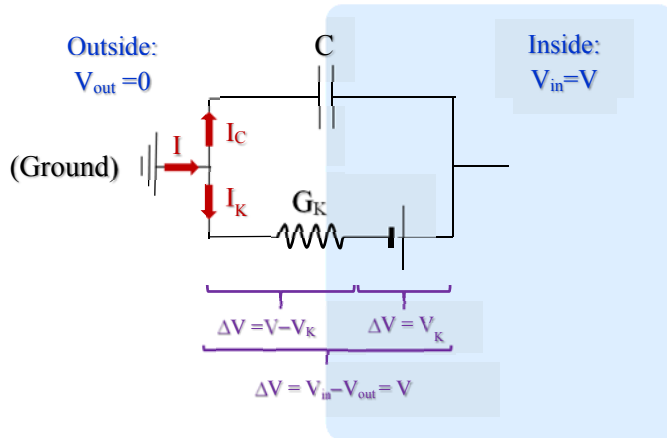


Equivalent circuit of a “passive” cell

Let's assume only K<sup>+</sup> channels are present:



Kirchhoff law:

total applied current (from outside to inside) = sum of currents through two branches of the circuit

$$I_C + I_K = I$$

$$\Rightarrow I = C \frac{dV}{dt} + G_K (V - V_K) \Rightarrow \boxed{C \frac{dV}{dt} = I - G_K (V - V_K)}$$

Here  $V_K = \frac{RT}{zF} \ln \frac{[K^+]_{out}}{[K^+]_{in}} = \frac{k_B T}{q} \ln \frac{[K^+]_{out}}{[K^+]_{in}}$  is the potassium reversal potential (Nernst potential)

• **NOTE:  $V_K < 0$ , since a very negative potential is required to force K<sup>+</sup> ions to move into the cell against their concentration gradient.** See proof of this expression in another file...

We can easily generalize to two different channel types are present, K<sup>+</sup> and Cl<sup>-</sup>:

$$I_C + I_K + I_{Cl} = I$$

$$\Rightarrow I = C \frac{dV}{dt} + G_K (V - V_K) + G_{Cl} (V - V_{Cl}) \Rightarrow \boxed{C \frac{dV}{dt} = I - G_K (V - V_K) - G_{Cl} (V - V_{Cl})}$$

Let's who that the two (or any number) of ionic currents can be combined into a single term:

$$\begin{aligned}
C \frac{dV}{dt} &= I - G_K (V - V_K) - G_{Cl} (V - V_{Cl}) \\
&= I - (G_K + G_{Cl})V + G_K V_K + G_{Cl} V_{Cl} \\
&= I - (G_K + G_{Cl}) \left( V - \frac{G_K V_K + G_{Cl} V_{Cl}}{G_K + G_{Cl}} \right) \\
&= I - G_L (V - V_R)
\end{aligned}$$

Where we introduce two quantities:

$$\left\{ \begin{array}{l}
\bullet \text{ Total "leak" / "input" conductance: } \boxed{G_L = G_K + G_{Cl}} \\
\bullet \text{ "Resting" / "equilibrium" potential: } \boxed{V_R = \frac{G_K V_K + G_{Cl} V_{Cl}}{G_K + G_{Cl}}} \\
= \text{average of reversal potentials weighted by their conductances}
\end{array} \right.$$

We may perform another simplification:

$$\begin{aligned}
C \frac{dV}{dt} &= I - G_L (V - V_R) \\
&= -G_L \left( V - V_R - \frac{I}{G_L} \right) \quad \text{Now let's denote } \frac{1}{G_L} = R_L \quad (\text{"Input resistance"}) \\
&= -G_L (V - (V_R + R_L I)) \\
&= -G_L (V - V_{RI}) \quad \text{where equilibrium potential in non-zero current is } V_{RI} = V_R + R_L I
\end{aligned}$$

Finally, we can divide both sides of the equation by C, and note that  $G_L / C = 1 / (R_L C) = 1 / \tau_m$

$$\frac{dV}{dt} = - \frac{V - V_{RI}}{\tau_m}$$

Denoting the deviation from equilibrium as  $v = V - V_{RI}$ , and noting that  $dv = dV$ , we obtain:

$$\begin{aligned}
\frac{dv}{dt} &= - \frac{v}{\tau_m} \Rightarrow \boxed{v(t) = v_o e^{-t/\tau_m}} \Rightarrow V(t) - V_{RI} = (V_o - V_{RI}) e^{-t/\tau_m} \\
&\Rightarrow \boxed{V(t) = V_{RI} + (V_o - V_{RI}) e^{-t/\tau_m}} \quad \text{potential decays exponentially to } V_{RI} \text{ with characteristic time } \tau_m
\end{aligned}$$