

ECE 232 - Circuits and Systems II
Midterm

Please provide clear and complete answers. Don't forget to specify the units of measure!

Q1. (1 point) Consider the parallel of a resistor with $R = 1k\Omega$ and a capacitor with $C = 1\mu F$, and denote as $v(t)$ the voltage at the common terminals of resistor and capacitor. Can we have $v(t) = \sin(10^{-3}t)$ [V] for $t \geq 0$? Justify your answer.

Sol.: No, since the current in the resistor, $i_R(t)$, and capacitor, $i_C(t)$, must satisfy the Kirchoff current law:

$$i_R(t) = -i_C(t),$$

but also the relationships for resistor and capacitor:

$$\begin{aligned} i_R(t) &= \frac{v(t)}{R} = 10^{-3} \sin(10^{-3}t) \text{ A} \\ \text{and } i_C(t) &= C \frac{dv}{dt} = 10^{-9} \cos(10^{-3}t) \text{ A}. \end{aligned}$$

These conditions are incompatible!

Q2. (1 point) Calculate the Laplace transform of

$$f(t) = e^{-10(t-0.03)} \cos(100t - 3)u(t - 0.03),$$

starting from the Laplace transform $\mathcal{L}\{\cos(\omega t)\} = \frac{s}{s^2 + \omega^2}$ and using the properties of the Laplace transform. (Hint: Recall the translation in time and frequency properties...)

Sol.: We can write

$$\begin{aligned} f(t) &= e^{-10(t-0.03)} \cos\left(100\left(t - \frac{3}{100}\right)\right) u(t - 0.03) \\ &= e^{-10(t-0.03)} \cos(100(t - 0.03)) u(t - 0.03). \end{aligned}$$

Using the translation in the frequency domain property, we get

$$\mathcal{L}\{e^{-10t} \cos(100t)u(t)\} = \frac{s + 10}{(s + 10)^2 + 10^4},$$

then, using the translation in time domain property, we get

$$\begin{aligned} &\mathcal{L}\{e^{-10(t-0.03)} \cos(100(t - 0.03)) u(t - 0.03)\} \\ &= \frac{s + 10}{(s + 10)^2 + 10^4} e^{-0.03s}. \end{aligned}$$

P1. (4 points) Consider the circuit in figure 1. It is known that $v_C(0^-) = 10$ V. Moreover, the switch has been in position a for a long time before moving to position b at time $t = 2$ ms.

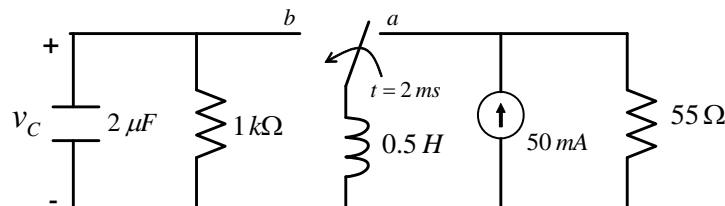


Figure 1:

- 1.a) Calculate $v_C(t)$ for $0 \leq t \leq 2 \text{ ms}$ (i.e., before the switch moves to position b).
 1.b) Calculate $v_C(t)$ for $t \geq 2 \text{ ms}$.

Sol.: 1.a) For $0 \leq t \leq 2 \text{ ms}$, we can concentrate on the RC circuit on the left, with $R = 1 \text{ k}\Omega$ and $C = 2 \mu\text{F}$. This has time constant

$$\tau = RC = 2 \text{ ms},$$

so that we have

$$v_C(t) = v_C(0^-)e^{-t/\tau} = 10e^{-500t}$$

for $0 \leq t \leq 2 \text{ ms}$.

1.b) For $t \geq 2 \text{ ms}$ we can concentrate on the RLC circuit on the left with $R = 1 \text{ k}\Omega$, $C = 2 \mu\text{F}$ and $L = 0.5 \text{ H}$, which is characterized by

$$\alpha = \frac{1}{2RC} = 250 \text{ rad/s}$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = 1000 \text{ rad/s}$$

Moreover, the initial conditions are $v_C(2 \times 10^{-3}) = 10e^{-1} = 3.67 \text{ V}$ and $i_L(2 \times 10^{-3}) = 50 \text{ mA}$. The latter fact follows from the analysis of the right part of the circuit for $t < 2 \text{ ms}$. The circuit operates in the underdamped regime ($\omega_0 > \alpha$) and the solution is given by

$$v_C(t) = B_1 e^{-250(t-2 \times 10^{-3})} \cos(968.2(t-2 \times 10^{-3}))$$

$$+ B_2 e^{-250(t-2 \times 10^{-3})} \sin(968.2(t-2 \times 10^{-3}))$$

with damped frequency given by

$$\omega_d = \sqrt{\omega_0^2 - \alpha^2} = 968.2 \text{ rad/s}.$$

Imposing the initial conditions, we get:

$$B_1 = 3.67$$

$$-250B_1 + 968.2B_2 = -\frac{1}{C} \left(\frac{v_C(2 \times 10^{-3})}{R} + i_L(2 \times 10^{-3}) \right)$$

$$= -\frac{1}{2 \times 10^{-6}} (3.67 \times 10^{-3} + 50 \times 10^{-3})$$

$$\rightarrow B_2 = \frac{1}{968.2} (250 \times 3.67 - 26.8 \times 10^3)$$

$$= -26.7,$$

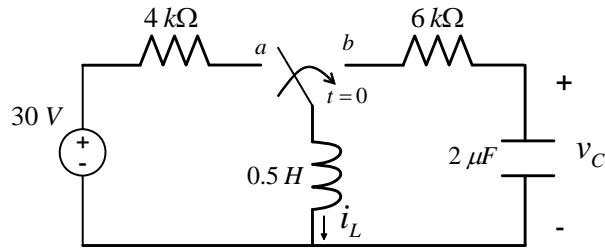


Figure 2:

so that

$$v_C(t) = 3.67e^{-250(t-2 \times 10^{-3})} \cos(968.2(t - 2 \times 10^{-3})) - 26.7e^{-250(t-2 \times 10^{-3})} \sin(968.2(t - 2 \times 10^{-3})).$$

P2. (4 points) Consider the circuit in figure 2. The switch has been in position *a* for a long time before it moves to position *b* at time $t = 0$. The energy stored in the capacitor at time $t = 0^-$ is zero.

2.a) Find initial current $i_L(0^-)$ and construct an equivalent circuit in the s -domain for $t > 0$ (use whatever representation you find more convenient for both inductor and capacitor in the s -domain).

2.b) Find $I_L(s)$ and $V_C(s)$ (Express all coefficients in numerical form).

2.c) Calculate poles and zeros of $I_L(s)$ and $V_C(s)$.

2.d) Now substitute the capacitor with a short circuit. Everything else remains the same. Find $I_L(s)$ and the time-domain current $i_L(t)$ for $t \geq 0$. What is the time constant of the circuit?

Sol.:

2.a) We have

$$i_L(0^-) = \frac{30}{4 \times 10^3} = 7.5 \text{ mA}$$

and

$$v_C(0^-) = 0 \text{ V},$$

since the circuit is in steady-state for $t = 0^-$.

An equivalent circuit in the s -domain is shown in figure 3 using the series equivalent for the inductor (the capacitor has zero initial conditions). Notice that the voltage source is $Li_L(0^-) = 0.5 \times 7.5 \times 10^{-3} = 3.75 \times 10^{-3} \text{ [V} \times \text{sec]}$.

2.b) Using the representation above for the circuit, we find

$$\begin{aligned} I_L(s) &= \frac{3.75 \times 10^{-3}}{0.5s + 6 \times 10^3 + \frac{1}{2s}10^6} \\ &= \frac{7.5 \times 10^{-3}s}{s^2 + 12 \times 10^3s + 10^6} \end{aligned}$$

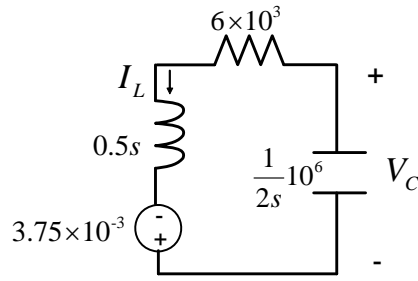


Figure 3:

and

$$\begin{aligned} V_C(s) &= -\frac{1}{2s} 10^6 \times I_L(s) \\ &= -\frac{3.75 \times 10^3}{s^2 + 12 \times 10^3 s + 10^6}. \end{aligned}$$

2.c) $I_L(s)$ has a zero in $s = 0$, unlike $V_C(s)$ that has no zeros. The poles are the same for both $I_L(s)$ and $V_C(s)$, and given by

$$\begin{aligned} s_1 &= -83.9 \\ s_2 &= -11,916 \end{aligned}$$

Notice that these are the roots of the characteristic polynomial of the RLC circuit at hand, namely

$$\begin{aligned} s_1 &= -\alpha + \sqrt{\alpha^2 - \omega_0^2} = -83.9 \\ s_2 &= -\alpha - \sqrt{\alpha^2 - \omega_0^2} = -11,916 \end{aligned}$$

where $\alpha = \frac{R}{2L} = 6 \times 10^3$ and $\omega_0 = \frac{1}{\sqrt{LC}} = 1000$.

d) If there is no capacitor, the circuit for $t \geq 0$ is RL and we have from figure 3

$$\begin{aligned} I_L(s) &= \frac{3.75 \times 10^{-3}}{0.5s + 6 \times 10^3} = \\ &= \frac{7.5 \times 10^{-3}}{s + 12 \times 10^3}, \end{aligned}$$

which leads to

$$i_L(t) = 7.5e^{-12000t} \text{ for } t \geq 0.$$

The time constant of the circuit is

$$\tau = \frac{L}{R} = \frac{1}{12000} = 0.08 \text{ ms.}$$