

**ECE 232 - Circuits and Systems II**  
**Test 3**

Please provide clear and complete answers. Don't forget to specify the units of measure!

1. Consider the circuit in Fig. 1-(a).
  - 1.a. Find the impulse response  $h(t)$ .
  - 1.b. Find the output voltage  $v_O(t)$  when the input is  $v_I(t)$  as shown in Fig. 1(b) (and the capacitor has zero energy at time  $t = 0^-$ ). To do so, evaluate the convolution integral  $v_O(t) = v_I(t) * h(t)$ .
  - 1.c. Sketch the result.

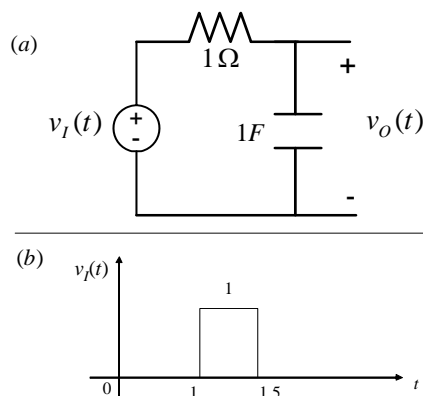


Figure 1:

*Sol.:* 1.a. The transfer function is

$$H(s) = \frac{1/s}{1 + 1/s} = \frac{1}{s + 1},$$

so that the impulse response is

$$h(t) = e^{-t}u(t).$$

1.b. The input  $v_I(t)$  can be written as

$$v_I(t) = \text{rect}(t - 1),$$

where  $\text{rect}(t)$  is a rectangle between 0 and 0.5 with height 1. In other words,  $v_I(t)$  is a regular rectangle of duration 0.5 delayed by 1. The output  $v_O(t)$  can thus be obtained by calculating the convolution

$$\text{rect}(t) * h(t)$$

and then delaying the result by 1 by time-invariance<sup>1</sup>.

The convolution  $\text{rect}(t) * h(t)$  is given by:

---

<sup>1</sup>You can also evaluate directly the convolution  $v_I(t) * h(t)$  but this approach is easier.

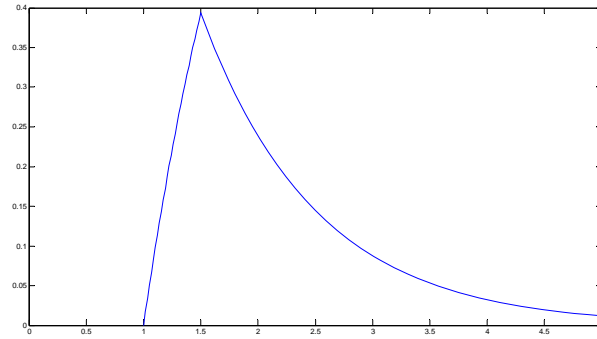


Figure 2:

- If  $t \leq 0$ ,  $rect(t) * h(t) = 0$ ;

- If  $0 \leq t \leq 0.5$

$$rect(t) * h(t) = \int_0^t e^{-\tau} d\tau = 1 - e^{-t};$$

- If  $t \geq 0.5$

$$\begin{aligned} rect(t) * h(t) &= \int_{t-0.5}^t e^{-\tau} d\tau = e^{-(t-0.5)} - e^{-t} \\ &= e^{-t}(e^{0.5} - 1). \end{aligned}$$

We thus obtain  $v_O(t)$  as

- If  $t \leq 1$

$$v_O(t) = 0;$$

- If  $1 \leq t \leq 1.5$

$$v_O(t) = 1 - e^{-(t-1)};$$

- If  $t \geq 1.5$

$$v_O(t) = e^{-(t-1)}(e^{0.5} - 1).$$

The result is shown in the figure below.

2. Add a resistor with resistance equal to  $1\Omega$  in parallel to the capacitor in the circuit of Fig. 1-(a).

2.a. What type of filter do you obtain? What is the cut-off frequency and the maximum amplitude response of this filter?

2.b. (Extra) Calculate and plot the amplitude and phase responses.

*Sol.*: 2.a. The transfer function is

$$\begin{aligned} H(s) &= \frac{(1||1/s)}{1 + (1||1/s)} \\ &= \frac{\frac{1/s}{1+1/s}}{1 + \frac{1/s}{1+1/s}} \\ &= \frac{1}{s + 2}. \end{aligned}$$

This is a low-pass filter with cut-off frequency  $\omega_c = 2$ . In fact, it can be written as

$$H(s) = \frac{1}{2} \cdot \frac{2}{s + 2},$$

where  $\frac{2}{s+2}$  is the standard transfer function of an RC low-pass filter with cut-off frequency  $\omega_c = 2$ . The maximum amplitude response of the low-pass filter is obtained for zero frequency and is given by  $1/2$ . Notice that the presence of the load resistor has modified both the cut-off frequency and the maximum amplitude response as compared to the original filter in Fig. 1-(a).

2.b. We obtain

$$\begin{aligned} |H(j\omega)| &= \frac{1}{\sqrt{4 + \omega^2}} \\ \theta(j\omega) &= -\angle(2 + j\omega). \end{aligned}$$