

ECE 232 - Circuits and Systems II
Final

Please provide clear and complete answers. Don't forget to specify the units of measure!

1. (2 points) a. Calculate the convolution between $x(t) = e^{-3(t-1)}u(t-1)$ and a rectangle $h(t) = 0.5(u(t) - u(t-3))$.

b. Sketch the resulting function.

Sol.: We calculate the convolution between $x(t) = e^{-3t}u(t)$ and $h(t) = 0.5(u(t) - u(t-3))$. We will then delay the obtained function by 1 s. Using the usual procedure, we get the output

$$y(t) = \frac{1}{6}(1 - e^{-3t}) \text{ for } 0 \leq t \leq 3,$$

$$y(t) = \frac{1}{6}e^{-3t}(e^9 - 1) \text{ for } t \geq 3$$

and $y(t) = 0$ otherwise. After delaying by 1 s, we get

$$y(t) = \frac{1}{6}(1 - e^{-3(t-1)}) \text{ for } 1 \leq t \leq 4,$$

$$y(t) = \frac{1}{6}e^{-3(t-1)}(e^9 - 1) \text{ for } t \geq 4$$


and $y(t) = 0$ otherwise.

2. (2 points) a. Draw the amplitude Bode plot for the transfer function (*Specify clearly the relevant values on the two axes*)

$$H(s) = \frac{s}{(s + 100)(s + 2000)}.$$

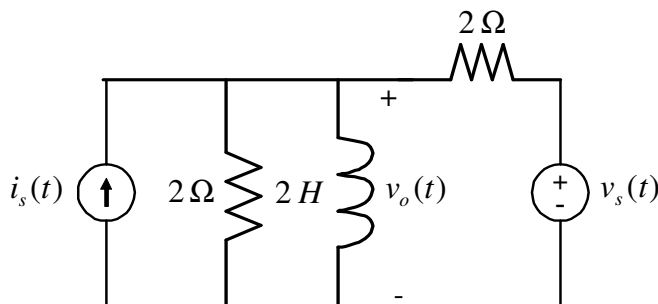b. What type of filter is it?

Sol.: Please see the textbook on how to draw the Bode plot. It is a band-pass filter.



3. (4 points) Consider the circuit in the figure on the left. The current source $i_s(t)$ has Laplace transform $I_s(s)$ and the voltage source $v_s(t)$ has Laplace transform $V_s(s)$. Assume that the initial energy in the inductor is zero.

a. Calculate the Laplace transform $V_o(s)$ of the voltage $v_o(t)$ as a function of the Laplace transforms $I_s(s)$ and $V_s(s)$.

- b. If $v_s(t) = 3 \cos(2t + \pi/2)u(t)$ and $i_s(t) = 0$, find the voltage $v_o(t)$ in steady state.
 c. Consider the transfer function $H(s)$ between $V_s(s)$ and $V_o(s)$. What type of filter is it? Find H_{\max} and the 3dB cut-off frequency ω_c .
 d. If $v_s(t) = 3 \cos(2t + \pi/2)u(t)$ and $i_s(t) = 0$, find the voltage $v_o(t)$ for all $t \geq 0$ (i.e., not only in steady state). Compare with your result at point b.

Sol.: a. Using the superposition principle, we get

$$\begin{aligned} V_o(s) &= I_s(s)(1||s) + V_s(s)\frac{2||2s}{2+2||2s} \\ &= I_s(s)\frac{s}{1+s} + V_s(s)\frac{s}{1+2s}. \end{aligned}$$

- b. The transfer function $H(s)$ between $V_s(s)$ and $V_o(s)$ is

$$H(s) = \frac{s}{1+2s}.$$

Therefore, we get

$$v_o(t) = 3|H(j2)| \cos(2t + \pi/2 + \theta(j2))u(t),$$

and, since

$$\begin{aligned} H(j2) &= \frac{j2}{1+j4} \\ &= 0.485e^{j0.245}, \end{aligned}$$

we can calculate

$$\begin{aligned} v_o(t) &= 1.455 \cos(2t + \pi/2 + 0.245)u(t) \\ &= 1.455 \cos(2t + 0.578\pi)u(t). \end{aligned}$$

- c. We can write $H(s) = \frac{1}{2} \frac{s}{s+1/2}$. It is a high-pass filter with $H_{\max} = 1/2$ and 3-dB cut-off frequency $\omega_c = 1/2$.

- d. We have


$$\begin{aligned} V_o(s) &= \frac{s}{1+2s} \frac{3s \cos(\pi/2) - 6 \sin(\pi/2)}{s^2 + 4} \\ &= -\frac{1}{2} \frac{s}{s+1/2} \frac{6}{s^2 + 4} \\ &= -3 \frac{s}{(s+1/2)(s^2 + 4)}. \end{aligned}$$

Therefore, we can now use partial fraction expansion. We have already calculated the steady-state response $1.455 \cos(2t + 0.578\pi)u(t)$, so we just need to consider the transient pole $s = -1/2$. The corresponding constant is

$$\begin{aligned} K &= -3 \frac{s}{s^2 + 4} \Big|_{s=-1/2} \\ &= \frac{6}{17}. \end{aligned}$$

Overall we have
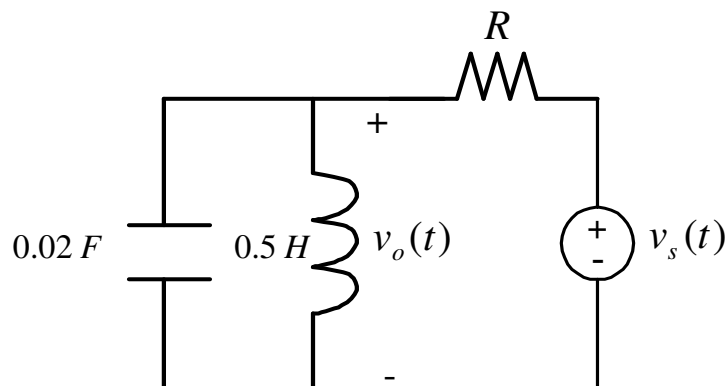
$$v_o(t) = 1.455 \cos(2t + 0.578\pi)u(t) + \frac{6}{17}e^{-\frac{1}{2}t}u(t).$$



4. (3 points) For the circuit in the

figure of the left, assume that the initial energy in the inductor and in the capacitor is zero.

- Calculate the transfer function between the voltage source $V_s(s)$ and the output voltage $V_o(s)$ as a function of R . What type of filter is it?
- Calculate R so that the bandwidth is 1.6 Hz.
- For $R = 5\ \Omega$ and $v_s(t) = 5u(t)$, calculate $v_o(t)$, $t \geq 0$, in the *time domain*, that is, *without* using the Laplace transform approach.

Sol.: a. The transfer function, as seen in class, is

$$H(s) = \frac{2\alpha s}{s^2 + 2\alpha s + \omega_0^2},$$

with $\omega_0 = 1/(\sqrt{LC}) = 10\text{ rad/s}$ and $\alpha = 1/(2RC) = 25/R\text{ rad/s}$, so that

$$H(s) = \frac{50s/R}{s^2 + 50s/R + 100}.$$

It is a bandpass filter.

b. We have

$$\begin{aligned} \beta &= 2\alpha = 50/R = 1.6 \cdot 2\pi \\ \rightarrow R &= 50/(1.6 \cdot 2\pi) \simeq 5\ \Omega. \end{aligned}$$

c. Since $\alpha < \omega_0$, we are in the underdamped regime. The damped frequency is $\omega_d = \sqrt{100 - 25} = 8.7\text{ rad/s}$. We thus have

$$v_o(t) = 0 + B_1 e^{-5t} \cos(8.7t) + B_2 e^{-5t} \sin(8.7t), \quad t \geq 0,$$

where

$$\begin{aligned} B_1 &= v_o(0) = 0 \\ -\alpha B_1 + \omega_d B_2 &= \frac{1}{C} i_C(0^+) \\ &= \frac{1}{0.02} \left(\frac{5}{5} \right) = 50 \\ &\rightarrow B_2 = \frac{50}{8.7} = 5.75. \end{aligned}$$

Overall, we get

$$v_o(t) = 5.75e^{-5t} \cos(8.7t), \quad t \geq 0.$$