

## ECE 232 - Circuits and Systems II


### Final

Please provide clear and complete answers. Don't forget to specify the units of measure!

- (4 points)** We wish to design a high-pass filter using a capacitor of capacitance  $C = 4 \times 10^{-2}$  F and a resistor of resistance  $R$ . We fix the 3-dB cut-off frequency to 4 Hz.
  - Draw the circuit by clearly specifying input and output voltages and calculate  $R$ .
  - Calculate the amplitude frequency response at 1 Hz, 4 Hz, 20 Hz.
  - Assume that the input is a constant voltage source of 2 V and that the initial voltage on the capacitor is 1 V (assume that the positive terminal is the same for both source and capacitor). Calculate the voltage  $v(t)$  across the *capacitor* for all  $t \geq 0$  using *time domain* analysis.
  - Confirm the result at the previous point by calculating  $v(t)$  for all  $t \geq 0$ , when the input is a constant voltage source of 2 V and the initial voltage on the capacitor is 1 V, via partial fraction expansion.
- (2 points)** Calculate the convolution between  $x(t) = t(u(t) - u(t - 1))$  and  $h(t) = (1 - t)(u(t) - u(t - 1))$  (don't forget to check for the continuity of the function).
- (2 points)** Calculate the Laplace transform of

$$(t - 4) \sin(3t - 12)u(t - 4)$$

by detailing all the steps.

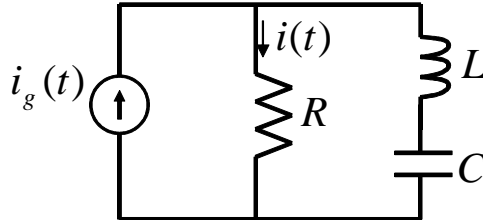

- (4 points)** Consider the circuit in the figure. The input is  $i_g(t)$  and the output is  $i(t)$ .
  - What kind of filter is it? Argue your response through considerations on the impedances in the circuit.
  - Calculate the transfer function  $H(s)$ .
  - Assume that  $L = 1$  H,  $C = 1$  F and  $R = 1$   $\Omega$ . Calculate and plot poles and zeros.
  - If the input is  $i_g(t) = 6 \cos(t + \pi/4)$  calculate the steady-state output  $i(t)$ .
- (1 point)** Draw the Bode plot for the transfer function  $H(s) = \frac{s+0.1}{s+1000}$ .

*Solutions:*

- a. Please see class notes or text. The input is a voltage source and the output is the voltage across the resistor. We also have  $\omega_c = 1/\tau$  and hence

$$\begin{aligned} R &= 1/(\omega_c C) = 1/(2\pi \cdot 4 \cdot 4) \times 10^2 \\ &= 0.995 \Omega. \end{aligned}$$

b. We have

$$H(s) = \frac{R}{R + 1/(sC)} = \frac{s}{s + 1/\tau}$$

and thus we can calculate  $|H(j2\pi)| = 0.24$ ,  $|H(j2\pi4)| = 1/\sqrt{2}$ , and  $|H(j2\pi20)| = 0.98$ .

c. This is a step response problem. We get

$$\begin{aligned}v(t) &= v(\infty) + (v(0) - v(\infty))e^{-t/\tau} \\ &= 2 + (1 - 2)e^{-2\pi4t} \\ &= 2 - e^{-2\pi4t}\end{aligned}$$

for  $t \geq 0$ .

d. In the Laplace domain, we use the equivalent series for the capacitor, which adds a voltage source of  $1/s$ , to get

$$\begin{aligned}V(s) &= \left(\frac{2}{s} - \frac{1}{s}\right) \frac{2\pi4}{s + 2\pi4} + \frac{1}{s} \\ &= \frac{2\pi4}{s(s + 2\pi4)} + \frac{1}{s},\end{aligned}$$

since the transfer function between the voltage source and the voltage on the capacitor is  $\frac{2\pi4}{s+2\pi4}$  and the second term is due to the equivalent series representation for the capacitor. Using partial fraction expansion, we write:

$$K_1 = 1$$

and

$$K_2 = \frac{2\pi4}{-2\pi4} = -1.$$

From which we get

$$v(t) = 1 - e^{-2\pi4t} + 1 = 2 - e^{-2\pi4t},$$

as desired.

2. For  $0 \leq t \leq 1$ , we have

$$\begin{aligned}y(t) &= \int_0^t (1 - \tau)(t - \tau)d\tau \\ &= \int_0^t (t - \tau - \tau t + \tau^2)d\tau \\ &= t^2 - \frac{1}{2}(1 + t)\tau^2 \Big|_0^t + \frac{1}{3}\tau^3 \Big|_0^t \\ &= t^2 - \frac{1}{2}(1 + t)t^2 + \frac{1}{3}t^3 = \\ &= \frac{1}{2}t^2 - \frac{1}{6}t^3.\end{aligned}$$

For  $1 \leq t \leq 2$ , we have

$$\begin{aligned}
 y(t) &= \int_{t-1}^1 (1-\tau)(t-\tau)d\tau \\
 &= t(1-t+1) - \frac{1}{2}(1+t)\tau^2 \Big|_{t-1}^1 + \frac{1}{3}\tau^3 \Big|_{t-1}^1 \\
 &= t(2-t) - \frac{1}{2}(1+t)(1-(t-1)^2) + \frac{1}{3}(1-(t-1)^3).
 \end{aligned}$$

And we also have  $y(t) = 0$  for  $t \leq 0$  and  $t \geq 2$ . Continuity at  $t = 0, 1, 2$  is easy to prove.

3. Since

$$\begin{aligned}
 \mathcal{L}(t \sin(3t)u(t)) &= -\frac{d}{ds} \frac{3}{s^2 + 9} \\
 &= \frac{6s}{(s^2 + 9)^2}
 \end{aligned}$$

then

$$\mathcal{L}((t-4) \sin(3(t-4))u(t-4)) = e^{-4s} \frac{6s}{(s^2 + 9)^2}.$$

4. a. It is a band-reject filter since it can be seen that  $I(j\omega) = I_g(j\omega)$  for both high and low frequencies: the system performs current division and the impedance of the series  $LC$  branch goes to infinity in both cases. Moreover, similar to the discussion in class, it can be easily seen that  $I(j\omega_c) = 0$  for  $\omega_c = 1/\sqrt{LC}$  since the impedance of the LC branch satisfies  $j\omega_c L + 1/(j\omega_c C) = 0$ .

b. We have

$$\begin{aligned}
 H(s) &= \frac{sL + \frac{1}{sC}}{R + sL + \frac{1}{sC}} \\
 &= \frac{s^2 + \omega_0^2}{s^2 + 2\alpha s + \omega_0^2}
 \end{aligned}$$

with  $\omega_0^2 = 1/(LC)$  and  $\alpha = R/(2L)$ .

c. With the given values, we can calculate  $\omega_0^2 = 1$  and  $\alpha = 1/2$ . The poles are

$$\begin{aligned}
 s &= -\alpha + j\sqrt{\omega_0^2 - \alpha^2} = -\alpha + j\frac{\sqrt{3}}{2} \\
 s &= -\alpha + j\sqrt{\omega_0^2 - \alpha^2} = -\alpha - j\frac{\sqrt{3}}{2}.
 \end{aligned}$$

The zeros are  $\pm j1$ .

d. The output is easily seen to be zero in steady state since  $H(j1) = 0$ .

5. We write

$$\begin{aligned} |H(j\omega)| &= \frac{0.1|1 + j\frac{\omega}{0.1}|}{1000|1 + j\frac{\omega}{1000}|} \\ &= 10^{-4} \frac{|1 + j\frac{\omega}{0.1}|}{|1 + j\frac{\omega}{1000}|}. \end{aligned}$$

Using the usual rules, the plot is constant and equal to  $-80$  dB up to  $\omega = 0.1$  rad/s. It then goes up by 20 dB/decade thus reaching 0 dB at  $\omega = 1000$  rad/s. It then stays flat at this value.