

ECE 232 - Circuits and Systems II Midterm

Please provide clear and complete answers. Don't forget to specify the units of measure!

Q1. (1 point) Plot the function $v(t) = 4e^{-2000t} \sin(2\pi \cdot 1000t)$ [V] for $0 \leq t \leq 2.5$ ms.

Sol.: The time constant of the exponential term is $1/2000 = 0.5$ ms and the period of the sinusoid is $1/1000 = 1$ ms.

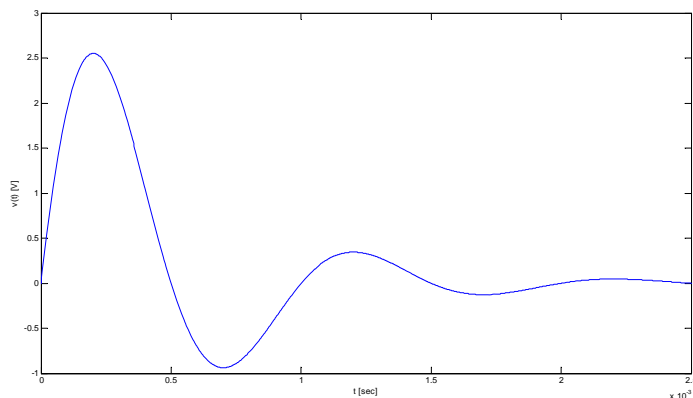


Figure 1:

Q2. (1 point) Calculate the Laplace transform of

$$f(t) = 2 \cdot (t - 1) \cdot e^{-20(t-1)} u(t - 1).$$

(Hint: Start with the Laplace transform of $te^{-20t}u(t)$)

Sol: We know that

$$\mathcal{L}(e^{-20t}u(t)) = \frac{1}{s + 20},$$

so that

$$\mathcal{L}(2te^{-20t}u(t)) = 2 \frac{d}{ds} \left(\frac{1}{s + 20} \right) = \frac{2}{(s + 20)^2}.$$

We finally have

$$\mathcal{L}(2 \cdot (t - 1) \cdot e^{-20(t-1)} u(t - 1)) = e^{-s} \frac{2}{(s + 20)^2}.$$

P1. (4 points) Consider the circuit in the figure below. Assume that for $t < 0$ switch 1 is closed and switch 2 open and that the circuit has been in this configuration for a long time.

a. Calculate $v_c(t)$ for $0 \leq t < 8$ ms. In this interval of time, switch 1 and 2 are open.

b. Calculate $v_c(t)$ for $t \geq 8$ ms. In this interval of time, switch 1 is open and 2 closed.

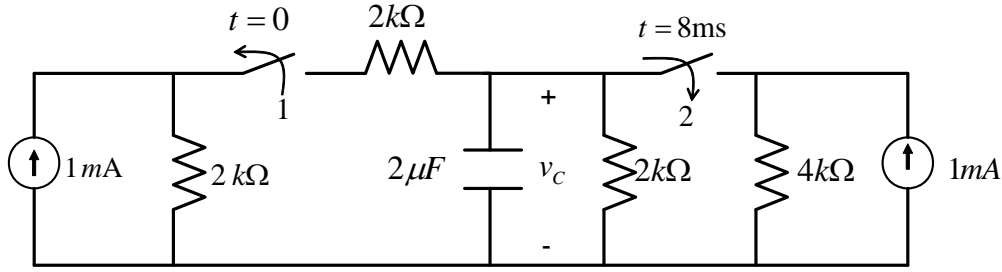


Figure 2:

- c. Calculate the initial energy available in the capacitor and the fraction of such energy dissipated by the resistors in the interval $0 \leq t < 8ms$.
- d. Double check your result at the previous point by calculating the energy remaining on the capacitor at time $t = 8ms$. Explain.

Sol.: a. We have

$$v_c(0) = 2 \cdot 10^3 \cdot \frac{2}{6} 10^{-3} = \frac{2}{3} \text{ V.}$$

Moreover, for $0 \leq t < 8ms$, the circuit is RC with $\tau = RC = 2 \cdot 10^3 \cdot 2 \cdot 10^{-6} = 4 \text{ ms}$. Therefore, we have

$$v_c(t) = \frac{2}{3} e^{-250t}.$$

b. For $t \geq 8ms$, the circuit is RC with $R = 2 \cdot 4/6 = 4/3 \text{ k}\Omega$, so that $\tau = 8/3ms$, and a source of 1 mA. Moreover, we can calculate

$$v_c(8 \cdot 10^{-3}) = \frac{2}{3} e^{-2} = 0.09 \text{ V}$$

and

$$v_c(\infty) = \frac{4}{3} \cdot 10^3 \cdot 10^{-3} = \frac{4}{3} \text{ V.}$$

Finally, we obtain

$$\begin{aligned} v_c(t) &= \frac{4}{3} + \left(0.09 - \frac{4}{3}\right) e^{-\frac{3000}{8}(t-8 \cdot 10^{-3})} \\ &= \frac{4}{3} - 1.24 e^{-375(t-8 \cdot 10^{-3})}. \end{aligned}$$

c. Initial energy available in the capacitor:

$$\frac{1}{2} C v_c(0)^2 = \frac{1}{2} 2 \cdot 10^{-6} \cdot \frac{4}{9} = \frac{4}{9} \cdot 10^{-6} \text{ J.}$$

Energy dissipated by the $2k\Omega$ resistor connected to the capacitor in the interval $0 \leq t < 8ms$

$$\begin{aligned} \int_0^{8 \cdot 10^{-3}} \frac{v_c(t)^2}{2000} dt &= \frac{2}{9000} \int_0^{8 \cdot 10^{-3}} e^{-500t} dt \\ &= \frac{2}{9000 \cdot (-500)} (e^{-500 \cdot 8 \cdot 10^{-3}} - 1) \\ &= 4.36 \cdot 10^{-7}, \end{aligned}$$

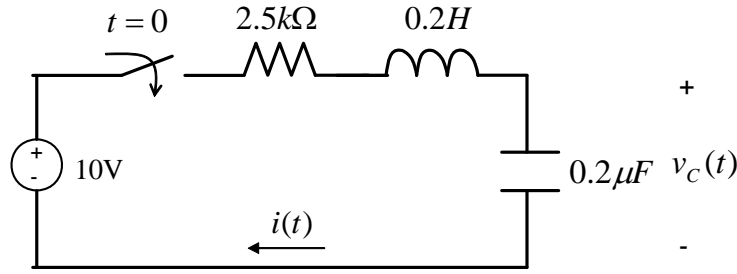


Figure 3:

which is a fraction

$$\frac{4.36 \cdot 10^{-7}}{\frac{4}{9} \cdot 10^{-6}} \cdot 100 = 98.1\%.$$

d. The energy remaining in the capacitor is

$$\frac{1}{2} C v_c(\infty)^2,$$

which can be seen to be around 1.9% of the initial energy.

P2. (4 points) In the circuit in the figure below, no energy is initially stored in inductor and capacitor.

- Calculate the roots of the characteristic equation and determine the regime.
- Find $v_C(0)$ and $\frac{dv_C(0^+)}{dt}$.
- Find $v_C(t)$ for $t \geq 0$.
- Find $i(t)$ for $t \geq 0$.

Sol.: a. We have

$$\alpha = \frac{R}{2L} = \frac{2.5 \cdot 10^3}{2 \cdot 0.2} = \frac{2.5 \cdot 10^3}{0.4} = 6.25 \cdot 10^3 \text{ rad/s}$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{0.2 \cdot 0.2 \cdot 10^{-6}}} = \frac{1}{\sqrt{4 \cdot 10^{-8}}} = 5 \cdot 10^3 \text{ rad/s}$$

so we are in the overdamped regime. The roots are

$$s_1 = -6.25 \cdot 10^3 + 10^3 \sqrt{6.25^2 - 5^2}$$

$$= -6.25 \cdot 10^3 + 3.75 \cdot 10^3 = -2500$$

$$s_2 = -6250 - 3750 = -10000.$$

b.

$$v_C(0) = 0 \text{ V}$$

$$\frac{dv_C(0^+)}{dt} = \frac{1}{C} i_C(0^+) = 0 \text{ V/s,}$$

since the initially stored energy is zero.

c. From the general formula for the overdamped regime, we have

$$v_C(t) = v_C(\infty) + A_1 e^{-2500t} + A_2 e^{-10000t} \text{ V}, \quad t \geq 0$$

where

$$v_C(\infty) = 10 \text{ V},$$

and imposing the initial conditions, we get

$$\begin{aligned} 10 + A_1 + A_2 &= 0 \\ -2500A_1 - 10000A_2 &= 0, \end{aligned}$$

and

$$\begin{aligned} A_1 &= -40/3 \\ A_2 &= 10/3, \end{aligned}$$

so that

$$v_C(t) = 10 - \frac{40}{3} e^{-2500t} + \frac{10}{3} e^{-10000t} \text{ V}, \quad t \geq 0.$$

d. From the general formula for the underdamped regime, we have

$$i(t) = A_1 e^{-2500t} + A_2 e^{-10000t} \text{ A}, \quad t \geq 0$$

and imposing the initial conditions

$$\begin{aligned} A_1 + A_2 &= i(0) = 0 \\ -2500A_1 - 10000A_2 &= \frac{di(0^+)}{dt} = \frac{1}{L} v_L(0^+) = \frac{1}{0.2} 10 = 50, \end{aligned}$$

and

$$\begin{aligned} A_1 &= 2/3 \cdot 10^{-3} \\ A_2 &= -2/3 \cdot 10^{-3}, \end{aligned}$$

so that

$$i(t) = \frac{2}{3} e^{-2500t} - \frac{2}{3} e^{-10000t} \text{ mA}, \quad t \geq 0.$$