

**ECE 232 - Circuits and Systems II**  
**Test 1**

Please provide clear and complete answers. Don't forget to specify the units of measure!

In the circuit shown in the figure, the first switch closes at time  $t = 0$  and the second closes at time  $2 \text{ ms}$ . Before time  $t = 0$ , the circuit was in the same condition for a long time.

- Find the current in the inductor,  $i_L(t)$ , for  $0 \leq t \leq 2 \text{ ms}$ .
- Find the current in the inductor,  $i_L(t)$ , for  $t \geq 2 \text{ ms}$  (Hint: it may be useful to remember that the Thevenin equivalent of a current source of current  $I_S$  in parallel with a resistance  $R_S$  is given by a voltage source of voltage  $R_S I_S$  in series with a resistor of resistance  $R_S$ ).
- Plot  $i_L(t)$  for  $0 \leq t \leq 4 \text{ ms}$ .
- Find the current  $i_0(t)$  (see figure) for  $t \geq -1 \text{ ms}$ .
- In the period  $0 \leq t \leq 2 \text{ ms}$ , how much overall energy is dissipated by the series of resistors of resistance  $4 \Omega$  and  $6 \Omega$  that are in series with the inductor?

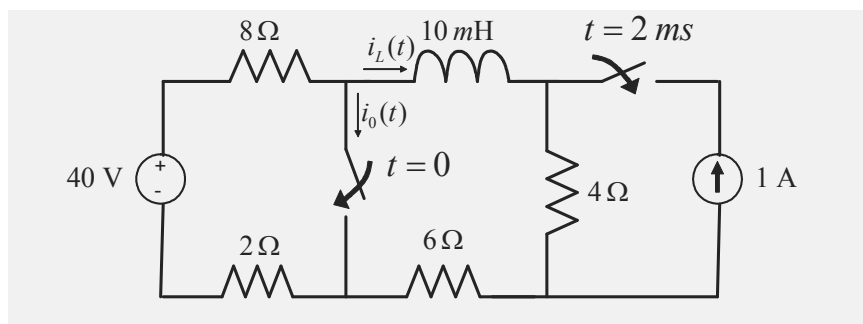


Figure 1:

Sol.:

- For  $t = 0^-$ , the inductor behaves as a short circuit, and from Ohm's law, we have

$$i_L(0^-) = \frac{40}{8 + 2 + 6 + 4} = 2 \text{ A}.$$

And, by continuity, we also have  $i_L(0^-) = i_L(0^+) = i_L(0) = 2 \text{ A}$ .

For  $0 < t < 2 \text{ ms}$ , in order to evaluate current  $i_L(t)$ , it is sufficient to focus on the RL circuit with equivalent resistance  $R_{eq} = 6 + 4 = 10 \Omega$ , and hence time constant  $\tau = L/R_{eq} = 1 \text{ ms}$ . This is because the part of the circuit that includes the voltage source is in parallel to a short circuit and thus does not contribute to the current  $i_L(t)$  (see also problems in the assignments). Therefore, we can write

$$i_L(t) = i_L(0)e^{-t/\tau} = 2e^{-1000t} \text{ A}$$

for  $0 \leq t \leq 2 \text{ ms}$ , where equality for  $t = 0$  and  $t = 2 \text{ ms}$  follows by continuity. Note that  $i_L(\infty) = 0$ .

b. For  $t \geq 2 \text{ ms}$ , we transform the current source into a voltage source using the Thevenin equivalent with resistance  $R_{Th} = 4 \Omega$  and voltage source  $V_{Th} = 4 \text{ V}$ . This way, we obtain that  $i_L(t)$  can be calculated from a RL circuit with  $R_{eq} = 6 + 4 = 10 \Omega$  and voltage source  $V_{Th} = 4 \text{ V}$ . Note that the time constant is still  $\tau = L/R_{eq} = 1 \text{ ms}$ , but

$$i_L(\infty) = -\frac{4}{10} = -0.4 \text{ A}.$$

We can then calculate

$$\begin{aligned} i_L(t) &= i_L(\infty) + (i_L(2 \cdot 10^{-3}) - i_L(\infty))e^{-1000(t-2 \cdot 10^{-3})} \\ &= -0.4 + (0.27 + 0.4)e^{-1000(t-2 \cdot 10^{-3})} \\ &= -0.4 + 0.67e^{-1000(t-2 \cdot 10^{-3})} \text{ A} \end{aligned}$$

where we have used the continuity of the current in the inductor to obtain  $i_L(2 \cdot 10^{-3}) = 2e^{-2} = 0.27 \text{ A}$ .

d. For  $-1 \text{ ms} \leq t \leq 0$ , we clearly have  $i_0(t) = 0$ . For all other times, we have

$$i_0(t) = 4 - i_L(t),$$

where  $i_L(t)$  was calculated above.

e. The initial energy stored in the inductor is

$$w(0) = \frac{1}{2}Li_L(0)^2 = 5 \cdot 10^{-3} \cdot 4 = 20 \text{ mJ},$$

while at  $t = 2 \text{ ms}$  the remaining energy is

$$w(2 \cdot 10^{-3}) = \frac{1}{2}Li_L(2 \cdot 10^{-3})^2 = 0.36 \text{ mJ}.$$

The energy that is lost, namely  $20 - 0.36 \text{ mJ} = 19.64 \text{ mJ}$ , has been dissipated by the two resistors at hand.