

ECE 232 - Circuits and Systems II
Test 1

Please provide clear and complete answers. Don't forget to specify the units of measure!

Consider the circuit in Fig. 1. The switch was in position *a* for a long time before it moves to position *b* at time $t = 0$. Then it moves to position *c* at time $t = 2 \text{ ms}$.

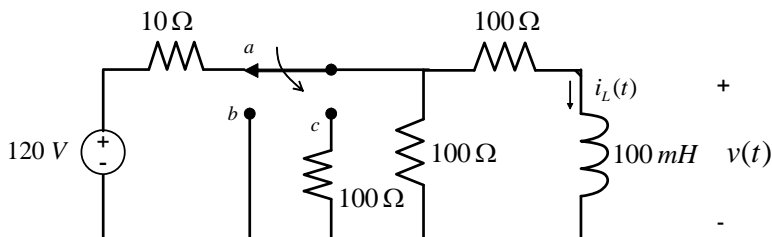


Figure 1:

- a. Calculate the current $i_L(0)$.
- b. Calculate $i_L(t)$ for $0 \leq t \leq 2 \text{ ms}$.
- c. Calculate $i_L(t)$ for $t \geq 2 \text{ ms}$.
- d. Calculate the voltage $v(t)$ across the inductors for $t \geq 0^+$.
- e. Plot $v(t)$ and $i_L(t)$.
- f. Calculate the energy stored on the inductor at time $t = 0$. What is the percentage of this energy that is released by the inductor in the interval $0 \leq t \leq 2 \text{ ms}$ and in the interval $t \geq 2 \text{ ms}$? Answer this question by integrating the power released by the inductor over time.

Sol.:

- a. For $t = 0^-$, the current that flows on the parallel of the two 100Ω resistors is $\frac{120}{10+50} = 2A$ so that, using the current division rule we get

$$i_L(0^-) = 2 \cdot \frac{1}{2} = 1 \text{ A},$$

and by continuity of the current over the inductor, we get $i_L(0^-) = i_L(0^+) = i_L(0) = 1 \text{ A}$.

- b. In this interval, the equivalent circuit is RL with time constant $\tau = \frac{100 \times 10^{-3}}{100} = 1 \text{ ms}$. The final value is zero, so that we obtain

$$i_L(t) = e^{-1000t}, \text{ for } 0 \leq t \leq 2 \text{ ms}.$$

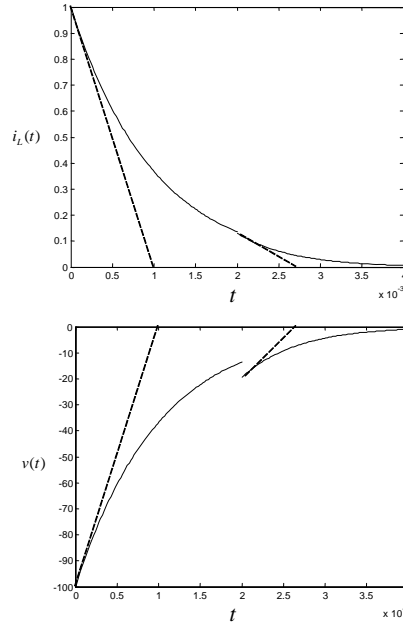


Figure 2:

c. In this interval, the circuit is RL with time constant $\tau = \frac{100 \times 10^{-3}}{150} = \frac{2}{3}$ ms. The initial value is

$$i_L(2 \times 10^{-3}) = e^{-2} = 0.13 \text{ A.}$$

so that

$$i_L(t) = 0.13e^{-1500(t-2 \times 10^{-3})}, \text{ for } t \geq 2 \text{ ms.}$$

d. The voltage is obtained as

$$\begin{aligned} v(t) &= L \frac{di(t)}{dt} \\ &= 100 \times 10^{-3} \times (-1000e^{-1000t}) \\ &= -100e^{-1000t} \text{ for } 0 < t < 2 \text{ ms} \end{aligned}$$

and

$$\begin{aligned} v(t) &= L \frac{di(t)}{dt} \\ &= 100 \times 10^{-3} \times \left(-\frac{3000}{2}\right) \times \left(0.13e^{-\frac{3000}{2}(t-2 \times 10^{-3})}\right) \\ &= -19.5e^{-1500(t-2 \times 10^{-3})} \text{ for } t > 2 \text{ ms} \end{aligned}$$

e. Plots are shown in the figure. Note that the voltage is discontinuous.

f. The initial energy is $E = \frac{1}{2}Li(0)^2 = \frac{1}{2}0.1 \cdot 1 = 0.05 \text{ J} = 50 \text{ mJ}$. The amount of power dissipated in the interval $0 \leq t \leq 2 \text{ ms}$ is the negative of

$$\begin{aligned} & \int_0^{2 \times 10^{-3}} v(t)i(t)dt \\ &= \int_0^{2 \times 10^{-3}} -100e^{-1000t} \cdot e^{-1000t} dt \\ &= -100 \int_0^{2 \times 10^{-3}} e^{-2000t} dt \\ &= \frac{-100}{-2000} [e^{-2000t}]_0^{2 \times 10^{-3}} \\ &= \frac{1}{20}(e^{-4} - 1) = -0.049, \end{aligned}$$

which is the $\frac{0.049}{0.05} = 0.98\%$ of the overall initial energy.