

ECE 232 - Circuits and Systems II
Test 2

Please provide clear and complete answers. Don't forget to specify the units of measure!

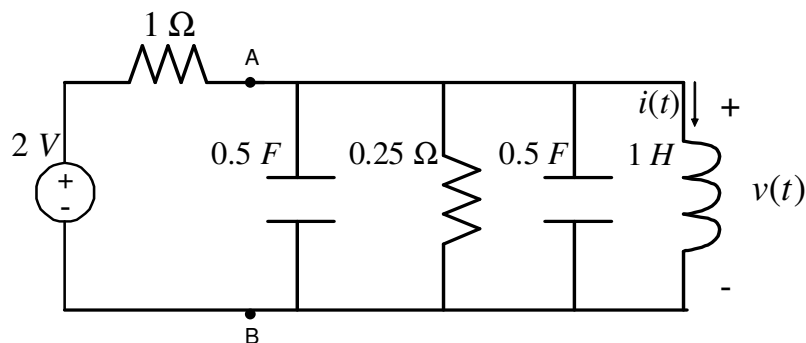


Figure 1:

Consider the circuit in the figure and assume at first that the initial energy is zero.

1. (1 point) Evaluate the impedance $Z(s)$ seen at the terminals A and B by the series of source and $1\ \Omega$ resistor.
2. (1 point) Calculate the Laplace transform $V(s)$ of the voltage $v(t)$.
3. (1 point) Calculate the poles and zeros of $V(s)$ and indicate which poles are steady-state and which poles are transient.
4. (1 point) Identify the transfer function between the voltage source and $V(s)$.
5. (2 points) Calculate $v(t)$.
6. (2 points) Calculate the Laplace transform $I(s)$ of the current $i(t)$. Evaluate the steady-state value of $i(t)$ using *partial fraction expansion*.
7. (2 points) Assume now that the initial current in the inductor is $1\ A$. Evaluate the Laplace transform $V(s)$.

Solution:

1. We have

$$Z(s) = \frac{2}{s} \parallel \left[\frac{2}{s} \parallel 0.25 \parallel s \right] = \frac{1}{4 + \frac{1}{s} + s} = \frac{s}{s^2 + 4s + 1}.$$

2. By the voltage division rule, we can write

$$\begin{aligned} V(s) &= \frac{2}{s} \frac{Z(s)}{1 + Z(s)} \\ &= \frac{2}{s^2 + 4s + 1 + s} \\ &= \frac{2}{s^2 + 5s + 1}. \end{aligned}$$

3. No zeros. Poles: $s_1 = -2.5 + \sqrt{(2.5)^2 - 1} = -0.2087$, $s_2 = -2.5 - \sqrt{(2.5)^2 - 1} = -4.7913$. All poles are transient.

4. We have

$$H(s) = \frac{Z(s)}{1 + Z(s)} = \frac{s}{s^2 + 5s + 1}.$$

5. Using partial fraction expansion,

$$\begin{aligned} V(s) &= \frac{2}{s^2 + 5s + 1} \\ &= \frac{2}{(s + 0.2087)(s + 4.7913)} \\ &= \frac{K_1}{s + 0.2087} + \frac{K_2}{s + 4.7913}, \end{aligned}$$

with

$$\begin{aligned} K_1 &= \frac{2}{-0.2087 + 4.7913} = 0.4364 \\ K_2 &= \frac{2}{-4.7913 + 0.2087} = -0.4364. \end{aligned}$$

It follows that

$$v(t) = 0.4364(e^{-0.2087t} - e^{-4.7913t}), \quad t \geq 0.$$

6. We have

$$\begin{aligned} I(s) &= \frac{V(s)}{s} \\ &= \frac{2}{s(s^2 + 5s + 1)}. \end{aligned}$$

The steady-state pole is $s=0$ and thus the steady-state value of $i(t)$ is obtained as

$$i(\infty) = \frac{2s}{s(s^2 + 5s + 1)} \Big|_{s=0} = 2.$$

7. Using the parallel representation of an inductor in the frequency domain, along with the superposition principle, we get

$$\begin{aligned} V(s) &= \frac{2}{s} \frac{Z(s)}{1 + Z(s)} - \frac{1}{s} (Z(s) \parallel 1) \\ &= \frac{2}{s} \frac{Z(s)}{1 + Z(s)} - \frac{1}{s} \frac{Z(s)}{1 + Z(s)} \\ &= \frac{1}{s} \frac{Z(s)}{1 + Z(s)} \\ &= \frac{1}{s^2 + 5s + 1}. \end{aligned}$$