

Electrical Engineering Technology

EET 157

Electronics Circuit Analysis


05

Revised by Dr. Athula Kulatunga

Overview

- ◆ **Multivibrators**
- ◆ **555 Timer**
- ◆ **555 Timer Monostable Multivibrators**
- ◆ **555 Timer Astable Multivibrators**

Waveforms

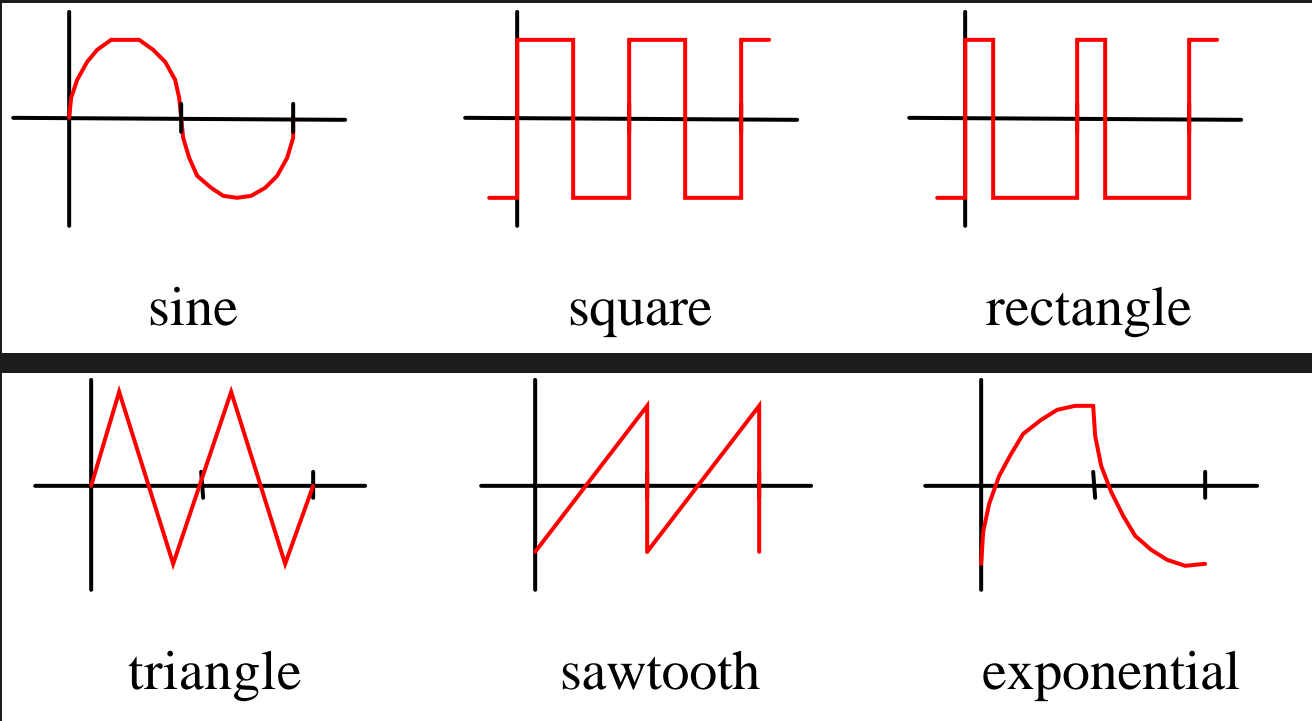

A dc source can be used to generate all the above shapes

Multivibrators

Pulse generators

Types

Astable or free-running

Monostable or one shot

Bistable



Characteristics

no stable state

one stable state

two stable states

Astable or Free-running

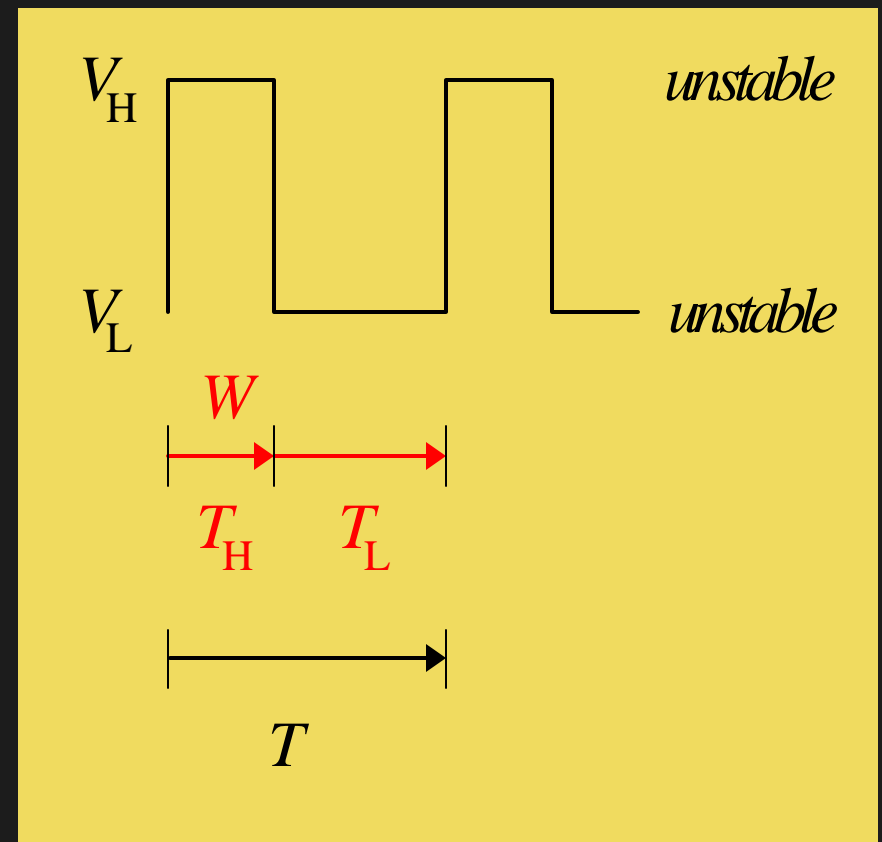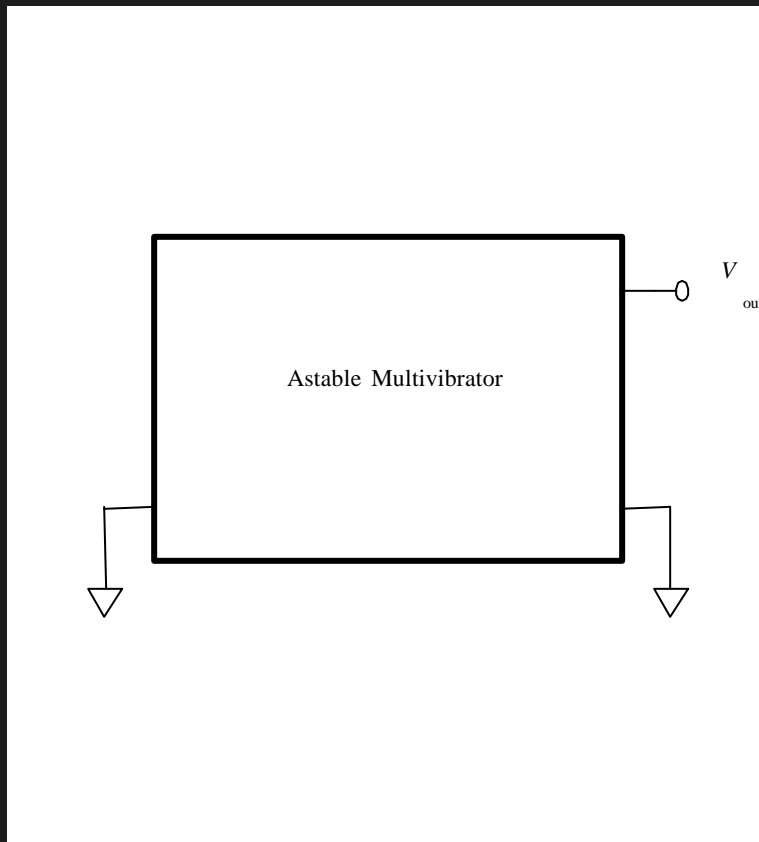

Duty Cycle

Defined for rectangular waveforms

$$D = \frac{W}{T} \times 100\%$$

Square wave has 50% duty cycle.

Why?

Duty Cycle Example 1


A rectangular signal is high for 4 ms and low for 6 ms. Find the signal's period, pulse width, duty cycle, and frequency.

Duty Cycle Example 2

A rectangular waveform has a frequency of 1k Hz and a duty cycle of 60%. Find the signal's repetition rate, period, and pulse width.


Monostable Operation

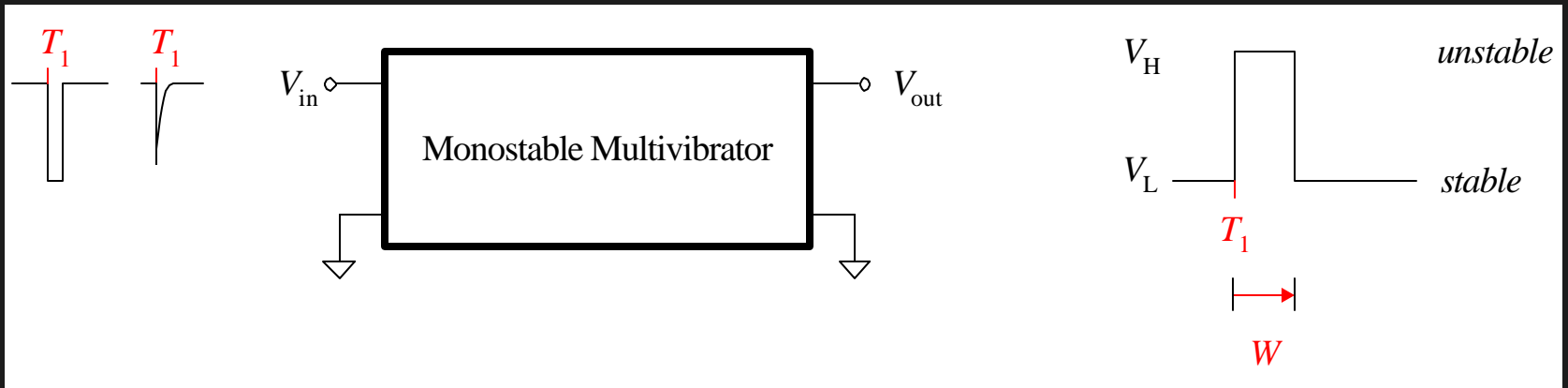The monostable multivibrator produces a well-defined pulse out for an input signal that may not be well defined (a narrow pulse or a spike)




Bistable Operation

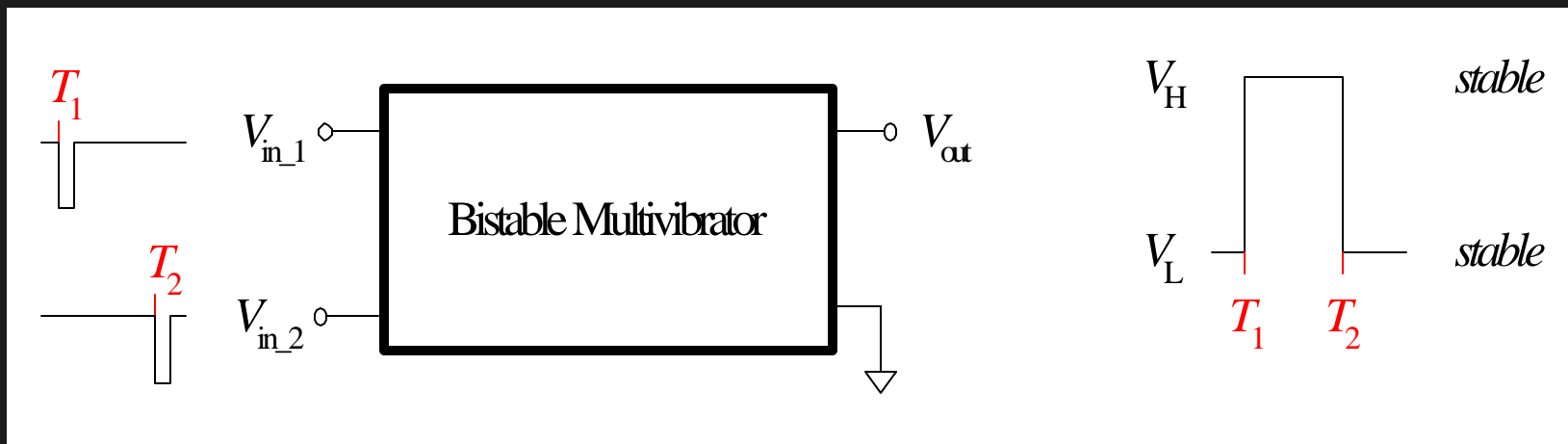The bistable multivibrator has two stable states and utilizes one input pulse to take the output high and another input pulse to take the output low.





555 Timer IC - Schematic

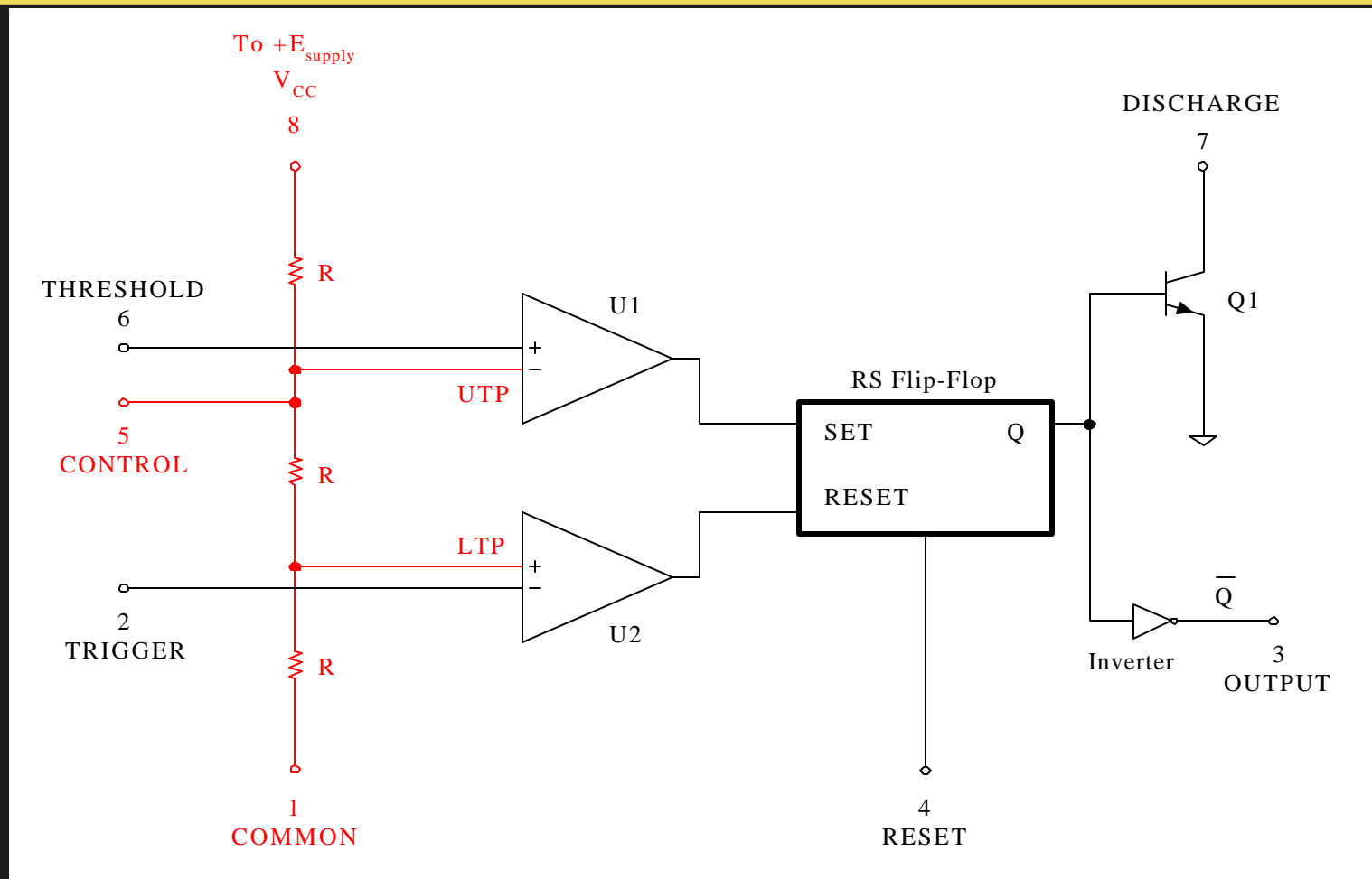


555 Timer IC - Features

- Q FF output—high or low output
- \overline{Q} Complement (opposite) of Q—low or high output
- SET FF input—high signal *sets* high and low
- RESET FF input—high signal *resets* low and high
- U1 Noninverting comparator driving the FF *set input*
- U2 Inverting comparator driving the FF *reset input*
- UTP Upper trip point for U1 set by $2R/3R$ of E_{supply}
- LTP Lower trip point for U2 set by $R/3R$ of E_{supply}
- Q1 BJT used to discharge external capacitor when Q high
- Pin 7 Open or tied to common through BJT circuit as shown


555 Timer - Symbol & Chip

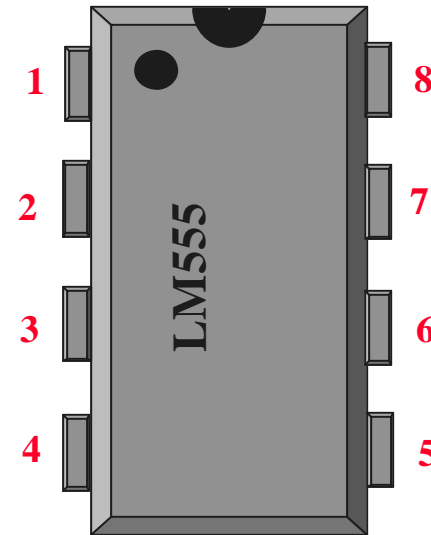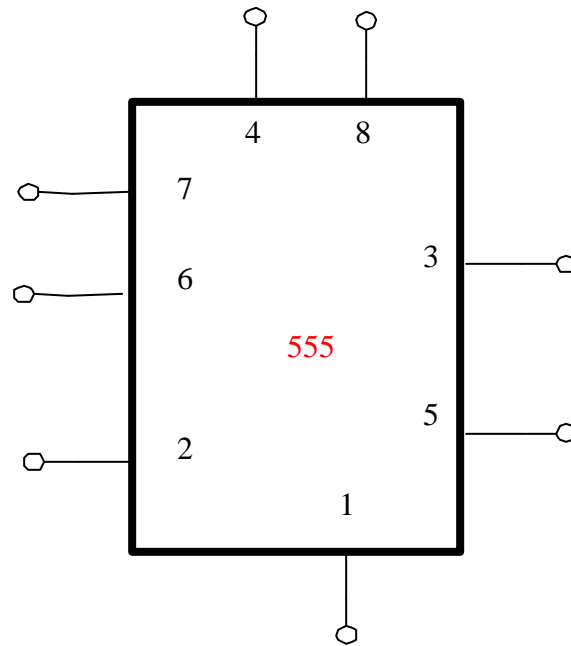


555 Timer – Monostable Connection

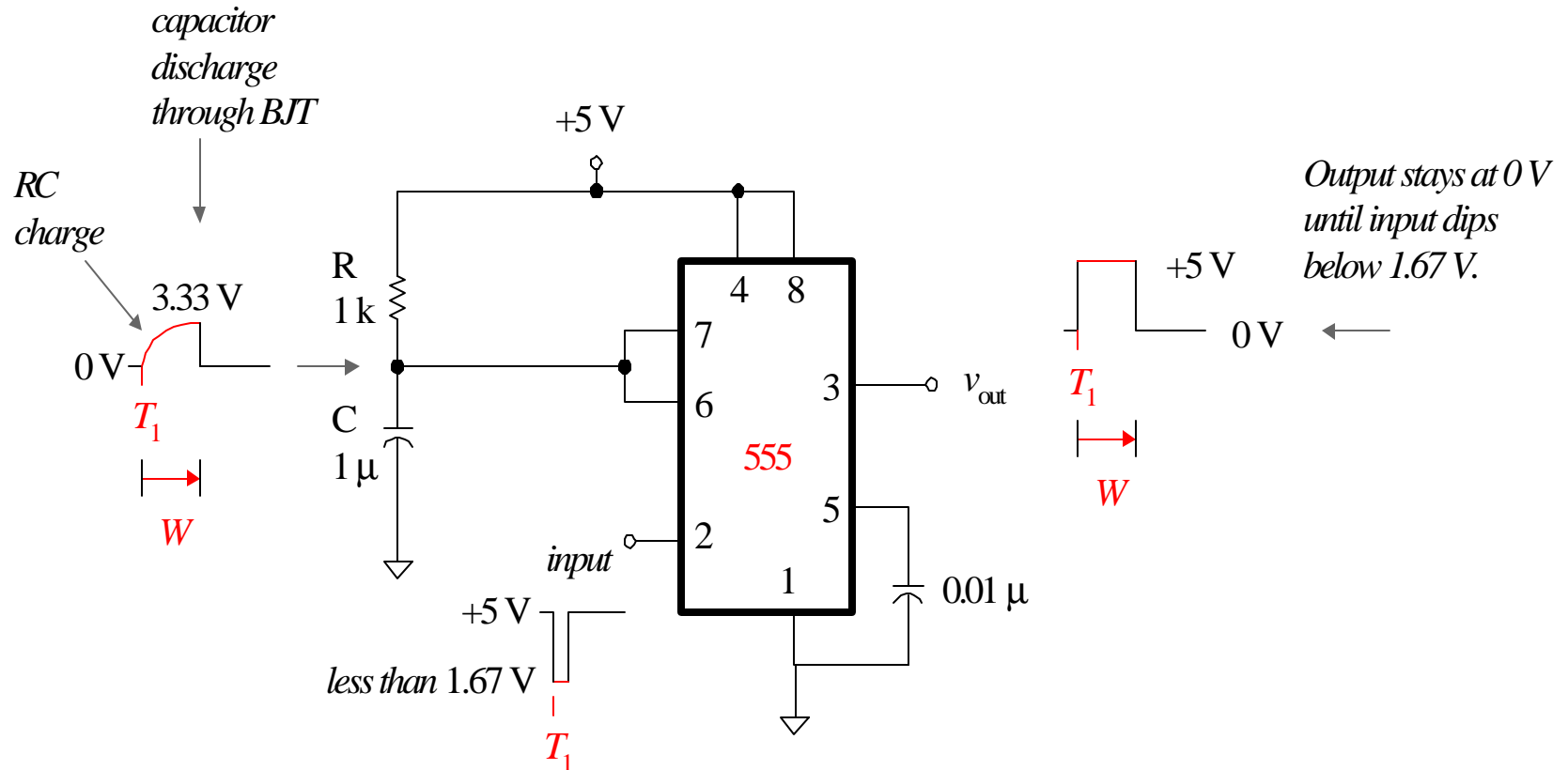

555 Timer – Monostable Operation

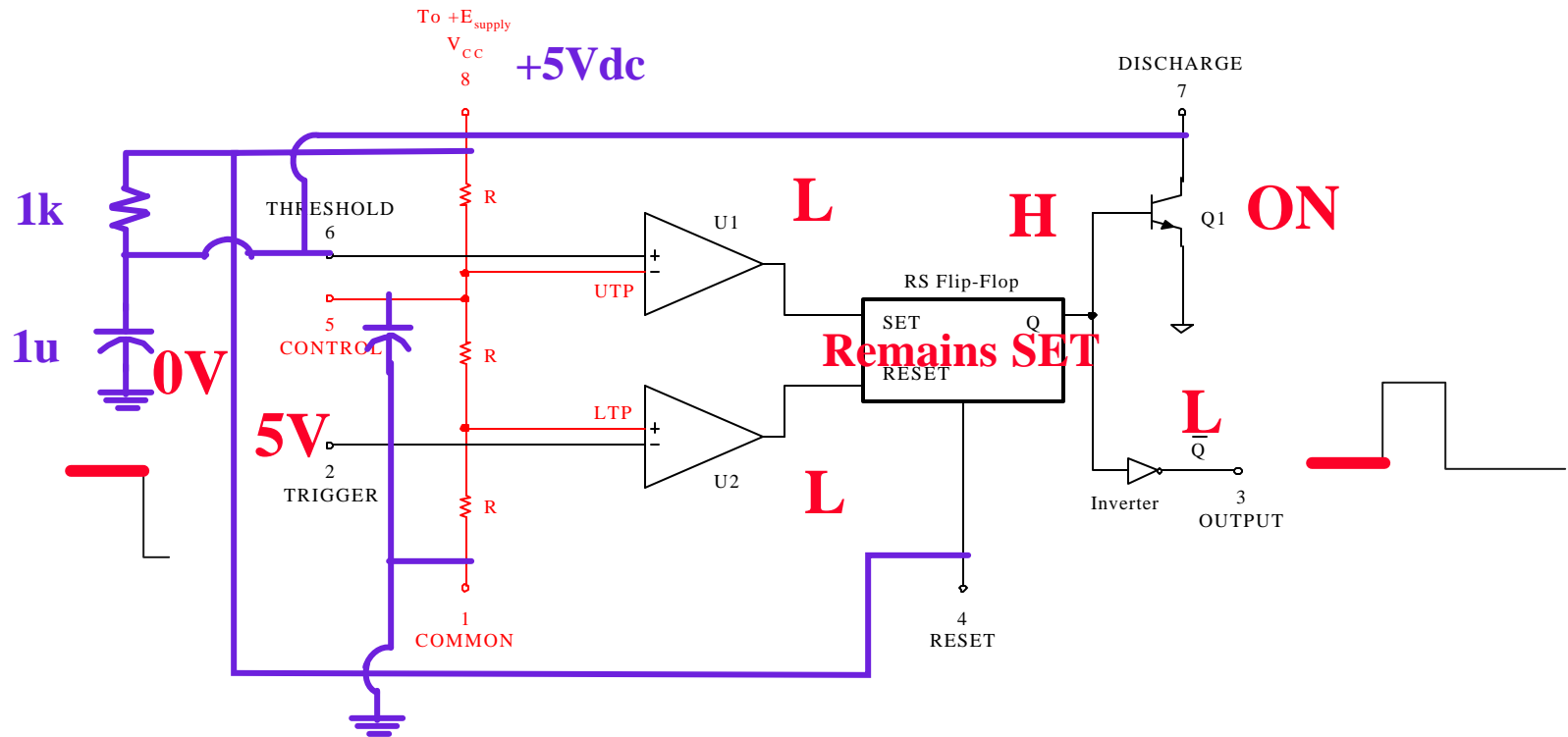

555 Timer – Monostable Operation

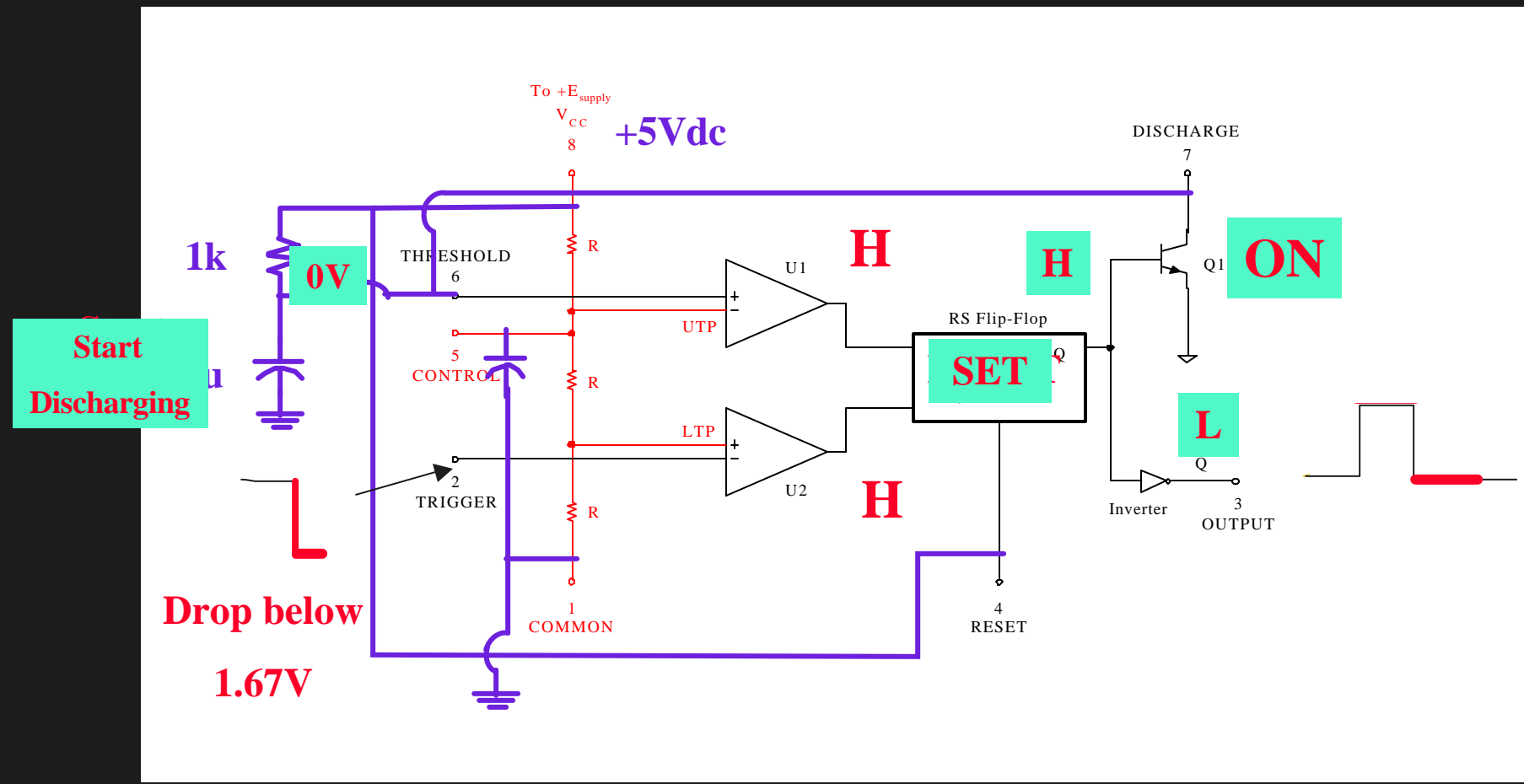

Monostable Pulse Width Calculation

The pulse width W is the time required to charge the capacitor; therefore,


$$\tau = RC = 1 \text{ k}\Omega \times 1 \text{ }\mu\text{F} = 1 \text{ ms}$$

$$v_C(t) = 5 \text{ V} + (0 \text{ V} - 5 \text{ V}) e^{-t/\tau}$$

$$v_C(t) = 5 \text{ V} - 5 \text{ V} e^{-t/1 \text{ ms}}$$


$$3.33 \text{ V} = 5 \text{ V} - 5 \text{ V} e^{-t/1 \text{ ms}}$$

$$t = 1.10 \text{ ms}$$

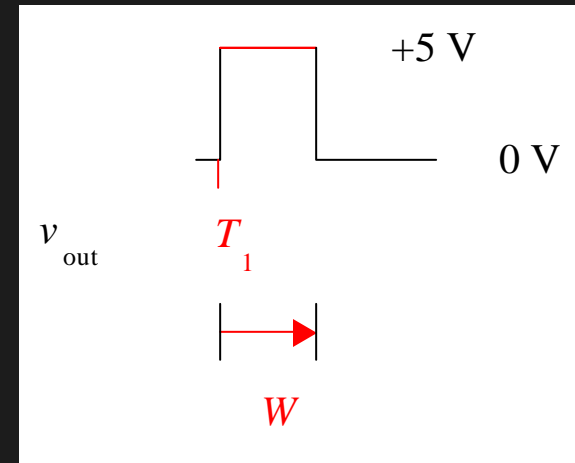


$$W = 1.10 \text{ ms}$$

555 Timer – Astable Connection

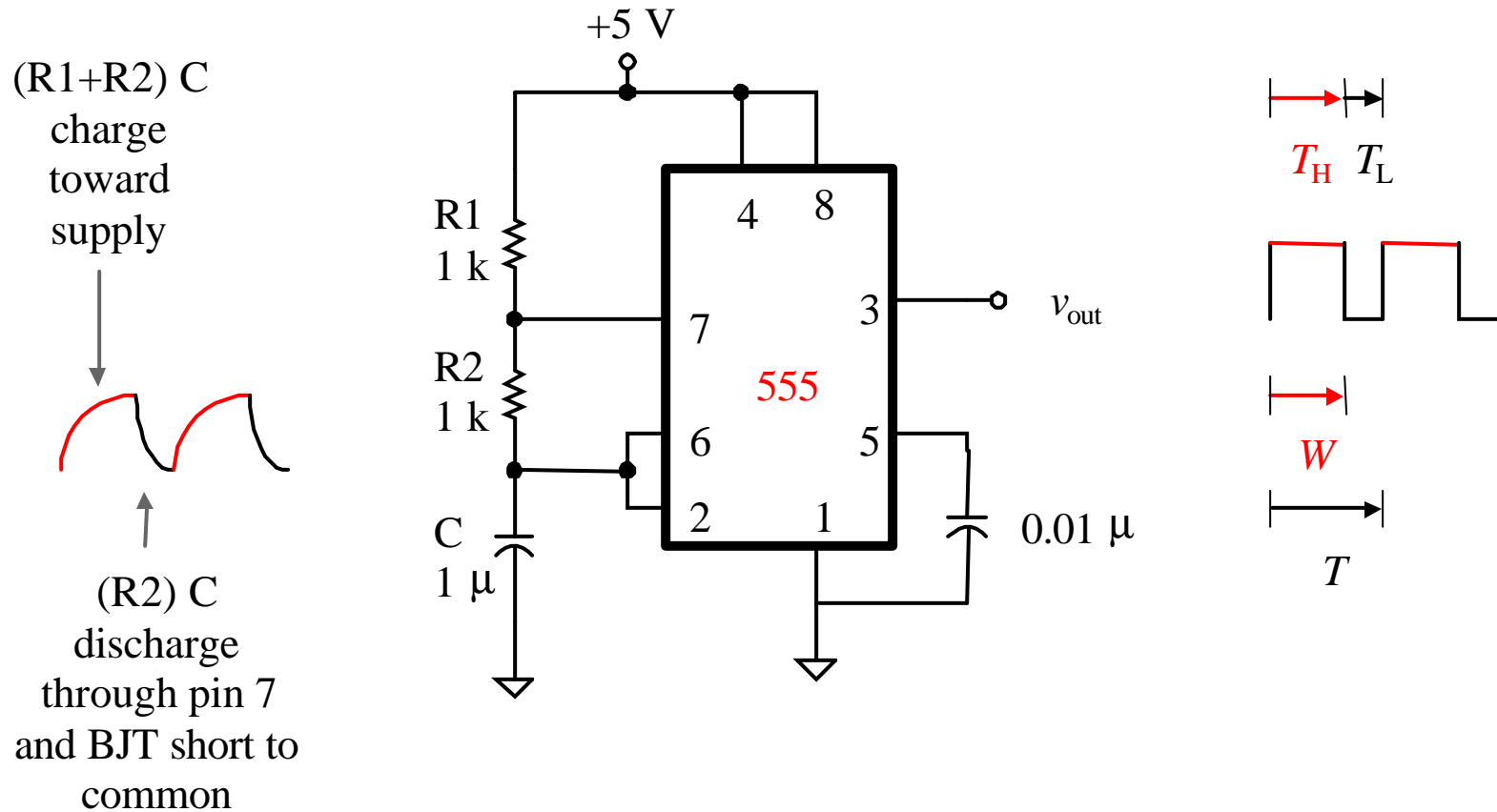

555 Timer – Astable Operation

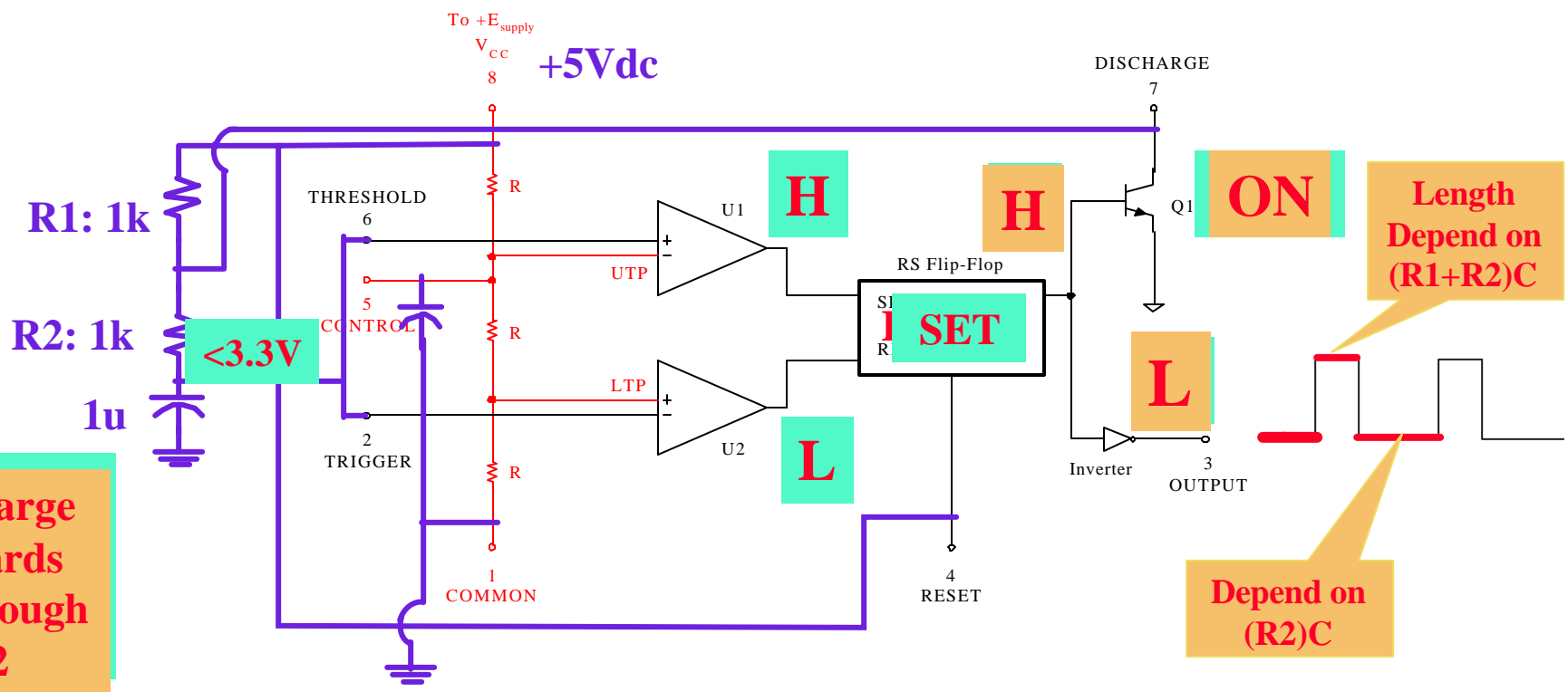

Discharge Towards 0V through R_2

Length Depend on $(R_1+R_2)C$

Depend on $(R_2)C$

Astable Pulse Width Calculation

The pulse width W depends upon the $(R1 + R2) C$ time constant τ_H and the capacitor charging from 1.67 V to 3.33 V while the output is in the high (or 5 V) state. The capacitor must follow the universal dc transient expression

$$v_C(t) = V_{ss} + (V_{init} - V_{ss}) e^{-t/\tau}$$

$$\tau = (R1 + R2) C = 2 \text{ k}\Omega \times 1 \text{ }\mu\text{F} = 2 \text{ ms}$$

$$v_C(t) = 5 \text{ V} + (1.67 \text{ V} - 5 \text{ V}) e^{-t/2 \text{ ms}}$$

$$v_C(t) = 5 \text{ V} - 3.33 \text{ V} e^{-t/2 \text{ ms}}$$

Astable Pulse Width Calculation

The capacitor charges to 3.33 V (or 2/3 of V_{CC}) when it transitions back to its stable state. Set the capacitor voltage expression equal to 3.33 V and solve the expression inversely for the time t required to charge the capacitor to 3.33 V.

$$3.33 \text{ V} = 5 \text{ V} - 3.33 \text{ V} e^{-t/2 \text{ ms}}$$

$$t = 1.386 \text{ ms}$$

Astable Pulse Width Calculation

The pulse width W is the time required to charge the capacitor, so

$$W = 1.386 \text{ ms}$$

Astable Pulse Space Calculation

- ◆ The time T_L of the pulse depends upon the (R2) C time constant τ_L and discharging the capacitor from 3.33 V to 1.67 V while the output is in the low (0 V) state. The capacitor must follow the universal dc transient expression

Astable Pulse Space Calculation

$$\tau_L = (R_2) C = 1 \text{ k}\Omega \times 1 \text{ }\mu\text{F} = 1 \text{ ms}$$

The capacitor starts with a value of 3.33 V (initial value) and attempts to fall to 0 V

$$v_C(t) = 0 \text{ V} + (3.33 \text{ V} - 0 \text{ V}) e^{-t/1 \text{ ms}}$$

$$v_C(t) = 3.33 \text{ V} e^{-t/1 \text{ ms}}$$

Astable Pulse Space Calculation

- ◆ The capacitor discharges to 1.67 V (or 1/3 of V_{CC}), when it transitions back to its stable state. Set the capacitor voltage expression equal to 1.67 V and solve the expression inversely for the time t required to discharge the capacitor to 1.67 V.

$$1.67 \text{ V} = 3.33 \text{ V} e^{-t/1 \text{ ms}} \rightarrow t = 0.693 \text{ ms}$$

$$T_L = 0.693 \text{ ms}$$

Astable Pulse Space Calculation


$$T = T_H + T_L$$

$$T = 1.386\text{ms} + 0.693\text{ ms}$$

$$T = 2.079\text{ ms}$$

$$f = 1/T$$

$$f = 481\text{ Hz}$$

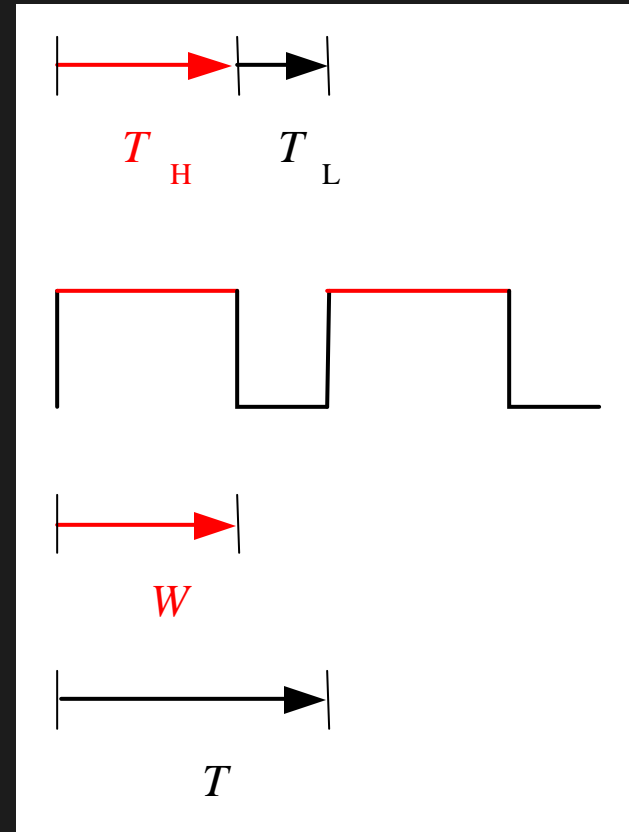

Overview

- ◆ **Multivibrators**
- ◆ **555 Timer**
- ◆ **555 Timer Monostable Multivibrators**
- ◆ **555 Timer Astable Multivibrators**