

# *Circuit Analysis*

## Lesson #1

# *Circuit Analysis*

- Circuit Elements
  - Passive Devices
  - Active Devices
- Circuit Analysis Tools
  - Ohms Law
  - Kirchhoff's Law
  - Impedances
  - Mesh and Nodal Analysis
  - Superposition
- Examples

## *Characterize Circuit Elements*

- **Passive Devices:** dissipates or stores energy
  - Linear
  - Non-linear
- **Active Devices:** Provider of energy or supports power gain
  - Linear
  - Non-linear

## *Circuit Elements – Linear Passive Devices*


- **Linear:** supports a linear relationship between the voltage across the device and the current through it.
  - **Resistor:** supports a voltage and current which are proportional, device dissipates heat, and is governed by Ohm's Law, units: resistance or ohms  $\Omega$



$V_R(t) = I_R(t)R$  where  $R$  is the value of the resistance associated with the resistor
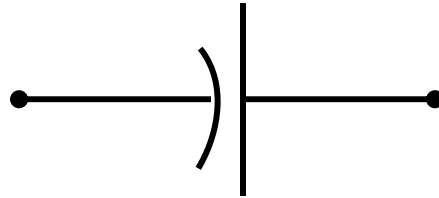
## *Circuit Elements – Linear Passive Devices*

- **Capacitor:** supports a current which is proportional to its changing voltage, device stores an electric field between its plates, and is governed by Gauss' Law, units: capacitance or farads,  $f$



$$I_C(t) = C \frac{dV_C(t)}{dt} \text{ where } C \text{ is the value of the capacitance associated with the capacitor}$$

## *Circuit Elements – Linear Passive Devices*

- **Inductor:** supports a voltage which is proportional to its changing current, device stores a magnetic field through its coils and is governed by Faraday's Law, units: inductance or henries,  $h$



$$V_L(t) = L \frac{dI_L(t)}{dt} \text{ where } L \text{ is the value of the inductance associated with the inductor}$$

## *Circuit Elements - Passive Devices Continued*


- **Non-linear:** supports a non-linear relationship among the currents and voltages associated with it
  - **Diodes:** supports current flowing through it in only one direction

## *Circuit Elements - Active Devices*

- **Linear**


- **Sources**

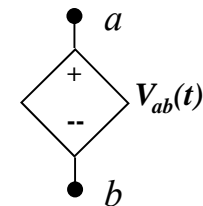- **Voltage Source:** a device which supplies a voltage as a function of time at its terminals which is independent of the current flowing through it, units: Volts



- DC, AC, Pulse Trains, Square Waves, Triangular Waves

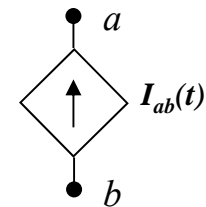- **Current Source:** a device which supplies a current as a function of time out of its terminals which is independent of the voltage across it, units: Amperes



- DC, AC, Pulse Trains, Square Waves, Triangular Waves




# Circuit Elements - Active Devices


## Continued
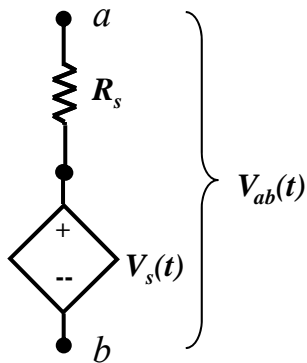
### – Ideal Sources vs Practical Sources

- An ideal source is one which only depends on the type of source (i.e., current or voltage)
- A practical source is one where other circuit elements are associated with it (e.g., resistance, inductance, etc. )



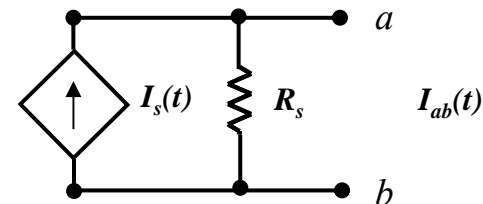
- A practical voltage source consists of an ideal voltage source connected in series with passive circuit elements such as a resistor
- A practical current source consists of an ideal current source connected in parallel with passive circuit elements such as a resistor




# *Circuit Elements - Active Devices*

## *Continued*

### – Independent vs Dependent Sources

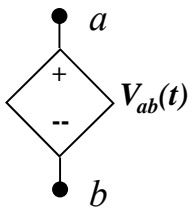

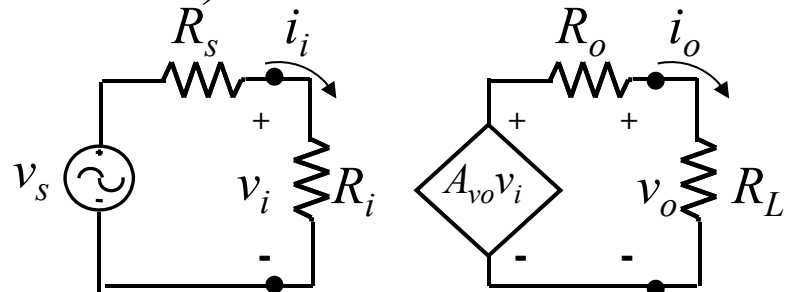- An independent source is one where the output voltage or current is not dependent on other voltages or currents in the device
- A dependent source is one where the output voltage or current is a function of another voltage or current in the device (e.g., a BJT transistor may be viewed as having an output current source which is dependent on the input current)



## *Circuit Elements - Active Devices* *Continued*

- **Non-Linear**
  - **Transistors:** three or more terminal devices where its output voltage and current characteristics are a function on its input voltage and/or current characteristics, several types BJT, FETs, etc.

## *Circuits*


- A circuit is a grouping of passive and active elements
- Elements may be connecting is series, parallel or combinations of both

## *Circuits Continued*

- Series Connection: Same current through the devices
  - The resultant resistance of two or more Resistors connected in series is the sum of the resistance
  - The resultant inductance of two or more Inductors connected in series is the sum of the inductances
  - The resultant capacitance of two or more Capacitors connected in series is the inverse of the sum of the inverse capacitances
  - The resultant voltage of two or more Ideal Voltage Sources connected in series is the sum of the voltages
  - Two or more Ideal Current sources can not be connected in series


## *Series Circuits*

- Resistors

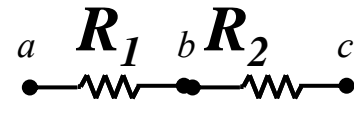


$$\begin{aligned}
 V_{ac} &= V_{ab} + V_{bc} = IR_1 + IR_2 \\
 R_T &= R_1 + R_2 \\
 &= I(R_1 + R_2) = IR_T
 \end{aligned}$$

- Inductors

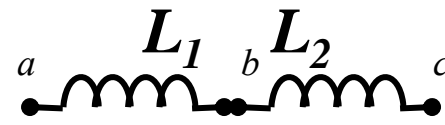

$$\begin{aligned}
 V_{ac} &= V_{ab} + V_{bc} = L_1 \frac{dI}{dt} + L_2 \frac{dI}{dt} \\
 L_T &= L_1 + L_2 \\
 &= (L_1 + L_2) \frac{dI}{dt} = L_T \frac{dI}{dt}
 \end{aligned}$$


- Capacitors

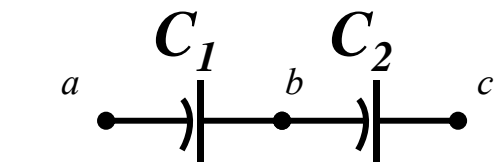

$$\begin{aligned}
 V_{ac} &= V_{ab} + V_{bc} = \frac{1}{C_1} \int Idt + \frac{1}{C_2} \int Idt \\
 C_T &= \frac{1}{\frac{1}{C_1} + \frac{1}{C_2}} = \frac{C_1 C_2}{C_1 + C_2} = \left( \frac{1}{C_1} + \frac{1}{C_2} \right) \int Idt = \frac{1}{C_T} \int Idt
 \end{aligned}$$

## *Series Circuits*

- Resistors

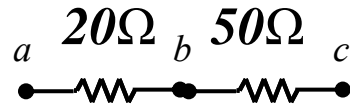


$$R_T = 20 + 50 = 70\Omega$$

$$\begin{aligned} V_{ac} &= V_{ab} + V_{bc} = I20 + I50 \\ &= I(20 + 50) = I70 \end{aligned}$$

## *Series Circuits*

- Inductors

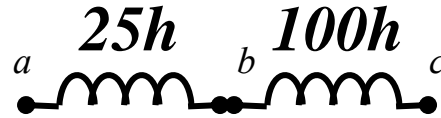


$$L_T = 25 + 100 = 125h$$

$$\begin{aligned} V_{ac} &= V_{ab} + V_{bc} = 25 \frac{dI}{dt} + 100 \frac{dI}{dt} \\ &= (25 + 100) \frac{dI}{dt} = 125 \frac{dI}{dt} \end{aligned}$$



## *Series Circuits*

- Capacitors

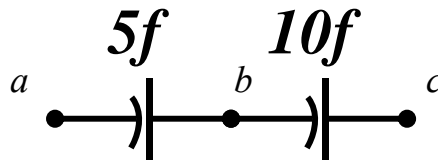


$$C_T = \frac{1}{\frac{1}{5} + \frac{1}{10}} = \frac{5 \times 10}{5 + 10} = \frac{50}{15} = \frac{10}{3} = 3.33 f$$

$$\begin{aligned} V_{ac} &= V_{ab} + V_{bc} = \frac{1}{5} \int Idt + \frac{1}{10} \int Idt \\ &= \left( \frac{1}{5} + \frac{1}{10} \right) \int Idt = \frac{3}{10} \int Idt \end{aligned}$$

## *Series Circuits*

- Capacitors

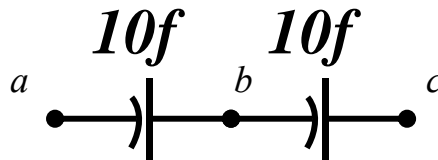

$$C_T = \frac{1}{\frac{1}{10} + \frac{1}{10}} = \frac{10 \times 10}{10 + 10} = \frac{100}{20} = \frac{10}{2} = 5f$$

$$\begin{aligned} V_{ac} &= V_{ab} + V_{bc} = \frac{1}{10} \int Idt + \frac{1}{10} \int Idt \\ &= \left( \frac{1}{10} + \frac{1}{10} \right) \int Idt = \frac{2}{10} \int Idt = \frac{1}{5} \int Idt \end{aligned}$$


## *Circuits Continued*

- Parallel Connection: Same Voltage across the devices
  - The resultant resistance of two or more Resistors connected in parallel is the inverse of the sum of the inverse resistances
  - The resultant inductance of two or more Inductors connected in parallel is the inverse of the sum of the inverse inductances
  - The resultant capacitance of two or more Capacitors connected in parallel is the sum of the capacitances
  - The resultant current of two or more Ideal Current Sources connected in parallel is the sum of the currents
  - Two or more Ideal Voltage sources can not be connected in parallel
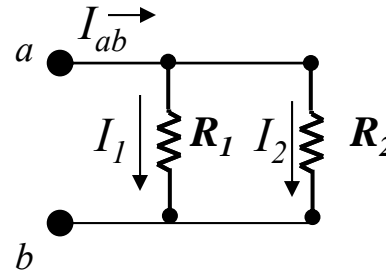
## Parallel Circuits

- Resistors

$$R_T = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2}} = \frac{R_1 R_2}{R_1 + R_2}$$




$$I_{ab} = I_1 + I_2 = \frac{V}{R_1} + \frac{V}{R_2}$$

$$= \left(\frac{1}{R_1} + \frac{1}{R_2}\right)V = \frac{V}{R_T}$$

- Inductors
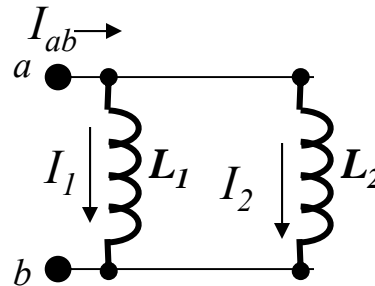
$$L_T = \frac{1}{\frac{1}{L_1} + \frac{1}{L_2}} = \frac{L_1 L_2}{L_1 + L_2}$$




$$I_{ab} = I_1 + I_2 = \frac{1}{L_1} \int V dt + \frac{1}{L_2} \int V dt$$

$$= \left(\frac{1}{L_1} + \frac{1}{L_2}\right) \int V dt = \frac{1}{L_T} \int V dt$$

- Capacitors

$$C_T = C_1 + C_2$$

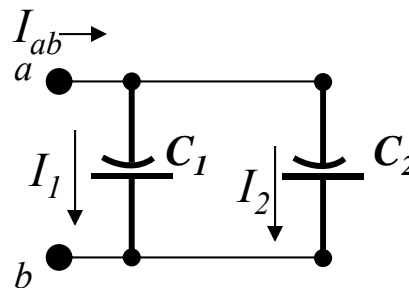

$$I_{ab} = I_1 + I_2 = C_1 \frac{dV}{dt} + C_2 \frac{dV}{dt}$$

$$= (C_1 + C_2) \frac{dV}{dt} = C_T \frac{dV}{dt}$$

## *Combining Circuit Elements*

### *Kirchhoff's Laws*


- Kirchhoff Voltage Law: The sum of the voltages around a loop must equal zero
- Kirchhoff Current Law: The sum of the currents leaving (entering) a node must equal zero

## Combining $R_s$ , $L_s$ and $C_s$

- We can use KVL or KCL to write and solve an equation associated with the circuit.
  - Example: a series Resistive Circuit

$$V(t) = I(t)R_1 + I(t)R_2$$

$$V(t) = I(t)(R_1 + R_2)$$

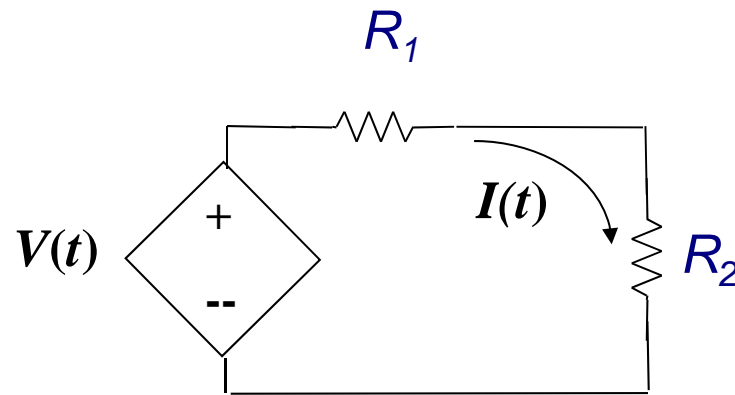

## Combining $R_s$ , $L_s$ , and $C_s$


- We can use KVL or KCL to write and solve an equation associated with the circuit.
  - Example: a series Resistive Circuit

$$I_1(t) + I_2(t) + I_3(t) = 0$$

$$I_2(t) = -V(t)/R_1; \quad I_3(t) = -V(t)/R_2;$$


$$I_1(t) - V(t)/R_1 - V(t)/R_2 = 0$$
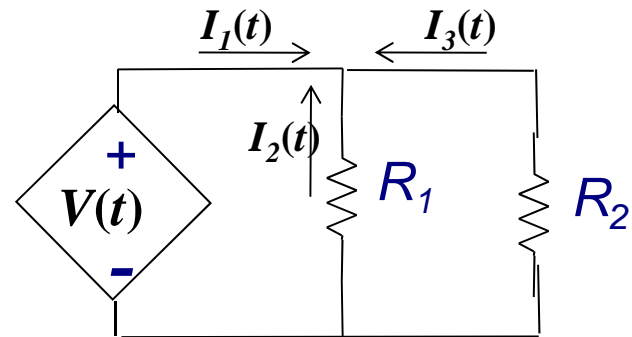
$$I_1(t) = V(t)/R_1 + V(t)/R_2 = V(t)[1/R_1 + 1/R_2]$$



## *Series Circuits*

- Resistors

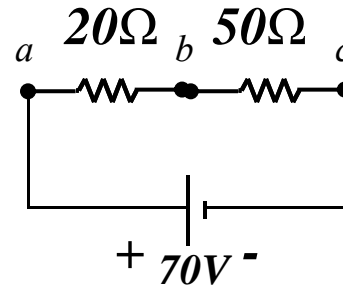

$$R_T = 20 + 50 = 70\Omega$$

$$\begin{aligned} V_{ac} &= V_{ab} + V_{bc} = I20 + I50 \\ &= I(20 + 50) = I70 = 70V \end{aligned}$$


$$I = 1A$$



## *Combining Rs, Ls and Cs*

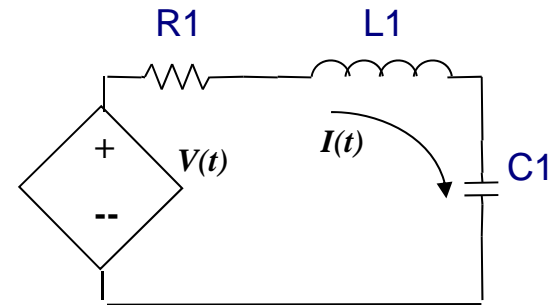- Example: a series RLC circuit

$$V(t) = I(t)R_1 + L_1 \frac{dI(t)}{dt} + \frac{1}{C_1} \int I(t)dt$$



- Or to simplify this analysis, we can concentrate on special cases

## *Impedances*

- Our special case, signals of the form:  $V(t)$  or  $I(t) = Ae^{st}$  where  $s$  can be a real or complex number

$$V(t) = I(t)R_1 + L_1 \frac{dI(t)}{dt} + \frac{1}{C_1} \int I(t)dt$$

Let's assume :

$$V(t) = 10e^{5t}; R_1 = 10\Omega; L_1 = 5h; C_1 = .2f$$

Let's try :

$$I(t) = Ae^{5t}$$

$$10e^{5t} = I(t)10 + 5 \frac{dI(t)}{dt} + \frac{1}{.2} \int I(t)dt$$

$$10e^{5t} = Ae^{5t}10 + 5 \frac{dAe^{5t}}{dt} + 5 \int Ae^{5t} dt$$

$$10e^{5t} = A(e^{5t}10 + 5 \times 5e^{5t} + \frac{5e^{5t}}{5})$$

$$= A(e^{5t} 36)$$

$$A = \frac{10}{36}; I(t) = \frac{10}{36} e^{5t}$$

- This is only one portion of the solution and does not include the transient response.

## *Impedances*

- Since the derivative [and integral] of  $Ae^{st} = sAe^{st}$  [ $= (1/s)Ae^{st}$ ], we can define the impedance of a circuit element as  $Z(s) = V/I$  where  $Z$  is only a function of  $s$  since the time dependency drops out.

# *Impedances*

For an inductor, let's assume  $I(t) = Ae^{st}$ ; then  $V(t) = L \frac{dI(t)}{dt} = LsAe^{st}$ ;

$$Z(s) = \frac{V}{I} = \frac{sLAe^{st}}{Ae^{st}} = sL$$

For a capacitor, let's assume  $V(t) = Ae^{st}$ ; then  $I(t) = C \frac{dV(t)}{dt} = CsAe^{st}$ ;

$$Z(s) = \frac{V}{I} = \frac{Ae^{st}}{sCAe^{st}} = \frac{1}{sC}$$

For a resistor, let's assume  $I(t) = Ae^{st}$ ; then  $V(t) = RI(t) = RAe^{st}$ ;

$$Z(s) = \frac{V}{I} = \frac{RAe^{st}}{Ae^{st}} = R$$

## *Impedances*

- What about signals of the type:  $\cos(\omega t + \theta)$ ;
- Recall Euler's formula  $e^{j\theta} = \cos \theta + j \sin \theta$   
where  $j$  is the imaginary number  $= \sqrt{-1}$
- A special case of our special case is for sinusoidal inputs, where  $s = j\omega$

## *Complex Numbers*

- Complex numbers: What are they?
- What is the solution to this equation?

$$ax^2+bx+c=0$$

- This is a second order equation whose solution is:

$$x_{1,2} = \frac{-b \pm \sqrt{b^2 - 4ac}}{2a}$$

*What is the solution to?*

1.  $x^2+4x+3=0$

$$\begin{aligned}x_{1,2} &= \frac{-4 \pm \sqrt{4^2 - 4 \times 3}}{2} = \frac{-4 \pm \sqrt{16 - 12}}{2} \\ &= \frac{-4 \pm \sqrt{4}}{2} = \frac{-4 \pm 2}{2} = -1, -3\end{aligned}$$

*What is the solution to?*

2.  $x^2+4x+5=0$

$$\begin{aligned}x_{1,2} &= \frac{-4 \pm \sqrt{4^2 - 4 \times 5}}{2} = \frac{-4 \pm \sqrt{16 - 20}}{2} \\ &= \frac{-4 \pm \sqrt{-4}}{2} \text{ ??????}\end{aligned}$$



## *What is the Square Root of a Negative Number?*

- We define the square root of a negative number as an imaginary number
- We define  
 $\sqrt{-1} \Rightarrow j$  for engineers ( $i$  for mathematicians)


- Then our solution becomes:

$$\begin{aligned}x_{1,2} &= \frac{-4 \pm \sqrt{4^2 - 4 \times 5}}{2} = \frac{-4 \pm \sqrt{16 - 20}}{2} \\ &= \frac{-4 \pm \sqrt{-4}}{2} = \frac{-4 \pm j\sqrt{4}}{2} = \frac{-4 \pm j2}{2} = -2 + j1, -2 - j1\end{aligned}$$

## *The Complex Plane*

- $z = x+jy$  is a complex number where:
  - $x = \text{Re}\{z\}$  is the real part of  $z$
  - $y = \text{Im}\{z\}$  is the imaginary part of  $z$
- We can define the complex plane and we can define 2 representations for a complex number:

$$z = x+jy$$

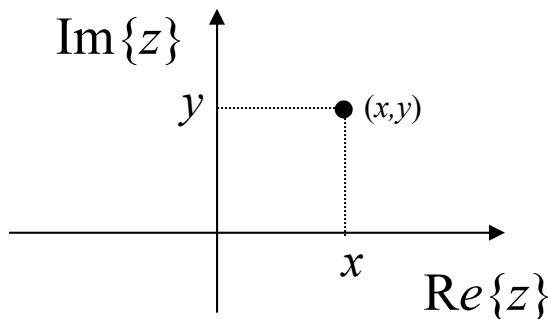

## *Rectangular Form*


- Rectangular (or cartesian) form of a complex number is given as

$$z = x + jy$$

$x = \text{Re}\{z\}$  is the real part of  $z$

$y = \text{Im}\{z\}$  is the imaginary part of  $z$


$$z = x + jy$$

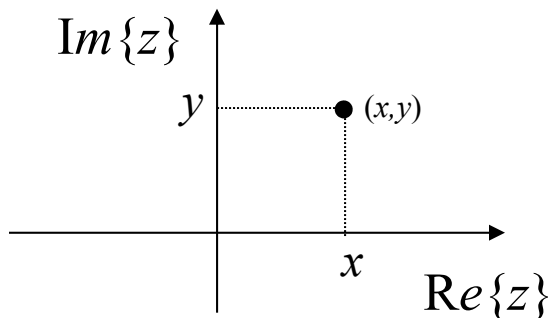

**Rectangular or Cartesian**
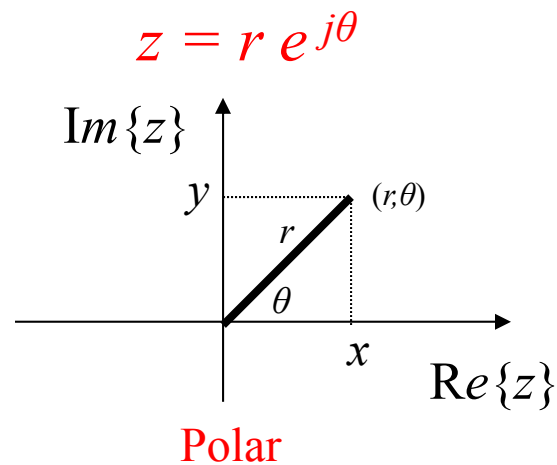
## *Polar Form*

- $z = r e^{j\theta} = r \angle \theta$  is a complex number where:
- $r$  is the magnitude of  $z$
- $\theta$  is the angle or argument of  $z$  (**arg  $z$** )



## *Relationships between the Polar and Rectangular Forms*

$$z = x + jy = r e^{j\theta}$$

- Relationship of Polar to the Rectangular Form:

$$x = \operatorname{Re}\{z\} = r \cos \theta$$

$$y = \operatorname{Im}\{z\} = r \sin \theta$$

- Relationship of Rectangular to Polar Form:

$$r = \sqrt{x^2 + y^2} \quad \text{and} \quad \theta = \arctan\left(\frac{y}{x}\right)$$

## *Addition of 2 complex numbers*


- When two complex numbers are added, it is best to use the rectangular form.
- The real part of the sum is the sum of the real parts and imaginary part of the sum is the sum of the imaginary parts.
- Example:  $z_3 = z_1 + z_2$

$$z_1 = x_1 + jy_1; z_2 = x_2 + jy_2$$

$$z_3 = z_1 + z_2 = x_1 + jy_1 + x_2 + jy_2$$


$$= x_1 + x_2 + jy_1 + jy_2$$

$$= (x_1 + x_2) + j(y_1 + y_2)$$

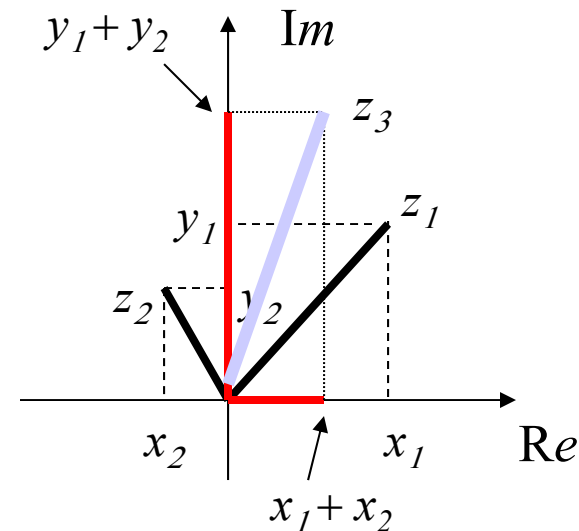

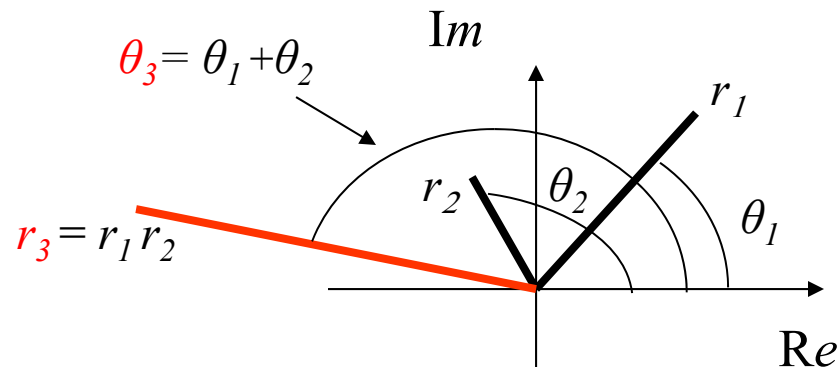
## Multiplication of 2 complex numbers

- When two complex numbers are multiplied, it is best to use the polar form:
- Example:  $z_3 = z_1 \times z_2$   
$$z_1 = r_1 e^{j(\theta_1)}; z_2 = r_2 e^{j(\theta_2)}$$
$$z_3 = z_1 \times z_2 = r_1 e^{j(\theta_1)} \times r_2 e^{j(\theta_2)}$$
$$= r_1 r_2 e^{j(\theta_1)} e^{j(\theta_2)} = r_1 r_2 e^{j(\theta_1 + \theta_2)}$$
- We multiply the magnitudes and add the phase angles


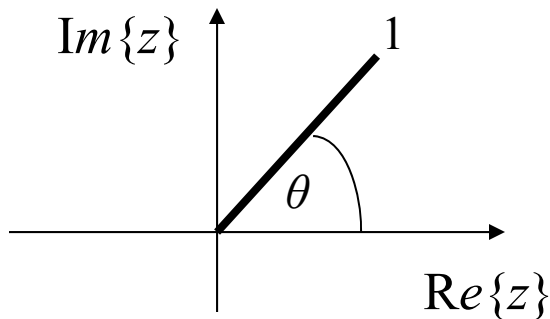
## *Euler's Formula*

$$e^{j\theta} = \cos \theta + j \sin \theta$$



- We can use Euler's Formula to define complex numbers

$$\begin{aligned} z &= r e^{j\theta} = r \cos \theta + j r \sin \theta \\ &= x + j y \end{aligned}$$



## *Complex Exponential Signals*

- A complex exponential signal is define as:

$$z(t) = Ae^{j(\omega_o t + \phi)}$$

- Note that it is defined in polar form where
  - the magnitude of  $z(t)$  is  $|z(t)| = A$
  - the angle (or argument,  $\arg z(t)$  ) of  $z(t) = (\omega_o t + \phi)$ 
    - Where  $\omega_o$  is called the radian frequency and  $\phi$  is the phase angle (phase shift)

## *Complex Exponential Signals*

- Note that by using Euler's formula, we can rewrite the complex exponential signal in rectangular form as:



$$\begin{aligned}z(t) &= Ae^{j(\omega_o t + \phi)} \\ &= A \cos(\omega_o t + \phi) + jA \sin(\omega_o t + \phi)\end{aligned}$$

- Therefore real part is the cosine signal and imaginary part is a sine signal both of radial frequency  $\omega_o$  and phase angle of  $\phi$
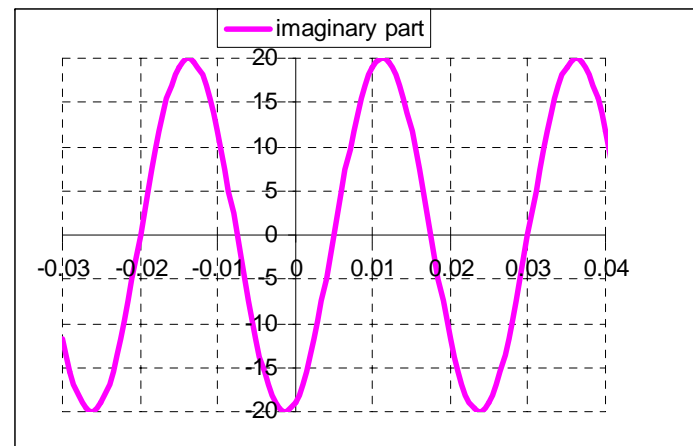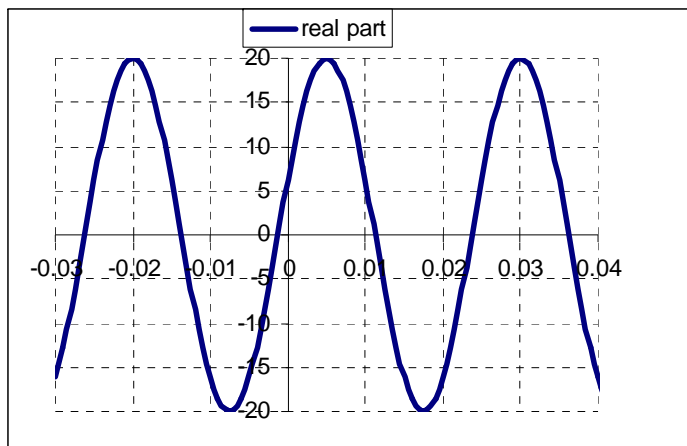
## *Plotting the waveform of a complex exponential signal*

- For an complex signal, we plot the real part and the imaginary part separately.
- Example:

$$\begin{aligned} z(t) &= 20e^{j(2\pi(40)t-0.4\pi)} = 20e^{j(80\pi t-0.4\pi)} \\ &= 20 \cos(80\pi t-0.4\pi) + j20 \sin(80\pi t-0.4\pi) \end{aligned}$$



## *NOTE!!!!*

- The reason why we prefer the complex exponential representation of the real cosine signal:

$$\begin{aligned}x(t) &= \Re\{z(t)\} = \Re\{Ae^{j(\omega_0 t + \phi)}\} \\ &= A \cos(\omega_0 t + \phi)\end{aligned}$$

- In solving equations and making other calculations, it is easier to use the complex exponential form and then take the Real Part.

## Complex Exponential Function as a function of time

- Let's look at this  $z(t) = 1e^{j2\pi(1)t} = e^{j2\pi t} = \cos 2\pi t + j \sin 2\pi t$

$t=8/8$  seconds

$$\arg(z(t))=2\pi \times 8/8 = 2\pi ; z(t) = 1 + j0$$

$t=2/8$  seconds

$$\arg(z(t))=2\pi \times 2/8 = \pi/2; z(t) = 0 + j1$$

$t=3/8$  seconds

$$\arg(z(t))=2\pi \times 3/8 = 3\pi/4;$$

$$z(t) = -0.707 + j0.707$$


$t=4/8$  seconds

$$\arg(z(t))=2\pi \times 4/8 = \pi; z(t) = -1 + j0$$

$t=5/8$  seconds

$$\arg(z(t))=2\pi \times 5/8 = 5\pi/4;$$

$$z(t) = -0.707 - j0.707$$

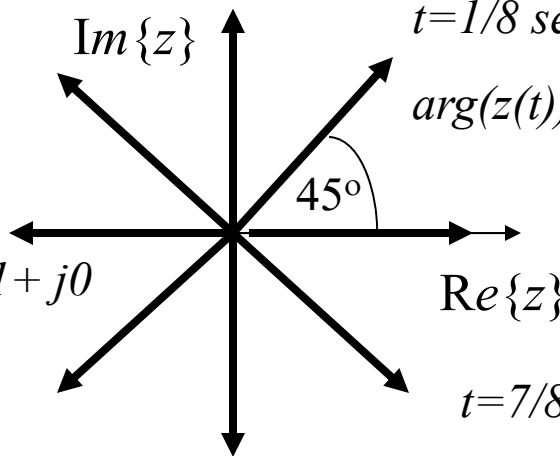

$t=1/8$  seconds

$$\arg(z(t))=2\pi \times 1/8 = \pi/4; z(t) = 0.707 + j 0.707$$

$t=0$  seconds

$$\arg(z(t))=2\pi \times 0 = 0; z(t) = 1 + j0$$

$\text{Re}\{z\}$

$t=7/8$  seconds

$$\arg(z(t))=2\pi \times 7/8 = 7\pi/4;$$

$$z(t) = 0.707 - j0.707$$

$t=6/8$  seconds

$$\arg(z(t))=2\pi \times 6/8 = 3\pi/2; z(t) = 0 - j$$

## *Phasor Representation of a Complex Exponential Signal*

- Using the multiplication rule, we can rewrite the complex exponential signal as

$$z(t) = Ae^{j(\omega_0 t + \phi)} = Ae^{j\omega_0 t} e^{j\phi} = Ae^{j\phi} e^{j\omega_0 t} = \mathbf{X}e^{j\omega_0 t}$$


where  $\mathbf{X}$  is a complex number equal to

$$\mathbf{X} = Ae^{j\phi}$$

- $\mathbf{X}$  is complex amplitude of the complex exponential signal and is also called a **phasor**

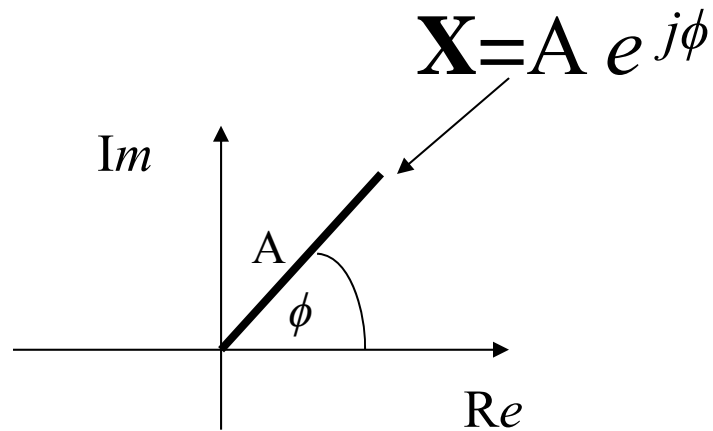
## *Graphing a phasor*

- $\mathbf{X} = A e^{j\phi}$  can be graphed in the complex plane with magnitude  $A$  and angle  $\phi$ :


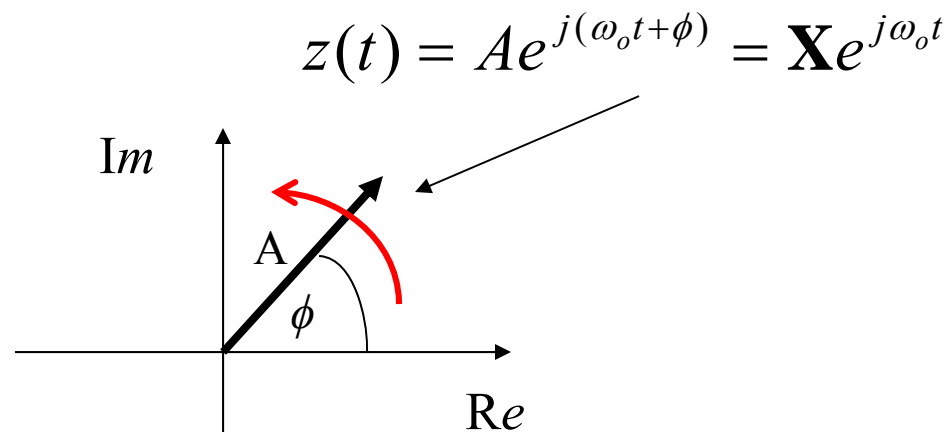
## *Graphing a Complex Signal in terms of its phasors*


- Since a complex signal,  $z(t)$ , is a phasor multiplying a complex exponential signal  $e^{j\omega_o t}$ , then a complex signal can be viewed as a phasor rotating in time:




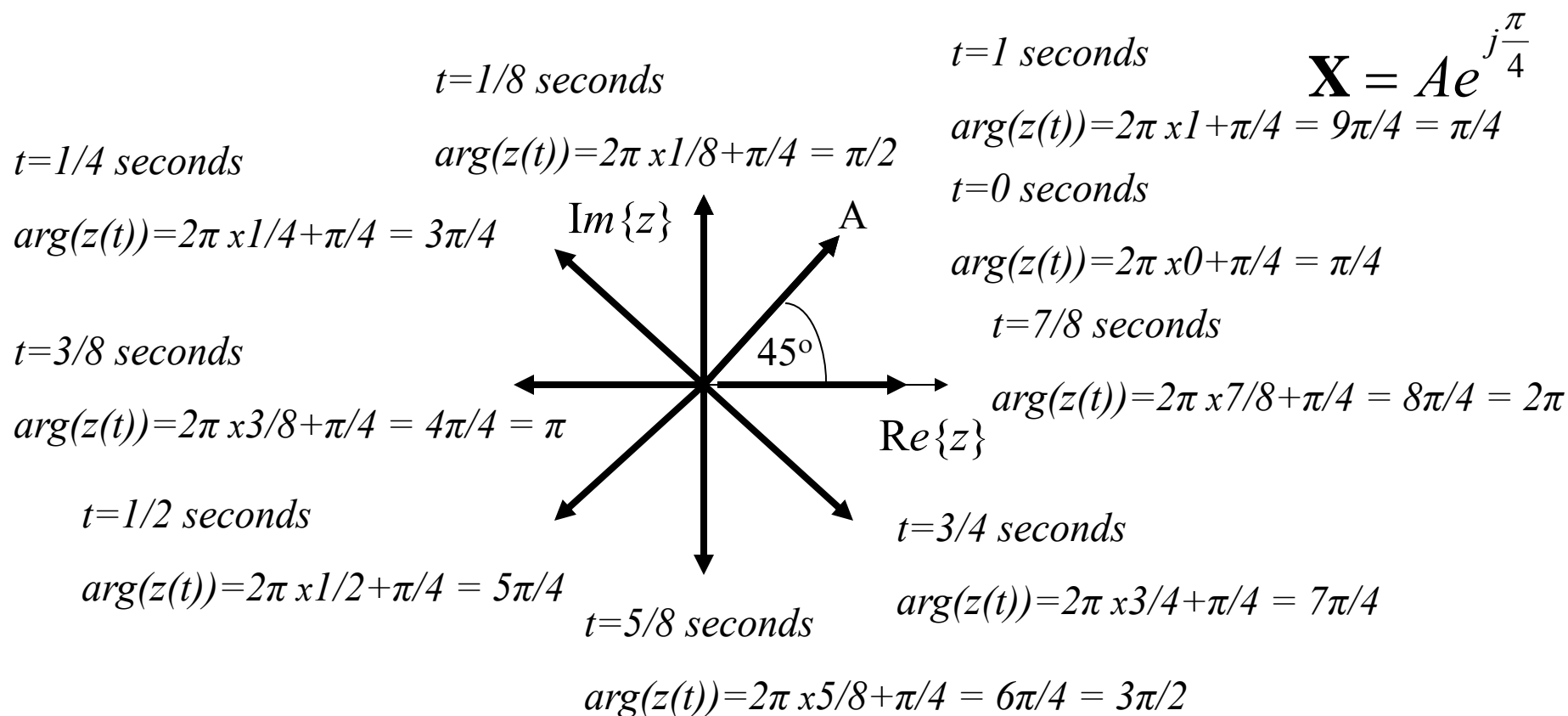
## Rotating Phasor

- Let's look at this  $z(t) = Ae^{j(2\pi t + \frac{\pi}{4})} = Ae^{j\frac{\pi}{4}} e^{j2\pi t} = \mathbf{X}e^{j2\pi t}$



## *Sinusoidal Steady State*

- If  $V(t) = A \cos(\omega t + \theta)$ , then we can represent  $V(t)$  as



$$\operatorname{Re}\{Ae^{j(\omega t + \theta)}\} = \operatorname{Re}\{Ae^{j\theta} e^{j\omega t}\}$$

Since from Euler's formula:

$$A e^{j(\omega t + \theta)} = A \cos(\omega t + \theta) + j A \sin(\omega t + \theta)$$
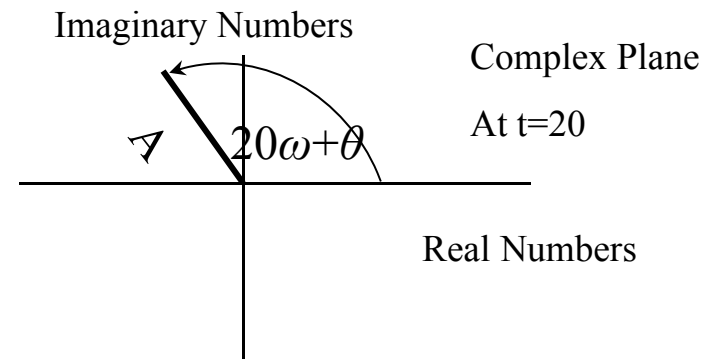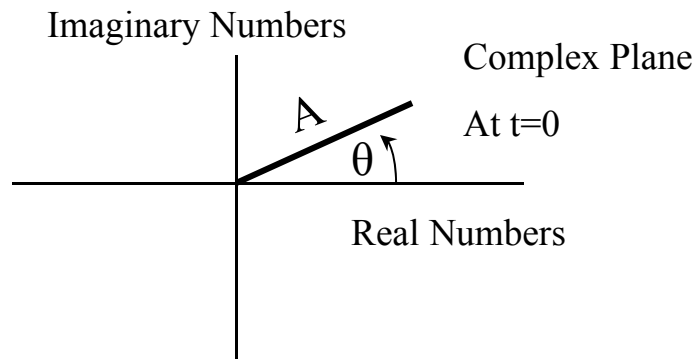
# Sinusoidal Steady State

- What is  $Ae^{j(\omega t + \theta)}$  ?
  - First, it is a complex function since it is a function of a complex number. If we plot on the complex plane, it has a magnitude of  $A$  and angle of  $\omega t + \theta$ . It can be viewed as a vector which rotates in time around the origin of the complex plane at angular velocity  $\omega$  and at  $t=0$  is at  $\theta$  degrees from the real axis.



- We can **represent** this function by a **PHASOR** in terms of rectangular coordinates or polar coordinates

*MAGNITUDE*  $\angle$  *ANGLE* (phasor notation)  $\Rightarrow$  or in this case  $V = A \angle \theta$

## *Sinusoidal Steady State Continued*

- We define the Voltage phasor as  $\mathbf{V}$  and current phasor as  $\mathbf{I}$
- Define SSS impedance as  $Z = \mathbf{V} / \mathbf{I}$  using Ohm's Law
- Then the impedances become:

– For an inductor  $V = j\omega L I$

$Z_L = j\omega L \Rightarrow \omega L \angle \frac{\pi}{2}$ ; Here we say the voltage across an inductor leads the current through it by  $90^\circ$ .

– For a capacitor  $V = \frac{1}{j\omega C} I$


$Z_C = \frac{1}{j\omega C} \Rightarrow \frac{1}{\omega C} \angle -\frac{\pi}{2}$ ; Here we say the voltage across a capacitor lags the current through it by  $90^\circ$ .

– For a resistor  $V = R I$

$Z_R = R \Rightarrow R \angle 0$ ; Here we say the voltage across a resistor is in phase with the current through it.
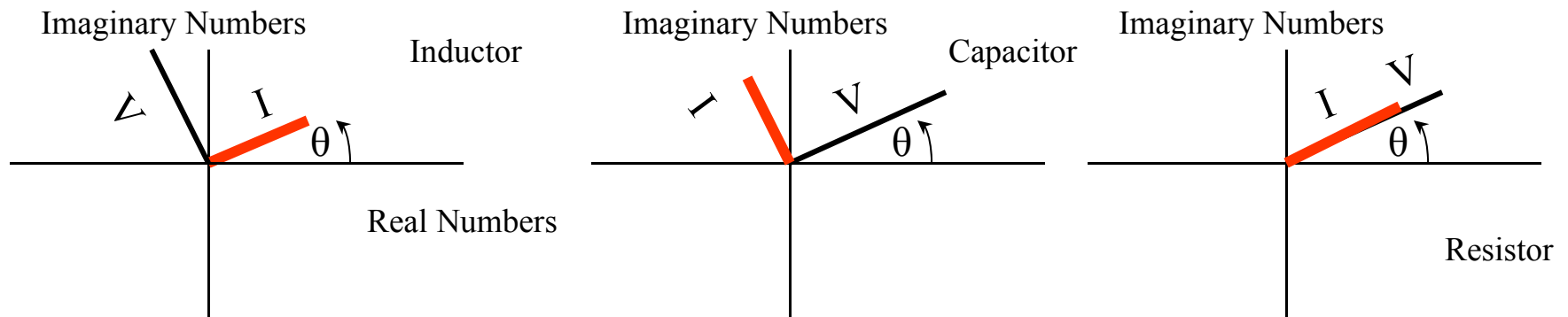
## *Sinusoidal Steady State Continued*

- For an inductor,  $Z_L = j\omega L \Rightarrow \omega L \angle \frac{\pi}{2}$
- For a capacitor,  $Z_C = \frac{1}{j\omega C} \Rightarrow \frac{1}{\omega C} \angle -\frac{\pi}{2}$ .
- For a resistor,  $Z_R = R \Rightarrow R \angle 0$



## *Sinusoidal Steady State Continued*

For  $V(t) = A \cos \omega t$ , using phasor notation for  $V(t) \rightarrow \mathbf{V} = A \angle 0$  and  $I(t) \rightarrow \mathbf{I}$ , our equation can be re-written:

$$V(t) = I(t)R_1 + L_1 \frac{dI(t)}{dt} + \frac{1}{C_1} \int I(t) dt$$

Converting to Phasor representation

$$\mathbf{V} = A \angle 0 = \mathbf{I}R_1 + j\omega L_1 \mathbf{I} + \frac{1}{j\omega C_1} \mathbf{I}$$


## *Sinusoidal Steady State Continued*

$$\mathbf{I} = \frac{A\angle 0}{R_1 + j\omega L_1 + \frac{1}{j\omega C_1}} = \frac{A\angle 0}{R_1 + j(\omega L_1 - \frac{1}{\omega C_1})} = \frac{A}{\sqrt{R_1^2 + (\omega L_1 - \frac{1}{\omega C_1})^2}} \angle -\tan^{-1}\left[\frac{(\omega L_1 - \frac{1}{\omega C_1})}{R_1}\right]$$

Converting back to the time representation,

$$I(t) = \frac{A}{\sqrt{R_1^2 + (\omega L_1 - \frac{1}{\omega C_1})^2}} \cos(\omega t - \tan^{-1}\left[\frac{(\omega L_1 - \frac{1}{\omega C_1})}{R_1}\right])$$

# Homework

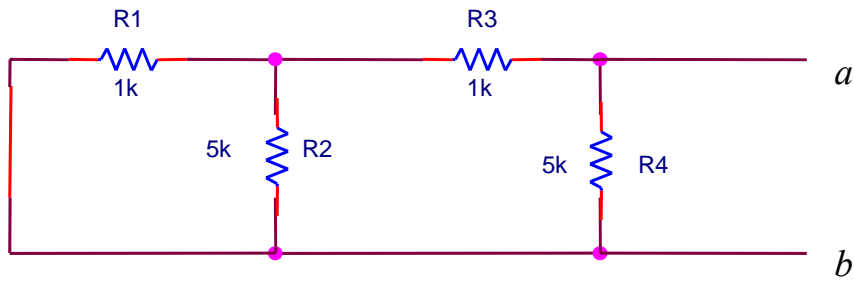


Find the total resistance


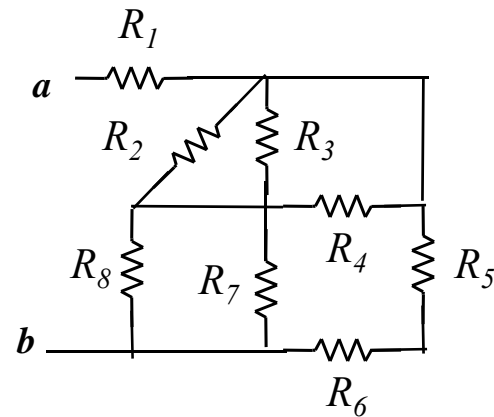
# Homework

Find the total resistance  $R_{ab}$  where


$$R_1 = 3\Omega, R_2 = 6\Omega, R_3 = 12\Omega, R_4 = 4\Omega, R_5 = 2\Omega, R_6 = 2\Omega, R_7 = 4\Omega, R_8 = 4\Omega$$


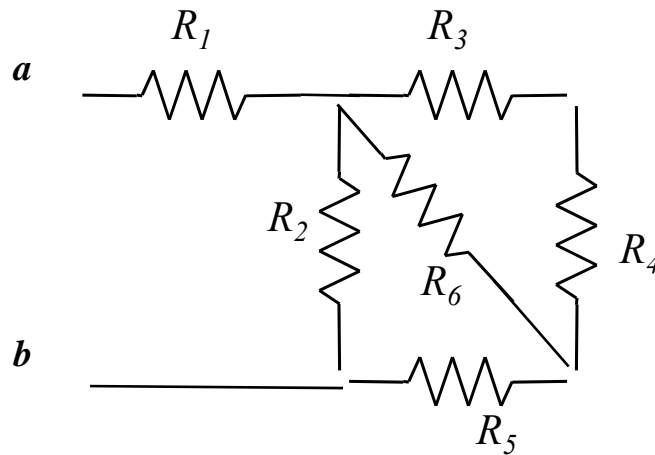
# Homework


Find the total resistance  $R_{ab}$  where

$$R_1 = 2\Omega, R_2 = 4\Omega, R_3 = 2\Omega, R_4 = 2\Omega, R_5 = 2\Omega, R_6 = 4\Omega,$$



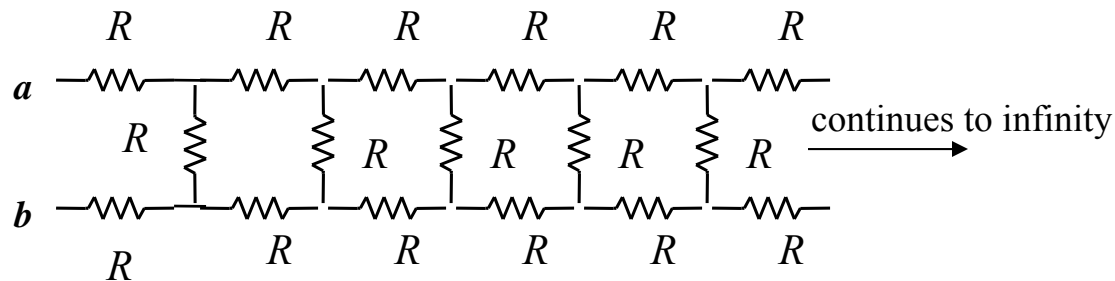
# Homework

Find the total resistance  $R_{ab}$  for this infinite resistive network




## Homework

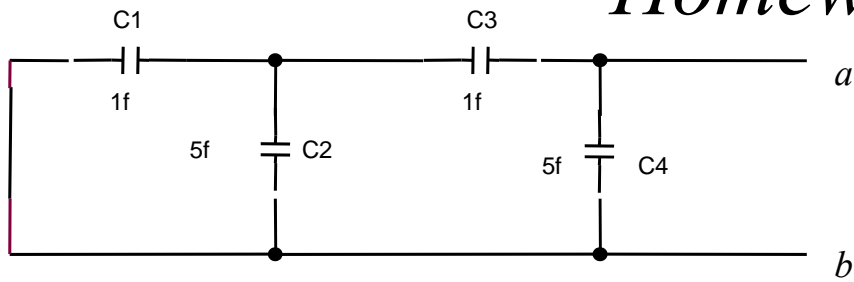

Find the total capacitance

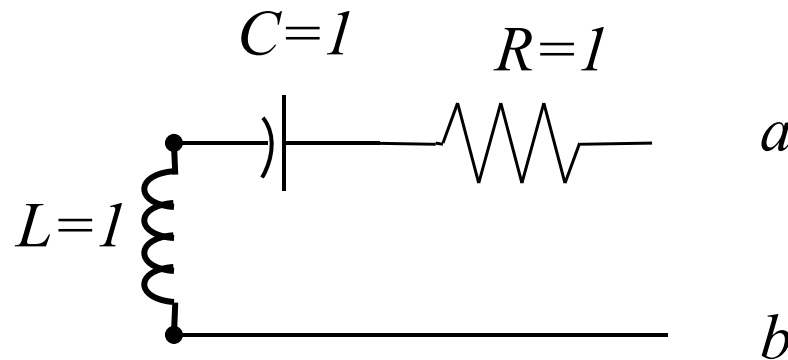
# Homework

Find and plot the impedance  $Z_{ab}(j\omega)$  as a function of frequency. Use Matlab to perform the plot.



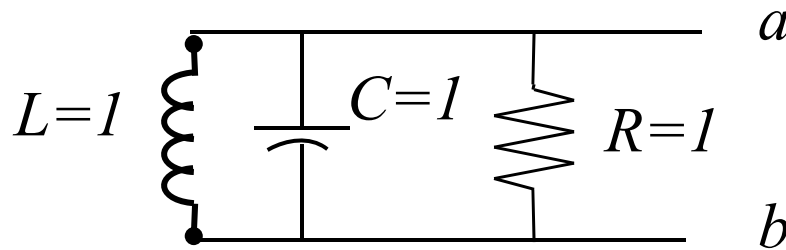
# Homework

Find and plot the impedance  $Z_{ab}(j\omega)$  as a function of frequency. Use Matlab to perform the plot.




## Homework

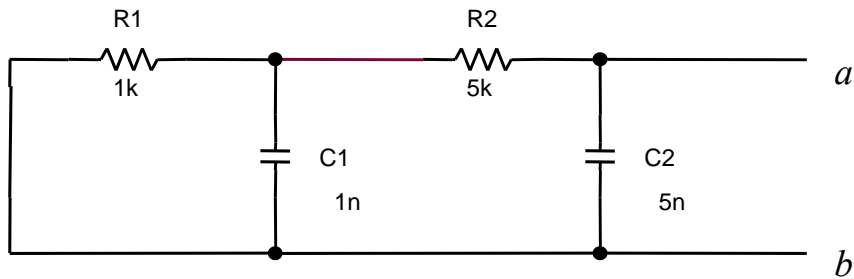

Find and plot the impedance  $Z_{ab}(j\omega)$  as function of  $\omega$ .  
Use Matlab to perform the plot.

# Homework

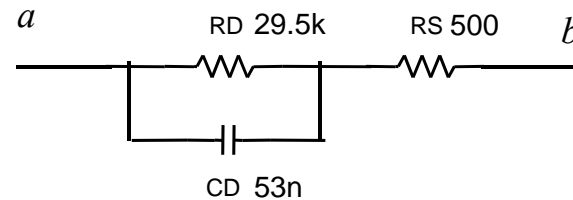

The circuit shown is an equivalent circuit of an electrode where  $R_D$  and  $C_D$  are the resistance and capacitance associated with the interface of the electrode and the body and  $R_S$  is the resistance of the device itself. Find and plot the impedance  $Z_{ab}(j\omega)$  as function of  $\omega$ . Use Matlab to perform the plot.