

Transistors

Lesson #10

Chapter 4

Small Signal Equivalent Circuits and Parameters for the BJT

- If the variable portion of the input signal is small (in amplitude), it is possible to approximate the (non-linear) transistor as a linear device by representing it by an equivalent circuit

- Here's how we do it:

- Recall $i_E = i_C + i_B$

- Define: $\alpha = \frac{i_C}{i_E}$; then $i_B = (1 - \alpha)i_E$

- and $i_C = \frac{\alpha}{1 - \alpha} i_B = \beta i_B$ where $\beta = \frac{\alpha}{1 - \alpha}$

- Since the base-emitter junction is a forward-biased diode and the current that crosses this junction is I_E , then we can use the Shockley equation

$$i_E = I_{ES} \left(e^{\frac{v_{BE}}{V_T}} - 1 \right)$$

Small Signal Equivalent Circuits and Parameters for the BJT

- Then: $i_B = (1 - \alpha)I_{ES} \left(e^{\frac{v_{BE}}{V_T}} - 1 \right)$
- Before we continue let's define the following notation:
 - A lower case signal (voltage or current) with upper case subscripts represents the total of the DC portion of the signal and the AC portion of the signal
 - An upper case signal with upper case subscripts represents the DC portion (the Q-point)
 - A lower case signal with lower case subscripts represents the AC portion

$$i_B(t) = I_{BQ} + i_b(t)$$
$$v_{BE}(t) = V_{BEQ} + v_{be}(t)$$

Small Signal Equivalent Circuits and Parameters for the BJT

$$i_B = (1 - \alpha) I_{ES} \left(e^{\frac{v_{BE}}{V_T}} - 1 \right)$$

$$I_{BQ} + i_b(t) = (1 - \alpha) I_{ES} \left(e^{\frac{V_{BE} + v_{be}(t)}{V_T}} - 1 \right)$$

Ignoring the -1 term since it is negligible compared to the exponential term

$$I_{BQ} + i_b(t) = (1 - \alpha) I_{ES} \left(e^{\frac{V_{BE}}{V_T}} e^{\frac{v_{be}(t)}{V_T}} \right)$$

Noting that the Q - point values must also satisfy the Shockley equation,

$$I_{BQ} = (1 - \alpha) I_{ES} e^{\frac{V_{BE}}{V_T}}$$

$$\therefore I_{BQ} + i_b(t) = I_{BQ} e^{\frac{v_{be}(t)}{V_T}}$$

Using the first two terms of the Taylor expansion of the exponential function : $e^x \approx 1 + x$

$$I_{BQ} + i_b(t) \approx I_{BQ} \left(1 + \frac{v_{be}(t)}{V_T} \right) = I_{BQ} + I_{BQ} \frac{v_{be}(t)}{V_T}$$

$$i_b(t) = I_{BQ} \frac{v_{be}(t)}{V_T}$$

Small Signal Equivalent Circuits and Parameters for the BJT

This is a relationship of the AC portion of the base current to the base - emitter voltage :

$$i_b(t) = I_{BQ} \frac{v_{be}(t)}{V_T} \Rightarrow v_{be}(t) = i_b(t) \frac{V_T}{I_{BQ}} = i_b(t) r_\pi$$

$$r_\pi = \frac{V_T}{I_{BQ}}$$

This resistance is a function of the Q - point and represents the input resistance of our equivalent circuit.

Secondly, since the collector current $i_c(t) = \beta i_b(t)$


$$I_C + i_c(t) = \beta I_B + \beta i_b(t)$$

$$\therefore i_c(t) = \beta i_b(t)$$


And we have a dependent current source in the collector to represent this relationship.

Small Signal Equivalent Circuits and Parameters for the BJT

- Here is our equivalent circuit:

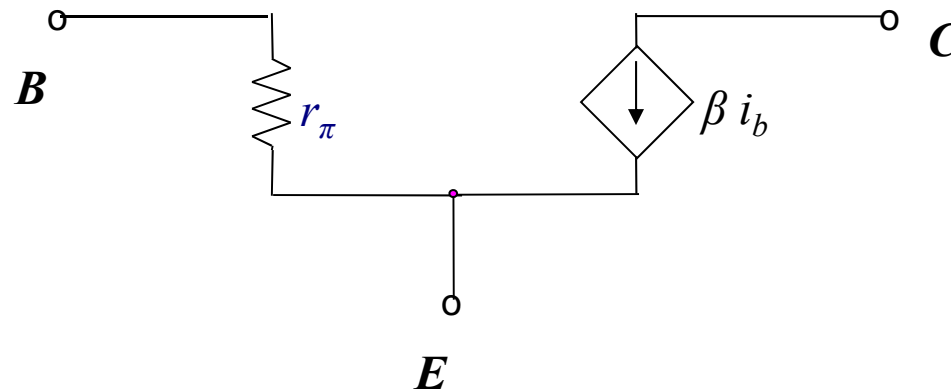


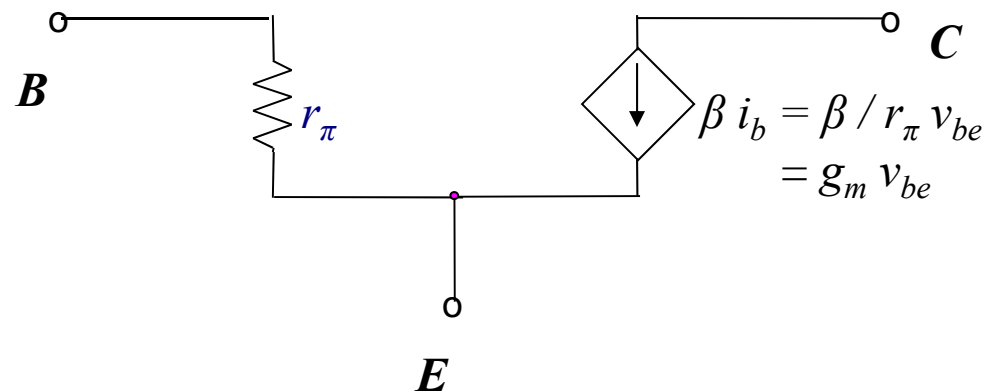- Here is a second version equivalent circuit:



Small Signal Equivalent Circuits


Example

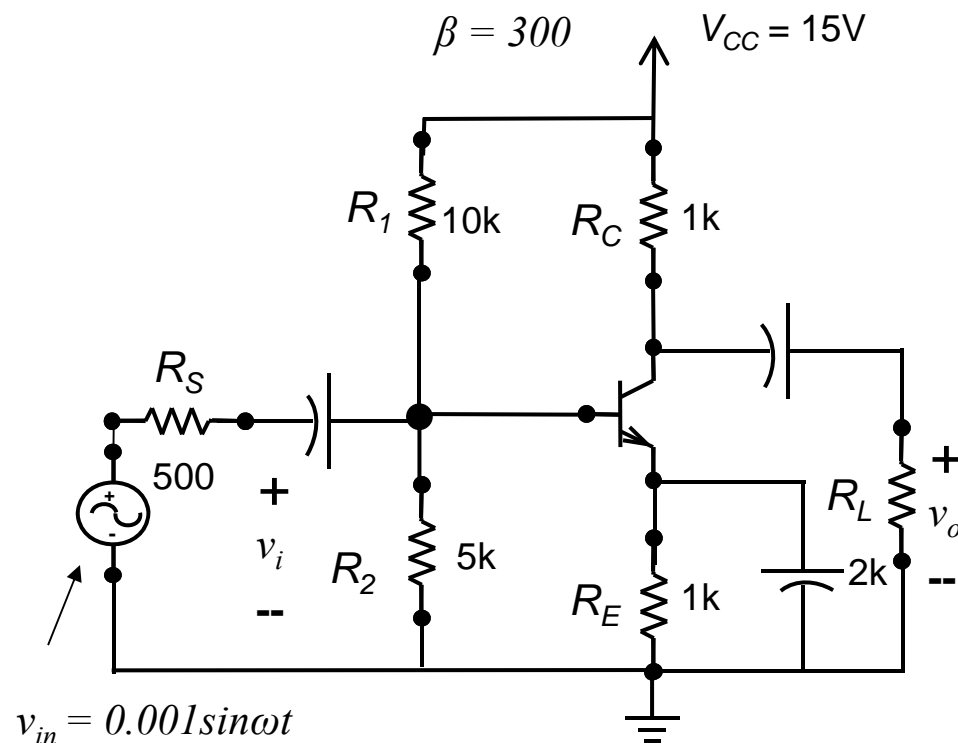

- We see that we have capacitors and extra resistors.
- The extra resistors represent
 - the load to the next stage (input impedance of the next stage)
 - the source resistance (output impedance of the previous stage)
- The extra capacitors are to:
 - protect the DC design of our amplifier
 - allow the passing the AC portion of the input signal from the source to our amplifier and on to the load (coupling capacitors)
 - eliminate the loading of the emitter resistor for the AC signal (bypass capacitors)

Small Signal Equivalent Circuits - Example


DC Analysis

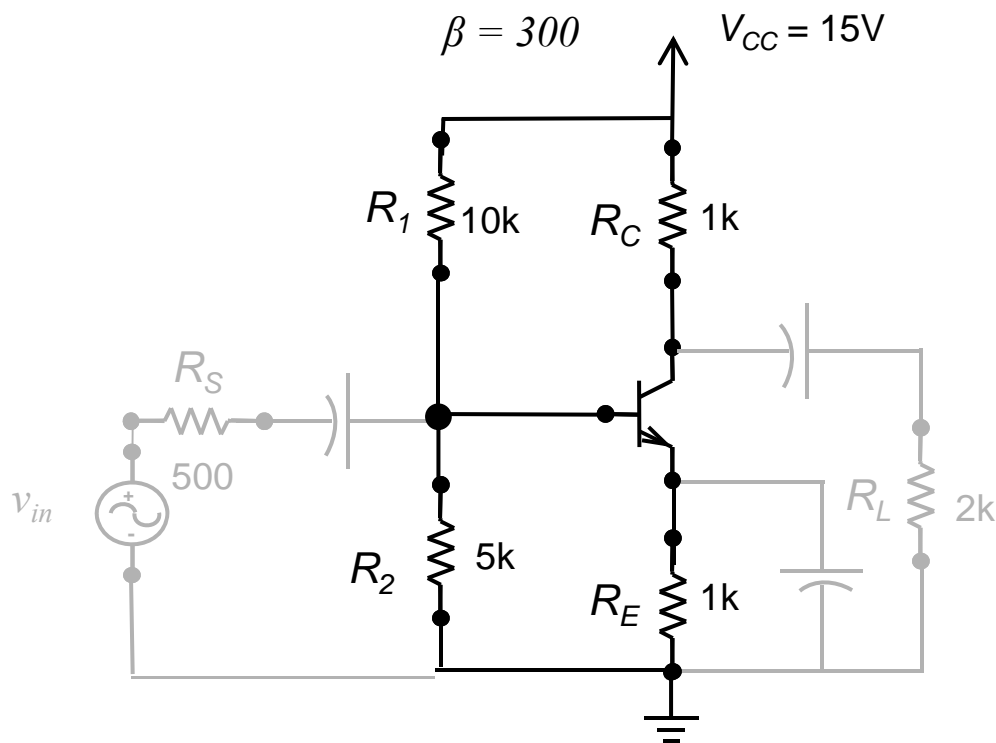

- For DC the capacitors are open-circuits so for DC analysis the circuit becomes the same circuit as we have just analyzed
- The components not affected by the DC voltage are “grayed out”.
- The next step is to perform the AC analysis.

Small Signal Equivalent Circuits-Example


AC Analysis

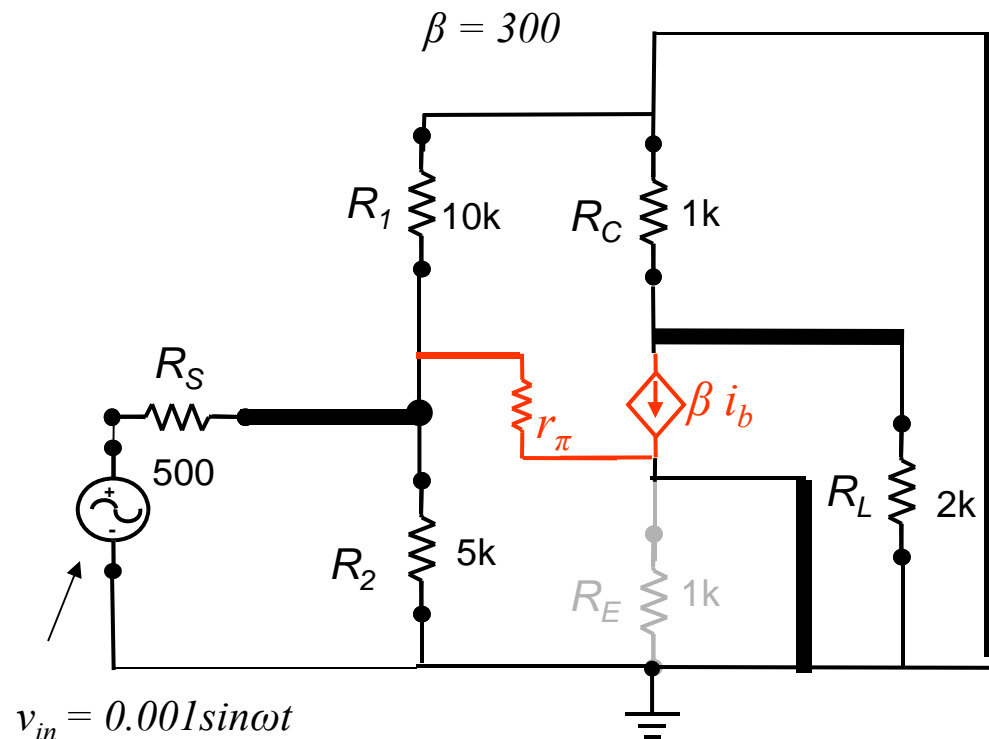


- The next step is to perform the AC analysis by
 - Shorting any DC voltage sources
 - Opening any DC current sources
 - Shorting the capacitors
 - Eliminating any resistors which are shorted by the capacitors (e.g., the emitter resistor)
 - Connecting the source, source resistance, and load resistance
 - Replace the transistor with its small signal equivalent circuit.
- Short circuits are drawn in thick lines, the removed capacitor is “greyed-out”, and the equivalent circuit is in red.
- This circuit looks too messy, let’s redraw

Small Signal Equivalent Circuits-Example

AC Analysis

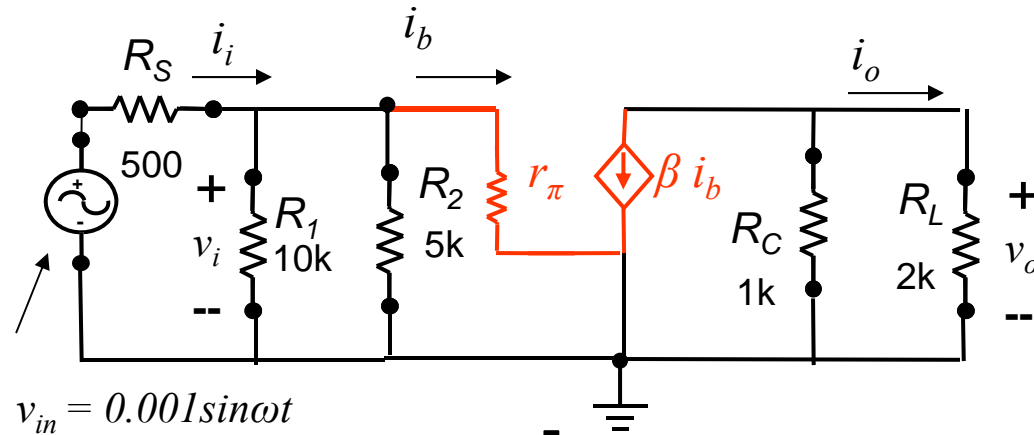

$$v_{in} = 0.001 \sin \omega t$$

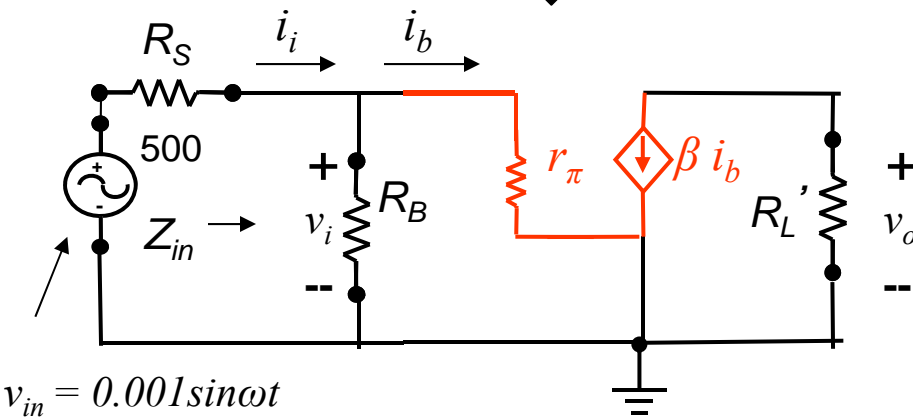

$$v_{in} = 0.001 \sin \omega t$$

$$R_L' = R_C \parallel R_L = \frac{R_C R_L}{R_C + R_L} = \frac{1 \times 2k}{1 + 2} = 667$$

$$R_B = R_1 \parallel R_2 = \frac{R_1 R_2}{R_1 + R_2} = \frac{5 \times 10k}{5 + 10} = 3.33k$$

$$r_\pi = \frac{V_T}{I_{BQ}} = \frac{26m}{14.1\mu} = 1844$$

$$v_o = -\beta i_b R_L'$$

$$v_i = i_b r_\pi$$

$$A_v = \frac{v_o}{v_i} = -\frac{\beta R_L'}{r_\pi} = -109$$

$$Z_{in} = R_B \parallel r_\pi = \frac{R_B r_\pi}{R_B + r_\pi} = 1.19k$$

$$i_o = \frac{v_o}{R_L} = \frac{-\beta i_b R_L'}{R_L} = -\frac{\beta R_L'}{R_L} \frac{v_i}{r_\pi} = A_v \frac{v_i}{R_L}$$


$$i_i = \frac{v_i}{Z_{in}}$$

$$A_i = \frac{i_o}{i_i} = A_v \frac{\frac{v_i}{R_L}}{\frac{v_i}{Z_{in}}} = A_v \frac{Z_{in}}{R_L} = -64.4$$

$$G = A_i A_v = 7000$$

Small Signal Equivalent Circuits-Example

AC Analysis Alternative Method for A_i

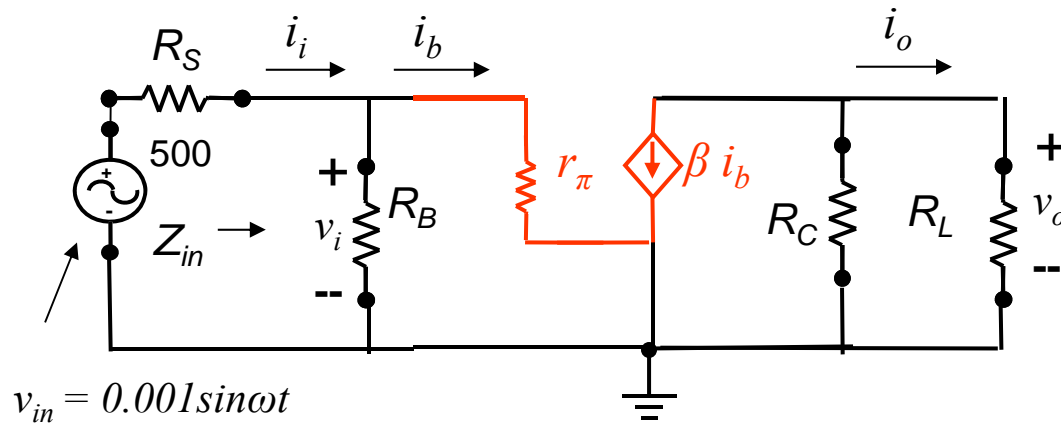

$$R_L' = R_C \parallel R_L = \frac{R_C R_L}{R_C + R_L} = \frac{1 \times 2k}{1 + 2} = 667$$

$$R_B = R_1 \parallel R_2 = \frac{R_1 R_2}{R_1 + R_2} = \frac{5 \times 10k}{5 + 10} = 3.33k$$

$$r_\pi = \frac{V_T}{I_{BQ}} = \frac{26m}{14.1\mu} = 1844$$

By current division

$$i_o = \frac{R_C}{R_C + R_L} (-\beta i_b)$$

$$i_b = \frac{R_B}{R_B + r_\pi} i_i$$

$$i_o = \frac{R_C}{R_C + R_L} \left(-\beta \frac{R_B}{R_B + r_\pi}\right) i_i$$

$$A_i = \frac{i_o}{i_i} = -\beta \frac{R_C}{R_C + R_L} \times \frac{R_B}{R_B + r_\pi}$$

$$= -300 \frac{1k}{1k + 2k} \times \frac{3.33k}{3.33k + 1.844k} = -64.36$$

Note they are the same:


$$A_i = A_v \frac{Z_{in}}{R_L} = -\frac{\beta R_L'}{r_\pi R_L} \times \frac{R_B r_\pi}{R_B + r_\pi}$$

$$= -\frac{\beta \frac{R_C R_L}{R_C + R_L}}{r_\pi R_L} \times \frac{R_B r_\pi}{R_B + r_\pi}$$

$$= -\beta \frac{R_C}{R_C + R_L} \times \frac{R_B}{R_B + r_\pi}$$

Small Signal Equivalent Circuits-Example

AC Analysis

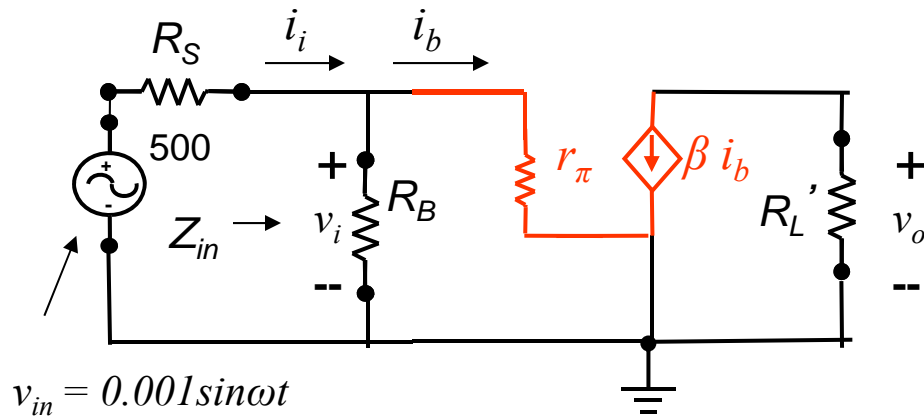

$$A_v = \frac{v_o}{v_i} = -\frac{\beta R_L'}{r_\pi} = -109$$

$$Z_{in} = R_B \parallel r_\pi = \frac{R_B r_\pi}{R_B + r_\pi} = 1.19k$$

$$A_{vs} = \frac{v_o}{v_{in}} = \frac{v_o}{v_i} \frac{v_i}{v_{in}}$$

$$v_i = \frac{Z_{in}}{Z_{in} + R_s} v_{in}$$


$$\frac{v_i}{v_{in}} = \frac{Z_{in}}{Z_{in} + R_s} = .7$$

$$A_{vs} = \frac{v_o}{v_{in}} = \frac{v_o}{v_i} \frac{v_i}{v_{in}} = A_v \frac{v_i}{v_{in}} = A_v \frac{Z_{in}}{Z_{in} + R_s} = -76.4$$

$$v_o = -76.4 v_i = -76.4 \sin \omega t \text{ mV}$$

Small Signal Equivalent Circuits-Example

AC Analysis

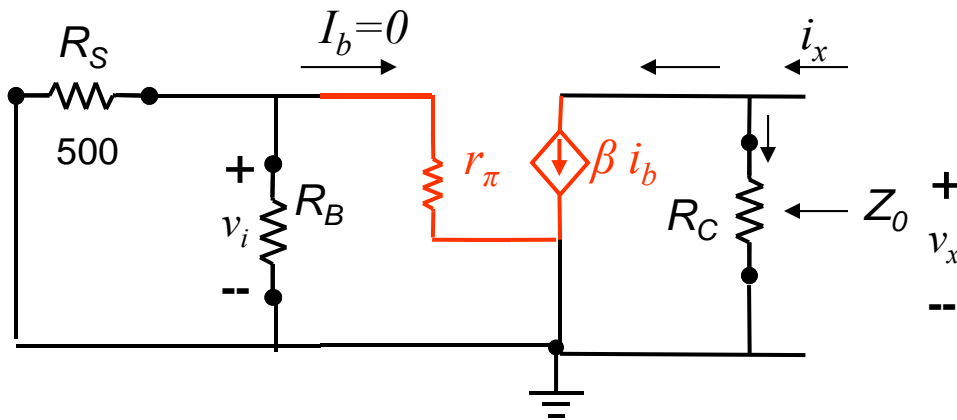

$$Z_o = \frac{v_x}{i_x}$$


$$i_x = \frac{v_x}{R_c} + \beta i_b$$

$$i_b = 0; i_x = \frac{v_x}{R_c}$$

$$Z_o = \frac{v_x}{i_x} = R_c = 1k$$

Small Signal Equivalent Circuits


Emitter Follower Example

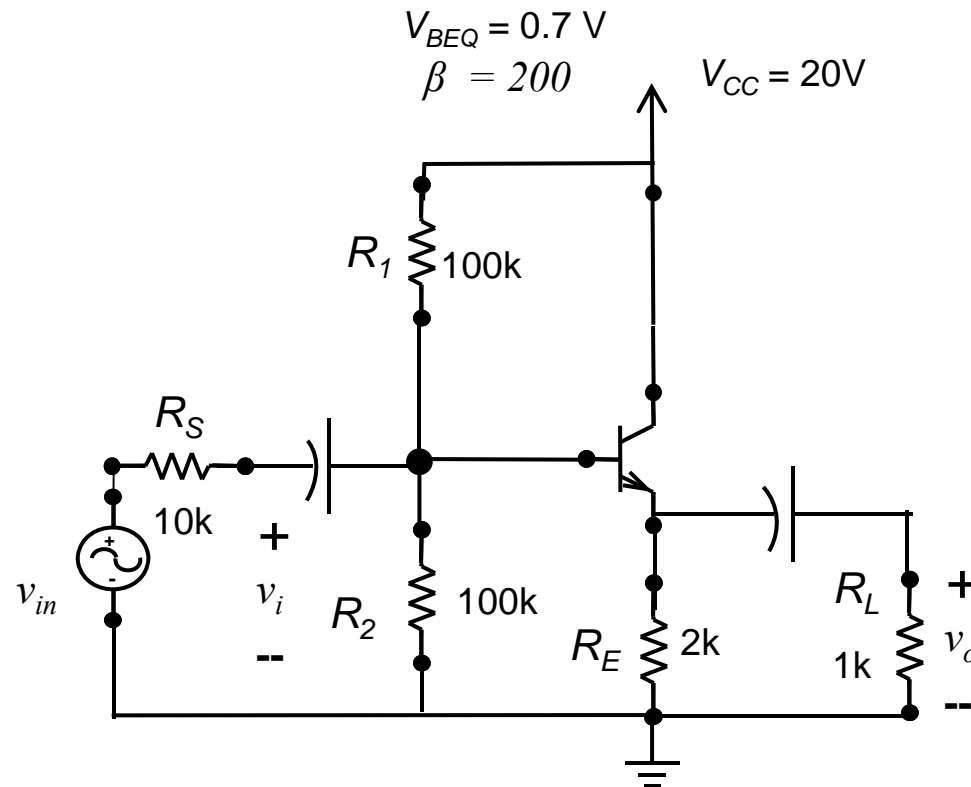

- We see that the load is across the emitter resistor
- The extra resistors and capacitors are represent
 - the load to the next stage (input impedance of the next stage)
 - the source resistance (output impedance of the previous stage)
 - Coupling capacitors
- Our analysis plan
 - First, DC analysis to determine Q-point and equivalent circuit parameters
 - AC analysis to calculate the gains

Small Signal Equivalent Circuits

Emitter Follower Example DC Analysis

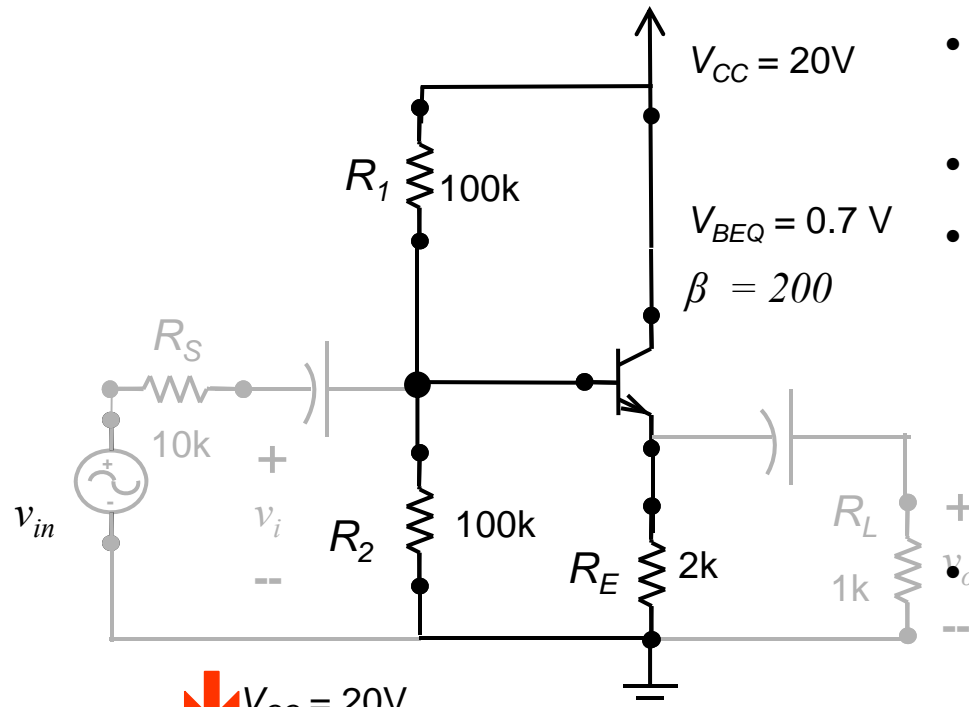

- Remove the circuit elements which are not affected by the DC voltages
- Opening the coupling capacitors
- Redraw the circuit and replace the base circuit with its Thevenin's equivalent

$$R_{TH} = R_1 \parallel R_2 = 50k$$

$$V_{TH} = \frac{R_2}{R_2 + R_1} V_{CC} = 10V$$


Next, use the DC equivalent circuit for the active region and then write KVL for the base circuit

$$V_{TH} = I_{BQ} R_{TH} + V_{BEQ} + I_{EQ} R_E = I_{BQ} R_{TH} + V_{BEQ} + (1 + \beta) I_{BQ} R_E$$

$$I_{BQ} = \frac{V_{TH} - V_{BEQ}}{R_{TH} + (1 + \beta) R_E} = \frac{10 - 0.7}{50k + (1 + 200)2k} = 20.6 \mu A$$


$$I_{CQ} = \beta I_{BQ} = 4.12 mA; I_{EQ} = (1 + \beta) I_{BQ} = 4.14 mA$$
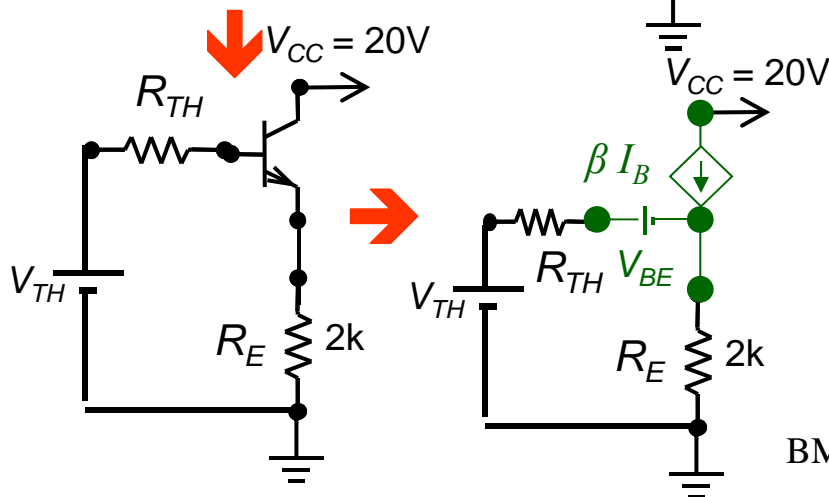
$$V_{CEQ} = V_{CC} - I_{EQ} R_E = 11.7V; r_{\pi} = \frac{V_T}{I_{BEQ}} = \frac{26m}{20.6 \mu} = 1260$$



Small Signal Equivalent Circuits



Emitter Follower Example AC Analysis

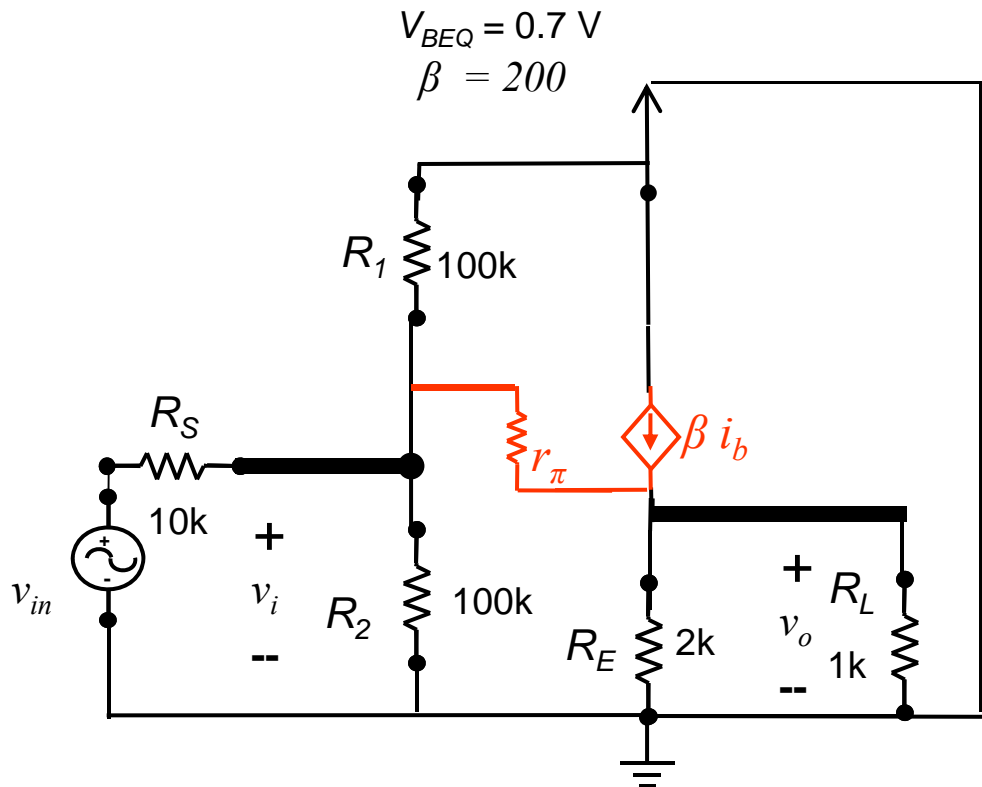

- The next step is to perform the AC analysis by
 - Shorting any DC voltage sources
 - Opening any DC current sources
 - Shorting the capacitors
 - Connecting the source, source resistance, and load resistance
 - Replace the transistor with its small signal equivalent circuit.
- And Redraw to simplify

Small Signal Equivalent Circuits

Emitter Follower Example AC Analysis

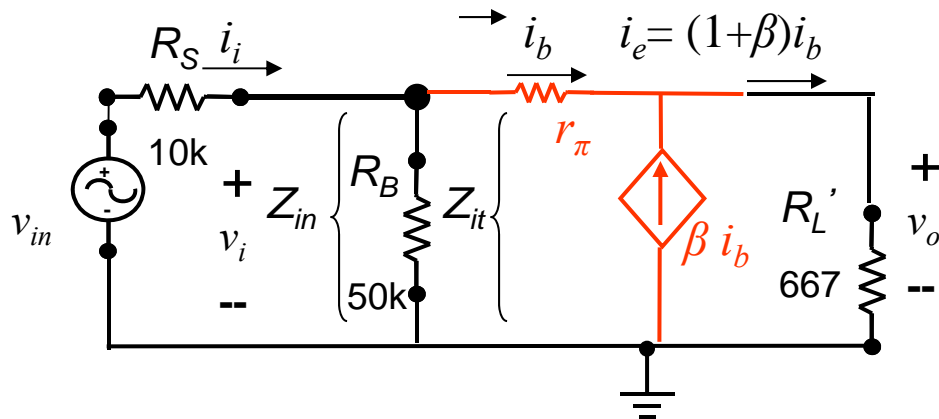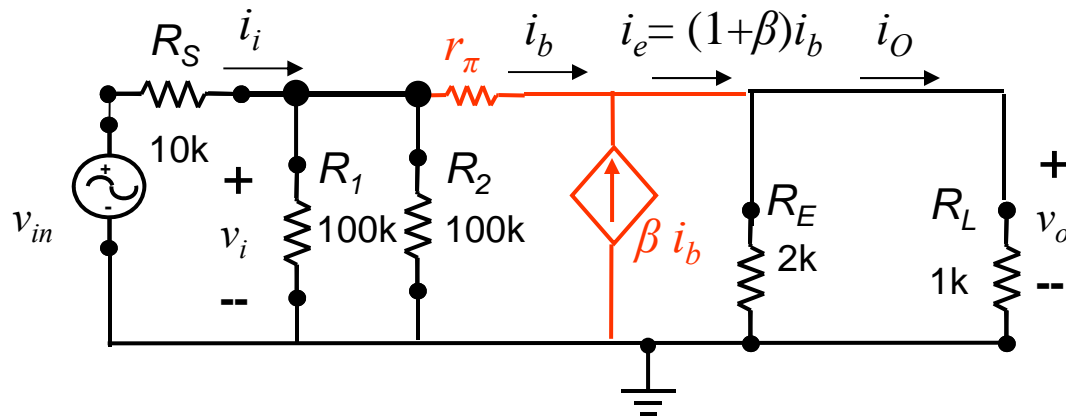

$$R_B = R_1 \parallel R_2 = 50k$$

$$R_L' = R_E \parallel R_L = 667$$

$$v_o = (1 + \beta)i_b R_L'$$

$$v_i = i_b r_\pi + v_o = \frac{v_o}{(1 + \beta)R_L'} r_\pi + v_o$$

$$A_v = \frac{v_o}{v_i} = \frac{(1 + \beta)R_L'}{(1 + \beta)R_L' + r_\pi}$$

$$A_v = \frac{(1 + 200) \times 667}{(1 + 200) \times 667 + 1260} = .991$$

$$Z_{it} = \frac{v_i}{i_b} = r_\pi + (1 + \beta)R_L' = 134k$$

$$Z_{in} = R_B \parallel Z_{it} = 36.5k$$


$$i_o = \frac{v_o}{R_L} = \frac{A_v v_i}{R_L}; \quad i_i = \frac{v_i}{Z_{in}}$$

$$A_i = \frac{i_o}{i_i} = A_v \frac{Z_{in}}{R_L} = 36.2$$

$$G = A_v A_i = 35.8$$

Small Signal Equivalent Circuits

Emitter Follower Example AC Analysis

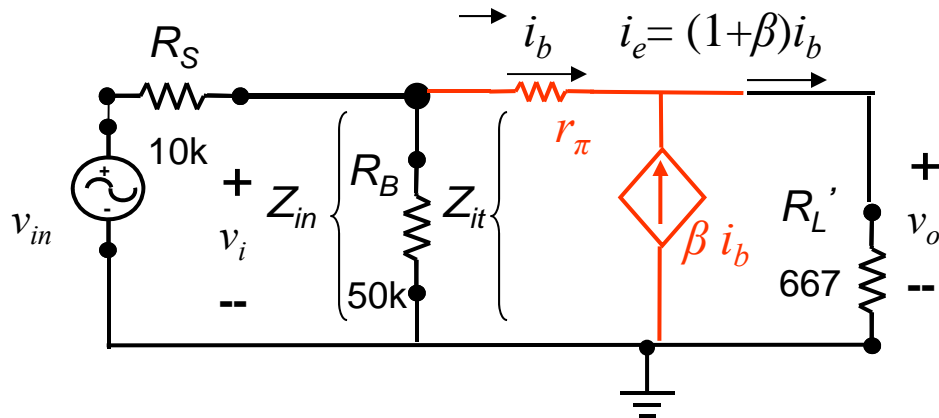


$$A_v = \frac{v_o}{v_i} = \frac{(1 + 200) \times 667}{(1 + 200) \times 667 + 1260} = .991$$

$$A_{v_s} = \frac{v_o}{v_s} = \frac{v_o}{v_i} \frac{v_i}{v_s} = 0.991 \frac{v_i}{v_s}$$


$$\frac{v_i}{v_s} = \frac{Z_{in}}{Z_{in} + R_s} = \frac{36.5}{36.5 + 10} = 0.78$$
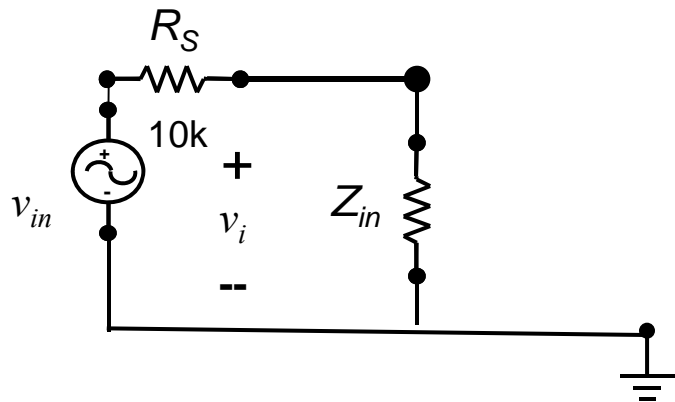
$$A_{v_s} = \frac{v_o}{v_s} = \frac{v_o}{v_i} \frac{v_i}{v_s} = 0.991 \times 0.78 = 0.78$$



Small Signal Equivalent Circuits

Emitter Follower Example AC Analysis

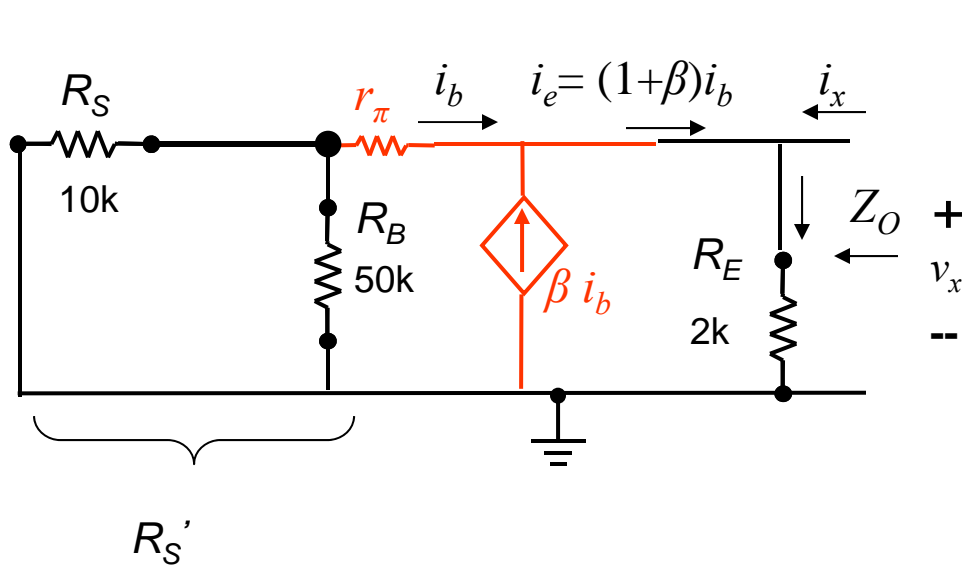

$$Z_o = \frac{v_x}{i_x}$$

$$i_x = \frac{v_x}{R_E} - i_e = \frac{v_x}{R_E} - (1 + \beta)i_b$$

$$R_S' = R_S \parallel R_B = 8.33\text{k}$$

$$v_x = -i_b (R_S' + r_\pi)$$

$$i_x = \frac{v_x}{R_E} + (1 + \beta) \frac{v_x}{R_S' + r_\pi}$$

$$v_x = i_x \left(\frac{1}{1/R_E + (1 + \beta)/(R_S' + r_\pi)} \right)$$


$$Z_o = \frac{1}{1/R_E + (1 + \beta)/(R_S' + r_\pi)} \Rightarrow R_E \parallel \frac{R_S' + r_\pi}{1 + \beta} = 46.6$$

The BJT as a Digital Switch

In Saturation, if

$$V_o = V_{CE} = V_{CC} - R_C i_C = V_{CC} - R_C \beta i_B = V_{CC} - R_C \beta \frac{V_{in} - V_{BEQ}}{R_B} < .2V$$


Then, $V_o = V_{CE} = .2$

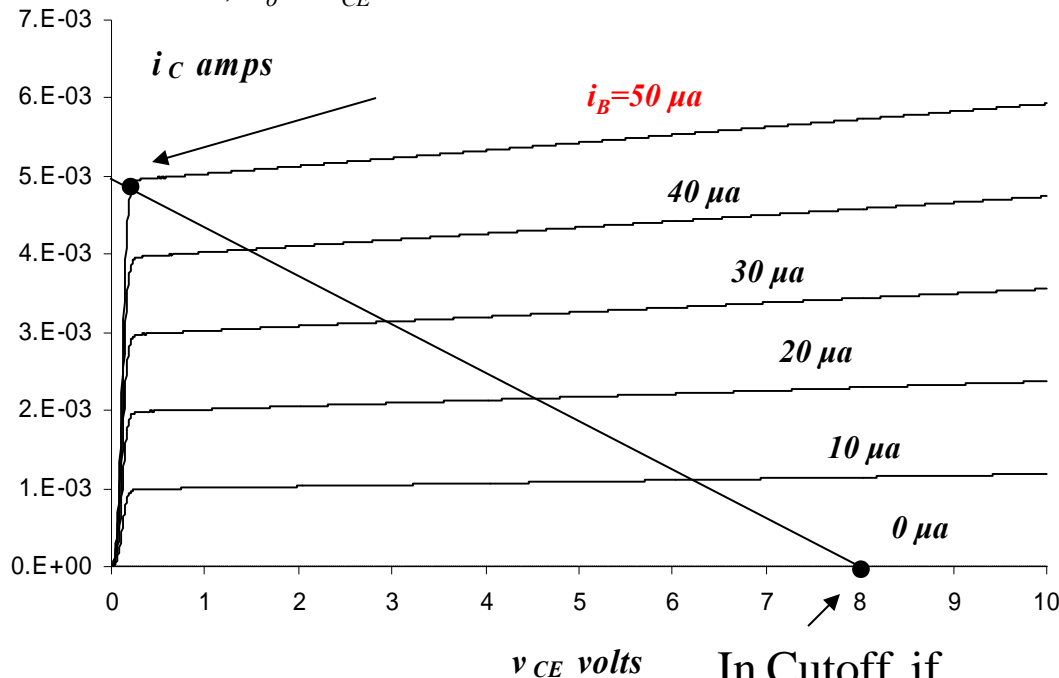

In Cutoff, if



$$V_{in} < .7V$$

Then, $V_o = V_{CC}$

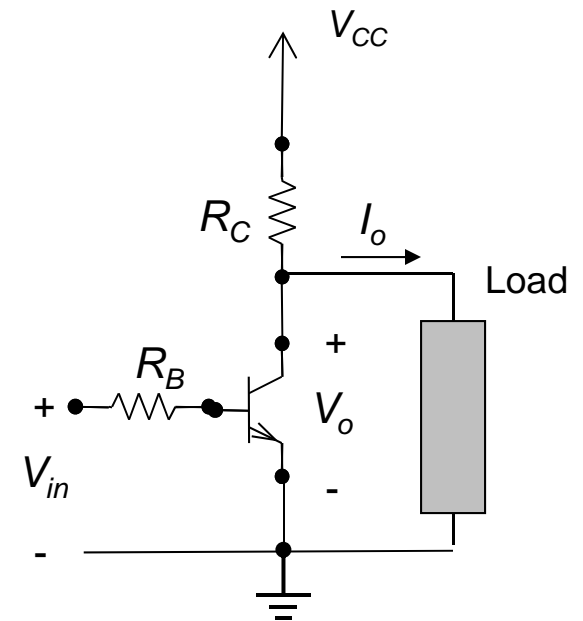

- Operating between cutoff and saturation (i.e., bypassing the active region), the BJT acts like an inverter.
- From this behavior, logic circuits such as NOR gates can be developed

The BJT as a Digital Switch

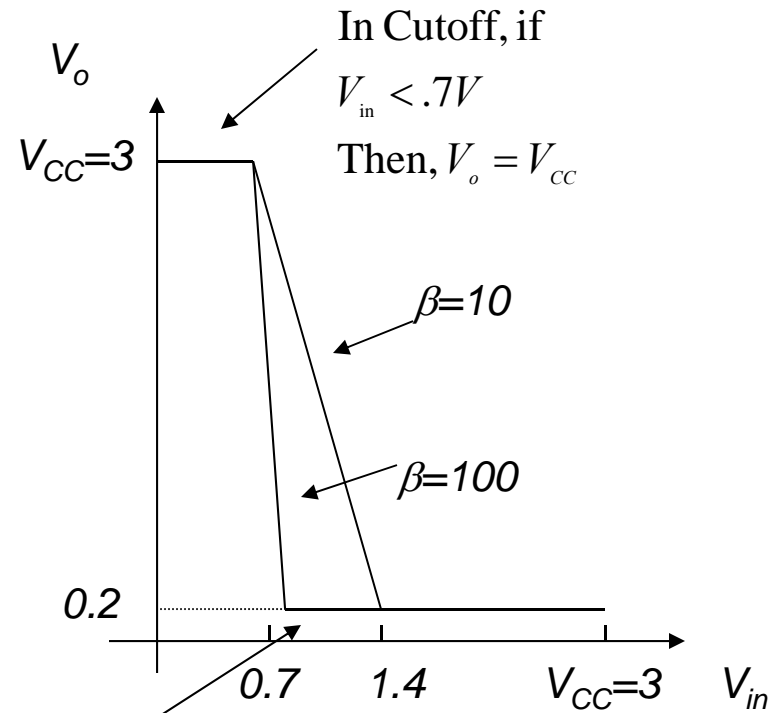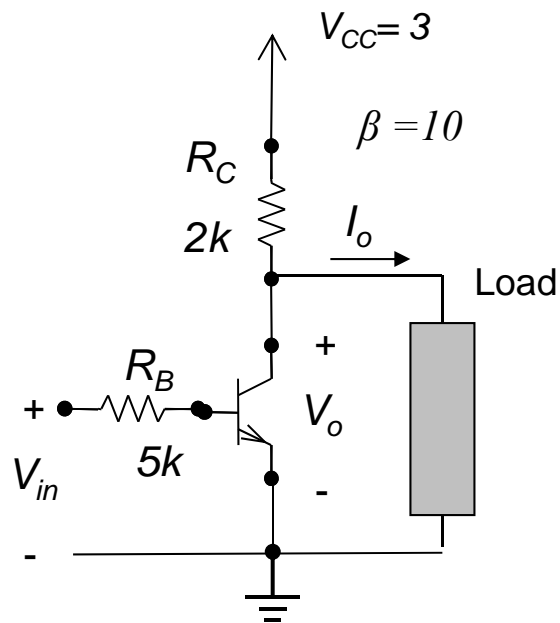


In Saturation, if

$$V_o = V_{CC} - R_C \beta \frac{V_{in} - V_{BEQ}}{R_B} < .2V$$

$$V_o = 3 - 2 \times \beta \frac{V_{in} - .7}{5} = .2$$

$$V_{in} = 5 \times \frac{3 - .2}{2\beta} + .7 = \frac{7}{\beta} + .7$$

Switching and Timing

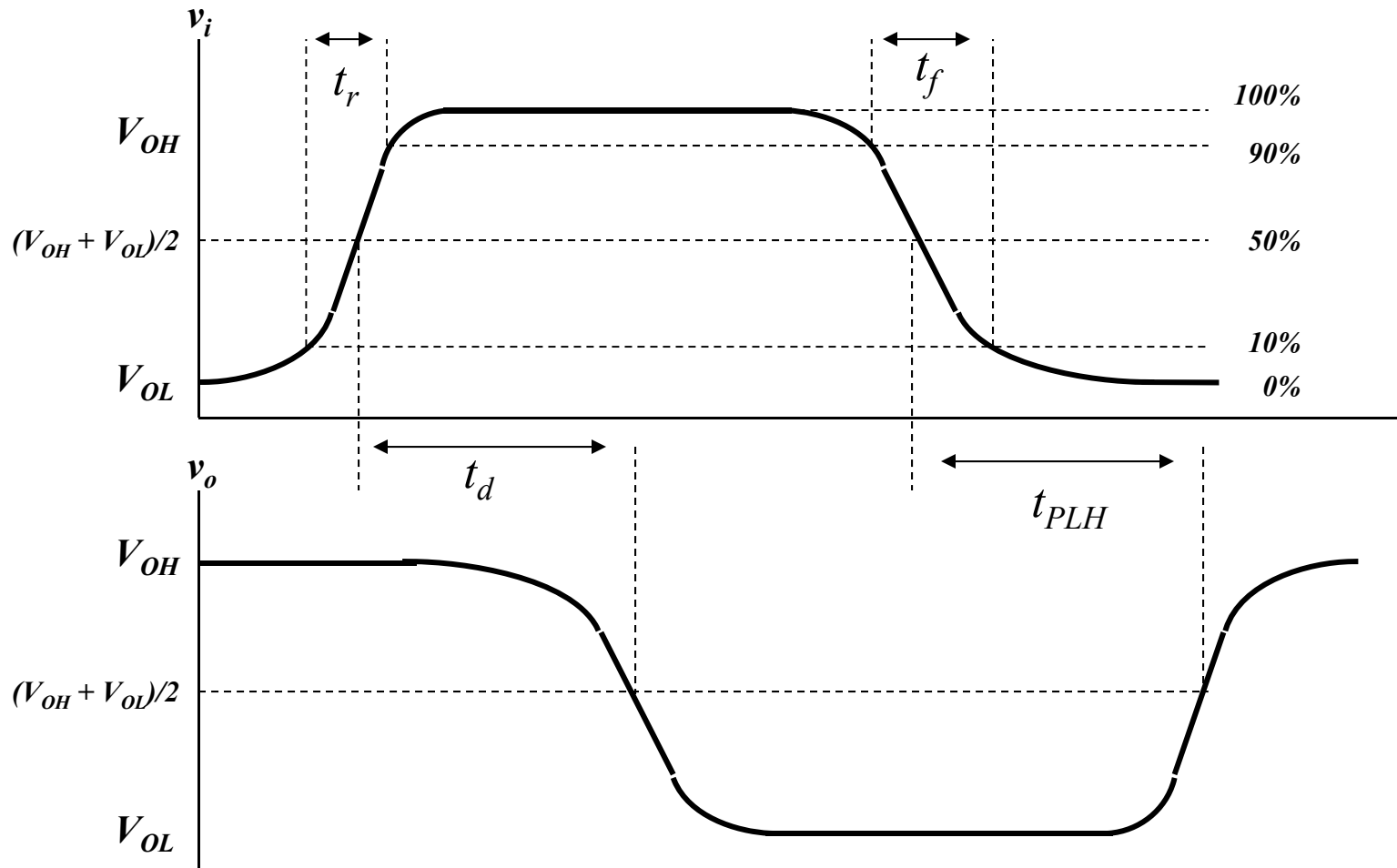

t_r = rise time

t_f = fall time

t_d = delay
time

(propagation
delay from
High to
Low)

t_s = storage
time

(propagation
delay from
Low to
High)

Homework

- Probs. 4.40, 4.42, 4.43, 4.45, 4.46, 4.51, 4.53, 4.54, 4.56,