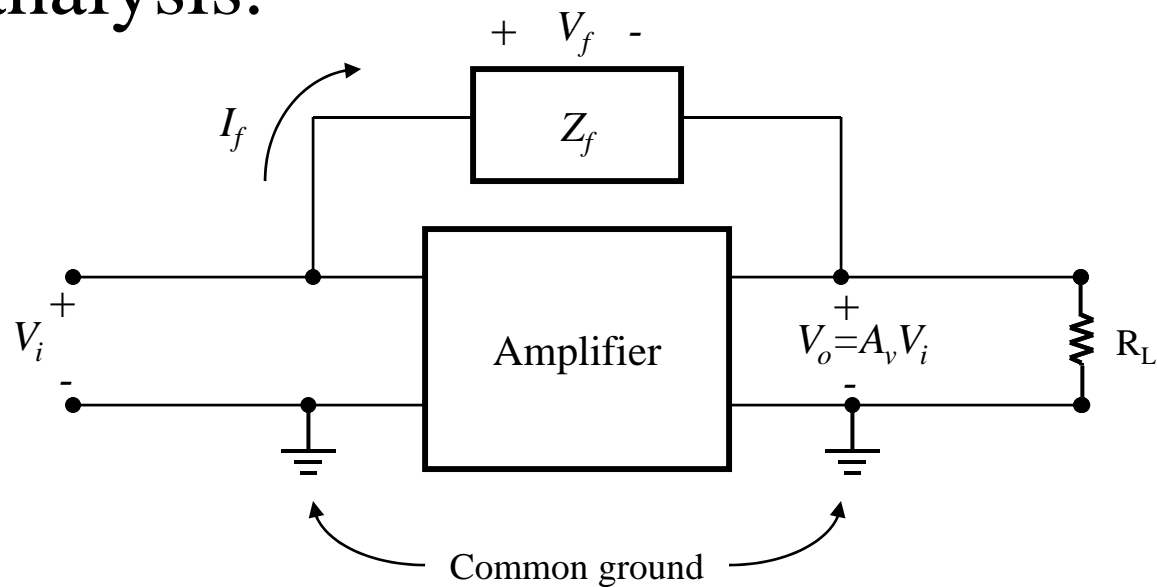


# *Frequency Response*


## Lesson #11 Miller Effect Section 8.3

## *Miller Effect for Feedback Amplifier*

- The transformation of a feedback impedance into the input and output for ease of analysis.



# Miller Effect Impedances

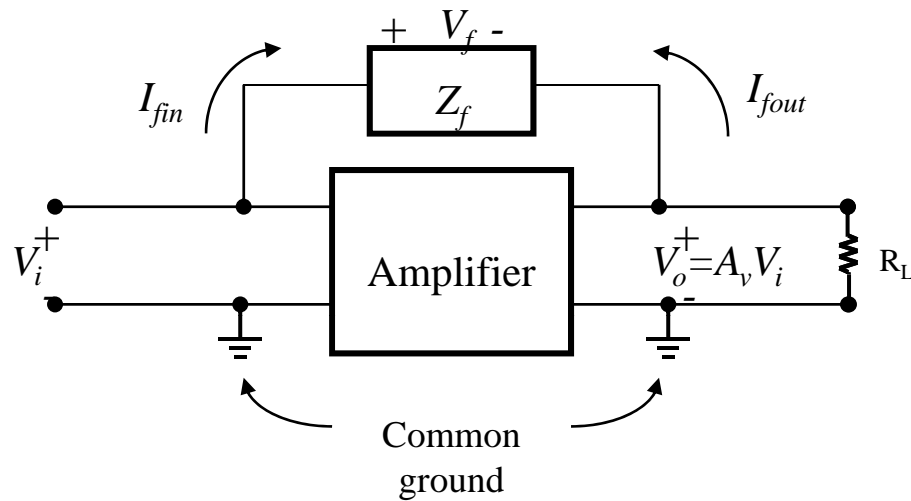

$$\mathbf{V}_f = \mathbf{V}_i - \mathbf{V}_o$$

$$\mathbf{V}_o = A_v \mathbf{V}_i$$

where  $A_v$  is the voltage gain

with  $Z_f$  in place and NOT  $A_{vo}$

$$\mathbf{V}_f = (1 - A_v) \mathbf{V}_i$$

In the input

$$\mathbf{I}_{fin} = \frac{\mathbf{V}_f}{Z_f} = \frac{(1 - A_v) \mathbf{V}_i}{Z_f} = \frac{\mathbf{V}_i}{Z_f / (1 - A_v)} = \frac{\mathbf{V}_i}{Z_{in\ Miller}}$$


In the output

$$\mathbf{V}_f = \mathbf{V}_i - \mathbf{V}_o; \mathbf{V}_o = A_v \mathbf{V}_i$$

$$\mathbf{V}_f = \frac{\mathbf{V}_o}{A_v} - \mathbf{V}_o = \frac{(1 - A_v)}{A_v} \mathbf{V}_o$$

$$\mathbf{I}_{fout} = -\frac{\mathbf{V}_f}{Z_f} = -\frac{\mathbf{V}_o / A_v}{Z_f / (1 - A_v)}$$

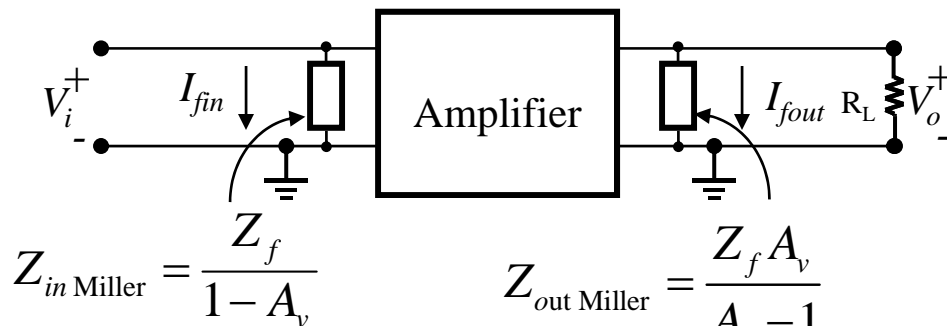
$$= \frac{\mathbf{V}_o}{Z_f A_v / (A_v - 1)} = \frac{\mathbf{V}_o}{Z_{out\ Miller}}$$



$$Z_{out\ Miller} = \frac{Z_f A_v}{A_v - 1}$$

For  $A_v \gg 1$ ,  $Z_{out\ Miller} = Z_f$

# Miller Effect Example

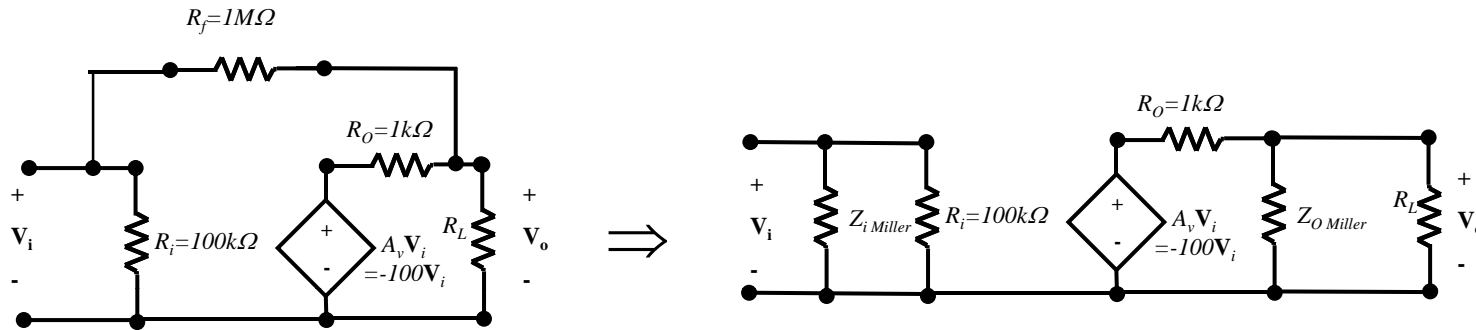

Case A: Let  $R_L = 9k\Omega$ ,

Case B: Let  $R_L = 1k\Omega$

$$Z_{o\text{ Miller}} = \frac{Z_f A_v}{A_v - 1} = \frac{Z_f}{1 - 1/A_v} \approx Z_f \text{ for } A_v \gg 1$$

$$Z_{o\text{ Miller}} = 1M\Omega$$

$$\text{Case A: } R'_L = Z_{o\text{ Miller}} \parallel R_L = Z_f \parallel R_L = 1M \parallel 9k = 9k\Omega$$

$$\text{Case B: } R'_L = Z_{o\text{ Miller}} \parallel R_L = Z_f \parallel R_L = 1M \parallel 1k = 1k\Omega$$

$$A_v = \frac{R'_L}{R'_L + R_o} A_{vo}$$

$$\text{Case A: } A_v = \frac{9k}{9k + 1k} (-100) = -90$$

$$\text{Case B: } A_v = \frac{1k}{1k + 1k} (-100) = -50$$

$$Z_{i\text{ Miller}} = \frac{Z_f}{1 - A_v}$$


$$\text{Case A: } Z_{i\text{ Miller}} = \frac{1M\Omega}{1 - (-90)} = 10.98k\Omega;$$

$$Z_{in} = Z_{i\text{ Miller}} \parallel R_i = 10.98k \parallel 100k = 9.9k\Omega$$

$$\text{Case B: } Z_{i\text{ Miller}} = \frac{1M\Omega}{1 - (-50)} = 19.6k\Omega;$$

$$Z_{in} = Z_{i\text{ Miller}} \parallel R_i = 19.6k \parallel 100k = 16.39k\Omega$$

# Miller Effect for Feedback Capacitance

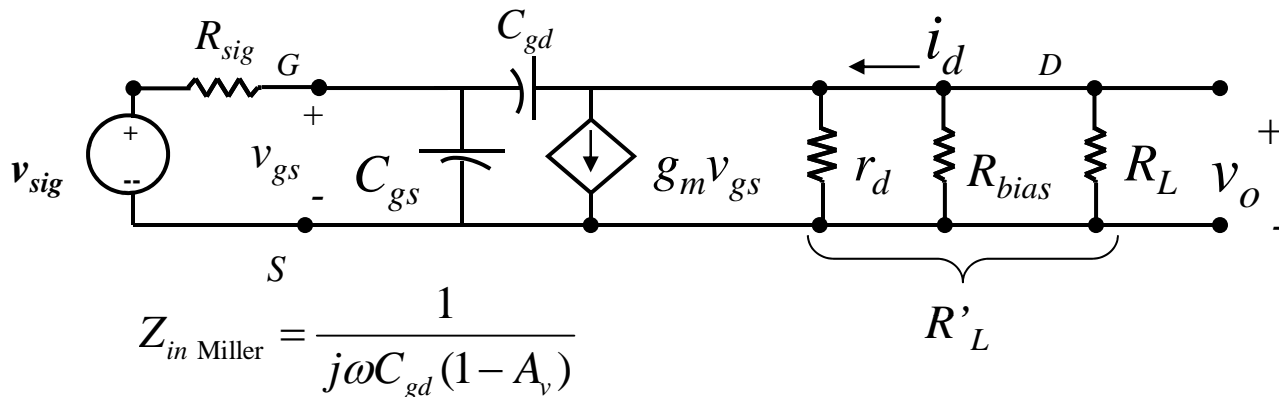


$$Z_{in \text{ Miller}} = \frac{1}{j\omega C_{gd} (1 - A_v)}$$


$$Z_{out \text{ Miller}} = \frac{A_v}{j\omega C_{gd} (A_v - 1)} \approx \frac{1}{j\omega C_{gd}}$$

Note:

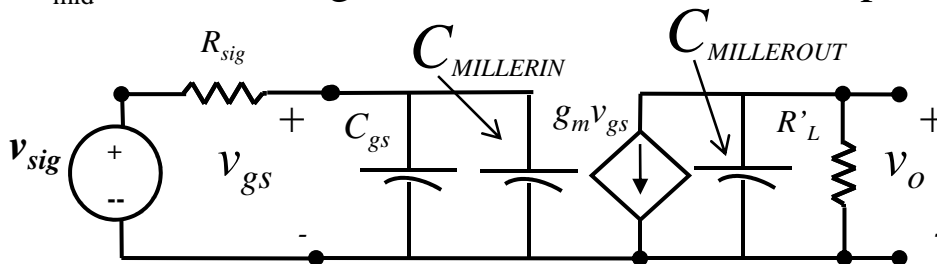$A_v = A_{mid}$  This is the gain w/o the effects of the capacitance i.e., all resistive.



# Miller Effect for Feedback Capacitance

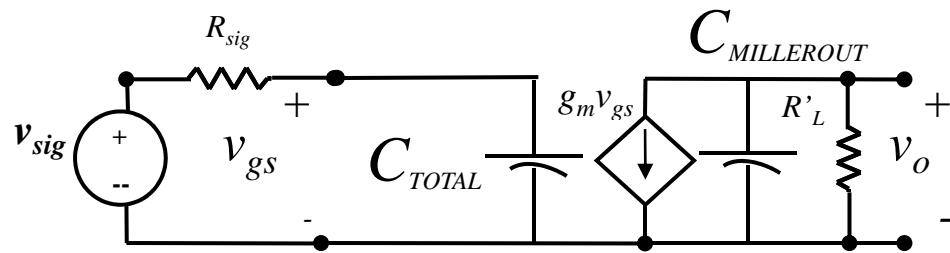

$$v_o = -g_m v_{gs} R'_L \parallel Z_{MILLEROUT} = -g_m v_{gs} \frac{R'_L \times \frac{1}{j\omega C_{MILLEROUT}}}{R'_L + \frac{1}{j\omega C_{MILLEROUT}}}$$

$$= -g_m v_{gs} \frac{R'_L}{j\omega C_{MILLEROUT} R'_L + 1} = -g_m v_{gs} \frac{R'_L}{j\left(\frac{f}{f_{bOUT}}\right) + 1}$$

$$f_{bOUT} = \frac{1}{2\pi R'_L C_{MILLEROUT}} = \frac{1}{2\pi R'_L C_{gd}}$$

## Miller Effect for Feedback Capacitance

$$v_{gs} = \frac{Z_{CTOTAL}}{Z_{CTOTAL} + R_{sig}} v_{sig} = \frac{\frac{1}{j\omega C_{TOTAL}}}{\frac{1}{j\omega C_{TOTAL}} + R_{sig}} v_{sig} = \frac{1}{1 + j\omega C_{TOTAL} R_{sig}} v_{sig} = \frac{1}{j\left(\frac{f}{f_{bIN}}\right) + 1} v_{sig}$$

$$f_{bIN} = \frac{1}{2\pi R_{sig} C_{TOTAL}} = \frac{1}{2\pi R_{sig} [C_{gs} + (1 - A_{mid}) C_{gd}]}$$


$$\frac{v_o}{v_{sig}} = A_{vs} = -g_m \frac{R_L'}{j\left(\frac{f}{f_{bOUT}}\right) + 1} \times \frac{1}{j\left(\frac{f}{f_{bIN}}\right) + 1} = -g_m R_L' \frac{1}{[j\left(\frac{f}{f_{bOUT}}\right) + 1][j\left(\frac{f}{f_{bIN}}\right) + 1]}$$

If  $R_{sig} [C_{gs} + (1 - A_{mid}) C_{gd}] \gg R_L' C_{gd}$ , then  $f_{bIN} \ll f_{bOUT}$

$$BW = f_{bIN} = \frac{1}{2\pi R_{sig} [C_{gs} + (1 - A_{mid}) C_{gd}]}$$

$$GB = A_{mid} f_{bIN} = A_{mid} \frac{1}{2\pi R_{sig} [C_{gs} + (1 - A_{mid}) C_{gd}]} \approx \left| \frac{1}{2\pi R_{sig} C_{gd}} \right| \text{ for } A_{mid} \gg 1$$

# Miller Effect for Feedback Capacitance

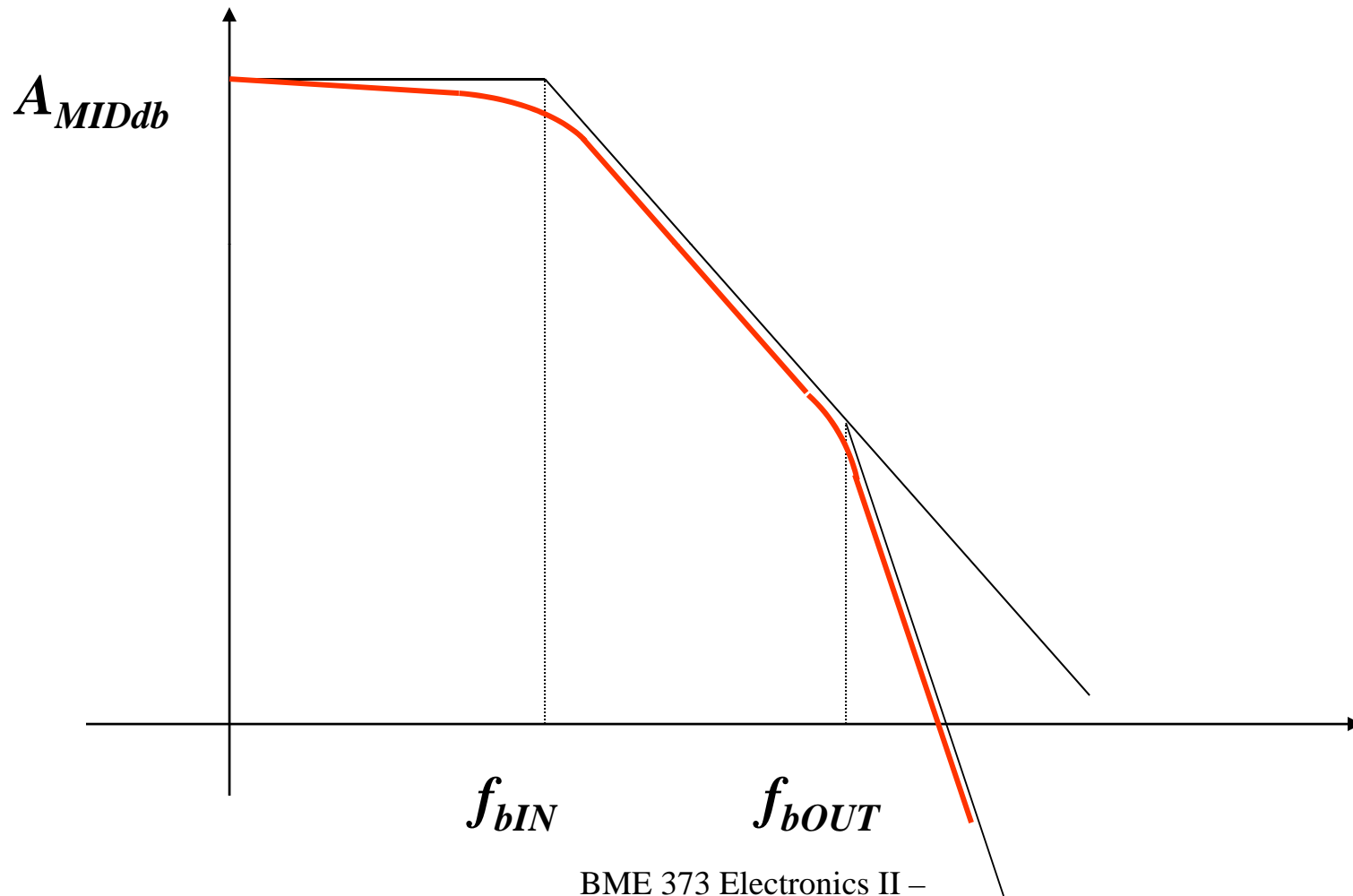



# *Homework*

- Miller Effect
  - Problems: 8.20-24, 8.27