

Feedback and Oscillators

Lesson #13


Feedback

Section 9.1-2

Feedback

- Types of Feedback
 - Positive: aids the input signal
 - Negative: reduces the input signal
- Positive Feedback Benefits
 - Oscillators
- Negative Feedback Benefits
 - Stabilization of Gain
 - Reduction of Nonlinear Distortion
 - Reduction of noise
 - Control of input and output impedances
 - Extension of Bandwidth
- Design of feedback amplifier to avoid unwanted oscillations

Closed-Loop Gain

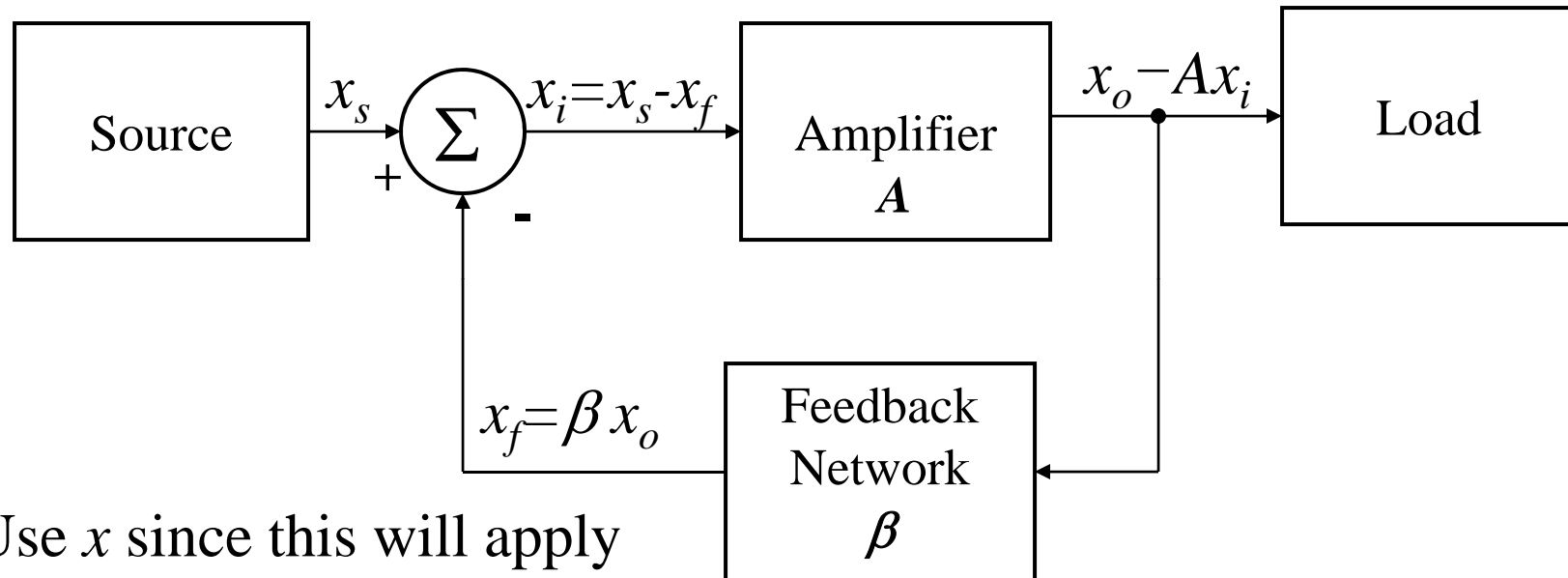

Use x since this will apply
equally to voltages and currents

$$x_i = x_s - x_f = x_s - \beta x_o$$

$$x_o = Ax_i$$

$$x_o = A(x_s - \beta x_o)$$

\Rightarrow

$$A_f = \frac{x_o}{x_s} = \frac{A}{1 + A\beta}$$

Closed – Loop Gain = A_f

Open – Loop Gain = A

Loop Gain = $A\beta$

Problems With Positive Feedback

- If $|A\beta| \leq 1$ and $A\beta$ is negative:
 - then $1+A\beta \leq 1$; and A_f (closed-loop gain) $> A$ (open-loop gain)
 - if $A\beta = -1$, then oscillations occur
 - POSITIVE FEEDBACK
- Example:
 - $A = -10, \beta = 0.0999 \Rightarrow A\beta = -0.999; 1+A\beta = 0.001; A_f = -10^4$
 - $A: -10 \rightarrow -9.9 \Rightarrow A\beta = -0.989; 1+A\beta = 0.011; \text{then } A_f: -10^4 \rightarrow -901$
 - For a 1% reduction in A there was a 91% reduction of A_f
 - POOR GAIN STABILITY: worse than the original amplifier

Problems (Continued)

- Another Example:
 - As $A\beta \rightarrow -1$, $A_f \rightarrow \infty$ and this implies for a zero input signal an output signal can be generated and a signal will flow around the loop w/o an input \Rightarrow oscillations. This is ok if an oscillator design is desired.
 - Clearly, a high gain amplifier can be designed with positive feedback; however, care must be taken because any change in the design (temperature shifts increase the power supply voltages) may cause $A\beta \rightarrow -1$ and oscillations result

Gain Stabilization Using Negative Feedback

- For Negative Feedback Amplifiers are designed with $A\beta \gg 1$ and $A_f \cong 1/\beta$
 - This is desirable since the value of β can be designed using solely stable passive components (e.g., resistors and capacitors)
 - On the other hand A is a function of active components (e.g., BJT, FET, etc.) whose operating point is highly dependent on temperature V_T and operating point (e.g., for a BJT $r_\pi = V_T/I_{BQ}$ and $g_m = \sqrt{2KP} \sqrt{W/L} \sqrt{I_{DQ}}$)
 - This occurs for op amps

Gain Stabilization Using Negative Feedback

Continued

- *Example:* $A = 10^4$ and $\beta = 0.01 \Rightarrow A_f = 99$
 - If $A \rightarrow 9000$, then $A_f \rightarrow 98.9$
 - For a 10% reduction in A there was only a 0.1% reduction of A_f
- Therefore, we can design precision amplifiers using Negative Feedback


$$\frac{dA_f}{dA} = \frac{1 + A\beta - A\beta}{(1 + A\beta)^2} = \frac{1}{(1 + A\beta)^2}$$

$$dA_f = \frac{dA}{A} \frac{A}{(1 + A\beta)^2} = \frac{dA}{A} \frac{A_f}{1 + A\beta}$$

$$\frac{dA_f}{A_f} = \frac{dA}{A} \frac{1}{1 + A\beta}$$

- This states that for small fractional changes of A_f is the fractional change in A divided by $1 + A\beta$
- Clearly, if the loop gain $A\beta \gg 1$ changes of A_f are less than A

Summing-Point Constraint Revised

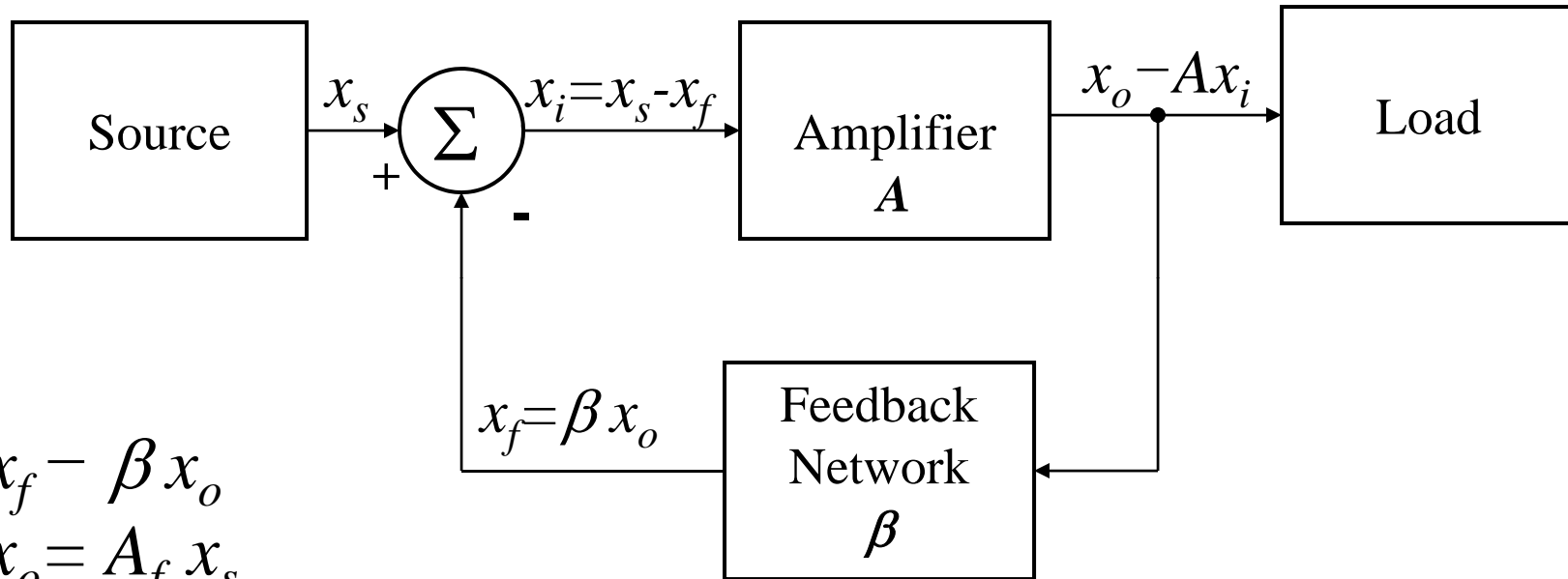

$$x_f = \beta x_o$$

$$x_o = A_f x_s$$

$$x_f = A_f \beta x_s$$

$$x_f = x_s \frac{A\beta}{1 + A\beta}$$


- If $A\beta \gg 1$ then $x_f \cong x_s$ and $x_i = x_s - x_f \cong 0$
- This is the summing point constraint
 - Here is how we can design operational amplifiers from negative feedback amplifiers with $A\beta \gg 1$

Examples

- Find A_f , x_o , x_f and x_i for a negative feedback amplifier with $A=10^5$, $\beta = 0.01$ and $x_s = 5 \sin(2000\pi t)$
 - $A_f = A / (1 + A\beta) = 10^5 / (1 + 10^5 * 0.01) = 99.9$
 - $x_o = A_f x_s = 499.5 \sin(2000\pi t)$
 - $x_f = \beta x_o = 4.995 \sin(2000\pi t)$
 - $x_i = x_s - x_f = .004995 \sin(2000\pi t)$
- What is the maximum value of A_f if we want it not to vary greater than $\pm 1\%$ (and $\pm 0.1\%$) for an amplifier with $A = 10^5 \pm 10\%$
 - $\Delta A/A = .10$; $\Delta A_f/A_f < .01$
 - $\Delta A_f/A_f = \Delta A/A * [1/(1+A\beta)]$
 - $A_f = A/(1+A\beta) \Rightarrow A_f = A * \Delta A_f/A_f * (A/\Delta A) = 10^5 * .01/.1 = 10^4$
 - $A_f = A * \Delta A_f/A_f * (A/\Delta A) = 10^5 * .001/.1 = 10^3$

Reduction of Non-linear Distortion

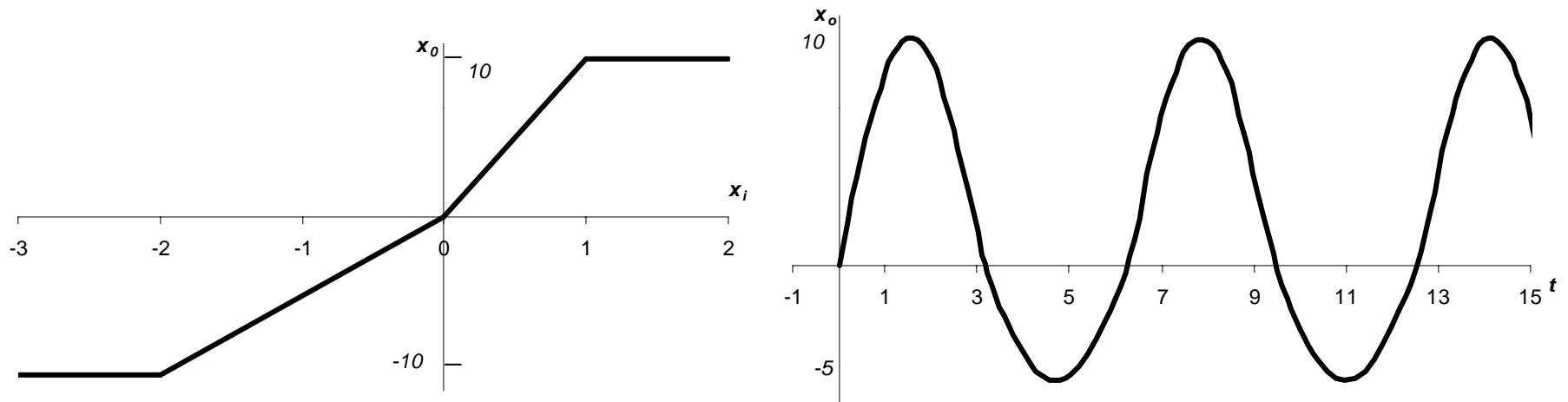
- Assume we have an amplifier which has the following non-linear gain characteristics.



- If we want to reduce this distortion with an amplifier of $A_f \cong 10$ and $\beta = .1$, we would need to have $A\beta \gg 1$, but $A = 10$ and 5 .

Reduction of Non-linear Distortion (Continued)

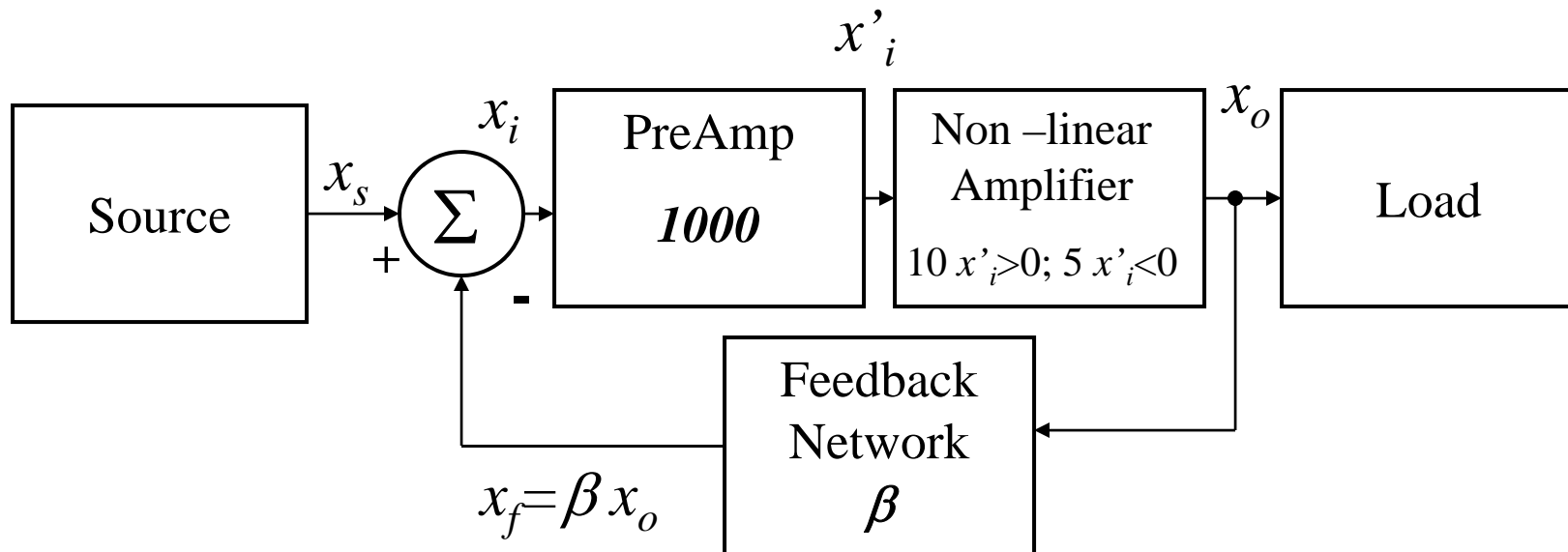- To solve this we can add a linear preamplifier of gain of 1000.
- The cascade has an open-loop gain of:
 - $10^4 (=10^3 \times 10)$ for $0 < x_o < 10$ and $5000 (=10^3 \times 5)$ for $-10 < x_o < 0$.
- And a closed loop gain of
 - 9.99 for $0 < x_o < 10$ and 9.98 for $-10 < x_o < 0$.



Compensation of Non-linear Distortion

- Let's look at the input signal at the amplifier:

$$x_i = x_s - x_f$$

$$x_i = x_s - x_s \frac{A\beta}{1 + A\beta} = x_s \frac{1}{1 + A\beta}$$

$$x_i = x_s / (1 + 10^4 \times .1) = x_s / 1001 \text{ for } 0 < x_s < 10$$

$$x_i = x_s / (1 + 5000 \times .1) = x_s / 501 \text{ for } -10 < x_s < 0$$

- We see that the negative feedback compensate for the non-linear distortion by altering (pre-distorting) the input signal to the amplifier.

Noise Reduction

- Sources of Noise
 - Power-supply (60 cycle) hum
 - Coupling of non-wanted signals
 - Thermal noise in resistors (heat dissipation)
 - Shot noise (current flow may not be continuous)
- Signal-to-Noise Ratio
 - A way of quantifying the noise performance of a circuit
 - Desired power divided by the noise power
 - Given in terms of rms values of the signals and dBs

Signal-to-Noise Ratio

$$P_{signal} = \frac{(A_1 X_s)^2}{R_L}$$


$$P_{noise} = \frac{(A_1 X_{noise})^2}{R_L}$$

$$SNR = \frac{P_{signal}}{P_{noise}} = \frac{(X_s)^2}{(X_{noise})^2}$$


$$SNR_{dB} = 10 \log(SNR)$$

$$SNR_{dB} = 10 \log \frac{P_{signal}}{P_{noise}}$$
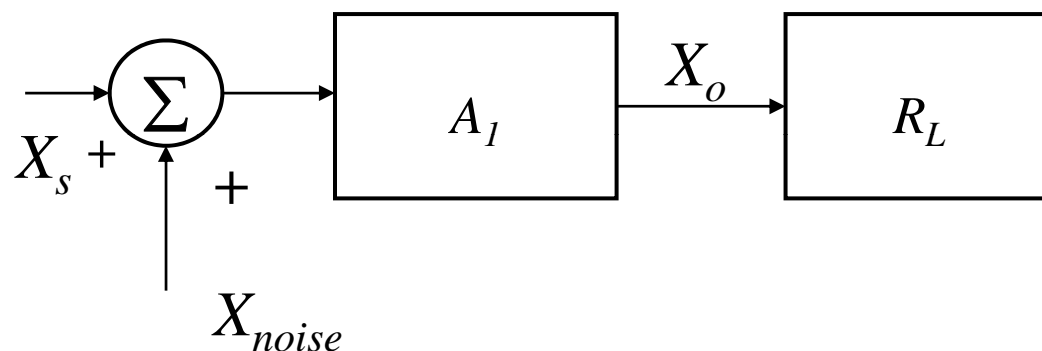
$$SNR_{dB} = 20 \log \frac{X_s}{X_{noise}}$$



SNR Analysis

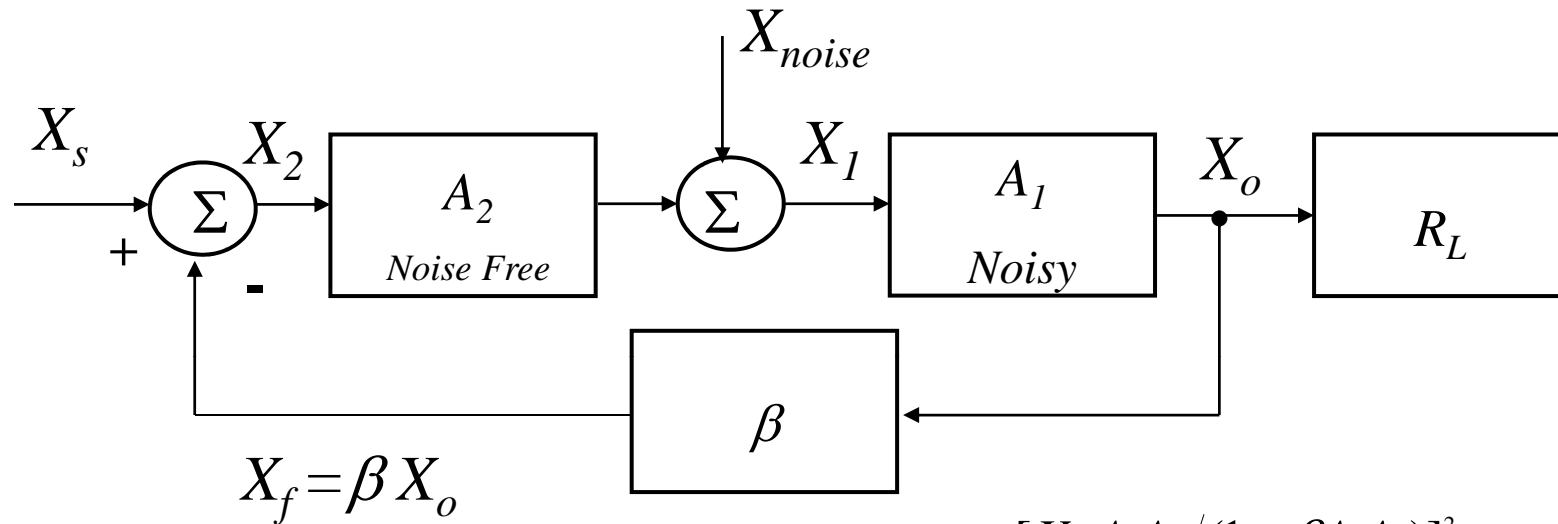

$$X_o = A_1 X_1$$

$$X_1 = X_{noise} + A_2 X_2$$

$$X_2 = X_s - \beta X_o$$

$$X_o = A_1 [X_{noise} + A_2 (X_s - \beta X_o)]$$

$$X_o = \frac{A_1 A_2}{1 + A_1 A_2 \beta} X_s + \frac{A_1}{1 + A_1 A_2 \beta} X_{noise}$$

$$SNR = \frac{[X_s A_1 A_2 / (1 + \beta A_1 A_2)]^2}{[X_{noise} A_1 / (1 + \beta A_1 A_2)]^2}$$

$$SNR = \frac{(X_s)^2}{(X_{noise})^2} \times (A_2)^2$$

This says that by using negative feedback, SNR can be improved by $(A_2)^2$.

Examples

- Power Supply output is 10 V rms and receives hum at .1 V rms. Compute the SNR in dB.
 - $SNR = 20 \log(10/.1) = 40 \text{ dB}$
- Using a low noise amp we want to improve the SNR by 20 dB, what is the gain of the amp?
 - $SNR_{pre-amp} = SNR_{original} A^2$
 - $SNR_{pre-amp \text{ db}} = SNR_{original \text{ db}} + 20 \log A$
 - $SNR_{pre-amp \text{ db}} = SNR_{original \text{ db}} + 20 \text{ dB}$
 - $20 \log A = 20$
 - $\log A = 1$
 - $A = 10$

Homework

- Effects of Feedback
 - Problems: 9.1-3,5-9
- Reduction of Nonlinear Distortion and Noise
 - Problems: 9.10,16,18-20