

# *Feedback and Oscillators*

## Lesson #15

### Transient and Frequency Response

### Section 9.6-10

## *Closed-Loop Gain in the Frequency Domain*

- Assume that both the open-loop gain,  $A(s)$  and the feedback,  $\beta(s)$  are functions of frequency and we apply the Laplace transform (complex) variable  $s = \sigma + j\omega$ :

$$A_f(s) = \frac{A(s)}{1 + A(s)\beta(s)}$$


- Therefore,
  - the zeros of  $A_f(s)$  are the values of  $s$  which satisfy  $A(s) = 0$
  - the poles of  $A_f(s)$  are the values of  $s$  which satisfy  $1 + A(s)\beta(s) = 0$

## *Poles*

- Solutions to  $1 + A(s)\beta(s) = 0$  define the transient response of the amplifier
- These solutions can be either real or complex values of  $s$
- For real values  $s = \pm \sigma$ , the transient response will have the form  $\exp(\pm \sigma t)$  and will dampen out ( $s = -\sigma$  with time constant  $1/\sigma$ ) or grow ( $s = +\sigma$ )
- Poles which are negative are desirable because the transient response dies out; while poles which are positive are undesirable because will cause the amplifier to function uncontrollably.

# Complex Plane


## Complex Number and Phasor Notation

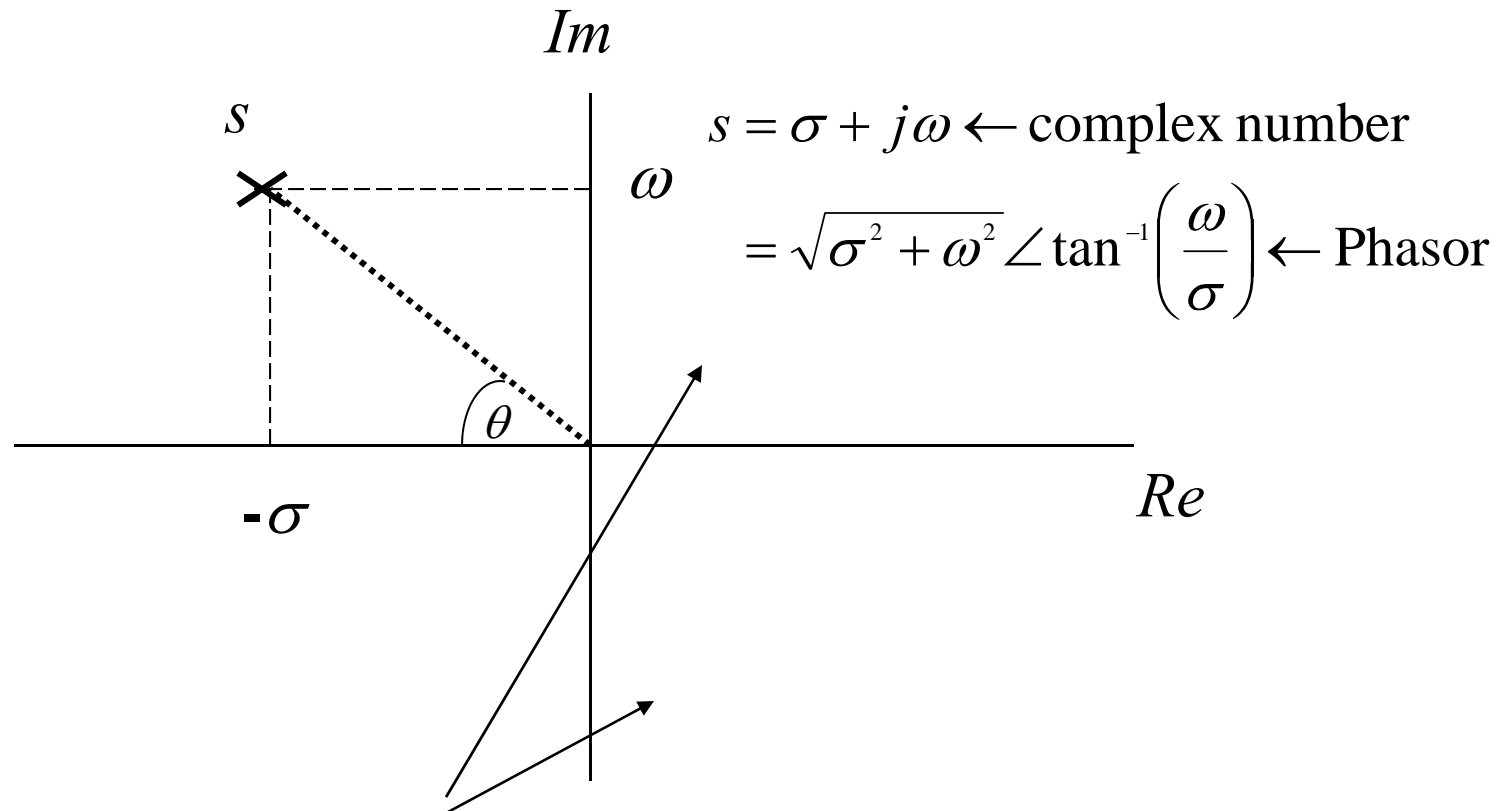

Note that poles in the right hand plane will have positive real parts and the transient response will grow exponentially

# Complex Plane

## Complex Conjugate Poles

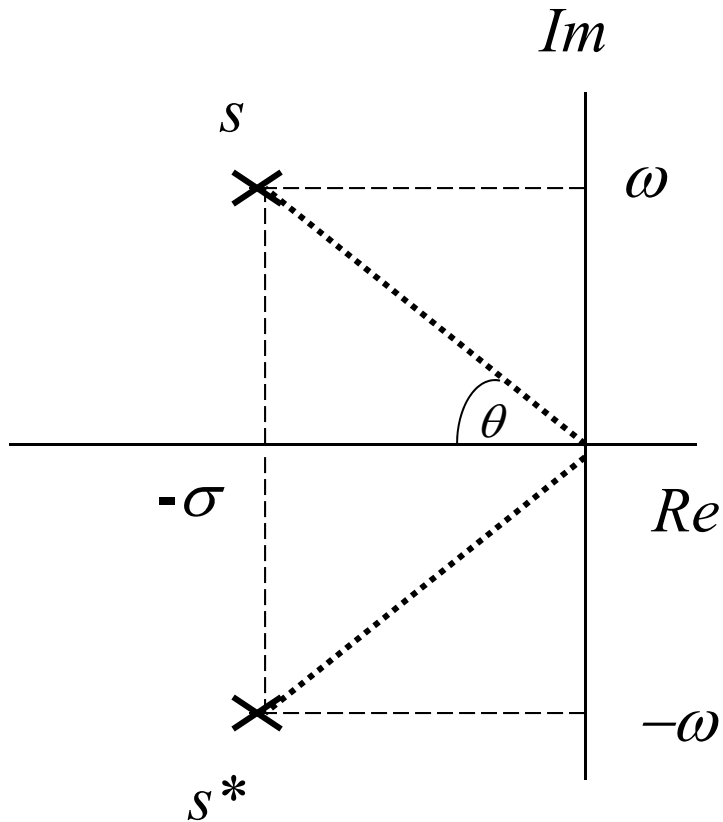

$$s = \sigma + j\omega$$

$$s^* = \sigma - j\omega$$

$$s = \sqrt{\sigma^2 + \omega^2} \angle \tan^{-1}\left(\frac{\omega}{\sigma}\right)$$


$$s^* = \sqrt{\sigma^2 + \omega^2} \angle -\tan^{-1}\left(\frac{\omega}{\sigma}\right)$$

Complex conjugates yield  
a transient response of the form :




$$e^{\pm\sigma t} (A \cos \omega t + B \sin \omega t)$$

Poles in the right hand plane will grow  
while poles in the left hand plane dampen
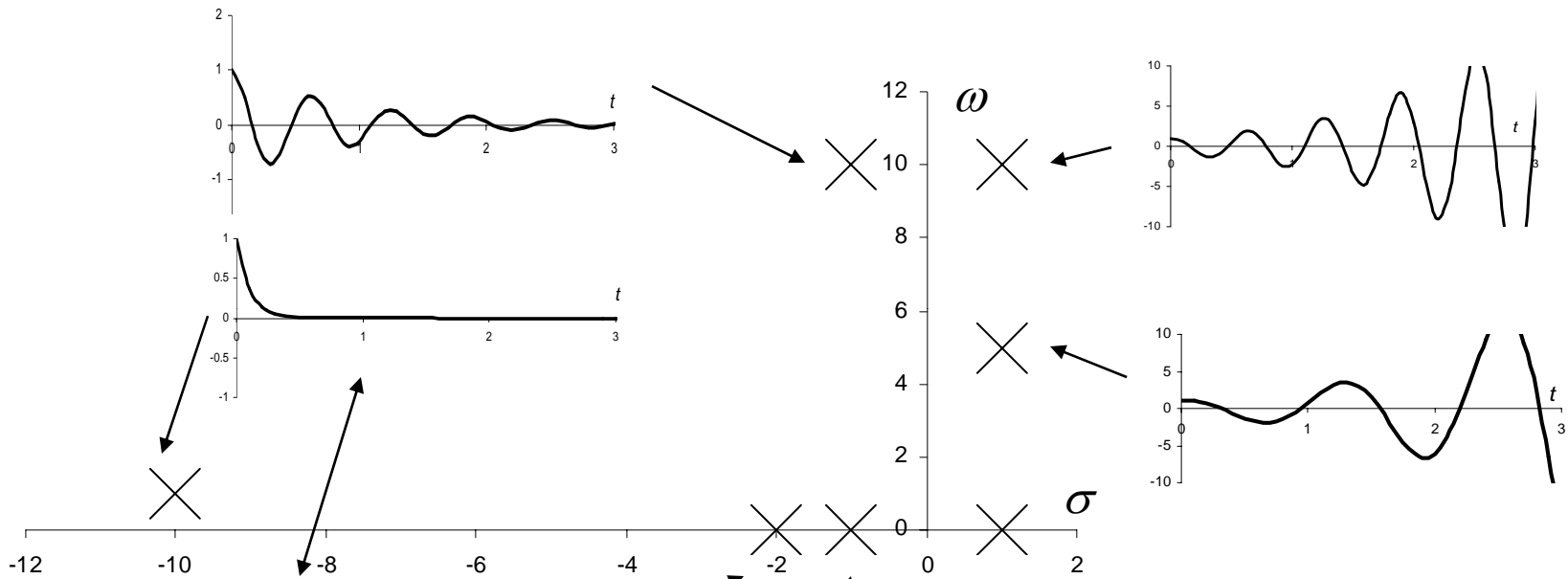
# Transient Solutions in the Complex Plane



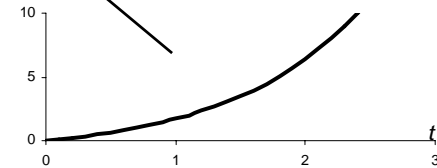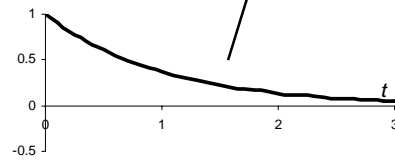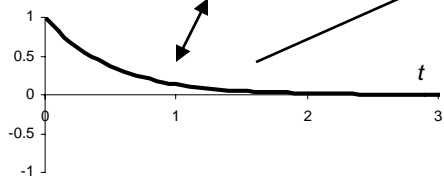Most desirable solutions since transient response dies out quickly




Note: Conjugates not shown

# *Frequency Response*

- Plot the magnitude network function as a function of  $s = j\omega$
- Sketch the magnitude by:
  - Calculate the magnitude for  $\omega=0$  and  $\omega \rightarrow \infty$
  - If there are real poles, estimate the breakpoint frequencies as  $\omega = 1/s_{pk}$  and the value of the magnitude of the network function
  - If there are complex poles, estimate the maximum of the network function at the value of  $\omega = \text{Imaginary part for each pole}$
  - Set the function to zero at the zeros of the network function
- For network functions with only real poles:
  - Those with poles furthest from the origin have higher 3-dB cutoff frequencies
- For network functions with complex poles:
  - A gain peak will occur at the imaginary part ( $j\omega$ ) of the pole
  - The gain peak will be smaller for those poles where the real part ( $\sigma$ ) is greater than the imaginary part ( $j\omega$ ).

# Example #1

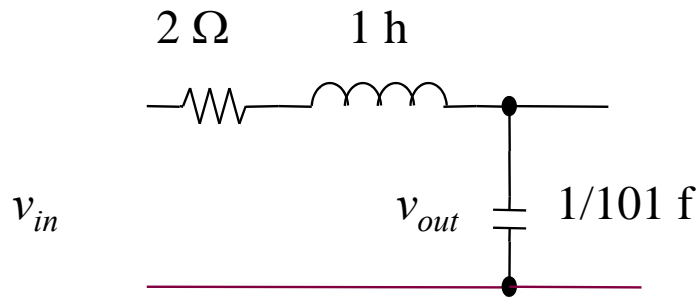

Frequency Response

$$\frac{V_o(s)}{V_{in}(s)} = \frac{101}{(s+1-j10)(s+1+j10)}$$

$$H(j\omega) = \frac{101}{(j\omega+1-j10)(j\omega+1+j10)}$$

$$|H(j\omega)| = \left| \frac{101}{(j\omega+1-j10)(j\omega+1+j10)} \right|$$

$$= \frac{101}{(\sqrt{1+(\omega-10)^2})(\sqrt{1+(\omega+10)^2})}$$

$$|H(0)| = \frac{101}{(\sqrt{1+(10)^2})(\sqrt{1+(10)^2})} = 1$$

$$|H(j10)| = \frac{101}{(\sqrt{1+(10-10)^2})(\sqrt{1+(10+10)^2})}$$

$$= \frac{101}{\sqrt{1+20^2}} = \frac{101}{\sqrt{401}} = 5.04$$

$$|H(j\omega)| \xrightarrow{\lim \omega \rightarrow \infty} 0$$

$$V_o(s) = \frac{1/sC}{R+sL+1/sC} V_{in}(s)$$

$$\frac{V_o(s)}{V_{in}(s)} = \frac{1}{sCR+s^2LC+1}$$



$$= \frac{1}{s \frac{1}{101} 2 + s^2 1 \frac{1}{101} + 1}$$

$$= \frac{101}{s^2 + 2s + 101} = \frac{101}{(s+1-j10)(s+1+j10)}$$


$s = -1 \pm j10$  transient response damped sinusoid



## Example #1 (Continued)

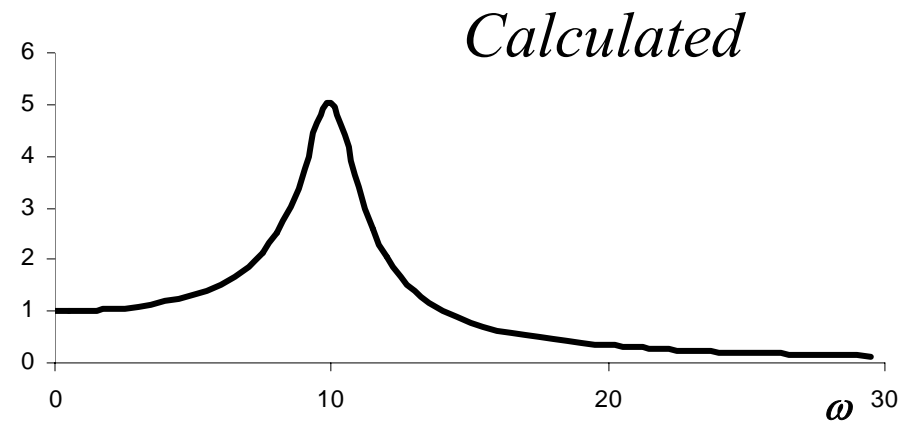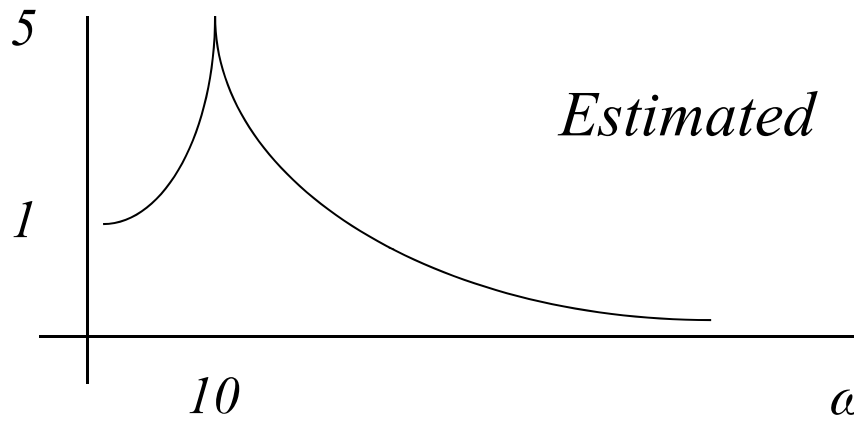

## Example #2

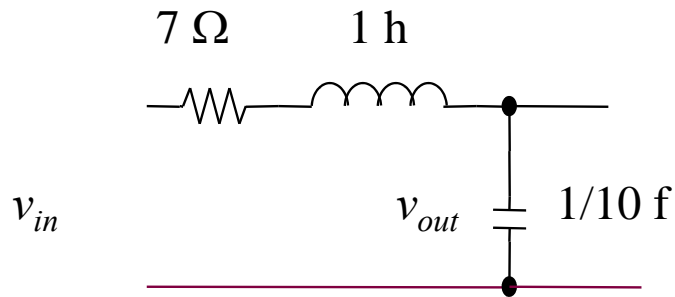

$$V_o(s) = \frac{1/sC}{R + sL + 1/sC} V_{in}(s)$$

$$\frac{V_o(s)}{V_{in}(s)} = \frac{1}{sCR + s^2LC + 1}$$

$$= \frac{1}{s \frac{1}{10} 7 + s^2 1 \frac{1}{10} + 1}$$

$$= \frac{10}{s^2 + 7s + 10} = \frac{10}{(s+2)(s+5)}$$

$s = -2, -5$  transient response

decaying exponentials

Frequency Response

$$\frac{V_o(s)}{V_{in}(s)} = \frac{10}{(s+2)(s+5)}$$

$$H(j\omega) = \frac{10}{(j\omega+2)(j\omega+5)}$$

$$|H(j\omega)| = \left| \frac{10}{(j\omega+2)(j\omega+5)} \right|$$

$$= \frac{10}{(\sqrt{4+\omega^2})(\sqrt{25+\omega^2})}$$

$$|H(0)| = \frac{10}{(\sqrt{4})(\sqrt{25})} = 1$$



$$|H(j\omega)| \xrightarrow{\lim \omega \rightarrow \infty} 0$$

$$|H(2)| = \frac{10}{(\sqrt{4+4})(\sqrt{25+4})}$$


$$= \frac{10}{(2\sqrt{2})(\sqrt{29})} = \frac{5}{1.41 * 5.39}$$

$$= \frac{5}{1.41 * 5.39} = .657$$

## Example #2 (Continued)

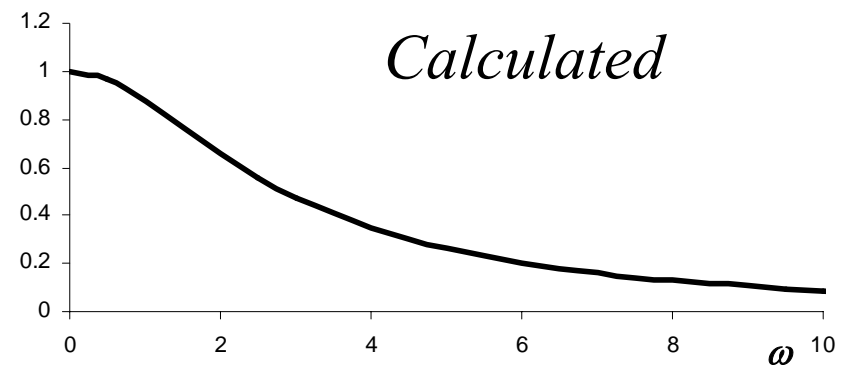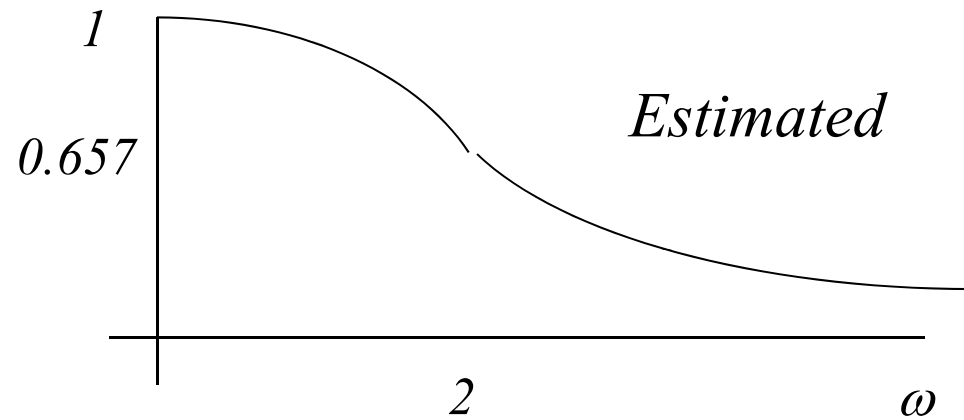

## Example #3

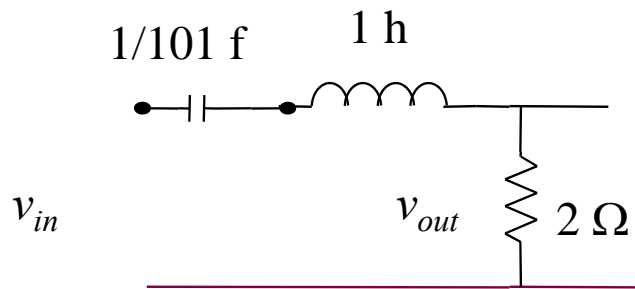

Frequency Response

$$\frac{V_o(s)}{V_{in}(s)} = \frac{2s}{(s+1-j10)(s+1+j10)}$$

$$H(j\omega) = \frac{2s}{(j\omega+1-j10)(j\omega+1+j10)}$$

$$|H(j\omega)| = \left| \frac{2j\omega}{(j\omega+1-j10)(j\omega+1+j10)} \right|$$

$$= \frac{2\omega}{(\sqrt{1+(\omega-10)^2})(\sqrt{1+(\omega+10)^2})}$$

$$|H(0)| = \frac{2 \times 0}{(\sqrt{1+(10)^2})(\sqrt{1+(10)^2})} = 0$$

$$|H(j10)| = \frac{20j}{(\sqrt{1+(10-10)^2})(\sqrt{1+(10+10)^2})}$$

$$= \frac{20}{\sqrt{1+20^2}} = \frac{20}{\sqrt{401}} = .998$$

$$|H(j\omega)| \xrightarrow{\lim \omega \rightarrow \infty} 0$$

$$V_o(s) = \frac{R}{R+sL+1/sC} V_{in}(s)$$



$$\frac{V_o(s)}{V_{in}(s)} = \frac{sCR}{sCR+s^2LC+1}$$

$$= \frac{s \frac{1}{101} 2}{s \frac{1}{101} 2 + s^2 1 \frac{1}{101} + 1}$$

$$= \frac{2s}{s^2 + 2s + 101} = \frac{2s}{(s+1-j10)(s+1+j10)}$$

$s = -1 \pm j10$  transient response damped sinusoid

## Example #3 (Continued)

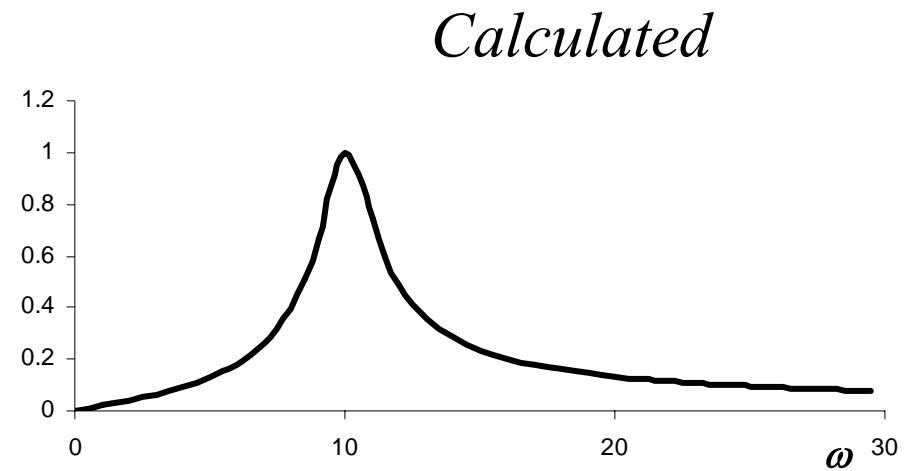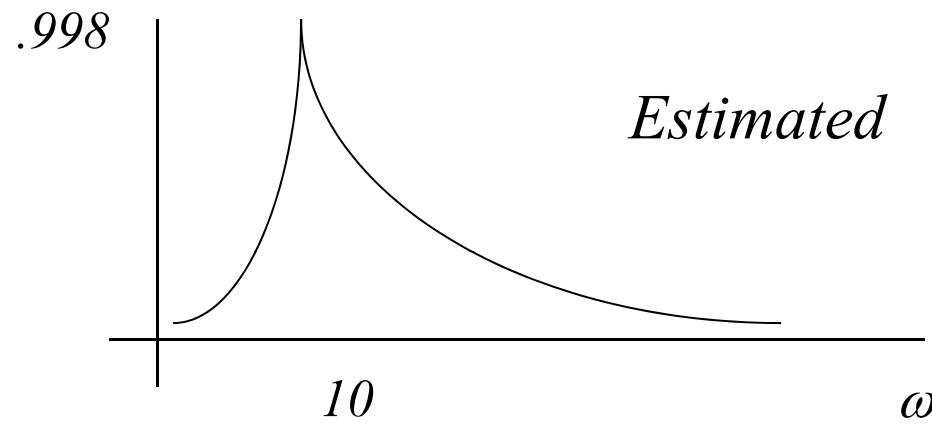

# *Effects of Feedback on Pole Location Single Pole Amplifiers*

Let's assume that the open - circuit gain of an amplifier is of the form :

$$A(s) = \frac{A_o}{(s/2\pi f_b) + 1}$$

Adding feedback to the amplifier :

$$\begin{aligned} A_f(s) &= \frac{\frac{A_o}{(s/2\pi f_b) + 1}}{1 + \beta \frac{A_o}{(s/2\pi f_b) + 1}} \\ &= \frac{A_o}{(s/2\pi f_b) + 1 + \beta A_o} \end{aligned}$$

$$\begin{aligned} A_f(s) &= \frac{A_o}{(s/2\pi f_b) + 1 + \beta A_o} \\ &= \frac{A_o / (1 + \beta A_o)}{[s/2\pi f_b (1 + \beta A_o)] + 1} \\ &= \frac{A_{of}}{(s/2\pi f_{bf}) + 1} \end{aligned}$$

where :

$$\begin{aligned} A_{of} &= \frac{A_o}{1 + \beta A_o}, \\ f_{bf} &= f_b (1 + \beta A_o) \end{aligned}$$

## Example #1

- Study the frequency response of an amplifier with open-loop mid-band gain  $=10^5$  and break frequency  $f_b=10$  Hz for feedback of  $\beta = 0.01, 0.1$  and  $1$

Without feedback :

$$\begin{aligned}A_{o\text{dB}} &= 20\log|A_o| = 20\log 10^5 \\ &= 20 \times 5 = 100\end{aligned}$$

$$f_b = 10 \text{ Hz}$$

With  $\beta = 0.01$ :

$$\begin{aligned}A_{of} &= \frac{A_o}{1 + A_o\beta} = \frac{10^5}{1 + .01 \times 10^5} \\ &= \frac{10^5}{1001} = 99.9\end{aligned}$$

$$\begin{aligned}A_{of\text{dB}} &= 20\log|A_{of}| = 20\log 99.9 \\ &= 40\end{aligned}$$

$$\begin{aligned}f_{bf} &= f_b(1 + \beta A_o) = 10 \times (1 + 0.01 \times 10^5) \\ &= 10 \text{ k Hz}\end{aligned}$$

With  $\beta = 0.1$ :

$$A_{of} = \frac{A_o}{1 + A_o\beta} = \frac{10^5}{1 + .1 \times 10^5} = 10$$

$$A_{of\text{dB}} = 20\log|A_{of}| = 20$$

$$f_{bf} = f_b(1 + \beta A_o) = 100 \text{ k Hz}$$

With  $\beta = 1$ :


$$A_{of} = \frac{A_o}{1 + A_o\beta} = \frac{10^5}{1 + 1 \times 10^5} = 1$$

$$A_{of\text{dB}} = 20\log|A_{of}| = 0$$

$$f_{bf} = f_b(1 + \beta A_o) = 1 \text{ M Hz}$$

## Example #1 (Continued)

### Gain-Bandwidth Product

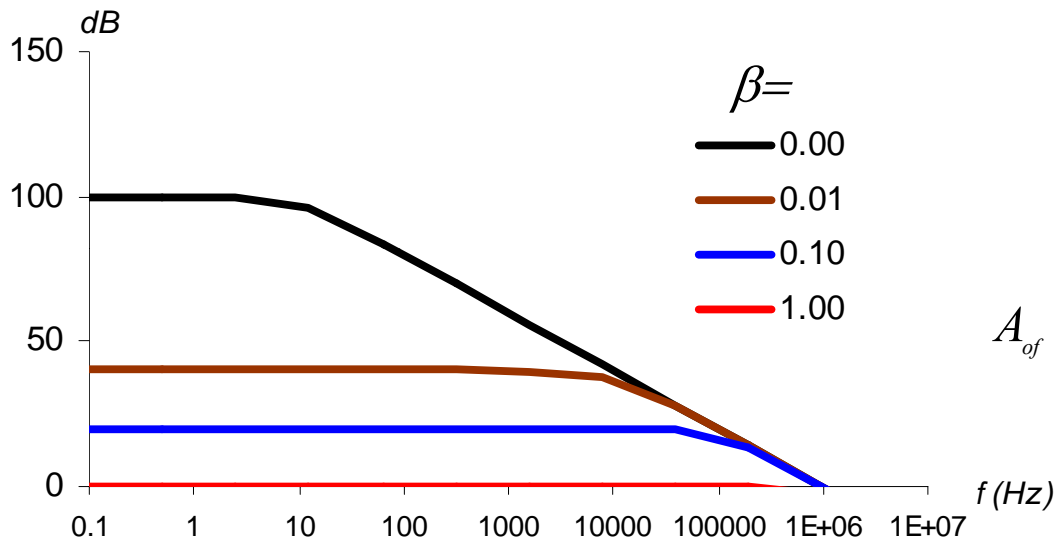

$$A_{of} = \frac{A_o}{1 + \beta A_o}$$

$$f_{bf} = f_b (1 + \beta A_o)$$

$$A_{of} \times f_{bf} = \frac{A_o}{1 + \beta A_o} \times f_b (1 + \beta A_o)$$


$$= A_o f_b$$

Note that as the feedback is increased (i.e.,  $\beta$  increases) the pole moves further away from the origin. For single pole amplifiers, this also implies that the transient time constant decreases since  $\tau = 1/2\pi f_{bf}$ .


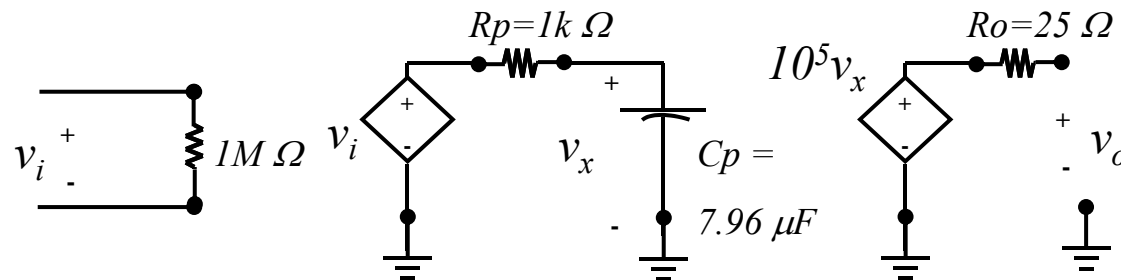
## Example #2a

- For the Single Pole amplifier, find the pole for the open loop gain.
- Prepare a Bode Plot
- Find the Gain-Bandwidth Product



$$v_o = 10^5 v_x = 10^5 \frac{1/sC_p}{1/sC_p + R_p} v_i$$

$$A_{vo}(s) = \frac{v_o}{v_i} = \frac{10^5}{1 + sR_p C_p} = \frac{10^5}{1 + sR_p C_p}$$

$$= \frac{10^5}{1 + s(10^3)(7.96 \times 10^{-6})} = \frac{10^5}{1 + 7.96 \times 10^{-3} s}$$

$$A_{vo}(j\omega) = \frac{10^5}{1 + 7.96 \times 10^{-3} j\omega}$$

$$A_{vo}(j0) = \frac{10^5}{1 + 0} = 10^5$$

$$A_{vo}(j0)_{dB} = 20 \log 10^5 = 100 \text{ dB}$$

$$f_b = \frac{1}{2\pi(7.96 \times 10^{-3})} = 20 \text{ Hz}$$


$$A_{vo}(j0) = A_o = \frac{10^5}{1 + 0} = 10^5$$

$$f_b = \frac{1}{2\pi(7.96 \times 10^{-3})} = 20 \text{ Hz}$$

$$A_o \times f_b = 10^5 \times 20 \text{ Hz} = 2 \text{ MHz}$$
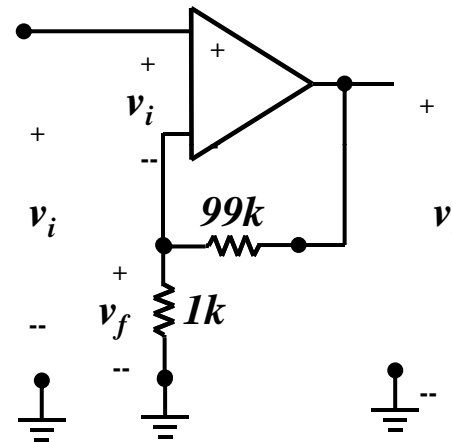
## Example #2b

- Using the amplifier in 1b in the following feedback circuit, calculate:
  - $\beta$
  - Closed-loop gain at DC
  - Closed-loop bandwidth



$$\beta = \frac{1k}{1k + 99k} = .01$$

$$A_{of} = \frac{A_o}{1 + \beta A_o} = \frac{10^5}{1 + .01 \times 10^5}$$

$$= \frac{10^5}{1 + 10^3} = 99.9$$

$$f_{bf} = f_b (1 + \beta A_o) = 20 \times (1 + 10^3)$$


$$= 20kHz$$

# *Gain and Phase Margin*

## *Stability of Feedback Amplifiers*

- Examine the Closed-loop gain as a function of frequency
- For a given frequency  $f_1$ ,  $\beta A(f_1) = -1$ , then the closed-loop gain will be infinite (i.e., a pole at  $s=j2\pi f_1$ )
  - Note that without a source signal, then the input signal equals the feedback signal and  $v_{in} = -\beta A(f_1) v_{out}$
  - When the phase of  $\beta A(f_1) = 180^\circ$ 
    - if  $|\beta A(f_1)| < 1$ , the looped signal decays in amplitude –Stable
    - if  $|\beta A(f_1)| > 1$ , the looped signal grows in amplitude - Unstable
- We define Gain Margin, which is the amount (in dB) of gain below 0 dB when the phase of  $\beta A(f_1) = 180^\circ$ .
  - The larger the gain margin the more stable the amplifier (i.e., the poles are deeper into the left hand  $s$ -plane.
- We define the Phase Margin, which is defined at the frequency,  $f_{pm}$ , at which  $\beta A(f_{pm})$  is unity and is equal to the difference between the phase of  $\beta A(f_{pm})$  and  $180^\circ$ .
  - The larger the phase margin the more stable the amplifier.

# Stability of a Feedback Amplifier

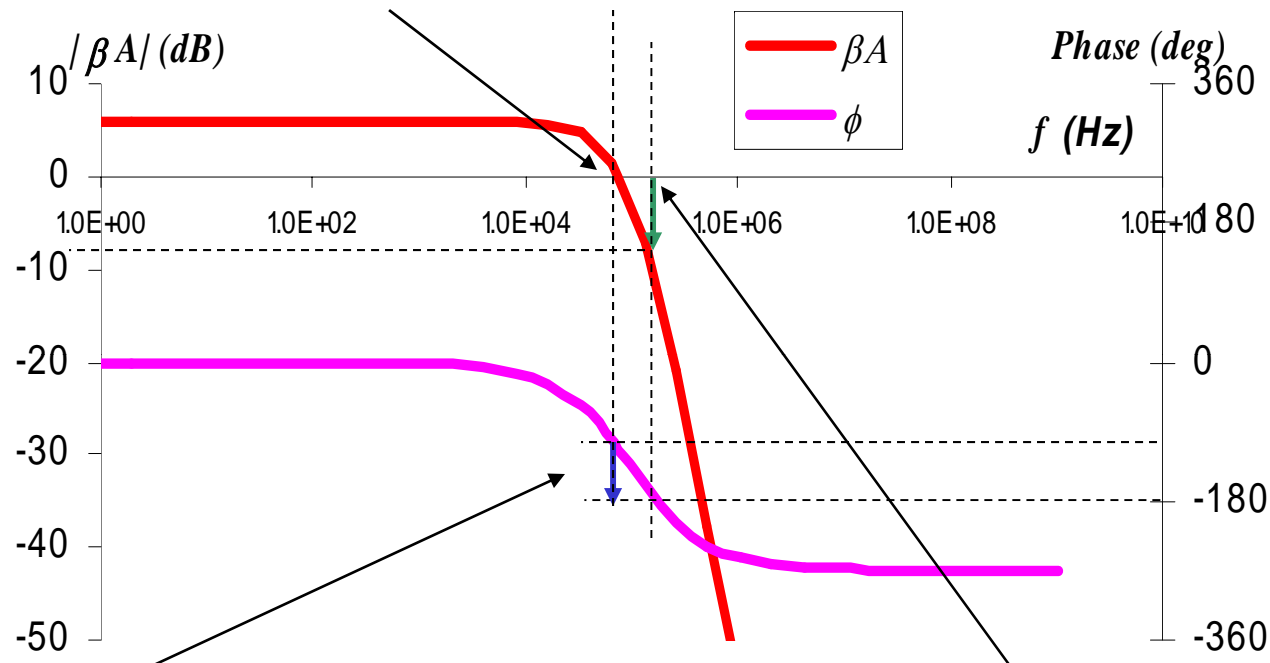

$$PM = 180 - 112 = 68^\circ \quad f_{PM} = 76.6 \text{ kHz}$$

$$GM = -9 \text{ dB} \quad f_{GM} = 173 \text{ kHz}$$

$$A(s) = \frac{1000}{(s/2\pi f_b + 1)^3}$$

$$f_b = 100 \text{ kHz}$$

$$\beta = 0.002$$

## *Homework*

- Transient Response
  - Problems: 9.58-59
- Effects of Feedback on Pole Locations
  - Problems: 9.63-66
- Gain and Phase Margin
  - Problems: 9.72-73