

Waveshapping Circuits and Data Converters

Lesson #17

Comparators and Schmitt Triggers

Section 12.1

Waveshapping Circuits and Data Converters

- Comparators and Schmitt Triggers
- Astable Multivibrators and Timers
- Rectifiers, Peak Detectors, Sample-and-Hold
- A/D and D/A Converters

Comparators

- Circuits which compare two input voltages, v_1 and v_2 , and produces a logic output

– E.g.




- High if $v_1 > v_2$
- Low if $v_1 < v_2$

– Inputs:

- Inverted and non-inverted
- $v_i = v_1 - v_2$


– Ideal Transfer Characteristics

- Symmetrical or Unsymmetrical

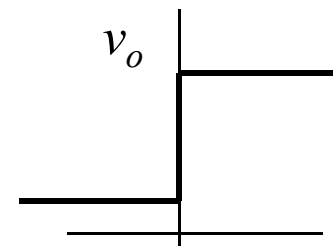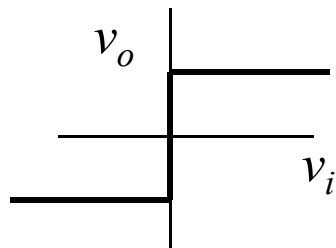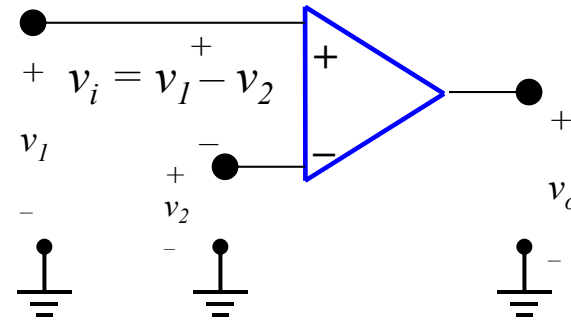

Real Comparators



- Real Comparators have a gradual transition
- $|v_i| > 0.2 \text{ mV}$ to cause a change in state.

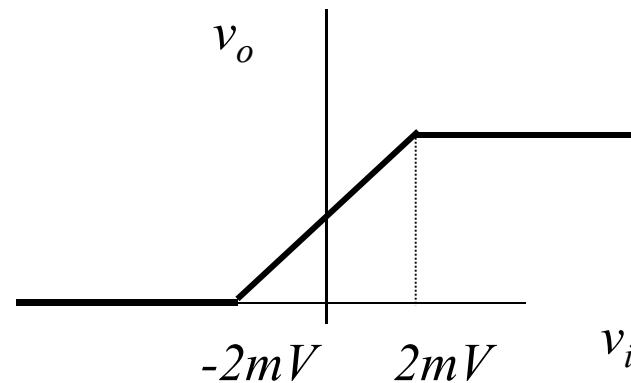

- Interface Analog to Digital signals and may have different voltage ranges
 - +15 to – 15 V on the analog side
 - +5 to 0 V on the digital side

Schmitt Triggers

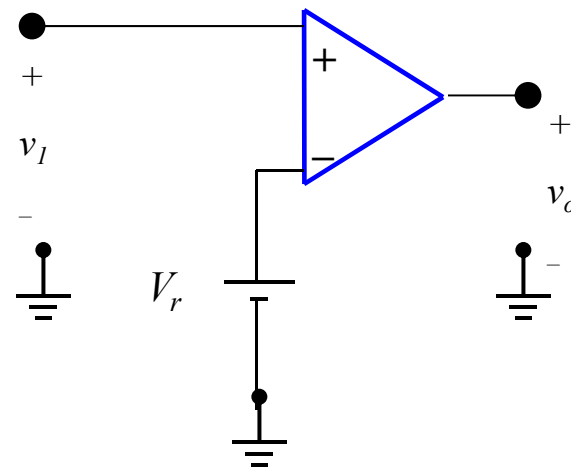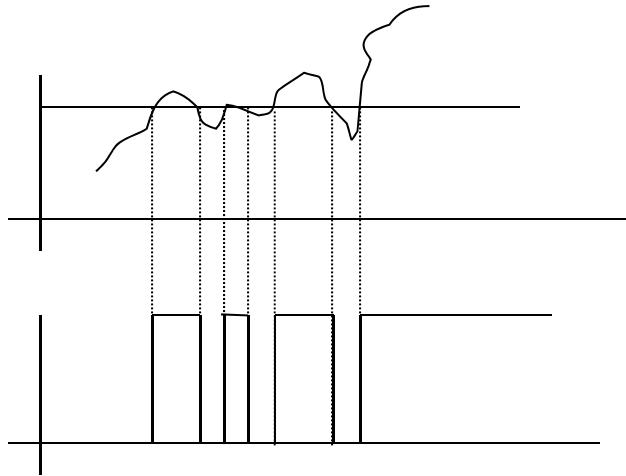
- Noise on the input can cause undesirable transitions in the output of a comparator.
 - Example: comparing a noisy signal to a reference voltage.



- Through the use of positive feedback to the comparator, this problem can be eliminated - The Schmitt Trigger

Effects of Positive Feedback


- From this circuit: $v_o = Av_i$ and $v_i = v_f - v_{in} = \beta v_o - v_{in}$
- Because of the positive feedback v_i is no longer equal to zero (not a virtual ground)
- So as v_i increases in the positive (negative) direction, increases in the positive (negative) direction.
- Because of the positive feedback, this will increase v_i in the positive direction (negative) which will further increase v_o which further increase v_i and so on.
- When will this stop?

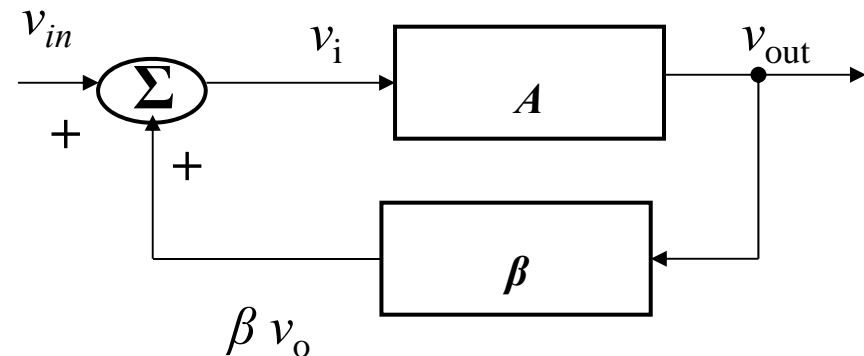

- If we had infinite power, then never.
- However, we have limited power which is given by the amplifier's DC voltage supplies: $+A$, $-A$.
- If v_i goes positive, then v_o “instantaneously” grows to $+A$ volts
- And if v_i goes negative, then v_o “instantaneously” grows to $-A$ volts

Hysteresis

- Assume that $\beta = R_2 / (R_1 + R_2) = 0.1$ and v_o levels are $+10$ (for $v_i > 0$) and -10 V (for $v_i < 0$).
- First, note that $v_i = v_f - v_{in}$. Now, let's assume $v_o = +10$ V and therefore $v_f = 1$ V then as long as v_{in} is less than 1 V, then $v_o = +10$ V (it's high state) since v_i , the input to the comparator, will be > 0 . Once v_{in} surpasses 1 , $v_i < 0$, and the output will switch to -10 V.
- At this point, $v_f = -1$ V and as long as the $v_{in} > -1$ V, the output will stay in its low state, -10 V.
- Note that has the characteristic of being a flip-flop. If one pulses it with high (> 1), then the output switches to a low and visa versa.

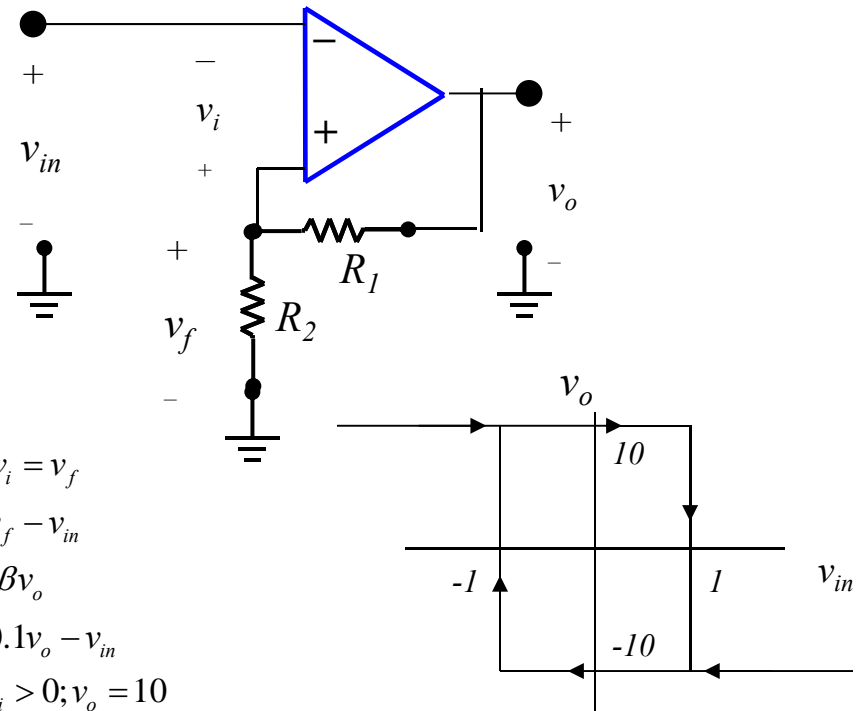

$$v_{in} + v_i = v_f$$

$$v_i = v_f - v_{in}$$

$$v_f = \beta v_o$$

$$v_i = 0.1v_o - v_{in}$$

$$\text{For } v_i > 0; v_o = 10$$

$$v_i = 0.1 \times 10 - v_{in} > 0 \Rightarrow 1 - v_{in} > 0 \Rightarrow 1 > v_{in}$$

$$v_{in} < 1$$

$$\text{For } v_i < 0; v_o = -10$$

$$v_i = 0.1v_o - v_{in} < 0 \Rightarrow -0.1 \times 10 - v_{in} < 0 \Rightarrow -1 < v_{in}$$

$$v_{in} > -1$$

This is characteristic is called **hysteresis**

Inverter

$$v_{in} + v_i = v_f$$

$$v_i = v_f - v_{in}$$

$$v_f = \beta v_o$$

$$v_i = \beta v_o - v_{in}$$

For $v_i > 0; v_o = A$

$$v_i = \beta v_o - v_{in} > 0 \Rightarrow \beta A - v_{in} > 0 \Rightarrow \beta A > v_{in}$$



$$v_{in} < \beta A$$

For $v_i < 0; v_o = -A$

$$v_i = \beta v_o - v_{in} < 0 \Rightarrow -\beta A - v_{in} < 0 \Rightarrow -\beta A < v_{in}$$



$$v_{in} > -\beta A$$

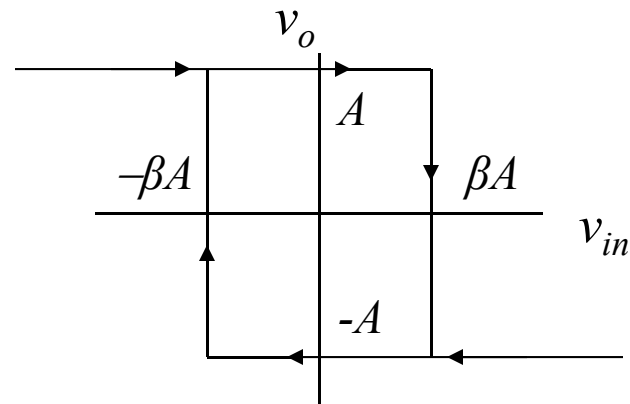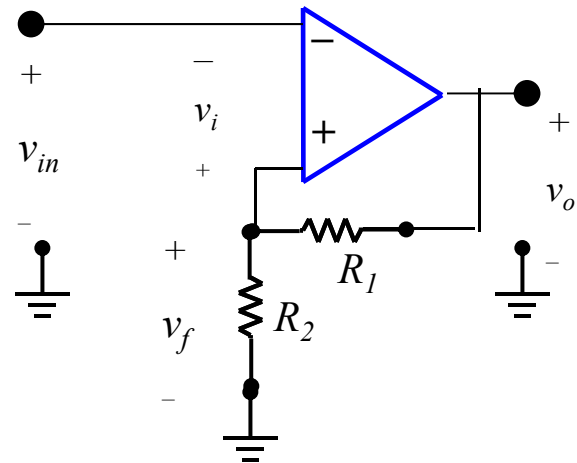Note that $\pm \beta A$ volts are the thresholds for when the circuit switches states.




Other Forms of Schmitt Triggers

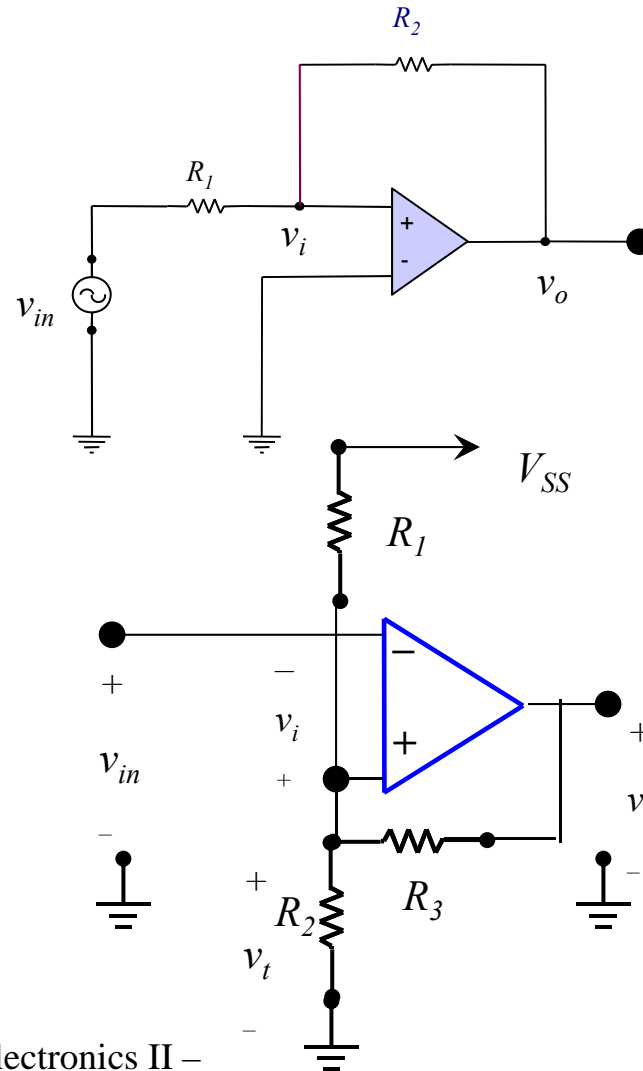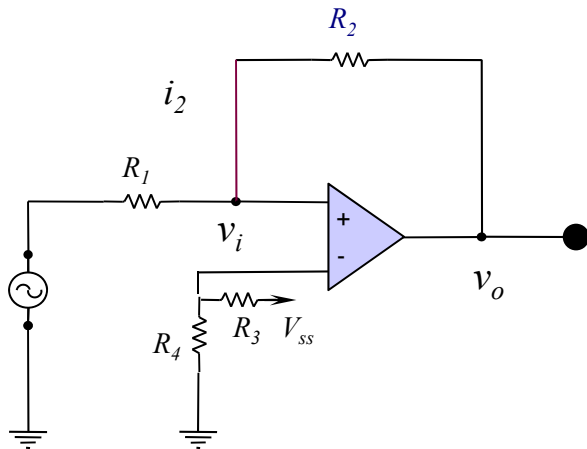- Non-inverting types
- Specified Thresholds



Specific Thresholds

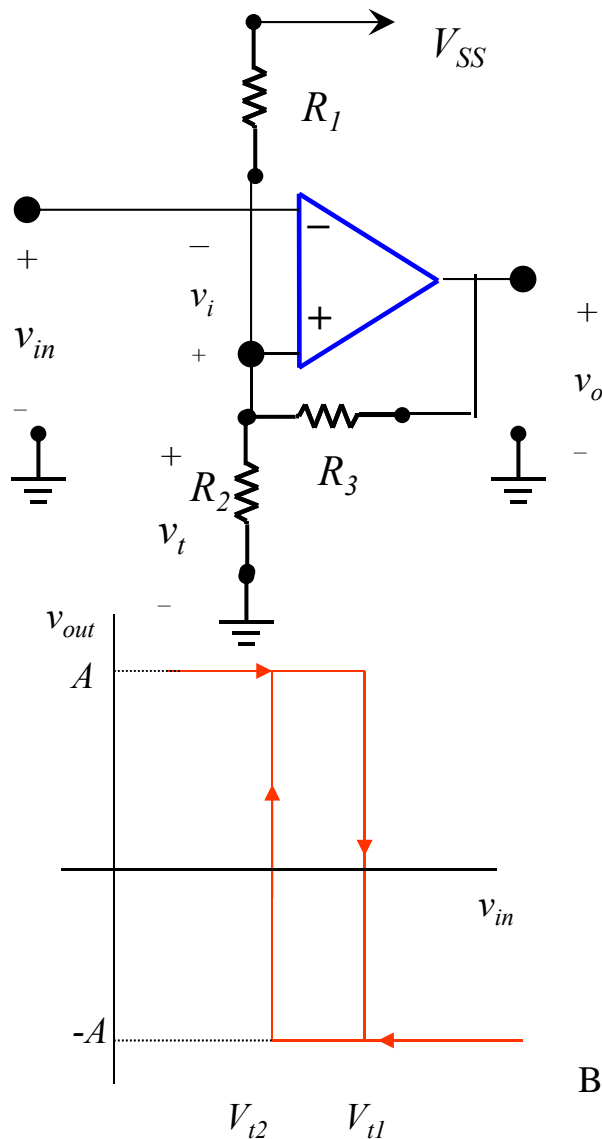

$$v_i = v_t - v_{in}$$

$$v_i > 0; v_o = +A$$

$$v_i < 0; v_o = -A$$

From node at noninverting input:

$$\frac{v_t}{R_2} + \frac{v_t - v_o}{R_3} + \frac{v_t - V_{SS}}{R_1} = 0$$

$$v_t = \frac{\frac{v_o}{R_3} + \frac{V_{SS}}{R_1}}{\frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_1}} = \frac{v_o}{G_T R_3} + \frac{V_{SS}}{G_T R_1}$$


$$v_i = \frac{v_o}{G_T R_3} + \frac{V_{SS}}{G_T R_1} - v_{in}$$

$$v_i = \frac{A}{G_T R_3} + \frac{V_{SS}}{G_T R_1} - v_{in} > 0; v_{in} < V_{t1} = \frac{A}{G_T R_3} + \frac{V_{SS}}{G_T R_1}$$

$$v_i = \frac{-A}{G_T R_3} + \frac{V_{SS}}{G_T R_1} - v_{in} < 0; v_{in} > V_{t2} = \frac{-A}{G_T R_3} + \frac{V_{SS}}{G_T R_1}$$

An Example

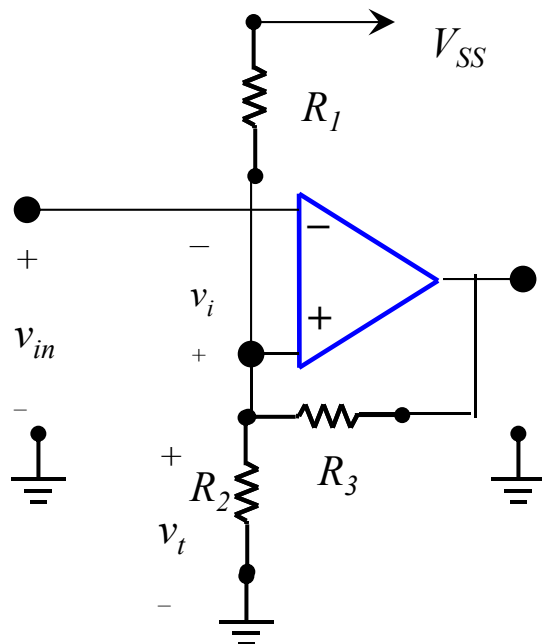- Choose the 3 resistors to provide thresholds of $5 \pm 0.1 V$ for output levels of $\pm 14.6 V$.



At the non - inverting mode, we have :

$$\frac{V_t}{R_2} + \frac{V_t - V_{SS}}{R_1} + \frac{V_t - v_o}{R_3} = 0$$

Using $15 V$ for V_{SS} and $V_t = 5.1$ for $v_o = +14.6$, we have

$$\frac{5.1}{R_2} + \frac{5.1 - 15}{R_1} + \frac{5.1 - 14.6}{R_3} = \frac{5.1}{R_2} + \frac{9.9}{R_1} + \frac{9.5}{R_3} = 0$$

Using $V_t = 4.9$ for $v_o = -14.6$, we have

$$\frac{4.9}{R_2} + \frac{4.9 - 15}{R_1} + \frac{4.9 + 14.6}{R_3} = \frac{4.9}{R_2} + \frac{10.1}{R_1} + \frac{19.5}{R_3} = 0$$

- We need to choose one of the 3 resistors. If we choose $R_3 = 1 M$, then $R_1 = 20.55 k$ and $R_2 = 10.38 k$. If we chose resistors too small then may draw excessive amounts of current from our $15 V$ supply and create a large power drain on the circuit.

Example continued

$$v_i = v_t - v_{in}$$

when $v_i > 0$; $v_o = +14.6v$

therefore,

$$v_i = v_t - v_{in} > 0$$

$$v_t > v_{in}; \text{ or } v_{in} < 5.1$$


$$v_i = v_t - v_{in}$$

when $v_i < 0$; $v_o = -14.6v$

therefore,

$$v_i = v_t - v_{in} < 0$$
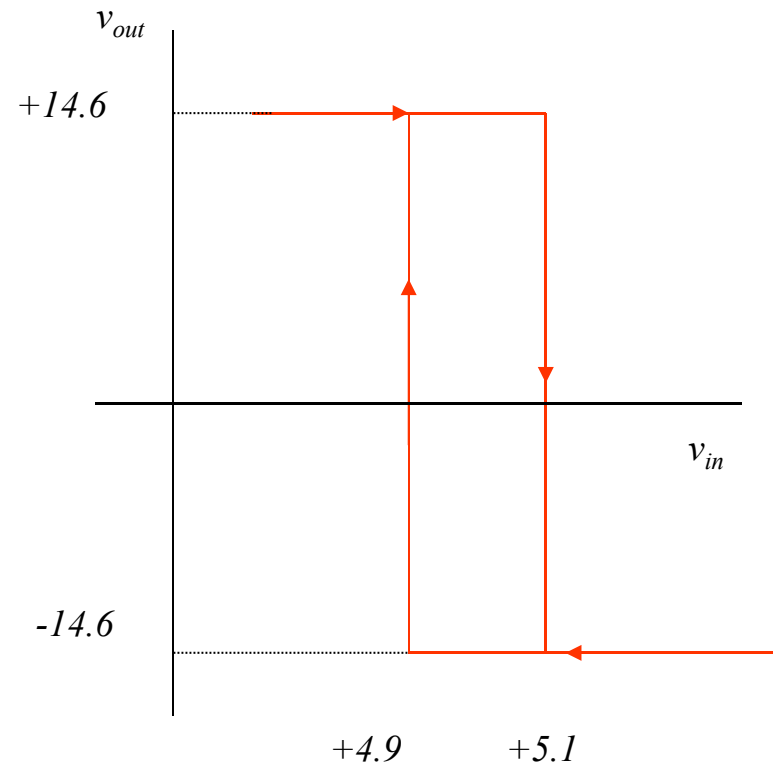
$$v_t < v_{in}; \text{ or } v_{in} > 4.9$$



Another Example

- What are the transfer characteristics for this circuit if $R_1 = 1k$ and $R_2 = 2k$ and the thresholds levels are $\pm 10 V$.

$$V_{in} = i(R_1 + R_2) + v_o$$

$$V_t = iR_1 = \frac{V_{in} - v_o}{R_1 + R_2} R_1$$

$$v_i = V_{in} - V_t = V_{in} - \frac{V_{in} - v_o}{R_1 + R_2} R_1$$


$$v_i = V_{in} - \frac{V_{in} - v_o}{3} = \frac{2}{3} V_{in} + \frac{v_o}{3}$$

For $v_o = +10 V$, $v_i > 0$

$$v_i = \frac{2}{3} V_{in} + \frac{v_o}{3} > 0; \frac{2}{3} V_{in} > -\frac{v_o}{3}; V_{in} > -5$$

For $v_o = -10 V$, $v_i < 0$
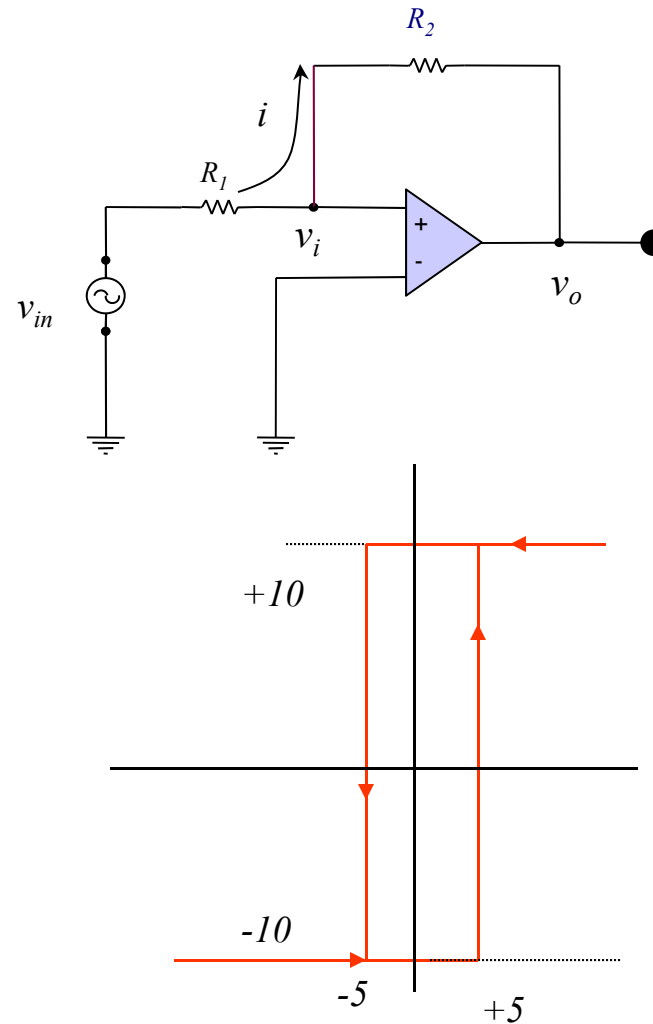
$$v_i = \frac{2}{3} V_{in} + \frac{v_o}{3} < 0; \frac{2}{3} V_{in} < -\frac{v_o}{3}; V_{in} < 5$$



Homework

- Comparators and Schmitt Trigger Circuits
– Problems: 12.8-9