

Waveshapping Circuits and Data Converters

Lesson #18

Astable Multivibrators

Section 12.2

Astable Multivibrators

- A switching oscillator or Astable Multivibrator can be formed from a Schmitt trigger as follows:
- Assume that output levels are $\pm A$ and the thresholds are $\pm A/2$ since the feedback voltage = $\frac{1}{2} v_o$.

$$v_i = v_t - v_{in}$$

when $v_i > 0$; $v_o = A$; therefore,

$$v_i = v_t - v_{in} > 0$$



$$v_t > v_{in}; \text{ or } v_{in} < \frac{A}{2}$$

$$v_i = v_t - v_{in}$$

when $v_i < 0$; $v_o = -A$; therefore,




$$v_i = v_t - v_{in} < 0$$
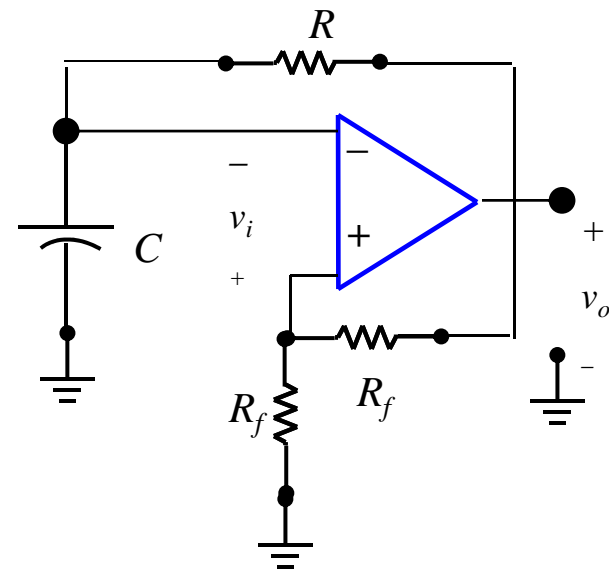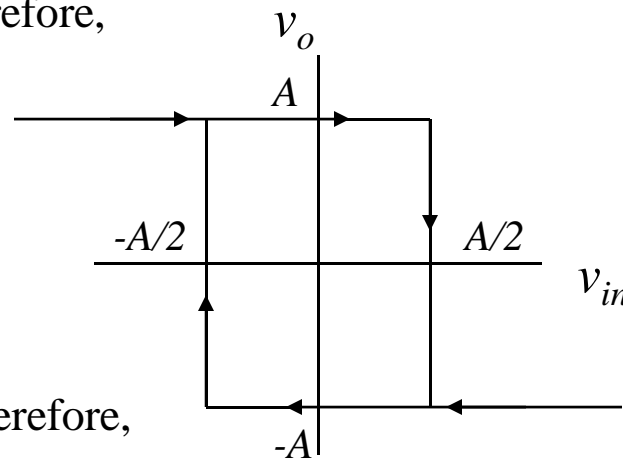
$$v_t < v_{in}; \text{ or } v_{in} > -\frac{A}{2}$$




Astable Multivibrators

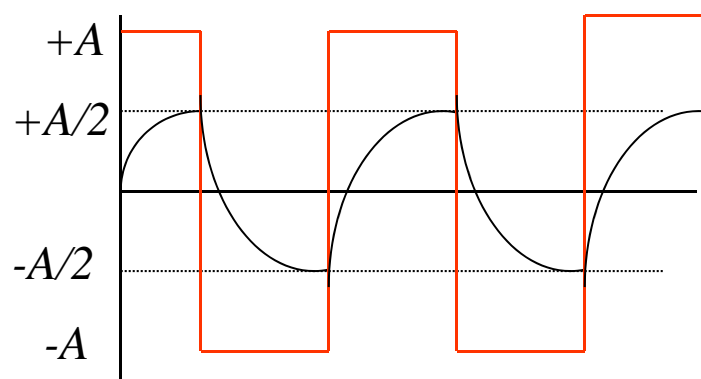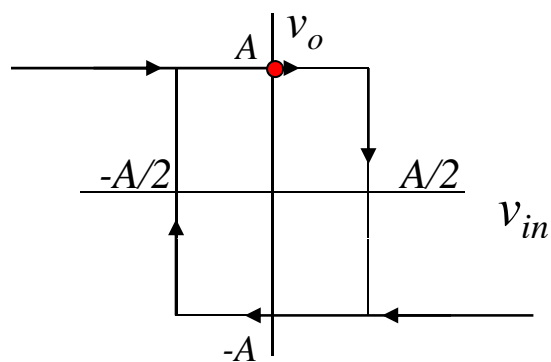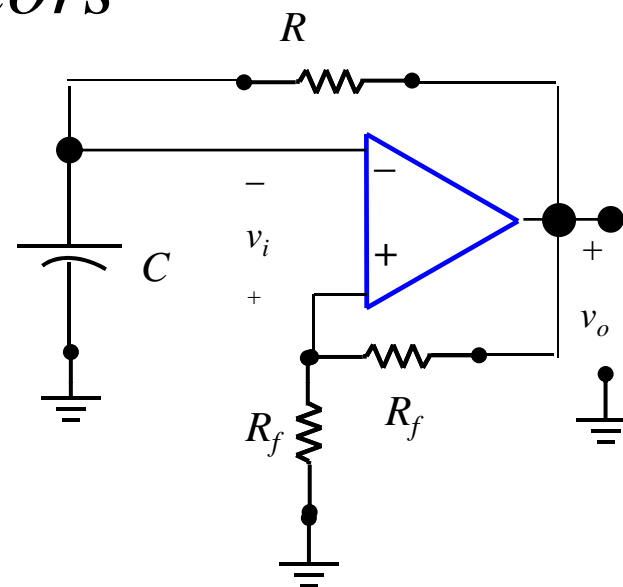- Assume that the output starts off at $+A$.
- The capacitor starts to charge to $+A$
- However, when it reaches $+A/2$, $v_i = 0$ and the output switches to $-A$.
- The capacitor then charges to $-A$.
- However, when it reaches $-A/2$, $v_i = 0$ and the output switches to $+A$
- And the capacitor charges to $+A$
- This process continues.



Timing Calculation

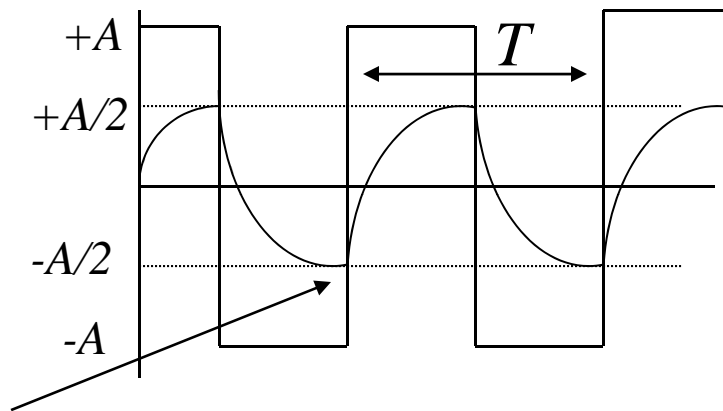

Start the timing calculation here

$$v_c(t) = K_1 + K_2 e^{-t/RC}$$

Initial Condition :

$$v_c(0) = -\frac{A}{2} = K_1 + K_2 e^{-0/RC} = K_1 + K_2 \text{ (eqn.1)}$$

Final Condition :

$$v_c(\infty) = +A = K_1 + K_2 e^{-\infty/RC} = K_1 \text{ (eqn.2)}$$

From eqns (1) and (2)

$$K_1 = A$$

$$K_2 = -\frac{A}{2} - K_1 = -\frac{3}{2}A$$

$$v_c(t) = A\left(1 - \frac{3}{2}e^{-t/RC}\right)$$

But

$$v_c\left(\frac{T}{2}\right) = \frac{A}{2} = A\left(1 - \frac{3}{2}e^{-T/2RC}\right)$$

$$\therefore e^{-T/2RC} = \frac{1}{3}$$

$$T = 2RC \ln(3)$$


An Example

- Assume output levels are $\pm A$

1. What are the thresholds?


$$\beta = 2R_f / (2R_f + R_f) \Rightarrow \pm 2/3A$$

2. Sketch v_c and v_o

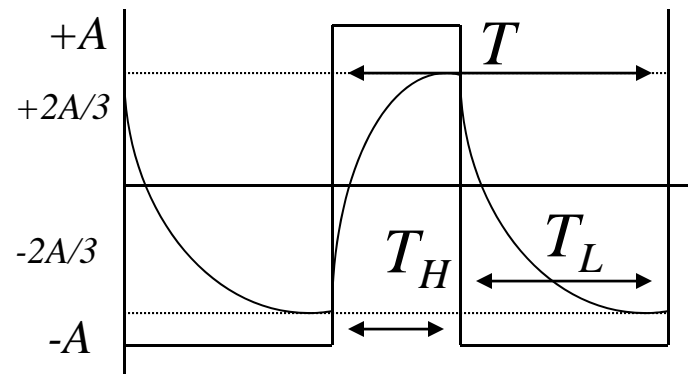

3. Duty Cycle of the Pulse $T_L = 2T_H$

4. Frequency of Oscillation

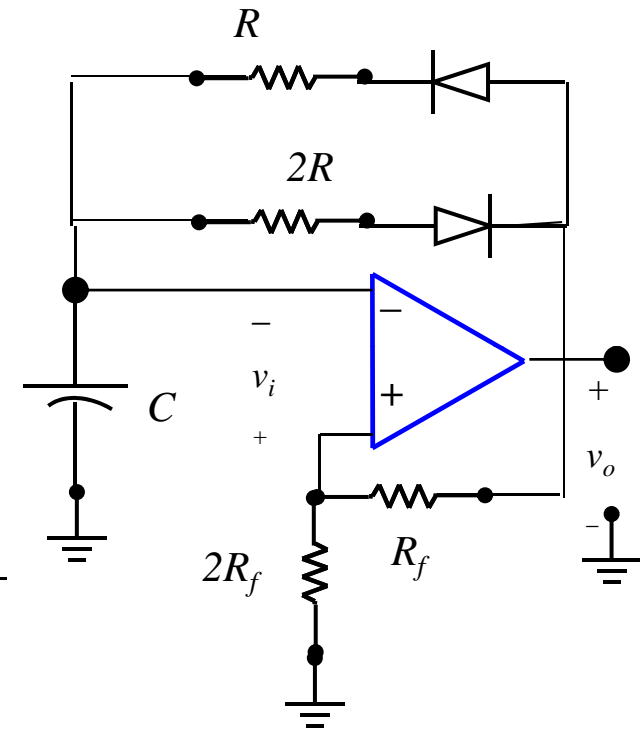

Frequency of Oscillation

For Charging to +A

$$v_c(t) = K_1 + K_2 e^{-t/RC}$$

Initial Condition :

$$v_c(0) = -\frac{2A}{3} = K_1 + K_2 e^{-0/RC} = K_1 + K_2 \text{ (eqn.1)}$$

Final Condition :

$$v_c(\infty) = +A = K_1 + K_2 e^{-\infty/RC} = K_1 \text{ (eqn. 2)}$$

From eqns (1) and (2)

$$K_1 = A$$

$$K_2 = -\frac{2A}{3} - K_1 = -\frac{5}{3}A$$

$$v_c(t) = A(1 - \frac{5}{3}e^{-t/RC})$$

But

$$v_c(T_H) = \frac{2A}{3} = A(1 - \frac{5}{3}e^{-T_H/RC})$$

$$\therefore e^{-T_H/RC} = \frac{1}{5}$$

$$T_H = RC \ln(5)$$

For Charging to -A

$$v_c(t) = K_1 + K_2 e^{-t/2RC}$$

Initial Condition :

$$v_c(0) = \frac{2A}{3} = K_1 + K_2$$

Final Condition :

$$v_c(\infty) = -A = K_1$$

$$K_2 = \frac{2A}{3} - K_1 = \frac{5}{3}A$$


$$v_c(t) = A(\frac{5}{3}e^{-t/2RC} - 1)$$

But

$$v_c(T_L) = -\frac{2A}{3} = A(\frac{5}{3}e^{-T_L/2RC} - 1)$$

$$\therefore e^{-T_L/2RC} = \frac{1}{5}$$

$$T_L = 2RC \ln(5)$$

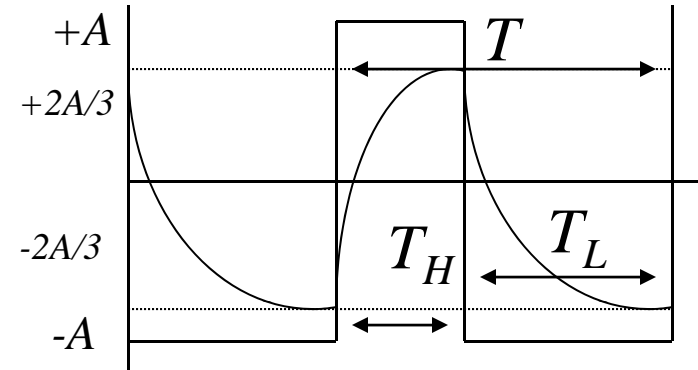

$$T = T_H + T_L = 3RC \ln(5)$$

$$f = \frac{1}{3RC \ln(5)}$$

Another Example

- Assume output levels are 0 and A
 - What are the Thresholds
 - Sketch v_c and v_o
 - Frequency of Oscillation



$$v_t = \frac{R_f \parallel R_f}{R_f + R_f \parallel R_f} A + \frac{R_f \parallel R_f}{R_f + R_f \parallel R_f} v_o$$

$$v_t = \frac{R_f/2}{R_f + R_f/2} A + \frac{R_f/2}{R_f + R_f/2} v_o$$

$$v_t = \frac{1}{3} A + \frac{1}{3} v_o$$

$$v_{t_{v_o=0}} = \frac{1}{3} A$$

$$v_{t_{v_o=A}} = \frac{2}{3} A$$

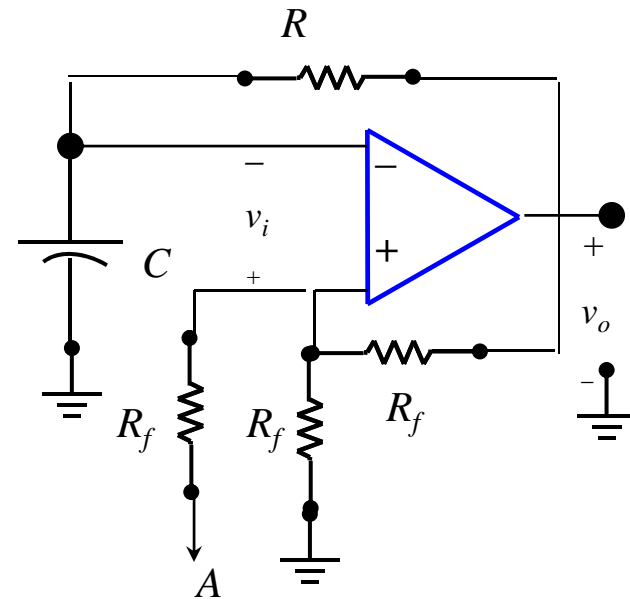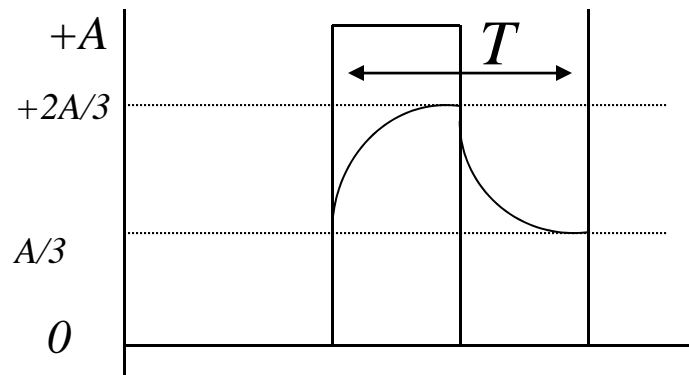

Frequency of Oscillation

For Charging to +A

$$v_c(t) = K_1 + K_2 e^{-t/RC}$$

Initial Condition :

$$v_c(0) = \frac{A}{3} = K_1 + K_2$$

Final Condition :

$$v_c(\infty) = +A = K_1$$

$$K_2 = \frac{A}{3} - K_1 = -\frac{2}{3}A$$

$$v_c(t) = A\left(1 - \frac{2}{3}e^{-t/RC}\right)$$


But

$$v_c\left(\frac{T}{2}\right) = \frac{2A}{3} = A\left(1 - \frac{2}{3}e^{-T/2RC}\right)$$

$$\therefore e^{-T/2RC} = \frac{1}{2}$$

$$T = 2RC \ln(2)$$

$$f = \frac{1}{2RC \ln(2)}$$

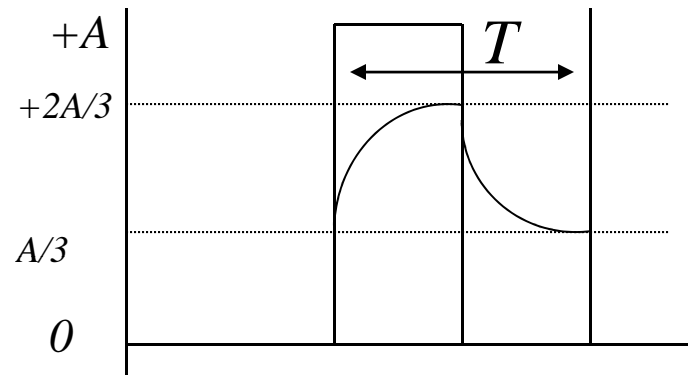

Homework

- Astable Multivibrators
 - Problems: 12.14