

MOSFET EQUIVALENT CIRCUITS

Lesson #4 Section 5.4-6

Small-Signal Equivalent Circuits

- As done for BJTs, we will investigate an equivalent circuit when the signal variations are small compared to the bias points
- Some nomenclature:
 - The values of the FET parameters at the Q point (i.e., the DC value) will be denoted by the capital letters with the subscript Q: I_{DQ} for the Q point drain current.
 - The portion of the signal which varies with time will be denoted by lower case letters and lower case subscripts: $i_d(t)$ for variable portion of the drain current
 - The total signal will be denoted by lower case letters with upper case subscripts: $i_D(t)$ is the total drain current and

$$i_D(t) = I_{DQ} + i_d(t)$$
$$v_{GS}(t) = V_{GSQ} + v_{gs}(t)$$

Small-Signal Equivalent Circuits (Continued)

$$i_D(t) = I_{DQ} + i_d(t)$$

$$v_{GS}(t) = V_{GSQ} + v_{gs}(t)$$

Recall that

$$i_D(t) = K(v_{GS}(t) - V_{to})^2$$

$$\begin{aligned} I_{DQ} + i_d(t) &= K(V_{GSQ} + v_{gs}(t) - V_{to})^2 \\ &= K(V_{GSQ} - V_{to})^2 + 2K(V_{GSQ} - V_{to})v_{gs}(t) + Kv_{gs}(t)^2 \end{aligned}$$

But the Q point is also given by

$$I_{DQ} = K(V_{GSQ} - V_{to})^2$$

Therefore,

$$i_d(t) = 2K(V_{GSQ} - V_{to})v_{gs}(t) + Kv_{gs}(t)^2$$

Small-Signal Equivalent Circuits (Continued)

Assuming the we are dealing with small signals
about the Q point and

$$|v_{gs}(t)| \ll |V_{GSQ} - V_{to}|$$

then

$$i_d(t) = 2K(V_{GSQ} - V_{to})v_{gs}(t)$$


Let's define, g_m , the transconductance

$$\text{as } g_m = 2K(V_{GSQ} - V_{to})$$

$$i_d(t) = g_m v_{gs}(t)$$

also

$$i_g(t) = 0$$

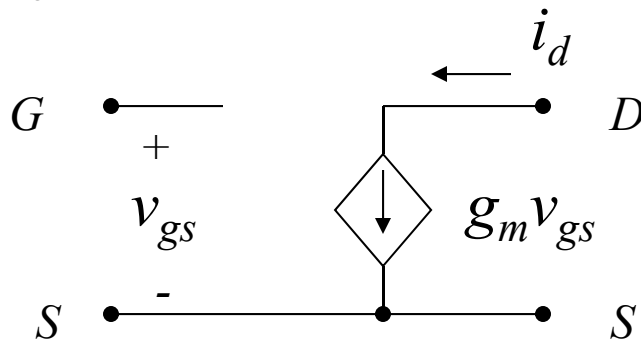

Other forms of g_m

$$\text{if } g_m = 2K(V_{GSQ} - V_{to})$$


And

$$I_{DQ} = K(V_{GSQ} - V_{to})^2 \Rightarrow (V_{GSQ} - V_{to}) = \sqrt{\frac{I_{DQ}}{K}}$$

Then

$$\begin{aligned} g_m &= 2K \sqrt{\frac{I_{DQ}}{K}} = 2\sqrt{KI_{DQ}} = 2\sqrt{K} \sqrt{I_{DQ}} = 2\sqrt{\left(\frac{W}{L}\right) \left(\frac{KP}{2}\right)} \sqrt{I_{DQ}} \\ &= \sqrt{(W/L)} \sqrt{2KP} \sqrt{I_{DQ}} \end{aligned}$$

Another More Complex Equivalent Circuit

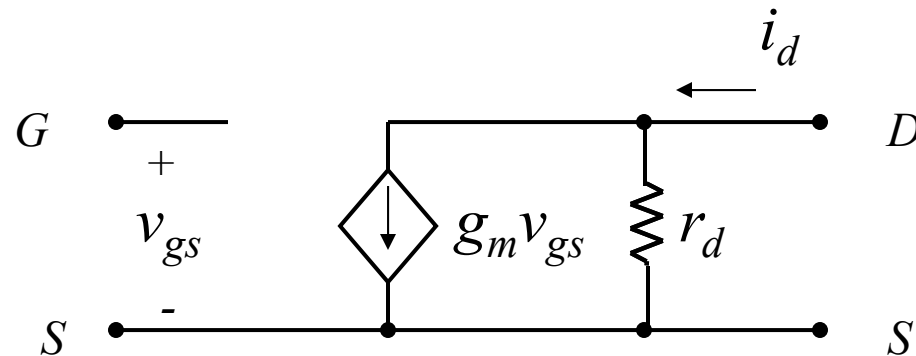

Up till now we assumed the the FET curves in the saturation region were flat; however, if there is a slight slope, a small resistance in the drain should be added to reflect this. So:

$$i_d(t) = g_m v_{gs}(t) + \frac{v_{ds}(t)}{r_d}$$

Therefore, And

$$g_m = \left. \frac{i_d}{v_{gs}} \right|_{v_{ds}=0} \cong \left. \frac{\Delta i_D}{\Delta v_{GS}} \right|_{v_{DS}=V_{DSQ}}$$


$$\frac{1}{r_d} = \left. \frac{i_d}{v_{ds}} \right|_{v_{gs}=0} \cong \left. \frac{\Delta i_D}{\Delta v_{DS}} \right|_{v_{GS}=V_{GSQ}}$$

$$g_m = \left. \frac{\partial i_D}{\partial v_{GS}} \right|_{Q\text{-point}}$$

$$\frac{1}{r_d} = \left. \frac{\partial i_D}{\partial v_{DS}} \right|_{Q\text{-point}}$$


Application of the Small Signal Equivalent Circuit

Common Source Amplifier

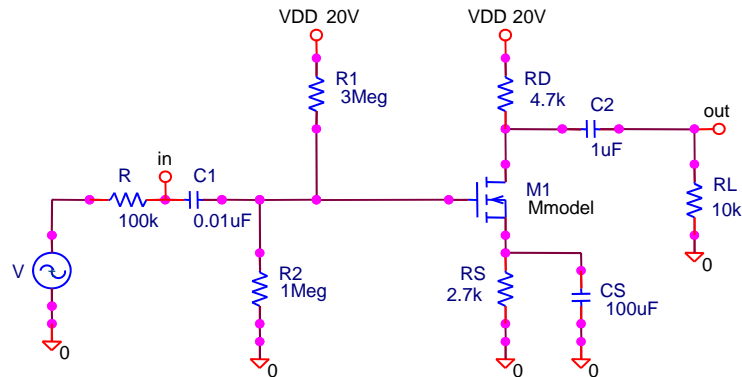


- Before we can apply the FET small signal equivalent circuit, we must review and reduce the circuit elements of this amplifier to those which are affected by a varying AC signal. In particular,
 - The coupling capacitors C1 and C2 are shorted
 - The bias resistor RS is shorted by the bypass capacitor CS
 - The DC voltage sources are shorted
- Note that the DC equivalent circuit is identical to the Self Bias circuit we previously investigated. Recall $I_{DQ} = 0.7833$ and $V_{DSQ} = 14.203$

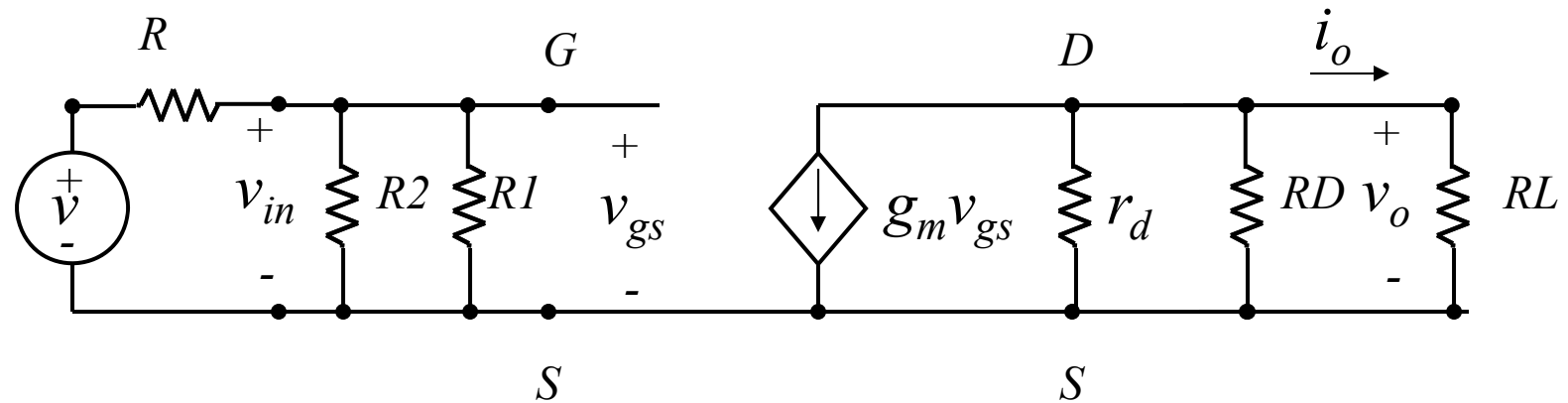Common Source Amplifier Equivalent Circuit




Assume that saturation region is flat and so $r_d = \infty$ and $KP = 50 \text{ mA/V}^2$, $V_{to} = 2$, $L = 10 \mu\text{m}$, $W = 400 \mu\text{m}$, $v = 100 \sin(2000\pi t) \text{ mV}$
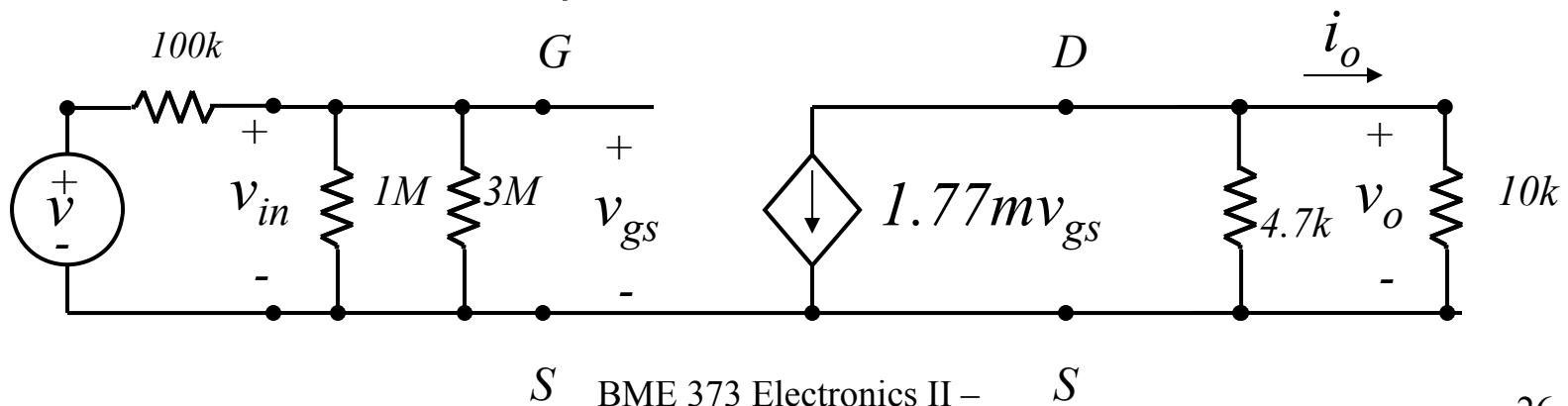
$$g_m = \sqrt{2KP} \sqrt{W/L} \sqrt{I_{DQ}} = \sqrt{100e^{-6}} \sqrt{40} \sqrt{0.7833} = 1.77 \text{ mS}$$



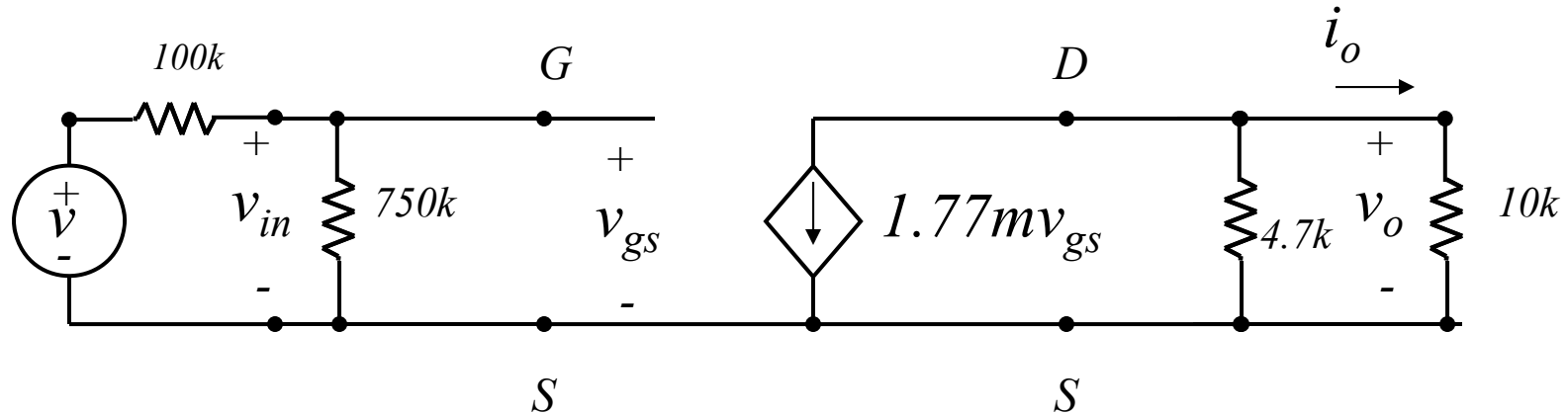Common Source Amplifier Equivalent Circuit



$$v_o = i_o 10k$$

$$= (-1.77 \times 10^{-3} v_{gs} \frac{4.7}{4.7 + 10}) \times 10k$$

$$= -5.66 v_{gs}$$


$$= -5.66 \times \left(\frac{750}{850} \times 100 \sin(2000\pi t) mV \right)$$

$$= -500 \sin(2000\pi t) mV$$

$$A_v = \frac{v_o}{v_{in}} = -5.66$$

$$A_{vi} = \frac{v_o}{v} = -5$$

Source Follower

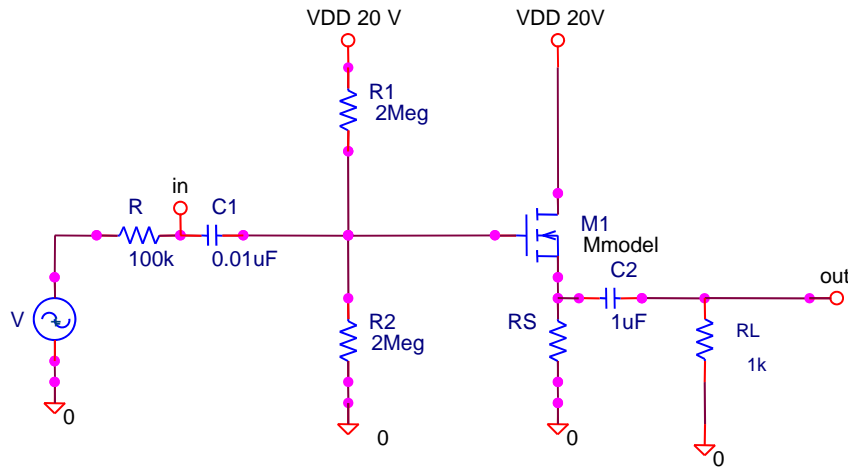


- In this circuit, we would like to find R_S to support a Q-point value of the drain current, I_{DQ} , equal to 10 mA .
- Then solve for the gain of the amplifier using the small signal equivalent circuit.
- Assume $KP = 50\mu\text{A}/\text{V}^2$, $L = 2\ \mu\text{m}$, $W = 160\ \mu\text{m}$, $V_{t0} = 1\ \text{V}$.

- To calculate R_S let's first draw the equivalent DC circuit for the Q-point.
- This becomes the self bias circuit and we have


$$V_{GSQ} = [R_2 / (R_1 + R_2)] \times V_{DD} - I_{DQ} * R_S$$

$$I_{DQ} = K(V_{GSQ} - V_{t0})^2$$

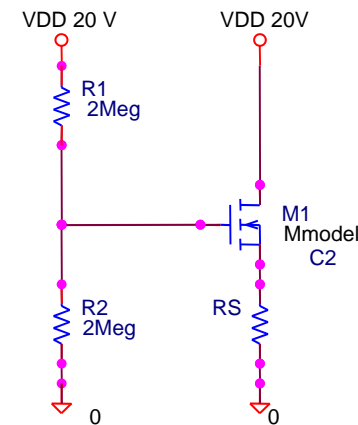- Solving the 2nd equation for $V_{GSQ} = 3.236\ \text{V}$ and substituting it into the 1st equation to yield $R_S = 426.4\ \Omega$



Source Follower (Continued)

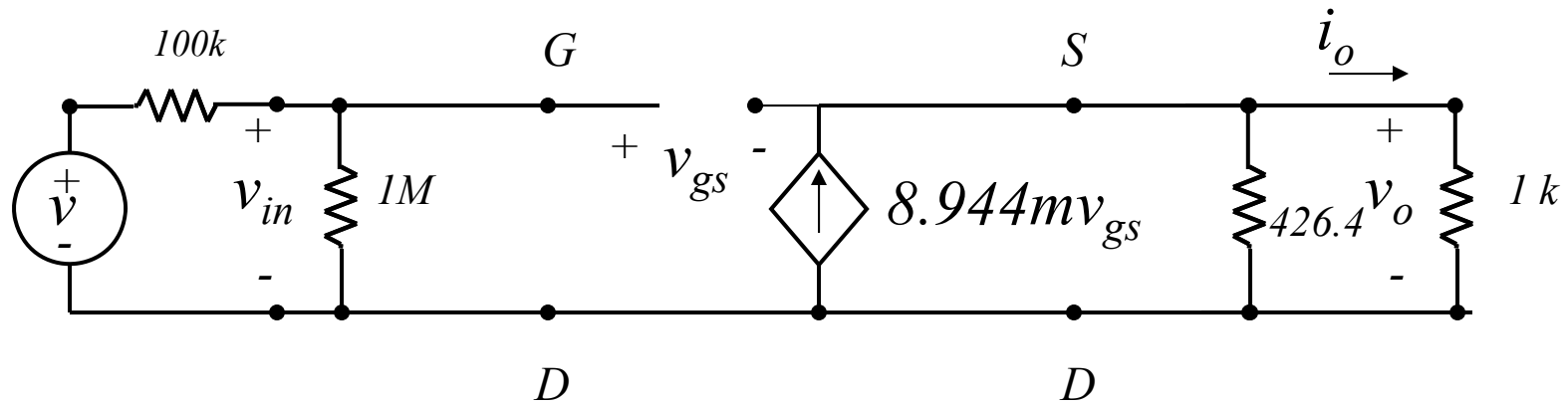

- Now we apply the small signal equivalent circuit realizing that the drain is grounded.


$$g_m = \sqrt{2KP} \sqrt{W/L} \sqrt{I_{DQ}} = \sqrt{100 \times 10^{-6}} \sqrt{80} \sqrt{10 \times 10^{-3}} = 8.944 \text{ mS}$$

$$v_o = g_m v_{GS} \times RL' = g_m v_{GS} \times \left(\frac{RS \times RL}{RS + RL} \right) = 8.944 \times 10^{-3} \times \left[\frac{(426.4)(1000)}{(1000 + 426.4)} \right] v_{GS}$$

$$v_{in} = v_{GS} + v_o = \frac{v_o}{g_m RL'} + v_o$$

$$\frac{v_o}{v_{in}} = \frac{g_m RL'}{1 + g_m RL'} = .7278$$

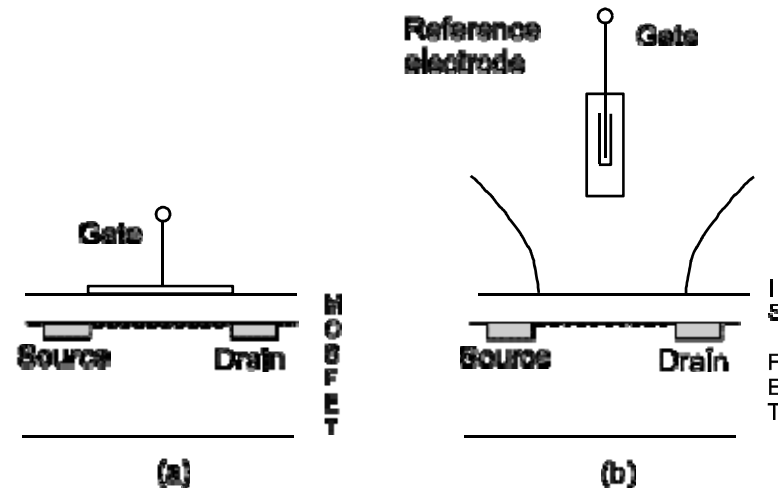Ion Sensing Field Effect Transistor (ISFET)



- $\Delta\phi = RT/F \ln(c_1/c_2)$
- R is the gas constant, T the absolute temperature (K) and F the Faraday constant and c_i , are ion concentrations in the solution and oxide.
- Using hydrogen ions can be used to measure pH¹ and DNA²

¹ Bergveld, P. **ISFET, Theory and Practice**, IEEE SENSOR CONFERENCE TORONTO, OCTOBER 2003

² DNA Electronics, <http://dnae.co.uk/technology/overview/>

Homework

- Small Signal Equivalent Circuits
 - Problems: 5.28, 5.29, 5.31, 5.32, 5.33
- Common-Source Amplifier
 - Problems: 5.36, 5.37, 5.38, 5.40
- Source Follower
 - Problems: 5.45, 5.47