


Digital Logic Circuits

Lesson #8

FET Gates

Sections 6.3-9

Resistor-Pull-up NMOS Inverter

 

Where R_{on} represents the resistance of the NMOS device when the device is on.

$$V_{OH} = V_{DD} = 5V$$

$$V_{OL} = V_{DD} \frac{R_{on}}{R_{on} + R_D}$$

$$v_{GS} = v_i$$

$$v_{DS} = v_o$$

Let's find R_{on} and the pull up resistor to make the static power in the low output state to 0.25 mW . Assume $V_{to} = 1 \text{ V}$, $KP = 50 \mu\text{A}/\text{V}^2$, $V_{OL} = .5 \text{ V}$, $V_{OH} = V_{DD} = 5 \text{ V}$

When v_o is close to zero then FET is in the Triode mode, recall:

$$i_{DS} = K[2(v_{GS} - V_{to})v_{DS} - v_{DS}^2] \approx K[2(v_{GS} - V_{to})v_{DS}]$$

$$K = \left(\frac{W}{L}\right) \frac{KP}{2}$$



$$R_{on} = \frac{v_{DS}}{i_{DS}} = \frac{v_{DS}}{K[2(v_{GS} - V_{to})v_{DS}]} = \frac{1}{K[2(v_{GS} - V_{to})]}$$

To make R_{on} small, we need to design the FET to have a large K .

$P_{static} = 0.25 \times 10^{-3} = I_{DS} V_{DD}$	$R_{on} = \frac{V_{OL}}{V_{DD}} (R_D + R_{on})$
$I_{DS} = \frac{0.25 \times 10^{-3}}{5} = 50 \mu\text{A}$	$= \frac{.5}{5} 100 \times 10^3 = 10 \text{ k}\Omega$
$I_{DS} = \frac{V_{DD}}{R_{on} + R_D} = \frac{5}{R_{on} + R_D} = 50 \mu\text{A}$	$K = \frac{1}{2R_{on}(v_i - V_{to})}$
$R_{on} + R_D = \frac{5}{50 \times 10^{-6}} = 100 \text{ k}\Omega$	$= 12.5 \mu\text{A}/\text{V}^2$
	$R_D = 90 \text{ k}\Omega$

Dynamic Response of the Resistor-Pull-up NMOS Inverter

Low to High Transition

 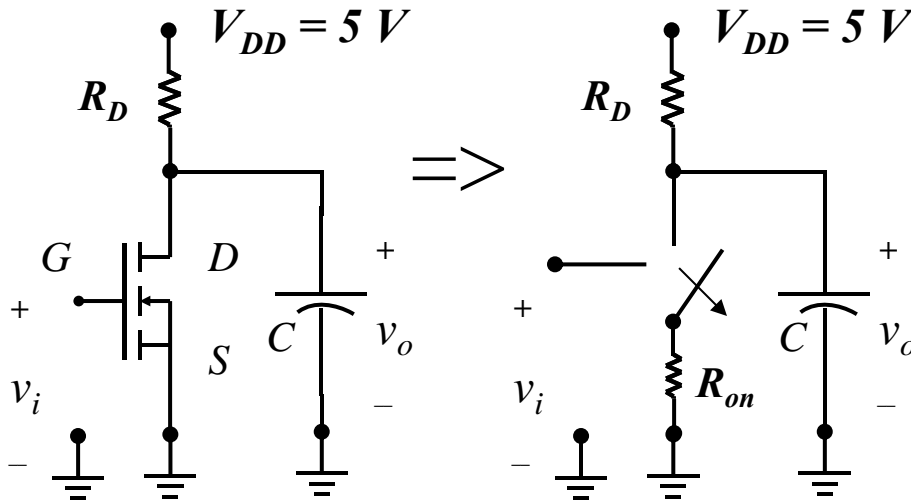

$$v_o(t) = V_{OH} - (V_{OH} - V_{OL})e^{-t/R_D C} = V_{OH} - \Delta V e^{-t/R_D C}$$

$$v_o(t_{10}) = V_{OL} + .1\Delta V = V_{OH} - \Delta V e^{-t_{10}/R_D C}$$

$$V_{OL} - V_{OH} + .1\Delta V = .1\Delta V - \Delta V = -.9\Delta V = -\Delta V e^{-t_{10}/R_D C}$$

$$t_{10} = -R_D C \ln(.9) = .1054 R_D C$$

$$t_{90} = -R_D C \ln(.1) = 2.3025 R_D C$$

$$t_r = 2.2 R_D C$$

$$t_{PLH} = -R_D C \ln(.5) = 0.6931 R_D C$$

The $R_D C$ time constant determines the parameters associated with the transition from Low to High, e.g. the rise time.

We then say that the capacitor charges to V_{OH} through the pull up resistor R_D

Calculation of $v_o(t)$

Using Kirchoff's Current Law at the output node, $v_o(t)$:

$$C \frac{dv_o(t)}{dt} + 0 = \frac{V_{DD} - v_o(t)}{R}$$

$$C \frac{dv_o(t)}{dt} + \frac{v_o(t)}{R} = \frac{V_{DD}}{R} = \frac{V_{OH}}{R}$$

Let's assume :

$$v_o(t) = A_1 e^{-\alpha t} + A_2$$

$$\therefore \dot{v}_o(t) = -\alpha A_1 e^{-\alpha t}$$

$$-\alpha A_1 e^{-\alpha t} C + \frac{A_1 e^{-\alpha t} + A_2}{R} = \frac{V_{OH}}{R}$$

$$\therefore \alpha = \frac{1}{RC}; A_2 = V_{OH}$$


Since $v_o(0) = V_{OL}$

$$v_o(0) = A_1 + V_{OH} = V_{OL}; A_1 = -(V_{OH} - V_{OL})$$


$$v_o(t) = -(V_{OH} - V_{OL}) e^{-t/RC} + V_{OH}$$

Complementary MOS CMOS

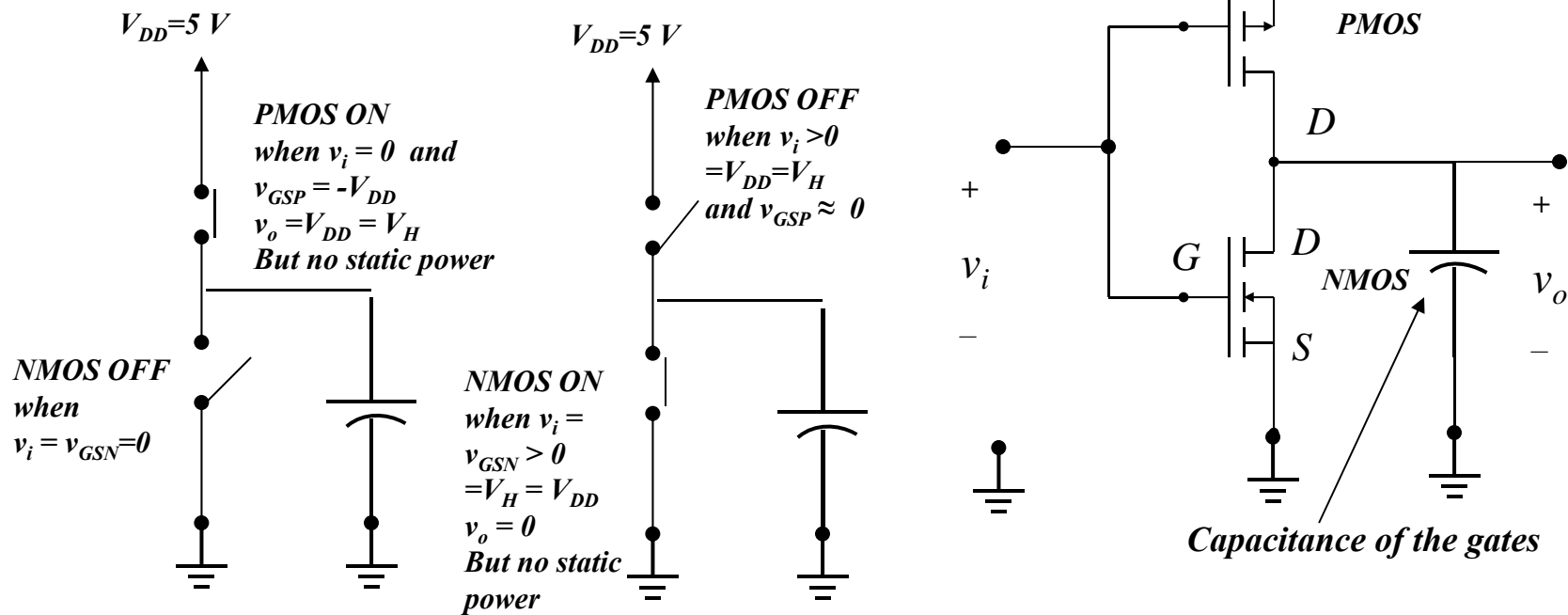- Taking NMOS (n -channel) and PMOS (p -channel) and using them in a complementary fashion (same characteristics) such that the static power is always zero (there will, of course, be dynamic power dissipated).
- Note that $V_{GSP} = v_i - V_{DD}$ and $V_{GSN} = v_i$




Graphical Analysis

 


- For CMOS, the load line of the NMOS is the characteristic curves of the PMOS.
- Let view the operation as v_i goes from 0 to 5 V
- Point A: $v_i = 0$, the NMOS is cutoff since $v_i = v_{GSN} < V_{ton}$; the PMOS is conducting since $v_{GSP} = v_i - V_{DD} = -V_{DD}$
- Point B: $v_i = 2$ and is the intersection of $v_{GSN} = 2$ and $v_{GSP} = -3$ where the NMOS is in saturation and the PMOS is in the triode region.
- Points C through D: $v_i = 2.5$ and is the intersection of $v_{GSN} = 2.5$ and $v_{GSP} = -3$ where the NMOS and the PMOS are both in saturation.
- Point E $v_i = 3$ and is the intersection of $v_{GSN} = 3$ and $v_{GSP} = -2$ where the NMOS is in the triode region and the PMOS is in the saturation region.
- Point F: $v_i = 5$, the NMOS is conducting but the PMOS is cutoff since $v_{GSP} < V_{top} = v_i - V_{DD} = 0$

Transfer Characteristics

- These characteristics approach the ideal characteristics we discuss previously.
- For $v_i < V_{top}$, $v_o = V_{DD}$
- For $v_i > V_{DD} - |V_{top}|$, $v_o = 0$
- The transfer characteristics fall abruptly at $v_i = V_{DD}/2$

 


CMOS Inverter Truth Table

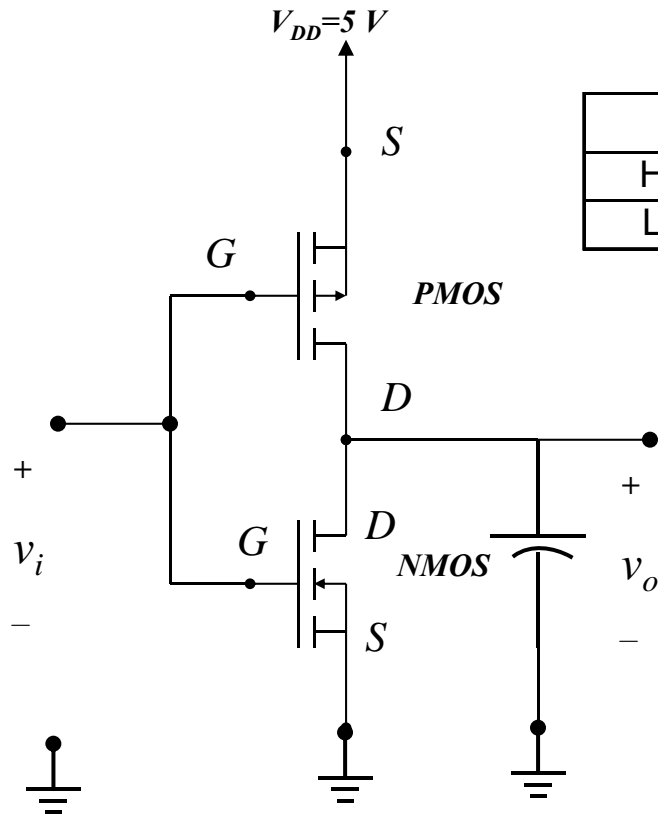

v_i		NMOS	PMOS	v_o	
High	1	ON	OFF	Low	0
Low	0	OFF	ON	High	1

Propagation Delay

 



- At $t=0^-$ (just before the switch, $v_i = 0$ and $v_o = V_{DD}$. (Point A)
- At $t=0$, v_i switches from LOW to HIGH and the NMOS goes ON and the PMOS goes OFF. (Transition from Point A to B)
- Because the voltage across C_L can not change instantly, at $t=0^+$ $v_o = V_{DD}$ and C_L begins to discharge through the NMOS at

$$i_{DN} = \left(\frac{W}{L}\right) \frac{KP_n}{2} (V_{DD} - V_{ton})^2$$

- Assuming that $V_{DD}/2$, the t_{PHL} point, then


$$t_{PHL} \approx \frac{C_L \Delta V}{i_{DN}} = \frac{C_L (V_{DD}/2)}{(W/L)_n (KP_n/2) (V_{DD} - V_{ton})^2}$$

$$t_{PLH} = \frac{C_L (V_{DD}/2)}{(W/L)_p (KP_p/2) (V_{DD} - |V_{top}|)^2}$$

  

CMOS NOR and NAND GATES

NOR Gate

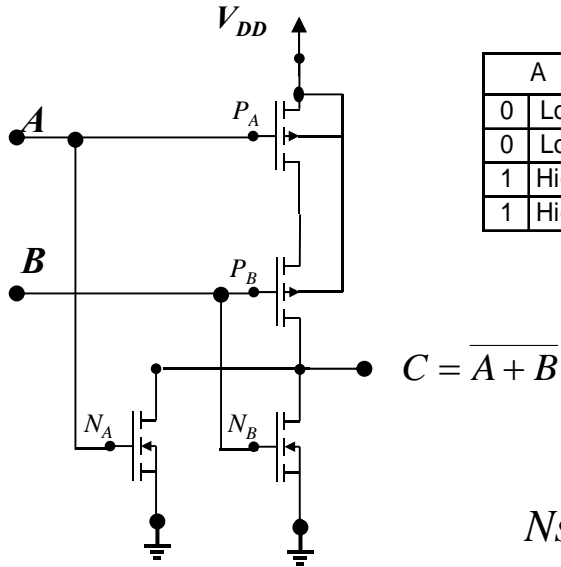

A	B	NA	PA	NB	PB	Nside	Pside	v_o	
0	Low	0	Low	OFF	ON	OFF	ON	High	1
0	Low	1	High	OFF	ON	ON	OFF	Low	0
1	High	0	Low	ON	OFF	OFF	ON	Low	0
1	High	1	High	ON	OFF	ON	OFF	Low	0


$$N_{side} = N_A + N_B$$

$$P_{side} = P_A \cdot P_B$$

$$N_{side} = N_A \cdot N_B$$

$$P_{side} = P_A + P_B$$


NAND Gate

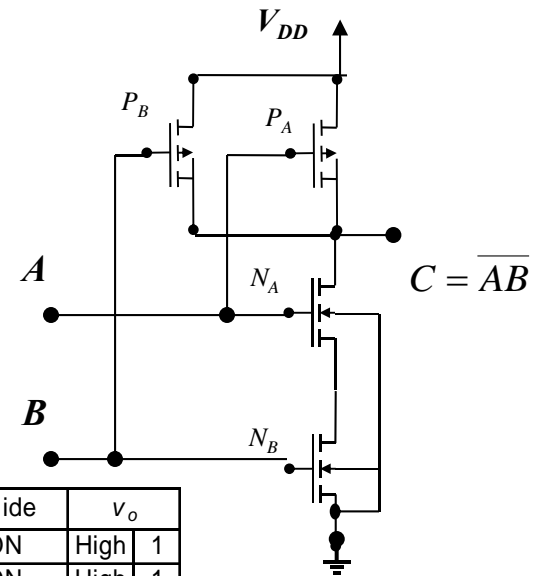

A	B	NA	PA	NB	PB	Nside	Pside	v_o	
0	Low	0	Low	OFF	ON	OFF	ON	High	1
0	Low	1	High	OFF	ON	OFF	ON	High	1
1	High	0	Low	ON	OFF	OFF	ON	High	1
1	High	1	High	ON	OFF	ON	OFF	Low	0

Dynamic Logic

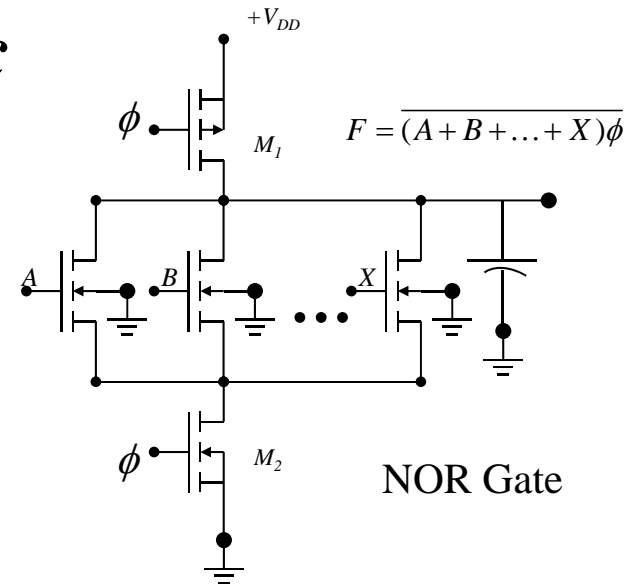
- In this circuit, only when the clock, ϕ , is high will the output be dependent on the inputs, $A, B, \dots X$.
- When ϕ is low, M_1 is ON, M_2 is OFF and capacitor will be charged to V_{DD} .
- When ϕ is high, M_1 is OFF, M_2 is ON, and the capacitor will discharge through the NMOS transistors provided that at least one of the inputs is ON.



A	B	X	ϕ	NA	NB	NX	N ϕ	P ϕ	Nside	Pside	v_o	
0	Low	0	Low	0	Low	0	Low	OFF	OFF	ON	High	1
0	Low	0	Low	1	High	0	Low	OFF	OFF	ON	High	1
0	Low	1	High	0	Low	0	Low	OFF	ON	OFF	High	1
0	Low	1	High	1	High	0	Low	OFF	ON	OFF	High	1
1	High	0	Low	0	Low	0	Low	ON	OFF	ON	High	1
1	High	0	Low	1	High	0	Low	ON	OFF	ON	High	1
1	High	1	High	0	Low	0	Low	ON	ON	OFF	High	1
1	High	1	High	1	High	0	Low	ON	ON	OFF	High	1
0	Low	0	Low	0	Low	1	High	OFF	OFF	OFF	High	1
0	Low	0	Low	1	High	1	High	OFF	OFF	ON	Low	0
0	Low	1	High	0	Low	1	High	OFF	ON	OFF	Low	0
0	Low	1	High	1	High	1	High	OFF	ON	OFF	Low	0
1	High	0	Low	0	Low	1	High	ON	OFF	ON	Low	0
1	High	0	Low	1	High	1	High	ON	OFF	ON	Low	0
1	High	1	High	0	Low	1	High	ON	ON	OFF	Low	0
1	High	1	High	1	High	1	High	ON	ON	OFF	Low	0

One More Example

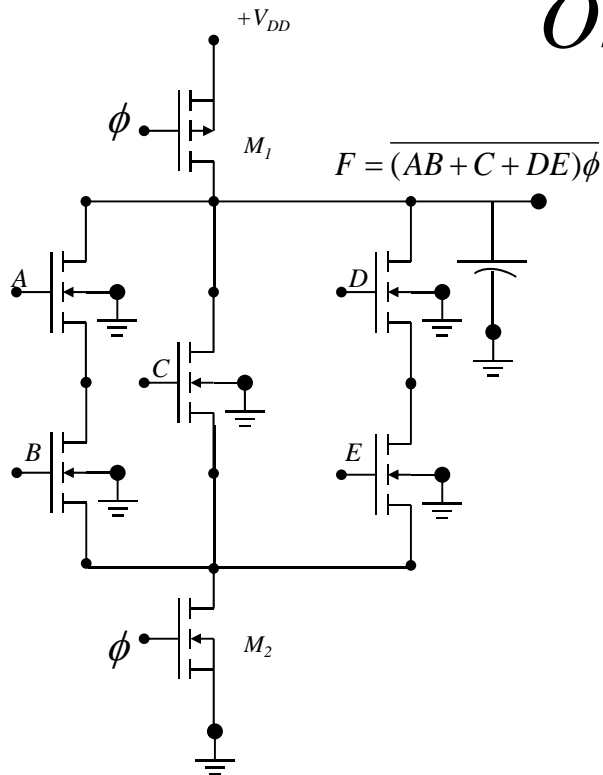- Using this design, we can design other logic functions.



ϕ	A	B	C	D	E	M2	M1	NA	NB	NC	NC	NE	P (NA*NB+NC+ND*NE)M2	N M1	F	
1	0	0	0	0	0	ON	OFF	OFF	OFF	OFF	OFF	OFF	OFF	OFF	ON	1
1	0	0	0	0	1	ON	OFF	OFF	OFF	OFF	OFF	ON	OFF	OFF	ON	1
1	0	0	0	1	0	ON	OFF	OFF	OFF	OFF	ON	OFF	OFF	OFF	ON	1
1	0	0	0	1	1	ON	OFF	OFF	OFF	OFF	ON	ON	OFF	OFF	OFF	0
1	0	0	1	0	0	ON	OFF	OFF	OFF	ON	OFF	OFF	ON	OFF	OFF	0
1	0	0	1	0	1	ON	OFF	OFF	OFF	ON	OFF	ON	OFF	OFF	OFF	0
1	0	0	1	1	1	ON	OFF	OFF	OFF	ON	ON	ON	OFF	ON	OFF	0
1	0	1	0	0	0	ON	OFF	OFF	ON	OFF	OFF	OFF	OFF	OFF	ON	1
1	0	1	0	0	1	ON	OFF	OFF	ON	OFF	OFF	ON	OFF	OFF	ON	1
1	0	1	0	1	0	ON	OFF	OFF	ON	OFF	ON	OFF	OFF	OFF	ON	1
1	0	1	0	1	1	ON	OFF	OFF	ON	OFF	ON	ON	OFF	OFF	OFF	0
1	0	1	1	0	0	ON	OFF	OFF	ON	ON	OFF	OFF	ON	OFF	OFF	0
1	0	1	1	0	1	ON	OFF	OFF	ON	ON	ON	ON	OFF	OFF	OFF	0
1	0	1	1	1	0	ON	OFF	OFF	ON	ON	ON	ON	OFF	OFF	OFF	0
1	0	1	1	1	1	ON	OFF	OFF	ON	ON	ON	ON	OFF	OFF	OFF	0
1	1	0	0	0	0	ON	OFF	ON	OFF	OFF	OFF	OFF	OFF	OFF	ON	1
1	1	0	0	0	1	ON	OFF	ON	OFF	OFF	OFF	ON	OFF	OFF	ON	1
1	1	0	0	1	1	ON	OFF	ON	OFF	OFF	ON	ON	OFF	OFF	OFF	0
1	1	0	1	0	0	ON	OFF	ON	OFF	ON	OFF	OFF	OFF	ON	OFF	0
1	1	0	1	0	1	ON	OFF	ON	OFF	ON	OFF	ON	OFF	OFF	OFF	0
1	1	0	1	1	0	ON	OFF	ON	OFF	ON	ON	OFF	ON	OFF	OFF	0
1	1	0	1	1	1	ON	OFF	ON	OFF	ON	ON	ON	OFF	OFF	OFF	0
1	1	1	0	0	0	ON	OFF	ON	ON	OFF	OFF	OFF	ON	OFF	OFF	0
1	1	1	0	0	1	ON	OFF	ON	ON	OFF	OFF	ON	OFF	OFF	OFF	0
1	1	1	0	1	0	ON	OFF	ON	ON	OFF	ON	OFF	ON	OFF	OFF	0
1	1	1	0	1	1	ON	OFF	ON	ON	OFF	ON	ON	OFF	OFF	OFF	0
1	1	1	1	0	0	ON	OFF	ON	ON	ON	OFF	OFF	ON	OFF	OFF	0
1	1	1	1	0	1	ON	OFF	ON	ON	ON	ON	OFF	ON	OFF	OFF	0
1	1	1	1	1	1	ON	OFF	ON	ON	ON	ON	ON	OFF	OFF	OFF	0

Homework

- Resistor-Pull-Up NMOS Inverter
 - Problem: 6.32
- Dynamic Response
 - Problem: 6.40
- CMOS Inverter
 - Problems: 6.48-6.50
- Propagation Delay
 - Problem: 6.58
- CMOS Gates
 - Problems: 6.69-6.70, 6.71-73