

Frequency Response

Lesson #9 Circuit Analysis Sections 8.1

Frequency Response


- To understand how electronic circuits are analyzed
- To understand electronic circuits responses to various frequencies

Bode Plots

- A method to understand how the frequency response of an electronic circuit can be viewed.
 - Signal processed by electronic circuits vary in frequency
 - Voice: 20 Hz to 20 kHz
 - Electrocardiograms: 0.05 Hz to 100 Hz
 - Video: DC to 4.5 MHz
 - Aids in designing how a circuit can be designed to avoid signal distortion.
- Some Mathematical Principles
 - Laplace Transform variable: s
 - Impedance of circuit parameters: Capacitance $\Rightarrow 1/(sC)$
Inductance $\Rightarrow sL$
Resistance $\Rightarrow R$
 - To study frequency response: replace $s \Rightarrow j\omega$

Example:

- Network Function of a Low Pass Filter:

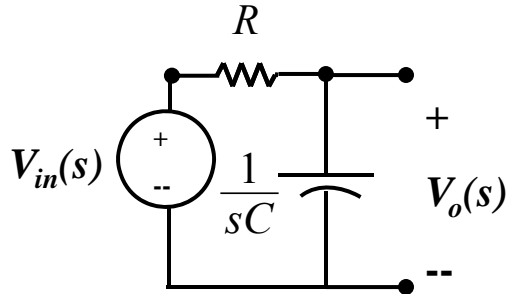

$$A_v(s) = \frac{V_o(s)}{V_{in}(s)} = \frac{1/sC}{R + 1/sC} = \frac{1}{RCs + 1}$$

$$= \frac{1/RC}{s + 1/RC} = \frac{p}{s + p} = \frac{1}{\frac{s}{p} + 1}$$

$$A_v(j\omega) = \frac{1}{\frac{j\omega}{p} + 1} = \frac{1}{\frac{j2\pi f}{p} + 1} = \frac{1}{j(\frac{f}{f_p}) + 1}; \text{ where } f_p = \frac{p}{2\pi}$$

- Poles and Zeroes:

- Poles: Values of s where the denominator of the network function are zero
- Zeroes: Values of s where the numerator of the network function are zero

- Sanity Checks: at $\omega=0$, $\omega \rightarrow \infty$, at other ω 's (e.g., at poles or zero break frequencies or resonance frequencies)

Break Frequency

Let's substitute $s \Rightarrow j\omega = j2\pi f$

$$A_v(f) = \frac{1}{j2\pi RCf + 1}$$

As an example: let's choose $f = 1/2\pi RC$

$$A_v(f) = \frac{1}{j1 + 1} = \frac{1}{\sqrt{1^2 + 1^2} \angle 45^\circ} = \frac{1}{\sqrt{2}} \angle -45^\circ = .707 \angle -45^\circ$$

So if $V_{in}(t) = A \cos(2\pi ft)$, then at $f = 1/2\pi RC$, $V_o(t) = .707A \cos(t/RC - 45^\circ)$

Now let's generalize:

$$A_v(f) = \frac{\mathbf{V}_o}{\mathbf{V}_{in}} = \frac{1}{j(f/f_b) + 1} = \frac{1}{\sqrt{1 + (f/f_b)^2} \angle \tan^{-1}(f/f_b)} = \frac{1}{\sqrt{1 + (f/f_b)^2}} \angle -\tan^{-1}(f/f_b);$$

where $f_b = \frac{1}{2\pi RC}$ and is called the break frequency (half power point or 3-dB point)

Bode Plot - Logarithmic Plot of Magnitude vs. Frequency

Magnitude

$$A_v(f) = \frac{1}{\sqrt{1+(f/f_b)^2}} \angle -\tan^{-1}(f/f_b)$$

$$|A_v(f)| = \frac{1}{\sqrt{1+(f/f_b)^2}}$$

$$|A_v(f)|_{dB} = -20 \log(\sqrt{1+(f/f_b)^2})$$


$$= -10 \log[1+(f/f_b)^2]$$

$$f_b = \pi / 2 = 1.57$$

We see that for $f \approx 0$, $|A_v(f)|_{dB} = 0$

But for $f \gg f_b$, $|A_v(f)|_{dB} = -10 \log[(f/f_b)^2] = -20 \log(f/f_b)$

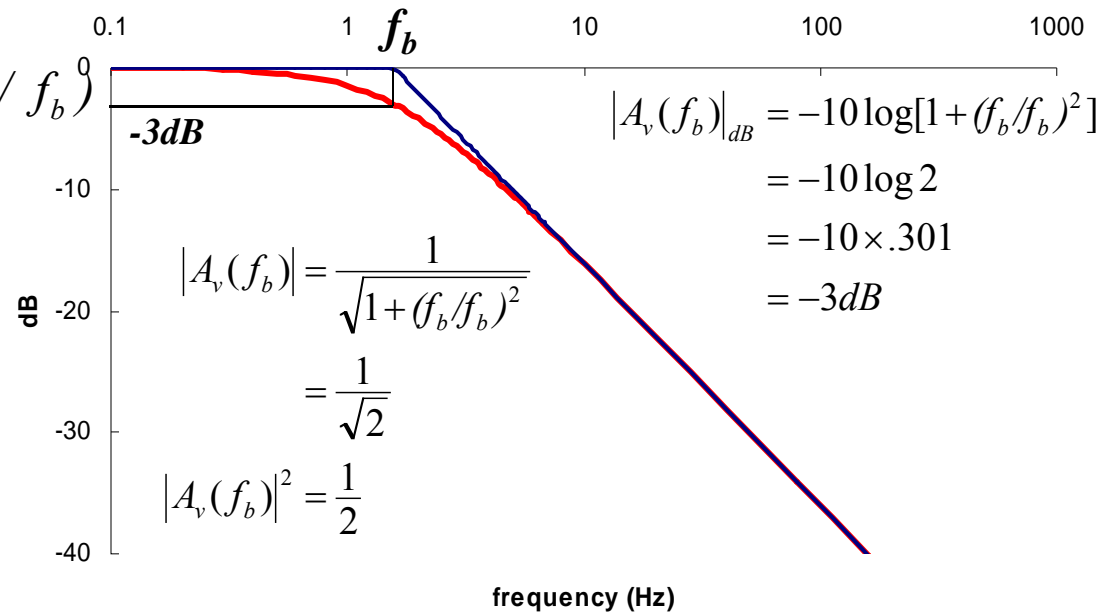which is a straight line of slope -20dB for each multiple of 10 (decade) in frequency and with intercept at f_b



Bode Plot - Logarithmic Plot of Angle vs. Frequency


$$\phi(f) = -\tan^{-1}(f/f_b)$$

$$f_b = \pi / 2 = 1.57$$


We see that for $f \approx 0$, $\phi(f) = 0^\circ$

for $f = f_b$, $\phi(f_b) = -45^\circ$

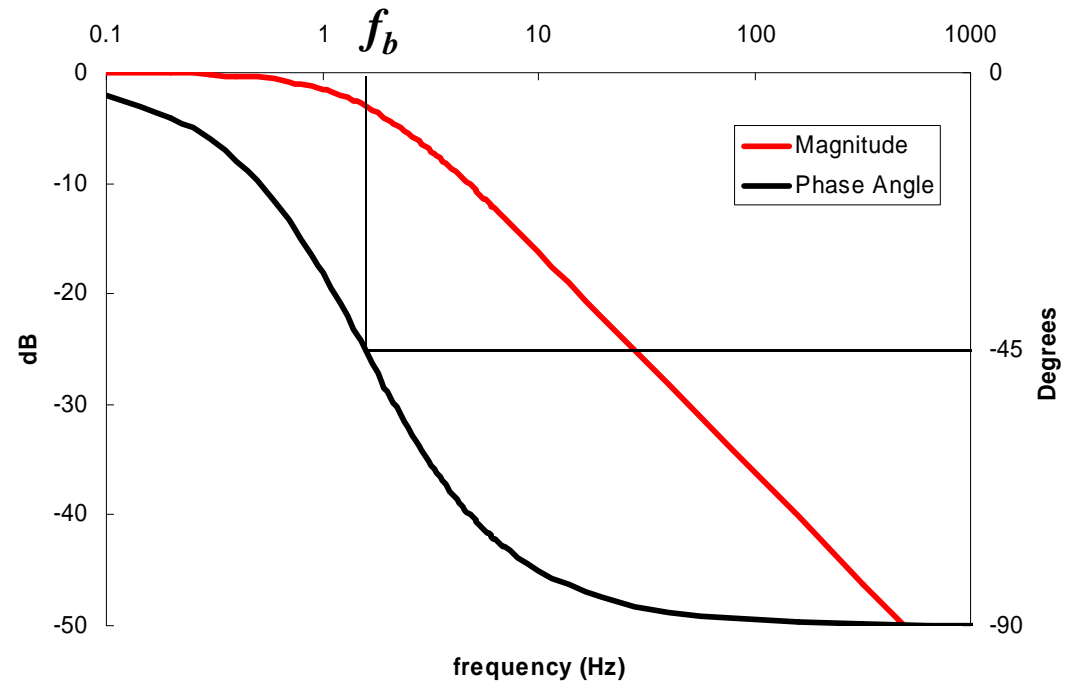But for $f \gg f_b$, $\phi(f) \Rightarrow -90^\circ$



An Example: One Pole and One Zero

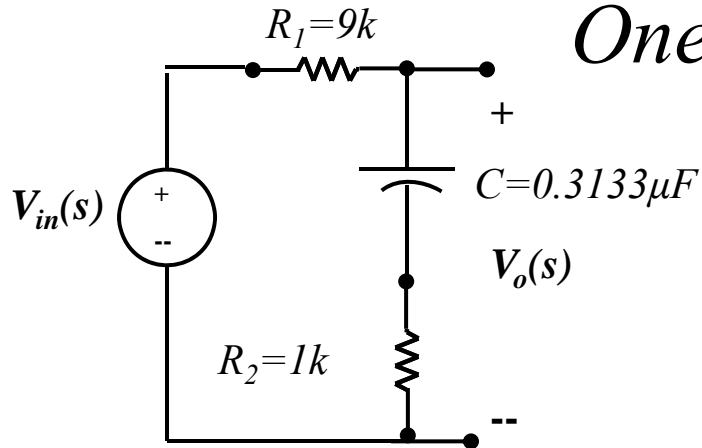

$$A_v(s) = \frac{V_o(s)}{V_{in}(s)} = \frac{R_2 + 1/sC}{R_1 + R_2 + 1/sC}$$

$$= \frac{sCR_2 + 1}{sC(R_1 + R_2) + 1}$$

$$A_v(f) = \frac{j2\pi fCR_2 + 1}{j2\pi fC(R_1 + R_2) + 1}$$


$$A_v(f) = \frac{j(f/f_z) + 1}{j(f/f_p) + 1} = \frac{\sqrt{1 + (f/f_z)^2}}{\sqrt{1 + (f/f_p)^2}} \angle \tan^{-1}(f/f_z) - \tan^{-1}(f/f_p),$$

where $f_z = \frac{1}{2\pi CR_2} = 500 \text{ Hz}$

and $f_p = \frac{1}{2\pi C(R_1 + R_2)} = 50 \text{ Hz}$

$$|A_v(f)|_{dB} = 20 \log \sqrt{1 + (f/f_z)^2} - 20 \log \sqrt{1 + (f/f_p)^2}$$
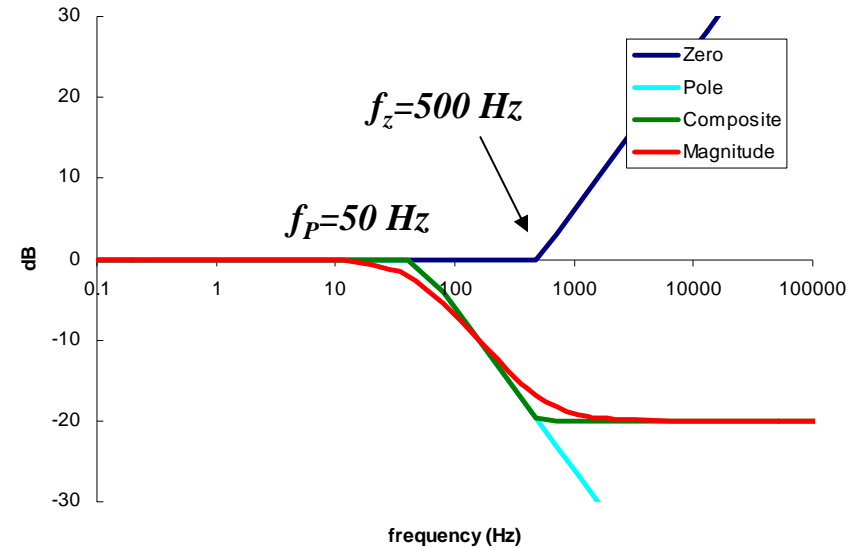
$$\varphi(f) = \tan^{-1}(f/f_z) - \tan^{-1}(f/f_p)$$




$$A_v(f) = \frac{j2\pi fCR_2 + 1}{j2\pi fC(R_1 + R_2) + 1}$$

$$A_v(f) = \frac{j2\pi fCR_2 + 1}{j2\pi fC(R_1 + R_2) + 1} \Rightarrow \frac{R_2}{(R_1 + R_2)} \text{ as } f \rightarrow \infty$$

$$A_v(f)_{f \rightarrow \infty} = \frac{1k}{(1k + 9k)} = .1$$


$$|A_v(f)|_{dB, f \rightarrow \infty} = 20 \log .1 = -20 \text{ dB}$$

Example (Continued)

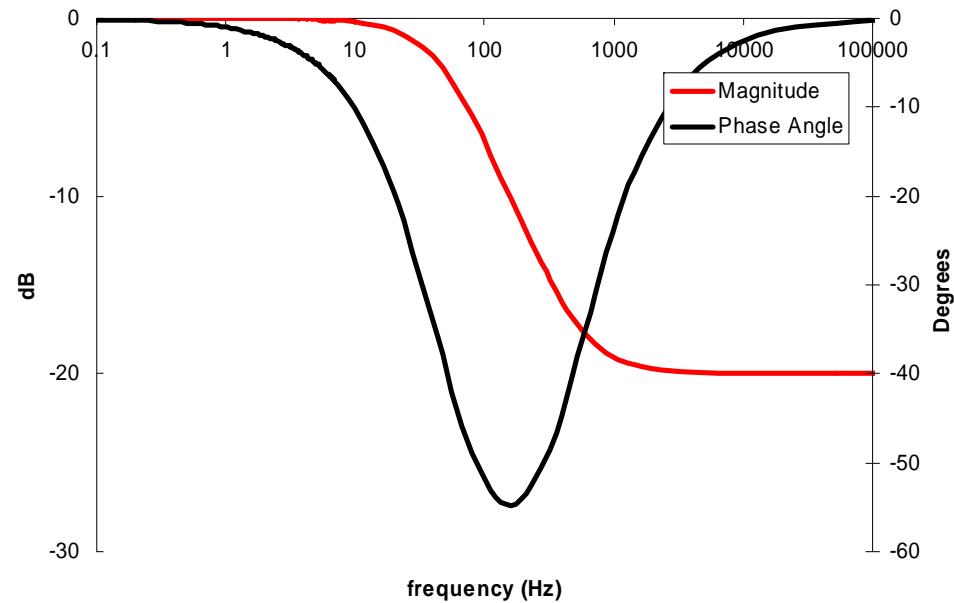

$$\varphi(f) = \tan^{-1}(f / f_z) - \tan^{-1}(f / f_p)$$

Another Example: High Pass Filter

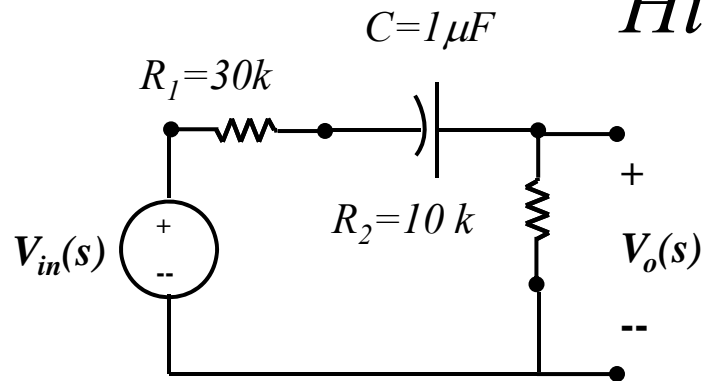

$$A_v(s) = \frac{V_o(s)}{V_{in}(s)} = \frac{R_2}{R_1 + R_2 + 1/sC}$$

$$= \frac{sCR_2}{sC(R_1 + R_2) + 1}, \text{ pole at } s = -1/[(R_1 + R_2)C] \text{ and zero at } s = 0$$

$$A_v(f) = \frac{j2\pi fCR_2}{j2\pi fC(R_1 + R_2) + 1} = \left(\frac{R_2}{R_1 + R_2} \right) \left(\frac{j(f/f_p)}{j(f/f_p) + 1} \right)$$

$$\text{where } f_p = \frac{1}{2\pi(R_1 + R_2)C}$$

$$A_v(f) = \left(\frac{R_2}{R_1 + R_2} \right) \frac{f/f_p}{\sqrt{1 + (f/f_p)^2}} \angle 90^\circ - \tan^{-1}(f/f_p),$$


$$\text{where } f_p = \frac{1}{2\pi C(R_1 + R_2)} = 3.98 \text{ Hz}$$

$$A_v(f) = .25 \frac{f/3.98}{\sqrt{1 + (f/3.98)^2}} \angle 90^\circ - \tan^{-1}(f/3.98_p)$$


$$|A_v(f)|_{dB} = 20 \log .25 + 20 \log f / 3.98 - 20 \log \sqrt{1 + (f/3.98)^2}$$

$$= -12 + 20 \log f / 3.98 - 20 \log \sqrt{1 + (f/3.98)^2}$$

$$|A_v(f)|_{dB, f \rightarrow \infty} = -12$$

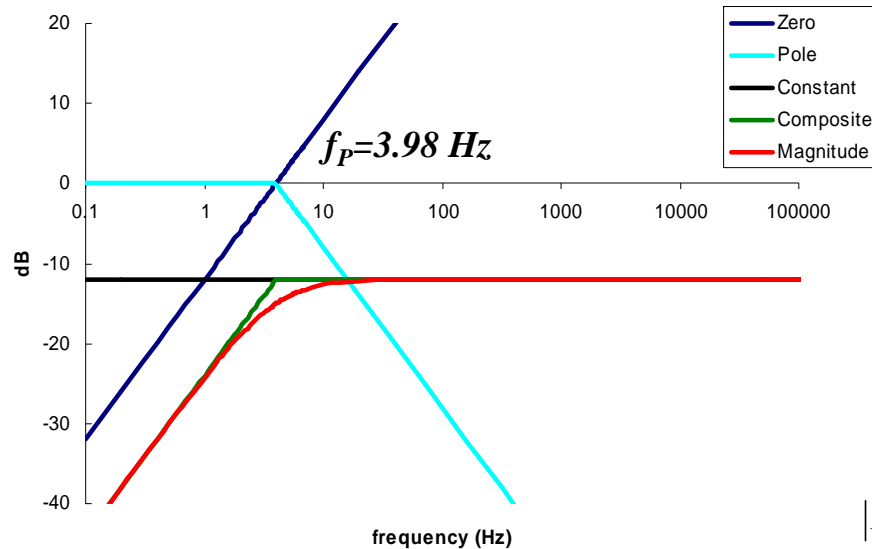


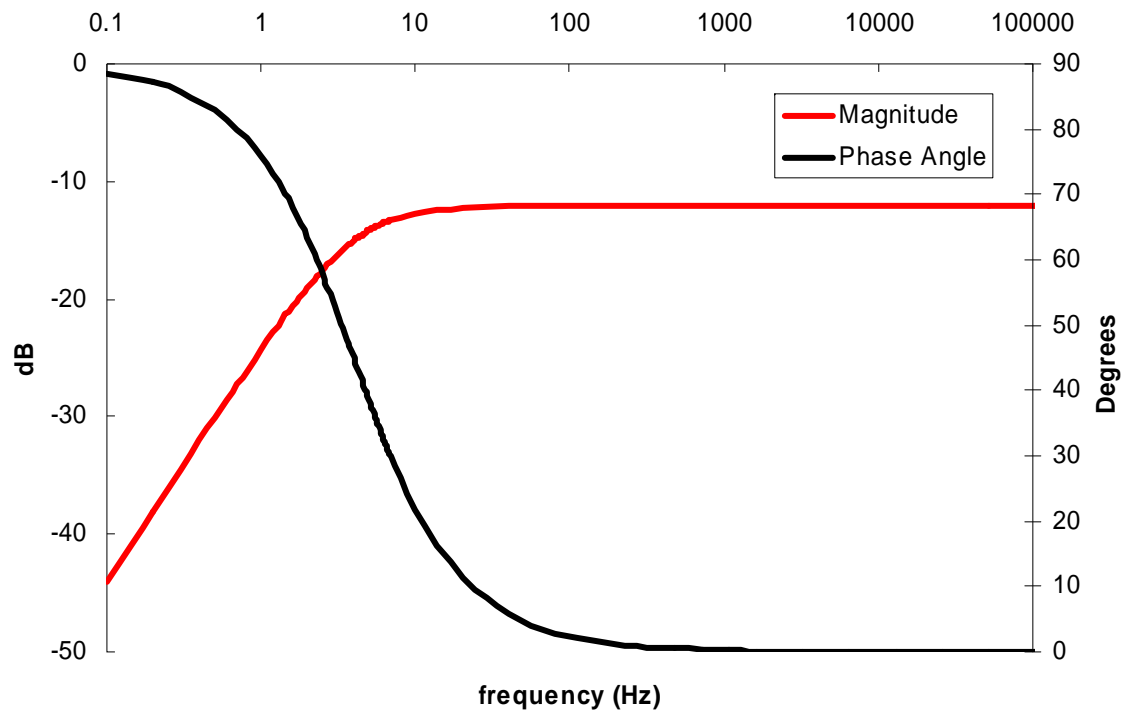Another Example: High Pass Filter (Continued)



$$\phi(f) = 90^\circ - \tan^{-1}(f/3.98)$$

RLC Circuits

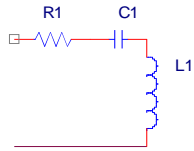

$$\begin{aligned}
 H(j\omega) &= \frac{j\omega L}{R + j\omega L + \frac{1}{j\omega C}} \\
 &= \frac{j\omega L}{R + j(\omega L - \frac{1}{\omega C})} \\
 &= \frac{\omega L}{\sqrt{R^2 + (\omega L - \frac{1}{\omega C})^2}} \angle 90^\circ - \tan^{-1}\left[\frac{(\omega L - \frac{1}{\omega C})}{R}\right]
 \end{aligned}$$


OR

$$\begin{aligned}
 &= \frac{-\omega^2 LC}{(1 - \omega^2 LC) + j\omega RC} \\
 &= \frac{\omega^2 LC}{\sqrt{(1 - \omega^2 LC)^2 + (\omega RC)^2}} \angle 180^\circ - \tan^{-1}\left[\frac{\omega RC}{(1 - \omega^2 LC)}\right]
 \end{aligned}$$

$$H(j0) = 0 \angle 180^\circ$$

$$H(j\frac{1}{\sqrt{LC}}) = \frac{1}{R} \sqrt{\frac{L}{C}} \angle 90^\circ$$
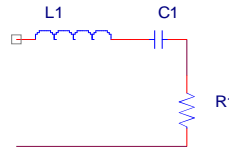
$$H(j\omega \rightarrow \infty) = 1 \angle 0^\circ$$



$$\begin{aligned}
 H(j\omega) &= \frac{R}{R + j\omega L + \frac{1}{j\omega C}} \\
 &= \frac{R}{R + j(\omega L - \frac{1}{\omega C})} \\
 &= \frac{R}{\sqrt{R^2 + (\omega L - \frac{1}{\omega C})^2}} \angle -\tan^{-1}\left[\frac{(\omega L - \frac{1}{\omega C})}{R}\right]
 \end{aligned}$$


OR

$$\begin{aligned}
 &= \frac{j\omega RC}{(1 - \omega^2 LC) + j\omega RC} \\
 &= \frac{\omega RC}{\sqrt{(1 - \omega^2 LC)^2 + (\omega RC)^2}} \angle 90^\circ - \tan^{-1}\left[\frac{\omega RC}{(1 - \omega^2 LC)}\right]
 \end{aligned}$$

$$H(j0) = 0 \angle 90^\circ$$

$$H(j\frac{1}{\sqrt{LC}}) = 1 \angle 0^\circ$$
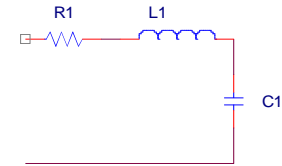
$$H(j\omega \rightarrow \infty) = 0 \angle -90^\circ$$



$$\begin{aligned}
 H(j\omega) &= \frac{1}{j\omega C} \\
 &= \frac{1}{R + j\omega L + \frac{1}{j\omega C}} \\
 &= \frac{1}{j\omega C} \\
 &= \frac{1}{R + j(\omega L - \frac{1}{\omega C})} \\
 &= \frac{1}{\omega C} \angle -90^\circ - \tan^{-1}\left[\frac{(\omega L - \frac{1}{\omega C})}{R}\right]
 \end{aligned}$$

OR


$$\begin{aligned}
 &= \frac{1}{(1 - \omega^2 LC) + j\omega RC} \\
 &= \frac{1}{\sqrt{(1 - \omega^2 LC)^2 + (\omega RC)^2}} \angle -\tan^{-1}\left[\frac{\omega RC}{(1 - \omega^2 LC)}\right]
 \end{aligned}$$

$$H(j0) = 1 \angle 0^\circ$$

$$H(j\frac{1}{\sqrt{LC}}) = \frac{1}{R} \sqrt{\frac{L}{C}} \angle -90^\circ$$

$$H(j\omega \rightarrow \infty) = 1 \angle 0^\circ$$

RLC Circuits

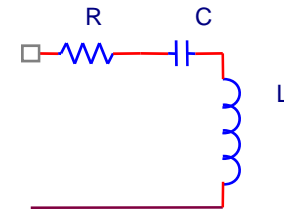

$$H(s) = \frac{sL}{R + sL + \frac{1}{sC}} = \frac{(sC)(sL)}{(sC)(sL) + sRC + 1} = \frac{s^2}{s^2 + s\frac{R}{L} + \frac{1}{LC}} = \frac{s^2}{(s - s_1)(s - s_2)}$$

$$\text{where } s_1, s_2 = \frac{-RC \pm \sqrt{(RC)^2 - 4LC}}{2LC} = \frac{-\frac{R}{L} \pm \sqrt{(\frac{R}{L})^2 - \frac{4}{LC}}}{2}; \text{ Let } p_1 = -s_1, p_2 = -s_2$$

$$p_1 + p_2 = \frac{\frac{R}{L} + \sqrt{(\frac{R}{L})^2 - \frac{4}{LC}}}{2} + \frac{\frac{R}{L} - \sqrt{(\frac{R}{L})^2 - \frac{4}{LC}}}{2} = \frac{R}{L}; p_1 \times p_2 = \frac{\frac{R}{L} + \sqrt{(\frac{R}{L})^2 - \frac{4}{LC}}}{2} \times \frac{\frac{R}{L} - \sqrt{(\frac{R}{L})^2 - \frac{4}{LC}}}{2} = \frac{1}{4} [(\frac{R}{L})^2 + \frac{R}{L}(\sqrt{(\frac{R}{L})^2 - \frac{4}{LC}} - \sqrt{(\frac{R}{L})^2 - \frac{4}{LC}}) - \{(\frac{R}{L})^2 - \frac{4}{LC}\}] = \frac{1}{LC}$$

$$H(s) = \frac{s^2}{(s + p_1)(s + p_2)} \Rightarrow H(j\omega) = \frac{(j\omega)^2}{(j\omega + p_1)(j\omega + p_2)} = \frac{-\frac{\omega^2}{p_1 p_2}}{(j\frac{\omega}{p_1} + 1)(j\frac{\omega}{p_2} + 1)} = \frac{-(2\pi f)^2}{(j\frac{2\pi f}{p_1} + 1)(j\frac{2\pi f}{p_2} + 1)} = \frac{-\frac{f^2}{f_1 f_2}}{(j\frac{f}{f_1} + 1)(j\frac{f}{f_2} + 1)}; \text{ where } f_1 = \frac{p_1}{2\pi}; f_2 = \frac{p_2}{2\pi}$$

$$= \frac{\frac{f^2}{f_1 f_2}}{\sqrt{(\frac{f}{f_1})^2 + 1} \sqrt{(\frac{f}{f_2})^2 + 1}} \angle \pi - \tan^{-1}(\frac{f}{f_1}) - \tan^{-1}(\frac{f}{f_2})$$

OR

$$= \frac{-\frac{f^2}{f_1 f_2}}{(1 - \frac{f^2}{f_1 f_2}) + j(\frac{f}{f_2} + \frac{f}{f_1})} = \frac{\frac{f^2}{f_1 f_2}}{\sqrt{(1 - \frac{f^2}{f_1 f_2})^2 + (\frac{f}{f_2} + \frac{f}{f_1})^2}} \angle \pi - \tan^{-1}(\frac{\frac{f}{f_2} + \frac{f}{f_1}}{1 - \frac{f^2}{f_1 f_2}})$$

RLC Circuits

$$H(j0) = 0 \angle 180^\circ$$

$$H(jf_1) = \frac{\frac{f_1}{f_2}}{\sqrt{2} \sqrt{\left(\frac{f_1}{f_2}\right)^2 + 1}} \angle \pi - \tan^{-1}(1) - \tan^{-1}\left(\frac{f_1}{f_2}\right) = \frac{f_1}{\sqrt{2} \sqrt{(f_1)^2 + (f_2)^2}} \angle \frac{3\pi}{4} - \tan^{-1}\left(\frac{f_1}{f_2}\right)$$

$$H(j\sqrt{f_1 f_2}) = \frac{1}{\frac{\sqrt{f_1 f_2}}{f_2} + \frac{\sqrt{f_1 f_2}}{f_1}} \angle \pi - \frac{\pi}{2} = \frac{1}{\frac{f_1 + f_2}{f_1 f_2}} \angle \frac{\pi}{2} = \frac{\sqrt{f_1 f_2}}{f_1 + f_2} \angle \frac{\pi}{2} = \frac{\sqrt{\frac{1}{LC}}}{\frac{R}{L}} \angle \frac{\pi}{2}$$


$$H(jf_2) = \frac{\frac{f_2}{f_1}}{\sqrt{2} \sqrt{\left(\frac{f_2}{f_1}\right)^2 + 1}} \angle \pi - \tan^{-1}\left(\frac{f_2}{f_1}\right) - \tan^{-1}(1) = \frac{f_2}{\sqrt{2} \sqrt{(f_1)^2 + (f_2)^2}} \angle \frac{3\pi}{4} - \tan^{-1}\left(\frac{f_2}{f_1}\right)$$

$$\text{If } f_2 \gg f_1; H(jf_2) = \frac{f_2}{\sqrt{2} \sqrt{(f_1)^2 + (f_2)^2}} \angle \frac{3\pi}{4} - \tan^{-1}\left(\frac{f_2}{f_1}\right) \approx \frac{1}{\sqrt{2}} \angle \frac{3\pi}{4} - \frac{\pi}{2} = \frac{1}{\sqrt{2}} \angle \frac{\pi}{4}$$


$$H(j\omega \rightarrow \infty) = 1 \angle 0^\circ$$

$$f_1 = 100 \text{ Hz}$$

$$f_2 = 1000 \text{ Hz}$$

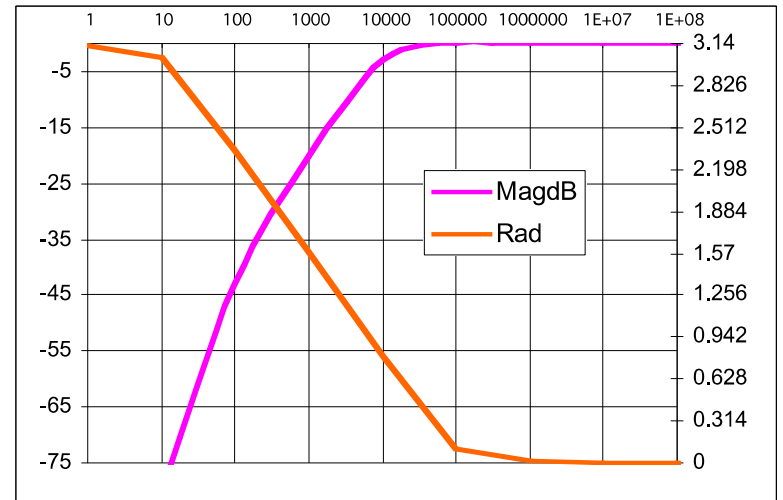

RLC Circuits

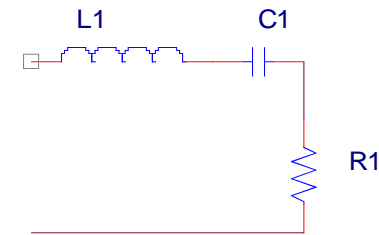

$$H(s) = \frac{R}{R + sL + \frac{1}{sC}} = \frac{(sC)(R)}{(sC)(sL) + sRC + 1} = \frac{s \frac{R}{L}}{s^2 + s \frac{R}{L} + \frac{1}{LC}} = \frac{s \frac{R}{L}}{(s - s_1)(s - s_2)}$$

$$\text{where } s_1, s_2 = \frac{-RC \pm \sqrt{(RC)^2 - 4LC}}{2LC} = \frac{-\frac{R}{L} \pm \sqrt{(\frac{R}{L})^2 - \frac{4}{LC}}}{2}; \text{ Let } p_1 = -s_1, p_2 = -s_2$$

$$p_1 + p_2 = \frac{\frac{R}{L} + \sqrt{(\frac{R}{L})^2 - \frac{4}{LC}}}{2} + \frac{\frac{R}{L} - \sqrt{(\frac{R}{L})^2 - \frac{4}{LC}}}{2} = \frac{R}{L}; p_1 \times p_2 = \frac{\frac{R}{L} + \sqrt{(\frac{R}{L})^2 - \frac{4}{LC}}}{2} \times \frac{\frac{R}{L} - \sqrt{(\frac{R}{L})^2 - \frac{4}{LC}}}{2} = \frac{1}{4} [(\frac{R}{L})^2 + \frac{R}{L} (\sqrt{(\frac{R}{L})^2 - \frac{4}{LC}} - \sqrt{(\frac{R}{L})^2 - \frac{4}{LC}}) - \{(\frac{R}{L})^2 - \frac{4}{LC}\}] = \frac{1}{LC}$$

$$H(s) = \frac{s(p_1 + p_2)}{(s + p_1)(s + p_2)} \Rightarrow H(j\omega) = \frac{j\omega(p_1 + p_2)}{(j\omega + p_1)(j\omega + p_2)} = \frac{j\omega \frac{(p_1 + p_2)}{p_1 p_2}}{(j \frac{\omega}{p_1} + 1)(j \frac{\omega}{p_2} + 1)} = \frac{jf \frac{(f_1 + f_2)}{f_1 f_2}}{(j \frac{f}{f_1} + 1)(j \frac{f}{f_2} + 1)}; \text{ where } f_1 = \frac{p_1}{2\pi}; f_2 = \frac{p_2}{2\pi}$$

$$= \frac{f \frac{(f_1 + f_2)}{f_1 f_2}}{\sqrt{(\frac{f}{f_1})^2 + 1} \sqrt{(\frac{f}{f_2})^2 + 1}} \angle \frac{\pi}{2} - \tan^{-1}(\frac{f}{f_1}) - \tan^{-1}(\frac{f}{f_2})$$

OR

$$= \frac{jf \frac{(f_1 + f_2)}{f_1 f_2}}{(1 - \frac{f^2}{f_1 f_2}) + j(\frac{f}{f_2} + \frac{f}{f_1})} = \frac{f \frac{(f_1 + f_2)}{f_1 f_2}}{\sqrt{(1 - \frac{f^2}{f_1 f_2})^2 + (\frac{f}{f_2} + \frac{f}{f_1})^2}} \angle \frac{\pi}{2} - \tan^{-1}(\frac{f_2 + f_1}{1 - \frac{f^2}{f_1 f_2}})$$

$$\frac{f_1 f_2}{f_1 + f_2} = \frac{f_1 f_2}{f_1(1 + \frac{f_2}{f_1})} = \frac{f_2}{(1 + \frac{f_2}{f_1})} < f_2; \frac{f_1 f_2}{f_1 + f_2} = \frac{f_1}{(1 + \frac{f_1}{f_2})} < f_1;$$

RLC Circuits

$$H(j0) = 0 \angle 90^\circ$$

$$H(jf_1) = \frac{(f_1 + f_2)}{f_2} \angle \frac{\pi}{2} - \tan^{-1}(1) - \tan^{-1}\left(\frac{f_1}{f_2}\right) = \frac{f_1 + f_2}{\sqrt{2}\sqrt{(f_1)^2 + (f_2)^2}} \angle \frac{\pi}{4} - \tan^{-1}\left(\frac{f_1}{f_2}\right)$$

$$H(j\sqrt{f_1 f_2}) = \frac{(f_1 + f_2)}{\left(\frac{1}{f_2} + \frac{1}{f_1}\right)} \angle \frac{\pi}{2} - \frac{\pi}{2} = 1 \angle 0$$


$$H(jf_2) = H(jf_1) = \frac{(f_1 + f_2)}{f_1} \angle \frac{\pi}{2} - \tan^{-1}\left(\frac{f_2}{f_1}\right) - \tan^{-1}(1) = \frac{f_1 + f_2}{\sqrt{2}\sqrt{(f_2)^2 + (f_1)^2}} \angle \frac{\pi}{4} - \tan^{-1}\left(\frac{f_2}{f_1}\right)$$

If $f_2 \gg f_1$; $H(jf_2) = \frac{f_1 + f_2}{\sqrt{2}\sqrt{(f_2)^2 + (f_1)^2}} \angle \frac{\pi}{4} - \tan^{-1}\left(\frac{f_2}{f_1}\right) \approx \frac{1}{\sqrt{2}} \angle -\frac{\pi}{4}$


$$H(j\omega \rightarrow \infty) = 0 \angle -90^\circ$$

$$f_1 = 100 \text{ Hz}$$

$$f_2 = 1000 \text{ Hz}$$

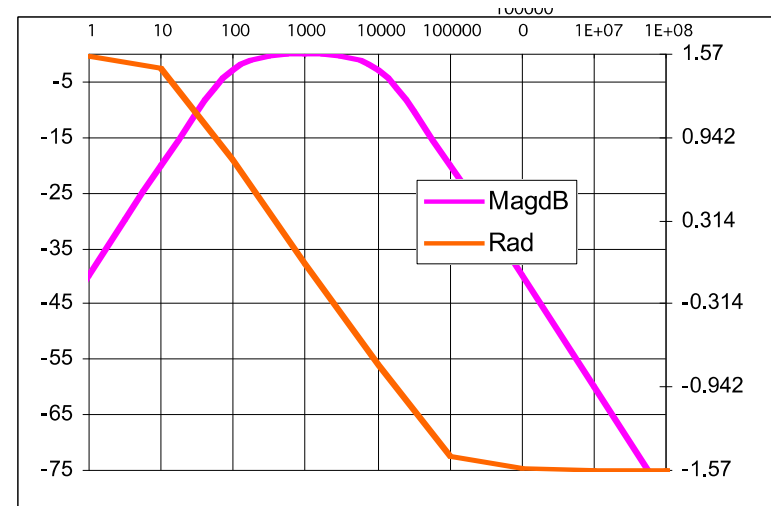

RLC Circuits

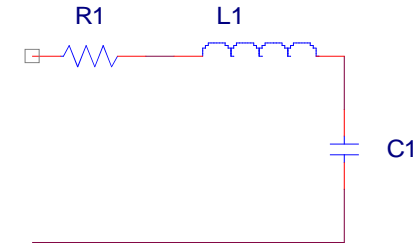

$$H(s) = \frac{\frac{1}{sC}}{R + sL + \frac{1}{sC}} = \frac{1}{(sC)(sL) + sRC + 1} = \frac{\frac{1}{LC}}{s^2 + s\frac{R}{L} + \frac{1}{LC}} = \frac{\frac{1}{LC}}{(s - s_1)(s - s_2)}$$

$$\text{where } s_1, s_2 = \frac{-RC \pm \sqrt{(RC)^2 - 4LC}}{2LC} = \frac{-\frac{R}{L} \pm \sqrt{(\frac{R}{L})^2 - \frac{4}{LC}}}{2}; \text{ Let } p_1 = -s_1, p_2 = -s_2$$

$$p_1 + p_2 = \frac{\frac{R}{L} + \sqrt{(\frac{R}{L})^2 - \frac{4}{LC}}}{2} + \frac{\frac{R}{L} - \sqrt{(\frac{R}{L})^2 - \frac{4}{LC}}}{2} = \frac{R}{L}; p_1 \times p_2 = \frac{\frac{R}{L} + \sqrt{(\frac{R}{L})^2 - \frac{4}{LC}}}{2} \times \frac{\frac{R}{L} - \sqrt{(\frac{R}{L})^2 - \frac{4}{LC}}}{2} = \frac{1}{4} [(\frac{R}{L})^2 + \frac{R}{L}(\sqrt{(\frac{R}{L})^2 - \frac{4}{LC}} - \sqrt{(\frac{R}{L})^2 - \frac{4}{LC}}) - \{(\frac{R}{L})^2 - \frac{4}{LC}\}] = \frac{1}{LC}$$

$$H(s) = \frac{p_1 p_2}{(s + p_1)(s + p_2)} \Rightarrow H(j\omega) = \frac{p_1 p_2}{(j\omega + p_1)(j\omega + p_2)} = \frac{1}{(j\frac{\omega}{p_1} + 1)(j\frac{\omega}{p_2} + 1)} = \frac{1}{(j\frac{f}{f_1} + 1)(j\frac{f}{f_2} + 1)}; \text{ where } f_1 = \frac{p_1}{2\pi}; f_2 = \frac{p_2}{2\pi}$$

$$= \frac{1}{\sqrt{(\frac{f}{f_1})^2 + 1} \sqrt{(\frac{f}{f_2})^2 + 1}} \angle -\tan^{-1}(\frac{f}{f_1}) - \tan^{-1}(\frac{f}{f_2})$$

OR

$$= \frac{1}{(1 - \frac{f^2}{f_1 f_2}) + j(\frac{f}{f_2} + \frac{f}{f_1})} = \frac{1}{\sqrt{(1 - \frac{f^2}{f_1 f_2})^2 + (\frac{f}{f_2} + \frac{f}{f_1})^2}} \angle -\tan^{-1}(\frac{\frac{f}{f_2} + \frac{f}{f_1}}{1 - \frac{f^2}{f_1 f_2}})$$

RLC Circuits

$$H(j0) = 1 \angle 0^\circ$$

$$H(jf_1) = \frac{1}{\sqrt{2} \sqrt{\left(\frac{f_1}{f_2}\right)^2 + 1}} \angle -\tan^{-1}(1) - \tan^{-1}\left(\frac{f_1}{f_2}\right) = \frac{f_2}{\sqrt{2} \sqrt{(f_1)^2 + (f_2)^2}} \angle -\frac{\pi}{4} - \tan^{-1}\left(\frac{f_1}{f_2}\right)$$

If $f_2 \gg f_1$; $H(jf_2) = \frac{f_2}{\sqrt{2} \sqrt{(f_2)^2 + (f_1)^2}} \angle -\frac{\pi}{4} - \tan^{-1}\left(\frac{f_1}{f_2}\right) \approx \frac{1}{\sqrt{2}} \angle -\frac{\pi}{4}$


$$H(j\sqrt{f_1 f_2}) = \frac{1}{\left(\frac{1}{f_2} + \frac{1}{f_1}\right)} \angle -\frac{\pi}{2} = \frac{f_1 f_2}{f_1 + f_2} \angle -\frac{\pi}{2}$$

$$H(jf_2) = H(jf_1) = \frac{1}{\sqrt{2} \sqrt{\left(\frac{f_2}{f_1}\right)^2 + 1}} \angle -\tan^{-1}\left(\frac{f_2}{f_1}\right) - \tan^{-1}(1) = \frac{f_1}{\sqrt{2} \sqrt{(f_2)^2 + (f_1)^2}} \angle -\frac{\pi}{4} - \tan^{-1}\left(\frac{f_2}{f_1}\right)$$

$$H(j\omega \rightarrow \infty) = 0 \angle -\pi$$

$$f_1 = 100 \text{ Hz}$$

$$f_2 = 1000 \text{ Hz}$$

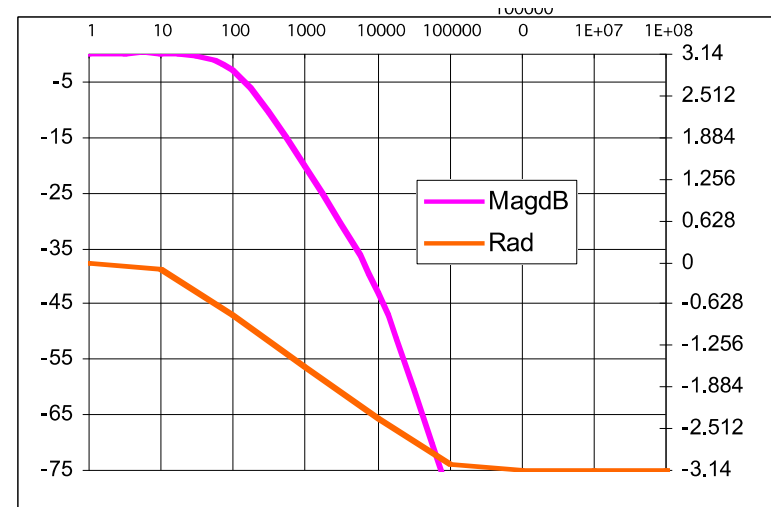

Homework

- Bode Plots
 - Problems: 8.7-9