

Modulation

Lesson 13

Sec 1.1.6

Homework

- Problem (1)
 - The signal $f(t) = (1 + m_o \cos t) \cos 100t$ is applied to a series RLC circuit where $L = 10$ h, $C = 10 \mu\text{F}$, $R = 10\text{k} \Omega$. Calculate $v(t)$, the voltage across the resistance.
- Problem (2)
 - The SSBSC version of $f(t)$ is applied to the same circuit. Calculate $v(t)$.

Homework Answers #1

- Problem (1)
 - The signal $f(t) = (1 + m_o \cos t) \cos 100t$ is applied to a series RLC circuit where $L = 10$ h, $C = 10 \mu\text{F}$, $R = 10\text{k} \Omega$. Calculate $v(t)$, the voltage across the resistance.

Recall:

$$\mathfrak{T}[f(t)] = \mathfrak{T}[K \{1 + m(t)\} \cos \omega_o t]$$

$$= K\pi \{ \delta(\omega - \omega_o) + \delta(\omega + \omega_o) \} + \frac{K}{2} \{ M[j(\omega - \omega_o)] + M[j(\omega + \omega_o)] \}$$

$$= \pi \{ \delta(\omega - 100) + \delta(\omega + 100) \} + \frac{1}{2} \{ M[j(\omega - 100)] + M[j(\omega + 100)] \}$$

since $m(t) = \cos t$

$$\text{then } \mathfrak{T}[m(t)] = \pi [\delta(\omega - 1) + \delta(\omega + 1)]$$

$$\mathfrak{T}[f(t)] = F(j\omega) = \pi \{ \delta(\omega - 100) + \delta(\omega + 100) \} + \frac{m_o}{2} \{ \pi [\delta(\omega - 1 - 100) + \delta(\omega + 1 - 100)] + \pi [\delta(\omega - 1 + 100) + \delta(\omega + 1 + 100)] \}$$

$$= \pi [\delta(\omega - 100) + \delta(\omega + 100)] + \frac{m_o}{2} \{ [\delta(\omega - 101) + \delta(\omega - 99)] + [\delta(\omega + 99) + \delta(\omega + 101)] \}$$

Homework Answers #2

- Problem (1)

- The signal $f(t) = (1 + m_o \cos t) \cos 100t$ is applied to a series RLC circuit where $L = 10 \text{ h}$, $C = 10 \mu\text{F}$, $R = 10\text{k} \Omega$. Calculate $v(t)$, the voltage across the resistance.

$$\begin{aligned}
 H(j\omega) &= \frac{R}{R + j\omega L + \frac{1}{j\omega C}} = \frac{10k}{10k + j\omega 10 + \frac{1}{j\omega 10 \times 10^{-6}}} \\
 &= \frac{j\omega 10 \times 10^{-6} \times 10k}{j\omega 10 \times 10^{-6} \times 10k + j\omega 10 \times 10^{-6} \times j\omega 10 + 1} \\
 &= \frac{j\omega 10^{-1}}{1 - \omega^2 10^{-4} + j\omega 10^{-1}}
 \end{aligned}$$

$$\begin{aligned}
 H(j\omega) &= \frac{j\omega 10^{-1}}{1 - \omega^2 10^{-4} + j\omega 10^{-1}} \\
 &= \frac{\omega 10^{-1}}{\sqrt{(1 - \omega^2 10^{-4})^2 + (\omega 10^{-1})^2}} \angle 90 - \tan^{-1} \left[\frac{\omega 10^{-1}}{(1 - \omega^2 10^{-4})} \right]
 \end{aligned}$$

$$F(j\omega) = \pi [\delta(\omega - 100) + \delta(\omega + 100) + \frac{m_o}{2} \{ [\delta(\omega + 99) + \delta(\omega - 99)] + [\delta(\omega + 101) + \delta(\omega - 101)] \}]$$

However, $F(j\omega)$ has value only at $\omega = 99, 100, 101$

Homework Answers #3

- Problem (1)
 - The signal $f(t) = (1 + m_o \cos t) \cos 100t$ is applied to a series RLC circuit where $L = 10$ h, $C = 10 \mu\text{F}$, $R = 10\text{k} \Omega$. Calculate $v(t)$, the voltage across the resistance.

$$H(j\omega) = \frac{j\omega 10^{-1}}{1 - \omega^2 10^{-4} + j\omega 10^{-1}}$$


$$= \frac{\omega 10^{-1}}{\sqrt{(1 - \omega^2 10^{-4})^2 + (\omega 10^{-1})^2}} \angle 90 - \tan^{-1} \left[\frac{\omega 10^{-1}}{(1 - \omega^2 10^{-4})} \right]$$

$$H(j99) = \frac{99 \times 10^{-1}}{\sqrt{(1 - 99^2 \times 10^{-4})^2 + (99 \times 10^{-1})^2}} \angle 90 - \tan^{-1} \left[\frac{99 \times 10^{-1}}{(1 - 99^2 \times 10^{-4})} \right]$$

$$= .9999 \angle 0.115^\circ$$

$$H(j100) = 1 \angle 0^\circ$$

$$H(j101) = .9999 \angle -0.115^\circ$$

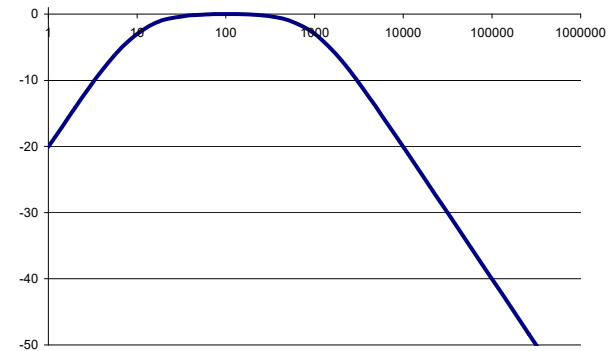

$$F(j\omega) = \pi [\delta(\omega - 100) + \delta(\omega + 100)] + \frac{m_o}{2} \{ [\delta(\omega + 99) + \delta(\omega - 99)] + [\delta(\omega + 101) + \delta(\omega - 101)] \}$$

$$v(t) = \cos 100t + .999m_o \cos(99t + 0.115) + .999m_o \cos(101t - 0.115)$$

Homework Answers #4

- Problem (2)
 - The SSBSC version of $f(t)$ is applied to the same circuit. Calculate $v(t)$.

Recall:

$$\begin{aligned}\mathfrak{T}[f(t)] &= \mathfrak{T}[SSBSC\{1 + m_o \cos t\} \cos 100t] = \mathfrak{T}[SSBSC\{\cos 100t + \frac{m_o}{2}(\cos 101t + \cos 99t)\}] \\ &= \mathfrak{T}[m_o(\cos 101t)] = \pi \frac{m_o}{2} [\delta(\omega + 101) + \delta(\omega - 101)]\end{aligned}$$

$$H(j\omega) = \frac{j\omega 10^{-1}}{1 - \omega^2 10^{-4} + j\omega 10^{-1}} \quad F(j\omega) = \pi \frac{m_o}{2} [\delta(\omega + 101) + \delta(\omega - 101)]$$

$$H(j101) = .9999 \angle -0.115^\circ \quad v(t) = .999m_o \cos(101t - 0.115)$$