

Sinusoidal Response and Discrete Systems

Lecture #5


3CT.2

BME 333 Biomedical Signals and Systems

- J.Schesser

Homework

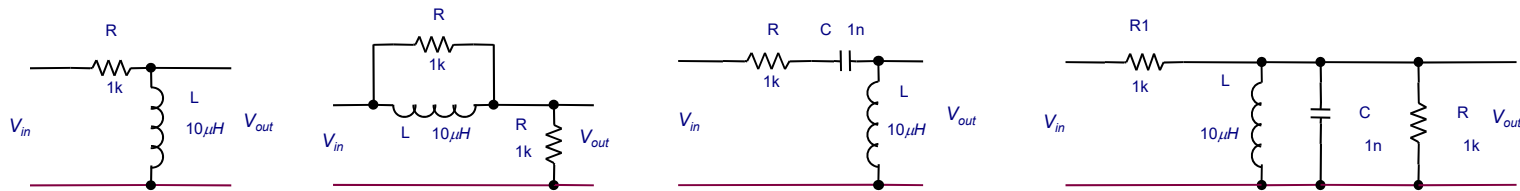
- Sinusoidal Steady State
 - Calculate the Sinusoidal Steady State Response of the network function for the following networks:



- Bode Plots
 - Draw the Bode Plots for these networks.
 - Use Matlab to plot the Bode Plot, submit your code.
- Discrete ODE
 - Calculate the monthly payment P_c
- 3CT.3.1, 3CT.3.2, 3CT.3.4

Homework Answers #1

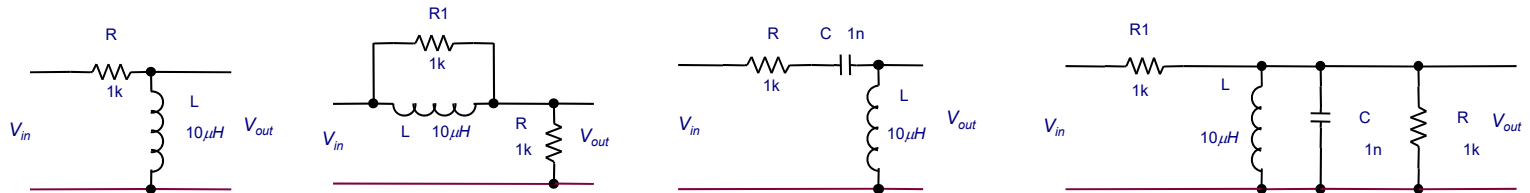- Sinusoidal Steady State
 - Calculate the Sinusoidal Steady State Response of the network function for the following networks:




$$a) v_{out}(t) = L \frac{di(t)}{dt} = pLi(t); v_{in}(t) = i(t)R + L \frac{di(t)}{dt} = i(t)(R + Lp); \frac{v_{out}(t)}{v_{in}(t)} = \frac{pLi(t)}{i(t)(R + Lp)} = \frac{pL}{(R + Lp)} \Rightarrow \frac{V_{out}(j\omega)}{V_{in}(j\omega)} = \frac{j\omega L}{(R + j\omega L)}$$

$$\frac{V_{out}(j\omega)}{V_{in}(j\omega)} = \frac{j\omega L}{j\omega L + R} = \frac{j\omega 10 \times 10^{-6}}{j\omega 10 \times 10^{-6} + 1 \times 10^3} = \frac{j\omega 1 \times 10^{-8}}{j\omega 1 \times 10^{-8} + 1} = \frac{\omega 10^{-8} \angle \frac{\pi}{2}}{\sqrt{1 + (\omega 10^{-8})^2} \angle \tan^{-1}(\omega 10^{-8})} = \frac{\omega 10^{-8}}{\sqrt{1 + (\omega 10^{-8})^2}} \angle \frac{\pi}{2} - \tan^{-1}(\omega 10^{-8})$$

Homework Answers #1

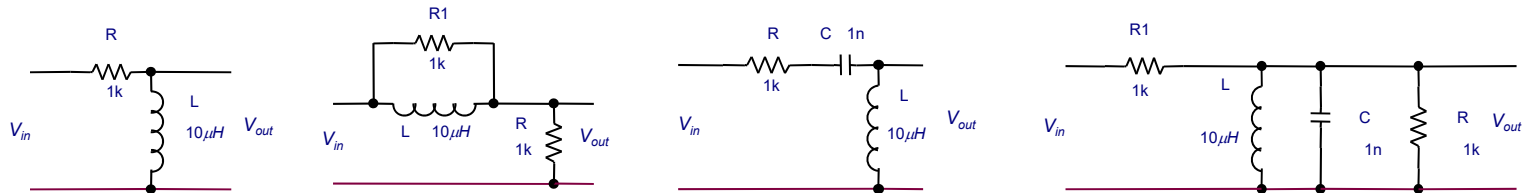- Sinusoidal Steady State
 - Calculate the Sinusoidal Steady State Response of the network function for the following networks:



$$b) v_{out}(t) = i(t)R; v_{in}(t) = i(t)R + v_{par}(t); v_{par}(t) = i_{R_1}(t)R_1 = L \frac{di_L(t)}{dt} = Lp i_L(t); i(t) = \frac{v_{par}(t)}{R_1} + \frac{v_{par}(t)}{Lp} \Rightarrow v_{par}(t) = \frac{i(t)}{\frac{1}{R_1} + \frac{1}{Lp}}$$

$$v_{in}(t) = i(t)R + v_{par}(t) = i(t)R + \frac{i(t)}{\frac{1}{R_1} + \frac{1}{Lp}}; \frac{v_{out}(t)}{v_{in}(t)} = \frac{i(t)R}{i(t)(R + \frac{1}{\frac{1}{R_1} + \frac{1}{Lp}})} = \frac{R}{(R + \frac{1}{\frac{1}{R_1} + \frac{1}{Lp}})} \Rightarrow \frac{V_{out}(j\omega)}{V_{in}(j\omega)} = \frac{R}{(R + \frac{1}{\frac{1}{R_1} + j\omega L})}$$


$$\frac{V_{out}(j\omega)}{V_{in}(j\omega)} = \frac{R}{R + R_1 \parallel j\omega L} = \frac{R}{R + \frac{j\omega LR_1}{R_1 + j\omega L}} = \frac{R(R_1 + j\omega L)}{R(R_1 + j\omega L) + j\omega LR_1} = \frac{RR_1 + j\omega LR}{RR_1 + j\omega L(R_1 + R)}$$

$$= \frac{(1 \times 10^3)^2 + j\omega(10 \times 10^{-6})(1 \times 10^3)}{(1 \times 10^3)^2 + j\omega 10 \times 10^{-6}(1 \times 10^3 + 1 \times 10^3)} = \frac{10^6 + j\omega 10^{-2}}{10^6 + j\omega 2 \times 10^{-2}} = \frac{\sqrt{1 + (\omega 10^{-8})^2}}{\sqrt{1 + (\omega 2 \times 10^{-8})^2}} \angle \tan^{-1}(\omega 10^{-8}) - \tan^{-1}(2\omega 10^{-8})$$

Homework Answers #1

- Sinusoidal Steady State

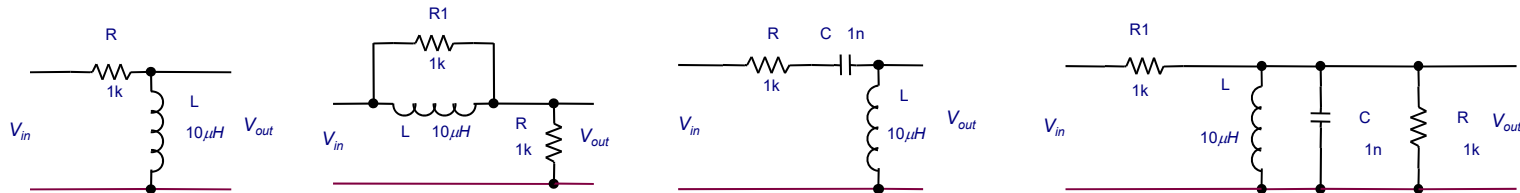- Calculate the Sinusoidal Steady State Response of the network function for the following networks:



$$c) v_{out}(t) = L \frac{di(t)}{dt} = pLi(t); v_{in}(t) = i(t)R + \frac{1}{C} \int i(t)dt + L \frac{di(t)}{dt} = i(t)R + \frac{1}{pC} i(t) + pLi(t) = i(t)(R + \frac{1}{pC} + pL);$$

$$\frac{v_{out}(t)}{v_{in}(t)} = \frac{pLi(t)}{(R + \frac{1}{pC} + pL)} \Rightarrow \frac{V_{out}(j\omega)}{V_{in}(j\omega)} = \frac{j\omega L}{R + 1/j\omega C + j\omega L}$$

$$\frac{V_{out}(j\omega)}{V_{in}(j\omega)} = \frac{j\omega L}{R + 1/j\omega C + j\omega L} = \frac{-\omega^2 LC}{1 - \omega^2 LC + j\omega CR} = \frac{-\omega^2(10 \times 10^{-6}) \times (1 \times 10^{-9})}{1 - \omega^2(10 \times 10^{-6}) \times (1 \times 10^{-9}) + j\omega(1 \times 10^{-9}) \times 1 \times 10^3} = \frac{-\omega^2 10^{-14}}{1 - \omega^2 10^{-14} + j\omega 10^{-6}}$$


$$= \frac{\omega^2 10^{-14}}{\sqrt{(1 - \omega^2 10^{-14})^2 + \omega^2 10^{-12}}} \angle \pi - \tan^{-1}[\omega 10^{-6} / (1 - \omega^2 10^{-14})]$$

$$\frac{-\omega^2 LC}{j\omega CR} = j\omega \frac{L}{R} = j \frac{1}{\sqrt{LC}} \frac{L}{R} = j \frac{1}{R} \sqrt{\frac{L}{C}} = \frac{10^7 10^{-14}}{10^{-6}} = \frac{10^{-7}}{10^{-6}} = 10^{-1}$$

Homework Answers #1

- Sinusoidal Steady State

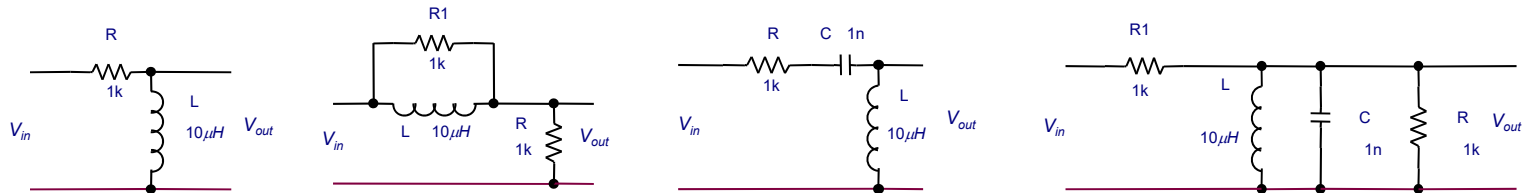- Calculate the Sinusoidal Steady State Response of the network function for the following networks:



$$d) v_{out}(t) = L \frac{di_L(t)}{dt} = pLi_L(t) = \frac{1}{C} \int i_C(t) dt = \frac{1}{pC} i_C(t) = Ri_R(t); v_{in}(t) = i(t)R_1 + v_{out}(t);$$

$$i(t) = i_L(t) + i_C(t) + i_R(t) = \frac{v_{out}(t)}{pL} + \frac{v_{out}(t)}{1/pC} + \frac{v_{out}(t)}{R} = \left(\frac{1}{pL} + \frac{1}{1/pC} + \frac{1}{R} \right) v_{out}(t); v_{out}(t) = \frac{i(t)}{\frac{1}{pL} + \frac{1}{1/pC} + \frac{1}{R}}$$




$$v_{in}(t) = i(t)R_1 + \frac{i(t)}{\frac{1}{pL} + \frac{1}{1/pC} + \frac{1}{R}}; \frac{v_{out}(t)}{v_{in}(t)} = \frac{\frac{i(t)}{\frac{1}{pL} + \frac{1}{1/pC} + \frac{1}{R}}}{i(t)R_1 + \frac{i(t)}{\frac{1}{pL} + \frac{1}{1/pC} + \frac{1}{R}}} = \frac{1}{R_1 + \frac{1}{\frac{1}{pL} + \frac{1}{1/pC} + \frac{1}{R}}} \Rightarrow \frac{V_{out}(j\omega)}{V_{in}(j\omega)} = \frac{1}{R_1 + \frac{1}{\frac{1}{j\omega L} + \frac{1}{1/j\omega C} + \frac{1}{R}}}$$

$$\frac{V_{out}(j\omega)}{V_{in}(j\omega)} = \frac{j\omega L \parallel 1/j\omega C \parallel R}{R_1 + j\omega L \parallel 1/j\omega C \parallel R} = \frac{j\omega LR}{R_1 + \frac{j\omega LR}{R(1 - \omega^2 LC) + j\omega L}} = \frac{j\omega LR}{R_1 R(1 - \omega^2 LC) + j\omega L(R + R_1)}$$

$$= \frac{j\omega 10^{-2}}{10^6(1 - \omega^2 10^{-14}) + j\omega 2 \times 10^{-2}} = \frac{\omega 10^{-8}}{\sqrt{(1 - \omega^2 10^{-14})^2 + \omega^2 4 \times 10^{-16}}} \angle \frac{\pi}{2} - \tan^{-1}[\omega 2 \times 10^{-8} / (1 - \omega^2 10^{-14})]$$


Homework Answers #2

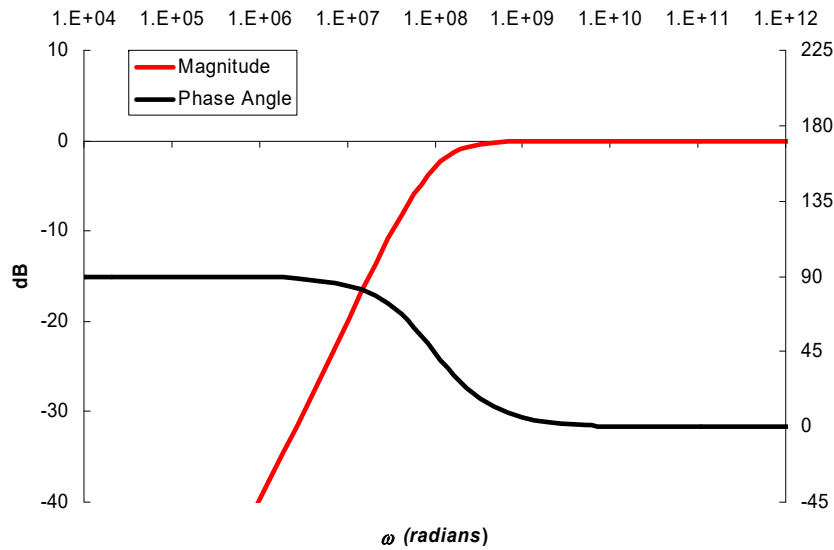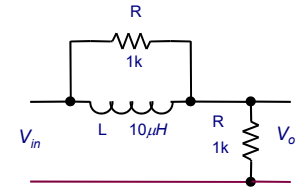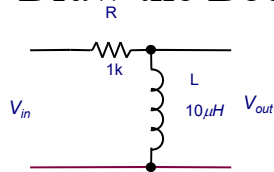- Bode Plots
 - Draw the Bode Plots for these networks.



$$a) \frac{V_{out}(j\omega)}{V_{in}(j\omega)} = H(j\omega) = \frac{\omega 10^{-8}}{\sqrt{1 + (\omega 10^{-8})^2}} \angle \frac{\pi}{2} - \tan^{-1}(\omega 10^{-8})$$
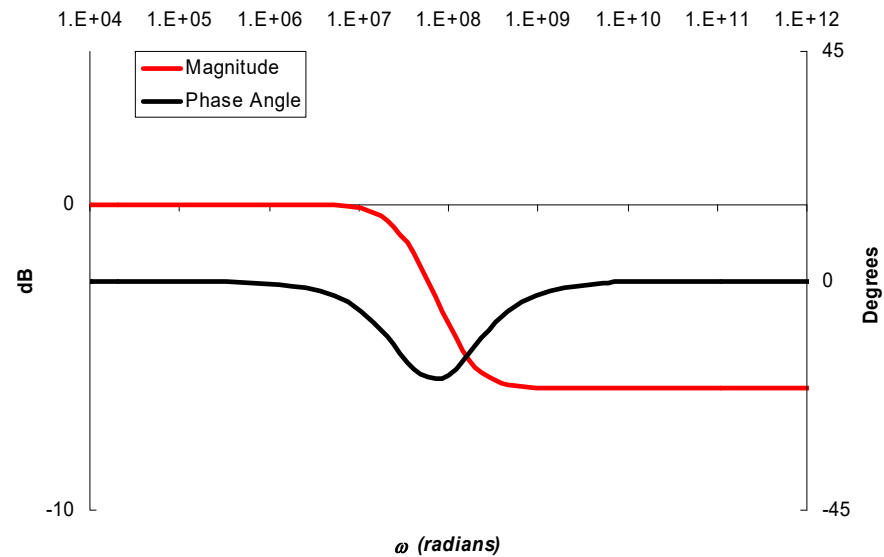
$$H(j0) = 0 \angle \frac{\pi}{2}; H(j10^8) = \frac{1}{\sqrt{2}} \angle \frac{\pi}{4}; H(j\infty) = 1 \angle 0$$





$$b) \frac{V_{out}(j\omega)}{V_{in}(j\omega)} = H(j\omega) = \frac{\sqrt{1 + (\omega 10^{-8})^2}}{\sqrt{1 + (\omega 2 \times 10^{-8})^2}} \angle \tan^{-1}(\omega 10^{-8}) - \tan^{-1}(2\omega 10^{-8})$$

$$H(j0) = 1 \angle 0; H(j0.5 \times 10^8) = 0.79 \angle -0.32; H(j\infty) = .5 \angle 0$$



Homework Answers #3

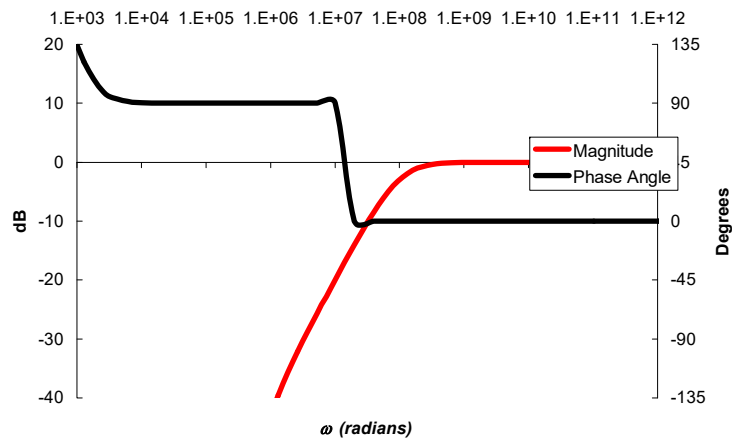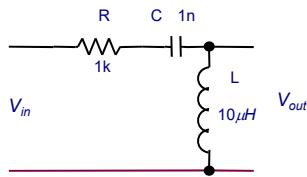- Bode Plots
 - Draw the Bode Plots for these networks.



$$c) H(j\omega) = \frac{\omega^2 10^{-14}}{\sqrt{(1 - \omega^2 10^{-14})^2 + \omega^2 10^{-12}}} \angle \pi - \tan^{-1}[\omega 10^{-6} / (1 - \omega^2 10^{-14})]$$
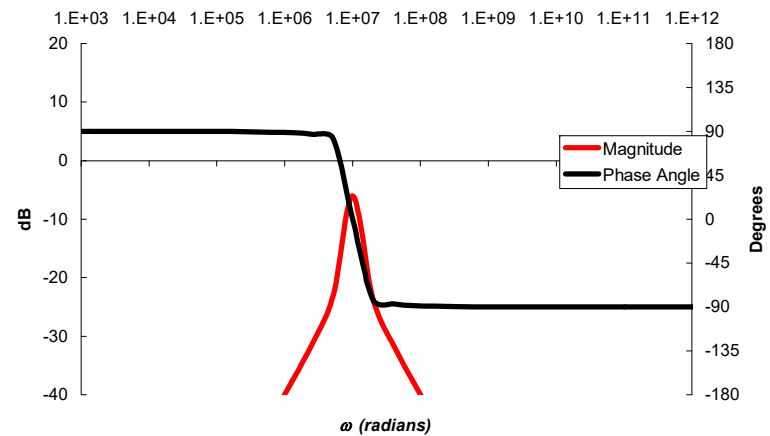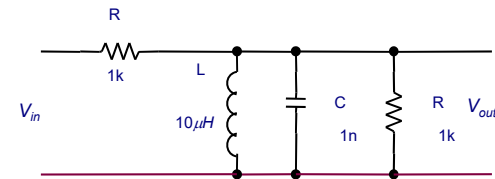
$$H(j0) = 0 \angle \pi; H(j10^7) = .1 \angle \frac{\pi}{2}; H(j\infty) = 1 \angle 0$$




$$d) H(j\omega) = \frac{\omega 10^{-2}}{\sqrt{10^{12}(1 - \omega^2 10^{-14})^2 + \omega^2 4 \times 10^{-4}}} \angle \frac{\pi}{2} - \tan^{-1}[\omega 2 \times 10^{-2} / 10^6 (1 - \omega^2 10^{-14})]$$

$$H(j0) = 0 \angle \frac{\pi}{2}; H(j10^7) = .5 \angle 0; H(j\infty) = 0 \angle -\frac{\pi}{2}$$


Matlab Code

```
clear all;
R=1000;L=1e-5;
omega=(R/L*0.01:R/L*0.01:R/L*100);
maxomega=length(omega);
for j=1:maxomega
    fr(j)=complex(0,omega(j)*L)/complex(R,omega(j)*L);
end
subplot(2,1,1);
semilogx(omega/(2*pi),abs(fr));
title(['Magnitude of RL circuit R=',num2str(R),' L=',num2str(L)]);
xlabel('Hz');
subplot(2,1,2)
semilogx(omega/(2*pi),angle(fr));
title(['Angle of RL circuit R=',num2str(R),' L=',num2str(L)]);
xlabel('Hz');
ylabel('Radians');
```

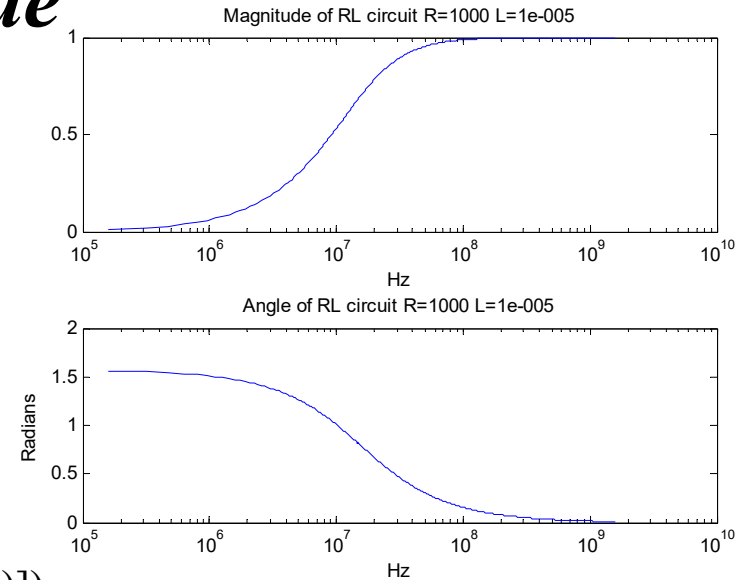


Matlab Code

```
clear all;
R1=1000;R=1000;L=1e-5;
wn=R1/L;wd=R1*R/(L*(R1+R));
w=max(wn,wd);
omega=(w*0.01:w*0.01:w*100);
maxomega=length(omega);
for j=1:maxomega
    fr(j)=R*complex(R1,omega(j)*L)/complex(R*R1,omega(j)*L*(R1+R));
end
subplot(2,1,1);
semilogx(omega/(2*pi),abs(fr));
title(['Magnitude of RL circuit R=',num2str(R),' R1=',num2str(R1),' L=',num2str(L)]);
xlabel('Hz');
subplot(2,1,2)
semilogx(omega/(2*pi),angle(fr));
title(['Angle of RL circuit R=',num2str(R),' R1=',num2str(R1),' L=',num2str(L)]);
xlabel('Hz');
ylabel('Radians');
```


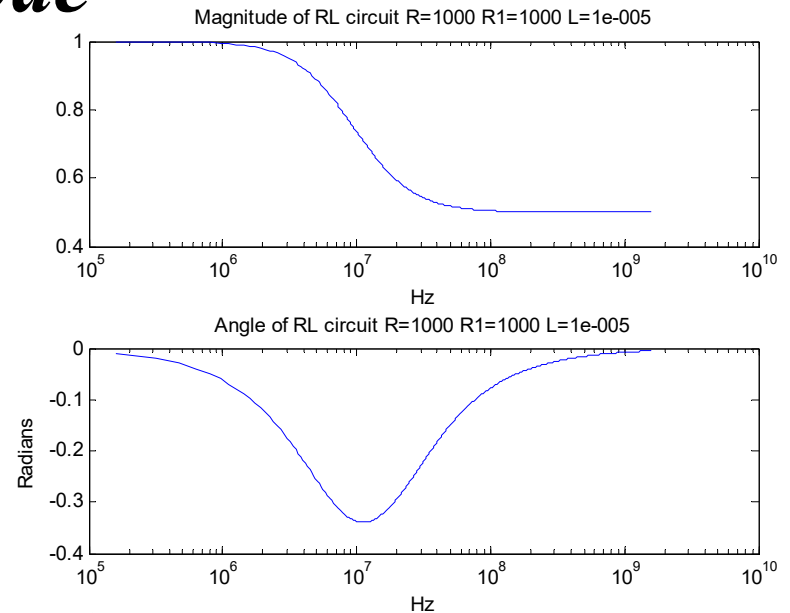


Homework Answers #3a

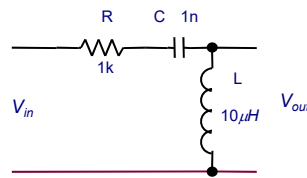- Bode Plots
 - Draw the Bode Plots for these networks.




R	Peak	Peak dB
10	10.00	20
100	1.00	0
200	0.50	-6
199	0.50	-6
200	0.50	-6
1000	0.10	-20

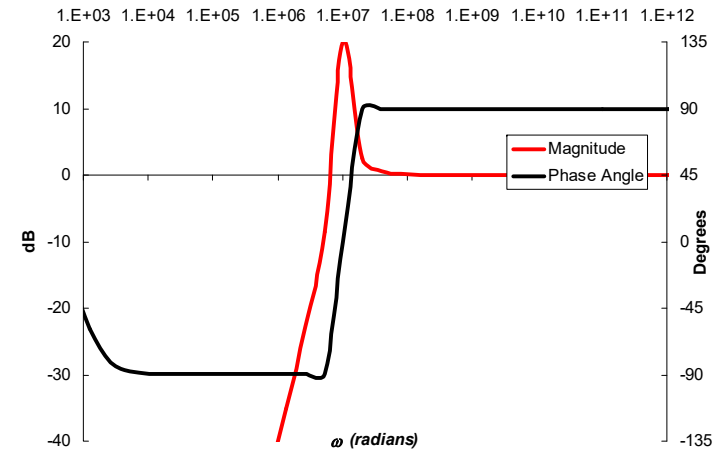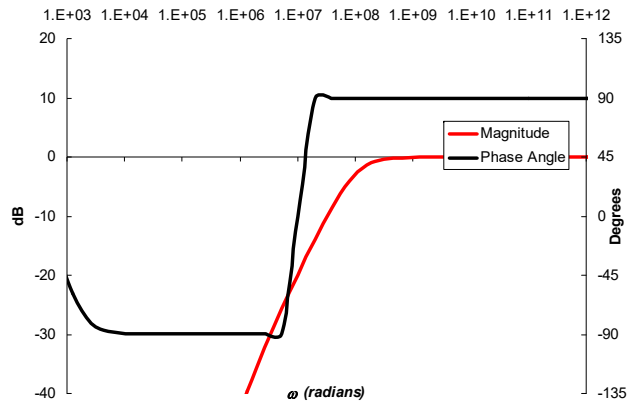


Matlab Code

```
clear all;
R1=1000;R=1000;L=1e-5;C=1e-9;
w=sqrt(1/(L*C));
omega=(w*0.01:w*0.01:w*100);
maxomega=length(omega);
for j=1:maxomega
    fr(j)=complex(0,omega(j)*L)/complex(R,(omega(j)*L-1/(omega(j)*C)));
end
subplot(2,1,1);
semilogx(omega/(2*pi),abs(fr));
title(['Magnitude of RLC circuit R=',num2str(R),' L=',num2str(L),' C=',num2str(C)]);
xlabel('Hz');
subplot(2,1,2)
semilogx(omega/(2*pi),angle(fr));
title(['Angle of RLC circuit R=',num2str(R),' L=',num2str(L),' C=',num2str(C)]);
xlabel('Hz');
ylabel('Radians');
```

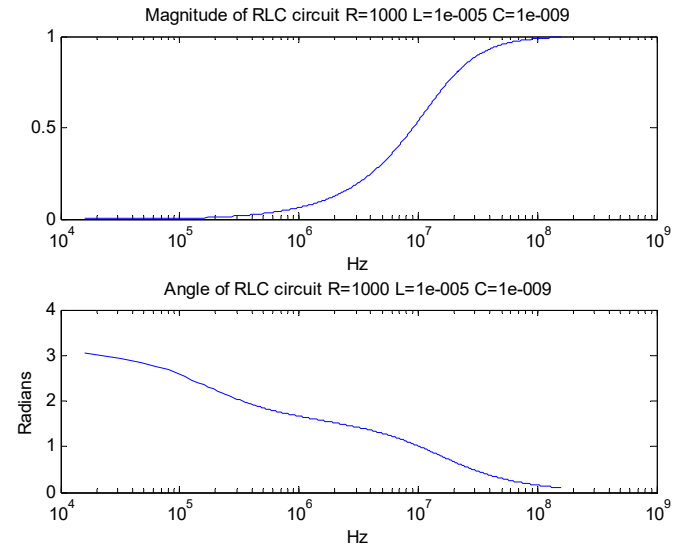

Matlab Code

```
clear all;
R1=1000;R=1000;L=1e-5;C=1e-9;
w=sqrt(1/(L*C));
omega=(w*0.01:w*0.01:w*100);
maxomega=length(omega);
for j=1:maxomega
    fr(j)=complex(0,omega(j)*L*R)/complex(R*R1*(1-omega(j)^2*L*C),omega(j)*L*(R1+R));
end
subplot(2,1,1);
semilogx(omega/(2*pi),abs(fr));
title(['Magnitude of RLC circuit R=',num2str(R),' R1=',num2str(R1),' L=',num2str(L),' C=',num2str(C)]);
xlabel('Hz');
subplot(2,1,2)
semilogx(omega/(2*pi),angle(fr));
title(['Angle of RLC circuit R=',num2str(R),' R1=',num2str(R1),' L=',num2str(L),' C=',num2str(C)]);
xlabel('Hz');
ylabel('Radians');
```

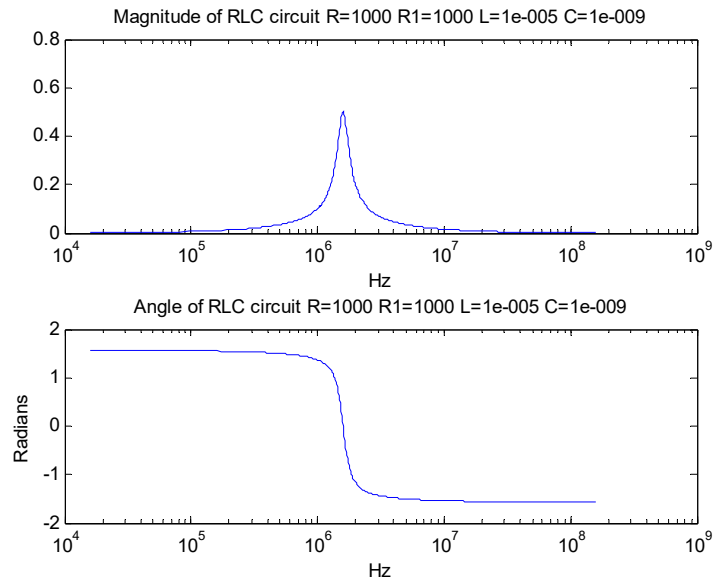

Homework Answers #4

- Discrete ODE
 - Calculate the monthly payment Pc

$$(1+r)P(i-1) - P(i) = Pc$$

$$(1+r)\{A_1 a^{i-1} + A_2\} - \{A_1 a^i + A_2\} = Pc$$

$$\{(1+r)A_1 a^{i-1} - A_1 a^i\} + (1+r)A_2 - A_2 = Pc$$

$$1) (1+r)A_1 a^{i-1} - A_1 a^i = 0 \Rightarrow a = (1+r)$$

$$2) \{(1+r) - 1\}A_2 = Pc \Rightarrow A_2 = \frac{Pc}{r}$$

$$P[i] = A_1(1+r)^i + \frac{Pc}{r}; P[N] = 0 \Rightarrow A_1 = -\frac{Pc}{r(1+r)^N}$$

$$\therefore P[i] = \frac{Pc}{r(1+r)^N} \{(1+r)^N - (1+r)^i\}$$

$$P[0] = P_{LOAN} = \frac{Pc}{r(1+r)^N} \{(1+r)^N - (1+r)^0\}$$

$$= \frac{Pc}{r(1+r)^N} \{(1+r)^N - 1\}$$

$$Pc = P_{LOAN} \frac{r(1+r)^N}{(1+r)^N - 1}$$

3CT.3.1

From 310 chapter 10:

$$\begin{aligned} H^*(F) &= \left(\int_{-\infty}^{\infty} h(t) e^{-j2\pi Ft} dt \right)^* = \int_{-\infty}^{\infty} h(t)^* e^{+j2\pi Ft} dt \\ &= \int_{-\infty}^{\infty} h(t) e^{-j(-2\pi F)t} dt = H(-F) \end{aligned}$$

$h(t)^* = h(t)$ Only if $h(t)$ is real-valued

If $H(F) = Me^{j\psi}$

Then $H(-F) = H^*(F) = (Me^{j\psi})^* = Me^{-j\psi}$

OR

$$H(F) = \int_{-\infty}^{\infty} h(t) e^{-j2\pi Ft} dt$$

$$H(-F) = \int_{-\infty}^{\infty} h(t) e^{j2\pi Ft} dt = H^*(F) = \left(\int_{-\infty}^{\infty} h(t) e^{-j2\pi Ft} dt \right)^* = \int_{-\infty}^{\infty} h(t)^* e^{+j2\pi Ft} dt \text{ since } h(t)^* = h(t)$$

3CT3.2

Again from 310 chapter 10:

$$H(F) = |H(F)| e^{j\angle H(F)}$$

$$H(-F) = |H(-F)| e^{j\angle H(-F)}$$

$$\text{Since } H(-F) = H^*(e^{j\hat{\omega}}) = |H(F)| e^{-j\angle H(F)}$$

Then

$$|H(-F)| = |H(F)| \quad \text{even function}$$

$$\angle H(-F) = -\angle H(F) \quad \text{odd function}$$

3CT3.4

$$\frac{d^2 y(t)}{dt^2} + 2 \frac{dy(t)}{dt} + y(t) = 3 \frac{dx(t)}{dt} + x(t)$$

$$y(t) = Ye^{j2\pi Ft}; x(t) = Xe^{j2\pi Ft}$$

$$\frac{dy(t)}{dt} = (j2\pi F)Ye^{j2\pi Ft}; \frac{dx(t)}{dt} = (j2\pi F)Xe^{j2\pi Ft}$$

$$\frac{d^2 y(t)}{dt^2} = (j2\pi F)^2 Ye^{j2\pi Ft}$$

$$(2\pi F)^2 Ye^{j2\pi Ft} + 2(2\pi F)Ye^{j2\pi Ft} + Ye^{j2\pi Ft} = 3(2\pi F)Xe^{j2\pi Ft} + Xe^{j2\pi Ft}$$

$$[(2\pi F)^2 + 2(2\pi F) + 1]Ye^{j2\pi Ft} = [3(2\pi F) + 1]Xe^{j2\pi Ft}$$

$$\frac{Y}{X} = \frac{3(j2\pi F) + 1}{(j2\pi F)^2 + 2(j2\pi F) + 1}$$