
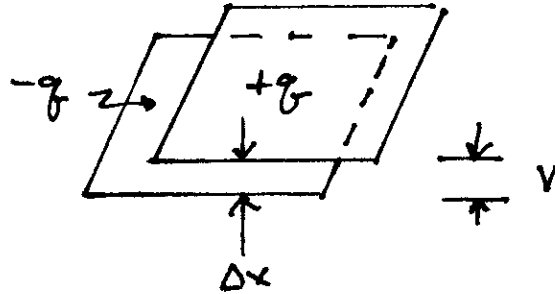


CAPACTANCE

USES

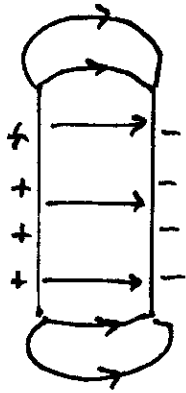1. STORE ENERGY
2. MICROSCOPIC MEMORY BANKS
3. ELEMENTS OF CIRCUITS



$$C = \frac{q}{V} \text{ [COUL/VOLT]} \quad 1 \text{ FARAD} = 1 \text{ C/V}$$

$$\Delta V = \int_{-}^{+} dV = - \int \vec{E} \cdot d\vec{s}$$

$$\Delta V = E \Delta x; \quad q = \epsilon_0 \int \vec{E} \cdot d\vec{A} = \epsilon_0 EA$$


IN TERMS OF GEOMETRY

$$C = \frac{\epsilon_0 A E}{\Delta x E} = \frac{\epsilon_0 A}{\Delta x}$$

EXAMPLE I A II PLATE CAPACITOR 4CM X 4CM HAS A PLATE SEPARATION OF 1/2 CM DETERMINE THE CAPACITORS VALUE

$$C = \frac{\epsilon_0 A}{\Delta x} = \frac{8.85 \times 10^{-12} (.04)^2}{0.005} = 2.83 \times 10^{-12} = 2.83 \text{ pF}$$

PARALLEL CAPACITORS

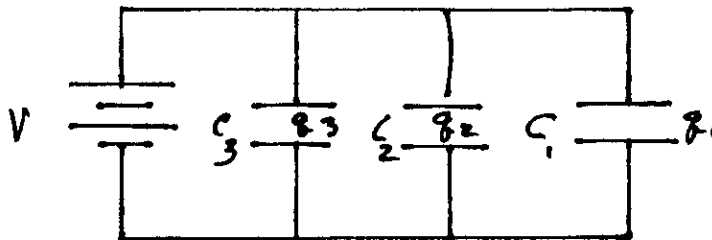


$$C_1 = \frac{q_1}{V}$$

$$C_2 = \frac{q_2}{V}$$

$$C_3 = \frac{q_3}{V}$$

$$q_{\text{TOT}} = q_1 + q_2 + q_3 = (C_1 + C_2 + C_3)V$$
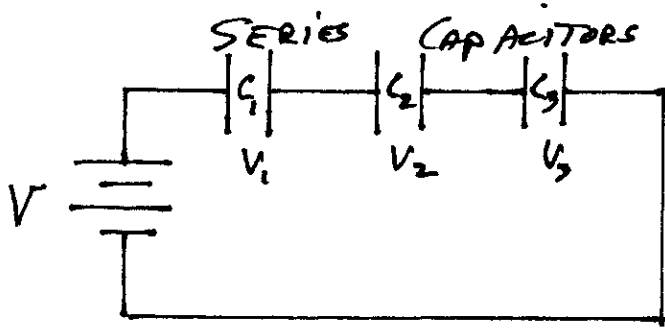
$$C_{\text{eq}} = C_1 + C_2 + C_3 \quad (\text{II CAPACITORS})$$



$$C = \frac{q}{V}$$

$$q_{C1} = q_{C2} = q_{C3}$$

$$V_1 = \frac{q}{C_1} \quad V_2 = \frac{q}{C_2} \quad V_3 = \frac{q}{C_3}$$

$$V = V_1 + V_2 + V_3 = q \left(\frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} \right) = \frac{q}{C_{eq}}$$

$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} \quad (\text{SERIES CAPACITORS})$$

$$C_{eq} = \frac{C_1 \times C_2}{C_1 + C_2} \quad (\text{FOR 2 CAPACITORS IN SERIES})$$

EXAMPLE II

A $33 \mu\text{f}$ CAPACITOR & A $47 \mu\text{f}$ CAPACITOR ARE CONNECTED IN SERIES FIND C_{eq}


$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} = \frac{1}{33} + \frac{1}{47} = .0303 + .0213 = .0516$$

$$C_{eq} = \frac{1}{.0516} = 19.4 \times 10^{-6}$$

(NOTE - I ALWAYS LEAVE OUT THE 10^{-6} UNTIL THE VERY END)

10μf CAPACITOR CIRCUITS

V-3

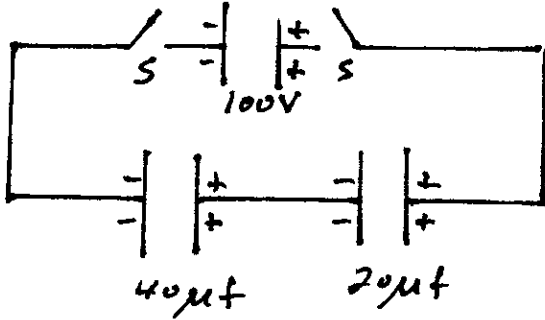

Loop EQUATION

$$V_{10} - V_{20} - V_{40} = 0$$

$$V_{10} = V_{20} + V_{40}$$

FIND THE VOLTAGE ACROSS EACH CAPACITOR WHEN THE SWITCHES ARE CLOSED

$$V_{10} = V_{20} + V_{40} \quad 10^{-3} = q_{\text{TOTAL}} = q_{10} + q_{20} \quad (\text{CHARGE ON } C_{40} \text{ IS NOT NEW BUT IS A REALIGNMENT})$$

$$\frac{q_{10}}{10\mu\text{f}} = \frac{q_{20}}{20\mu\text{f}} + \frac{q_{40}}{40\mu\text{f}} = \frac{q_{20}}{20\mu\text{f}} + \frac{q_{20}}{40\mu\text{f}} \quad \text{SINCE } q_{20} = q_{40}$$

$$\frac{q_{10}}{10} = q_{20} \left(\frac{1}{20} + \frac{1}{40} \right) = q_{20} \left(\frac{40+20}{40 \times 20} \right) = 0.075 q_{20}$$

$$q_{10} = 0.75 q_{20}$$

FROM THE CHARGE EQUATION

$$10^{-3} = 0.75 q_{20} + q_{20} = 1.75 q_{20}$$

$$q_{20} = 0.00057 \text{ C}$$

$$q_{10} = 0.75 q_{20} = 0.75 (0.00057) = 0.000428$$


$$q_{\text{TOTAL}} = q_{10} + q_{20} = 0.000428 + 0.000571 = 9.99 \times 10^{-3} \approx 10 \times 10^{-3}$$

$$V_{20} = \frac{q_{20}}{C_{20}} = \frac{0.000571}{20 \times 10^{-6}} = 28.5 \text{ V}$$

$$V_{40} = \frac{q_{40} (= q_{20})}{C_{40}} = \frac{0.000571}{40 \times 10^{-6}} = 14.25 \text{ V}$$

$$V_{10} = \frac{q_{10}}{C_{10}} = \frac{0.000428}{10 \times 10^{-6}} = 42.8 \text{ V}$$

ENERGY STORED IN A CAPACITOR

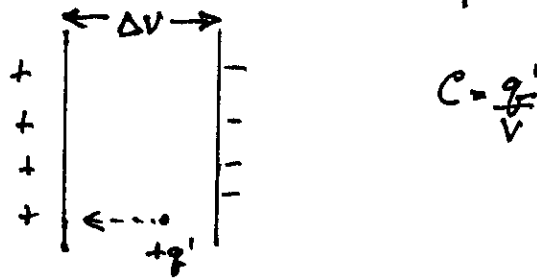


TO MOVE AN INCREMENT OF CHARGE $+dq'$ FROM THE - PLATE TO THE + PLATE REQUIRES WORK dW

$$W_{TOT} = \int dW = \int V dq' = \int \frac{q'}{C} dq' = \frac{q^2}{2C}$$


ENERGY REQUIRED $U = \frac{q^2}{2C} = \frac{1}{2} CV^2 = \frac{1}{2} qV$

CAPACITORS WITH DIELECTRICS

THE CAPACITY OF A CAPACITOR TO STORE CHARGE MAY BE INCREASED BY INSERTING A NON CONDUCTING MATH BETWEEN THE PLATES

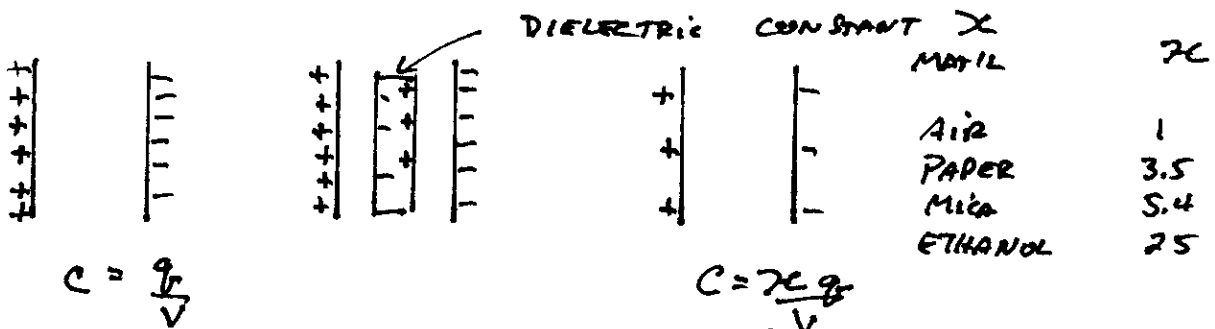

EXAMPLE III

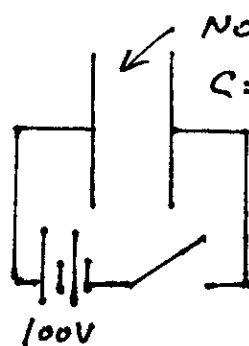

$q_{ON THE PLATES} = C \cdot V = 10 \times 10^{-6} (100) = 10^{-3} C$

NOW INSERT A DIELECTRIC

WITH $\epsilon = 3$

$C' = \epsilon C$

$q' = VC' = VC\epsilon = 100(10 \times 10^{-6})(3) = 3 \times 10^{-3} C$

SO THE CHARGE HAS TRIPLED

REMOVING THE BATTERY & ϵ $V = \frac{q'}{C} = \frac{3 \times 10^{-3}}{10 \times 10^{-6}} = 300V$