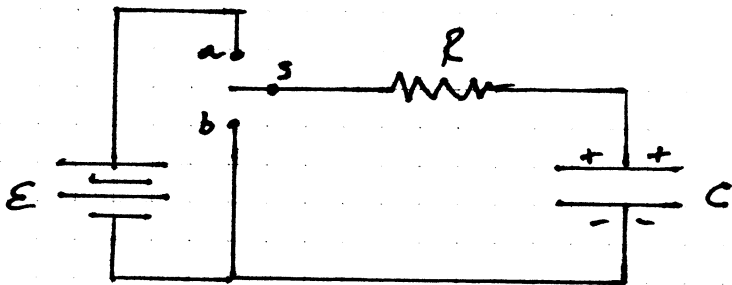


RC CIRCUITS

VIII - 1



$$V_c = \frac{q}{C} \Rightarrow q_{cap} = EC$$

FIRST WE CLOSE THE SWITCH TO 'a' TO CHARGE THE CAPACITOR.

THE CHARGING PROCESS IS GOVERNED BY THE LOOP EQ.

$$E - iR - \frac{q}{C} = 0 \quad \text{BUT } i = \frac{dq}{dt}$$


$$R \frac{dq}{dt} + \frac{q}{C} = E$$

WITH THE INITIAL CONDITION THAT AT $t=0$ $q=0$

SO THE SOLUTION IS

$$q = CE(1 - e^{-t/RC}) \quad \text{AT } t=0 \quad q=0$$

$$\text{AT } t=\infty \quad q=CE$$

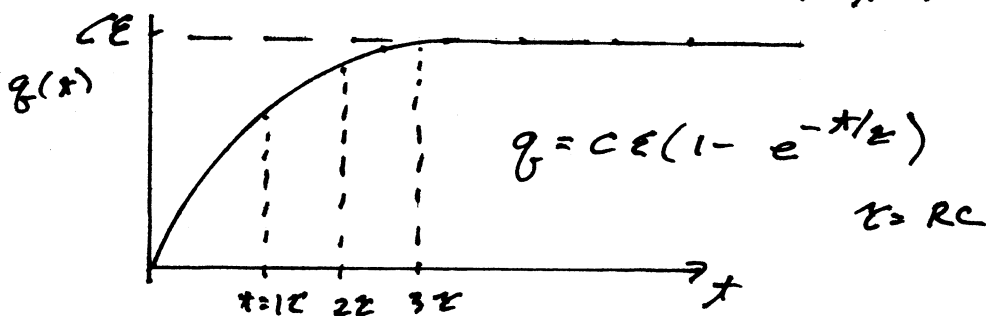

$$t = \tau \quad \left(1 - \frac{1}{e}\right) = 1 - .367 = 63\% \quad q = .63 CE$$

$$t = 2\tau \quad \left(1 - \frac{1}{e^2}\right) = 1 - \frac{1}{7.38} = 86\% \quad q = .86 CE$$


$$t = 3\tau \quad \left(1 - \frac{1}{e^3}\right) = 1 - \frac{1}{20} = 95\% \quad q = .95 CE$$

$$t = 4\tau \quad \left(1 - \frac{1}{e^4}\right) = 1 - \frac{1}{55} = 98\% \quad q = .98 CE$$

VOLTAGE ACROSS THE CAPACITOR DURING CHARGING IS

$$V_c = \frac{q}{C} = E(1 - e^{-t/RC})$$
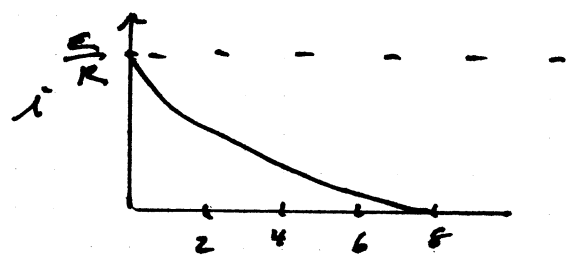
$$i = \frac{dq}{dt} = \frac{E}{R} e^{-t/RC}$$




UNITS OF THE TIME CONSTANT

$$RC \Rightarrow \left[\frac{\text{VOLTS}}{\text{AMP}} \right] \left[\frac{\text{COUL}}{\text{VOLT}} \right]$$

$$= \frac{\text{COUL}}{\text{COUL/SEC}} \Rightarrow \text{SEC}$$

$$R = \frac{V}{I} \quad C = \frac{Q}{V}$$

DISCHARGING A CAPACITOR

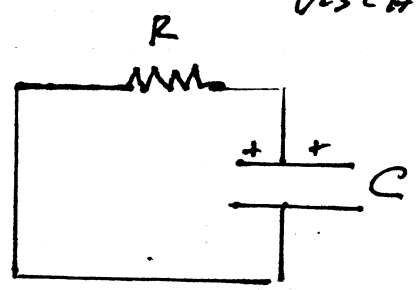


Loop EQUATION YIELDS

$$R \frac{dq}{dt} + \frac{q}{C} = 0$$


YIELDING A SOLUTION

$$q = q_0 e^{-t/RC}$$

WHERE AT $t=0$ $q=q_0$

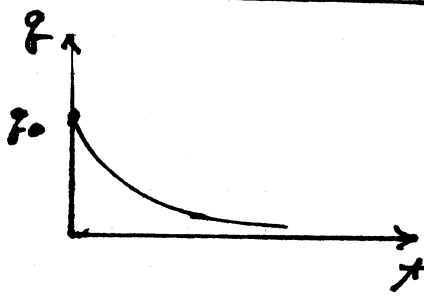

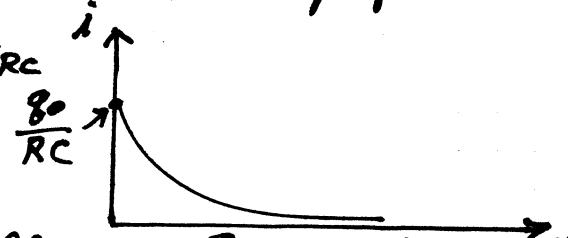
$$i = \frac{dq}{dt} = - \left(\frac{q_0}{RC} \right) e^{-t/RC}$$



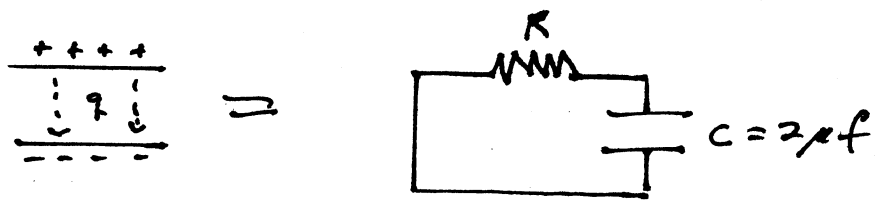EXAMPLE I A CAPACITOR LEAKS CHARGE SUCH THAT

$V_0 \Rightarrow V_0/4$ in SEC. WHAT IS THE EQUIVALENT RESISTANCE BETWEEN THE PLATES



$$V = V_0 e^{-t/2} \quad \tau = RC$$

$$\ln V = \ln V_0 + \frac{-t}{\tau}$$

MULTIPLY THROUGH BY -1

$$-\ln V = -\ln V_0 + \frac{t}{\tau}$$

$$\ln V_0 - \ln V = t/\tau$$

$$\ln\left(\frac{V_0}{V}\right) = \frac{t}{\tau} = \frac{t}{RC}$$

$$R = \frac{t}{C \ln(V_0/V)} = \frac{2}{2 \times 10^{-6} \ln(4/1)} = \frac{2}{2 \times 10^{-6} (1.386)} = 0.722 \times 10^6 = 0.722 \text{ M}\Omega$$

EXAMPLE II

HOW MANY TIME CONSTANTS MUST ELAPSE FOR AN INITIALLY UNCHARGED CAPACITOR IN AN RC CIRCUIT TO BE CHARGED TO A 99% VALUE

$$q = CE(1 - e^{-t/\tau})$$

$$\frac{q}{CE} = 0.99 = 1 - e^{-t/\tau}$$


$$e^{-t/\tau} = 1 - 0.99 = 0.01$$

$$-\frac{t}{\tau} = \ln(0.01) = -4.605$$

$$t = 4.605 (\text{TIME CONSTANTS})$$

EXAMPLE IV

$$C = \frac{q}{V}$$

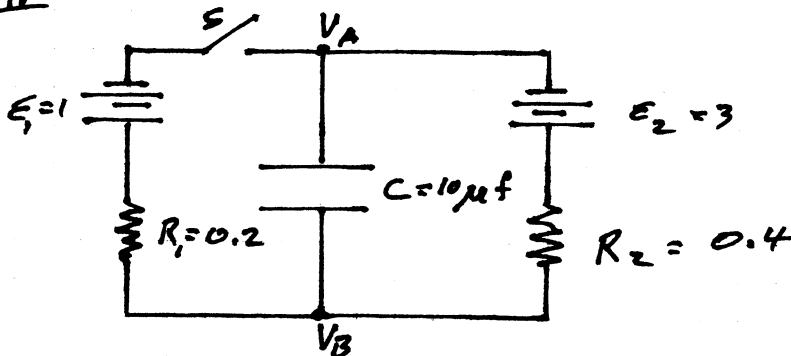

INITIALLY S IS OPEN FOR A LONG TIME. IT IS THEN CLOSED FOR A LONG TIME. BY HOW MUCH DOES q ON THE CAPACITOR CHANGE? (WHEN S IS CLOSED)

$$q_{\text{initial}} = CV = 10 \times 10^{-6} (3) = 3 \times 10^{-5} \text{ C}$$

AFTER A LONG TIME THE CURRENT i IN THE RIGHT HAND LOOP IS ZERO SO $V_{\text{CAP}} = E_{\text{BATTERY}} = 3$

NOW WHEN S IS CLOSED FOR A LONG TIME FOR THE OUTER LOOP

$$+3 - 0.4i - 0.2i - 1 = 0$$

$$i = \frac{2}{0.6} = 3.33 \text{ A}$$

NOW WE FIND THE VOLTAGE ACROSS THE CAPACITOR

$$V_A + 3 - 0.4(3.33) = V_B$$

$$V_B - V_A = 3 - \frac{0.4(3.33)}{1.33} = 1.67 \text{ VOLTS}$$

$$q_{\text{final}} = C(V_B - V_A) = 10 \times 10^{-6} (1.67) = 1.67 \times 10^{-5} \text{ C}$$


ACROSS THE CAPACITOR

$$q_f - q_i = 1.67 \times 10^{-5} - 3 \times 10^{-5} = -1.33 \times 10^{-5} \text{ C}$$

THE CHARGE HAS DECREASED BY $1.33 \times 10^{-5} \text{ C}$

EXAMPLE V

VIII-5

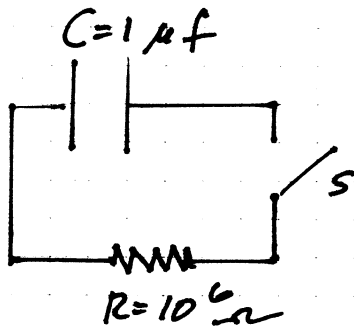

$$U_{cap} = \frac{1}{2} \text{ JOULE}$$

a) find the initial charge on the capacitor

$$U_{cap} = \frac{1}{2} = \frac{q^2}{2C} \quad q_i = \sqrt{\frac{1}{2}(2)(1 \times 10^{-6})} = 1 \times 10^{-3} \text{ C}$$

b) WHAT IS THE CURRENT THRU THE RESISTOR

$$i = -\frac{dq}{dt} = \frac{q_0}{\tau} (e^{-t/\tau})$$

$$\tau = RC = 10^6 (1 \times 10^{-6}) = 1$$

$$i = \frac{1 \times 10^{-3}}{1} e^{-0/1} = 1 \times 10^{-3} \text{ A}$$

c) DETERMINE $V_C(x)$ & $V_R(x)$

$$V_C = \frac{q_0}{C} e^{-t/\tau} = \frac{1 \times 10^{-3}}{1 \times 10^{-6}} e^{-t/1.0} = 1 \times 10^3 e^{-t}$$

$$V_R = \frac{q_0 R}{\tau} = \frac{1 \times 10^{-3} (10^6)}{1} e^{-t/(1.0)} = 1 \times 10^3 e^{-t}$$