
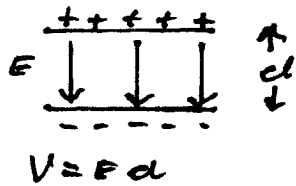


INDUCTANCE

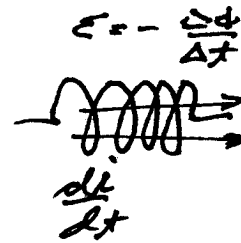


$V = iR$



$L = \frac{N\Phi}{i}$

$[L] = \frac{[\Phi]}{[i]} = \frac{T \cdot m^2}{Amp} = 1 \text{ HENRY}$

SOLENOID

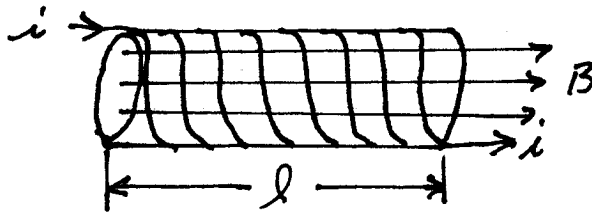

$B = \mu_0 n i$


$L = \frac{N\Phi}{i} = \frac{(n\ell)(BA)}{i} = \frac{n\ell(\mu_0 i n)A}{i} = \mu_0 n^2 \ell A$

$\frac{L}{\ell} = \mu_0 n^2 A$ INDUCTANCE / LENGTH (H/m)

EXAMPLE I GIVEN A SOLENOID 20 CM LONG WITH A 5 CM RADIUS & 1000 TURNS FIND

$L = \mu_0 n^2 \ell A = (1.26 \times 10^{-6}) \left(\frac{1000}{0.2} \right)^2 (0.2) \underbrace{(0.05)^2}_{0.0025} \pi = 49 \text{ mH}$


i INCREASING

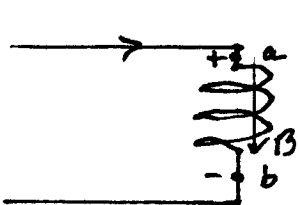

$V_a > V_b$
 $\uparrow \epsilon_L = -N \frac{\Delta\Phi}{\Delta t}$

VOLTAGE OPPOSES THE CURRENT INCREASE

i DECREASING

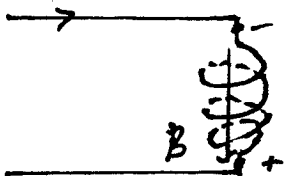

$\downarrow \epsilon_L = -N \frac{\Delta\Phi}{\Delta t}$

VOLTAGE OPPOSES THE CURRENT DECREASE


$$E_L = -N \frac{d\phi}{dt} = -\frac{d}{dt}(N\phi) \quad \text{BUT } N\phi = Li$$

$$E_L = -\frac{d}{dt}(Li) = -L \frac{di}{dt}$$


$$E_L = -L \frac{di}{dt}$$

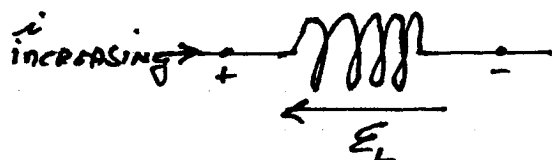EXAMPLE II i GOES FROM 0 \rightarrow 1 AMP IN 0.1 SEC. FIND THE INDUCED VOLTAGE ACROSS A 50 mH INDUCTOR

$$E_L = -L \frac{di}{dt} = -L \frac{\Delta i}{\Delta t} = -(0.05) \left(\frac{1-0}{0.1} \right) = -0.5 \text{ VOLTS}$$



RL CIRCUITS

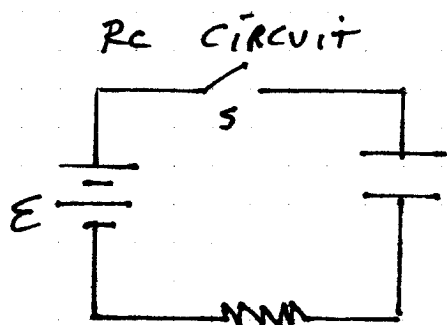


$$E_0 - R \frac{dq}{dt} - \frac{q}{C} = 0$$

$$V_c = V_0 (1 - e^{-t/\tau}) \quad \tau = RC$$

$$q_c = q_0 (1 - e^{-t/\tau})$$

$$i = \frac{E}{R} e^{-t/\tau}$$

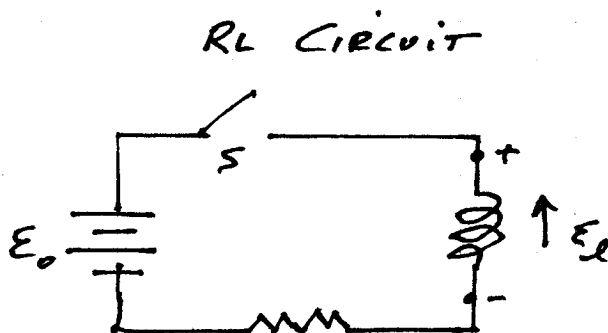




WHEN S IS CLOSED AT $t=0$

$$E_0 - iR - L \frac{di}{dt} = 0$$


$$i = \frac{E_0}{R} (1 - e^{-t/\tau}) \quad \tau = \frac{L}{R}$$

$$V_L = E_0 e^{-t/\tau}$$

LR CIRCUIT

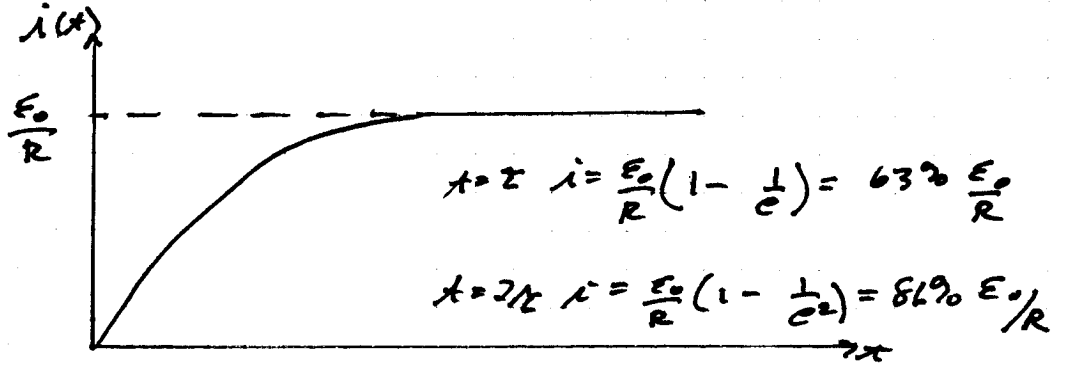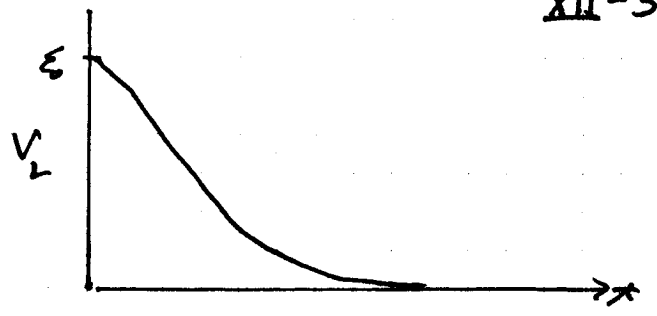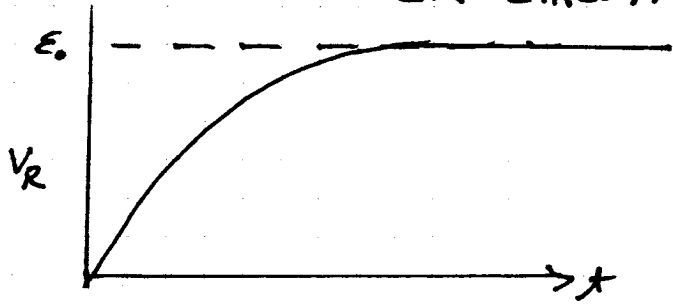

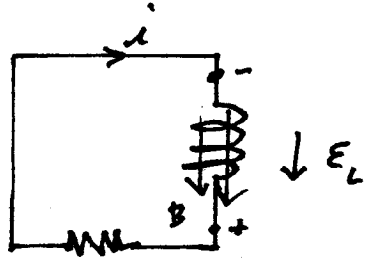
NEXT HAVING REACHED EQUILIB THE BATTERY IS NOW REMOVED FROM THE CIRCUIT



$$iR + L \frac{di}{dt} = 0$$

$$i = i_0 e^{-t/\tau}$$

$$i_0 = \frac{E_0}{R}$$

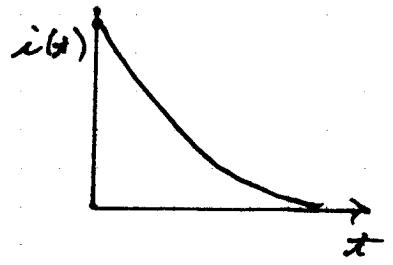

$t = \tau \quad i = 37\% E_0/R$
 $t = 2\tau \quad i = 14\% E_0/R$

ENERGY STORED IN AN INDUCTOR

FOR CAPACITORS $U_C = \frac{q^2}{2C} = \frac{CV^2}{2}$ (JOULES)


FOR INDUCTORS $U_B = \frac{1}{2} Li^2$ (JOULES)

MAGNETIC ENERGY DENSITY

$$u_B = \frac{B^2}{2\mu_0} \quad (\text{Joules } m^3)$$

EXAMPLE III

$L = 6.3 \mu H$

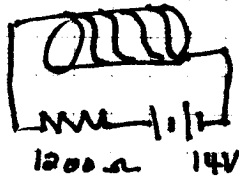

a) How much time is req'd for the current thru the resistor to reach 80% of its final value

$$i = \frac{E_0}{R} (1 - e^{-t/\tau_L})$$

$$\tau_L = \frac{L}{R} = \frac{6.3 \times 10^{-6}}{1.2 \times 10^3} = 5.25 \times 10^{-9}$$

$$\frac{E_0}{R} = \frac{14}{1200} = 0.117 = i_c$$

$$\frac{i}{i_c} = 0.80 = 1 - e^{-t/\tau_L}$$

$$e^{-t/\tau_L} = 1 - 0.8 = 0.2$$

$$\ln(e^{-t/\tau_L}) = -\frac{t}{\tau_L} = \ln(0.2) = -1.609$$

$$t = -\tau_L (-1.609) = 8.4 \times 10^{-9} \text{ SEC}$$

b) What is the current thru the resistor at $t = \tau$

$$i = \frac{E_0}{R} (1 - e^{-t/\tau_L}) = \frac{E_0}{R} (1 - e^{-1}) = \frac{E_0}{R} (1 - \frac{1}{2.718})$$

$$i = 0.632 \left(\frac{E_0}{R} \right)$$

$$= 0.632 \left(\frac{14}{1200} \right) = 0.632 (0.117) = 0.739 \text{ Amps}$$