
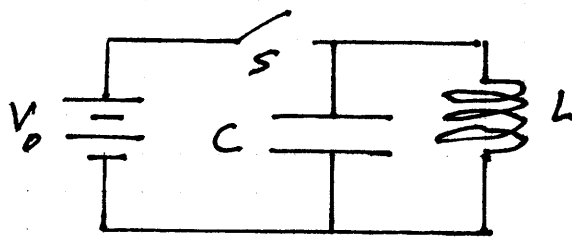


## LC CIRCUITS

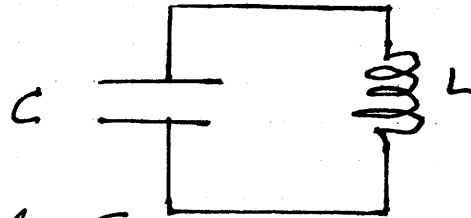

FIRST WE CHARGE THE CAPACITOR SO  $q_0 = CV_0$  THEN WE DISCONNECT THE BATTERY



$$V - E_L = 0$$

$$\frac{q}{C} + L \frac{di}{dt} = 0 \quad i = \frac{dq}{dt}$$

$$q = q_0 \cos \omega t$$

$$q_0 \cos \omega t - L \omega^2 q_0 \cos \omega t = 0$$




$$1 - LC \omega^2 = 0$$

$$\omega = \frac{1}{\sqrt{LC}} \quad f = \frac{1}{2\pi \sqrt{LC}}$$

EXAMPLE I A  $4 \mu\text{F}$  CAPACITOR IS CHARGED TO 5V & THEN DISCHARGED INTO A 0.3H INDUCTOR

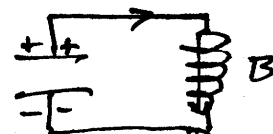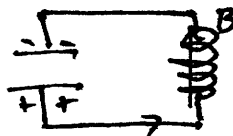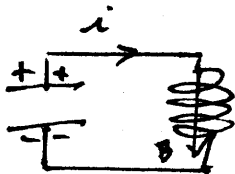a) WHAT IS THE FREQUENCY OF OSCILLATION



$$f = \frac{1}{2\pi \sqrt{LC}} = \frac{1}{6.28 \sqrt{(0.3)(4 \times 10^{-6})}} = 145 \text{ Hz}$$



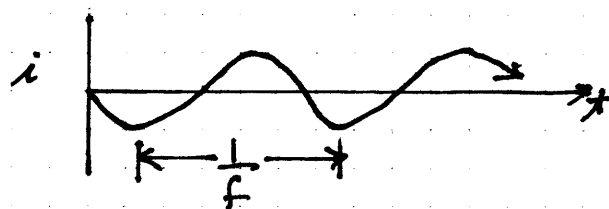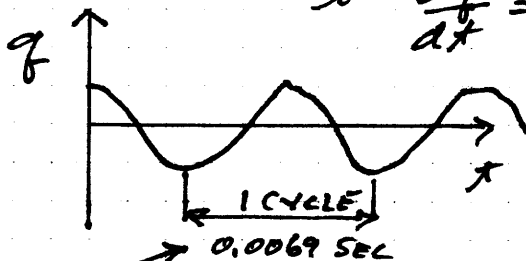b) WHAT IS THE MAX CURRENT FLOWING IN THE CIRCUIT

$$q = q_0 \cos \omega t \quad q_0 = CV_0 = 4 \times 10^{-6} (5) = 2 \times 10^{-5}$$

$$i = \frac{dq}{dt} = -q_0 \omega \sin \omega t$$



$$f = 145$$

$$i_{\text{MAX}} = \underbrace{q_0}_{\text{AMPLITUDE}} \omega = q_0 2\pi f = 2 \times 10^{-5} (6.28) 145 = 18.2 \text{ mA}$$

c) AT WHAT TIME DOES THE MINIMUM CURRENT OCCUR



$$1 \text{ CYCLE} = \text{PERIOD } T = \frac{1}{f}$$

$$\text{TIME FOR } I_{\text{MIN}} = \frac{T}{4} = \frac{1}{4f} = \frac{1}{4(145)} = 1.72 \times 10^{-3} = 1.72 \text{ mSEC}$$


### AC CIRCUITS

APPLIED VOLTAGE VARIES WITH TIME

$$E(t) = E_{\text{MAX}} \sin \omega t$$

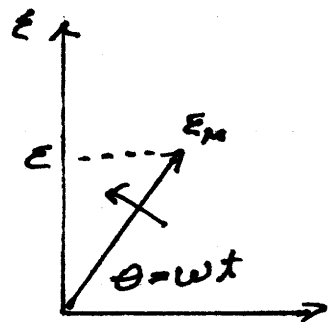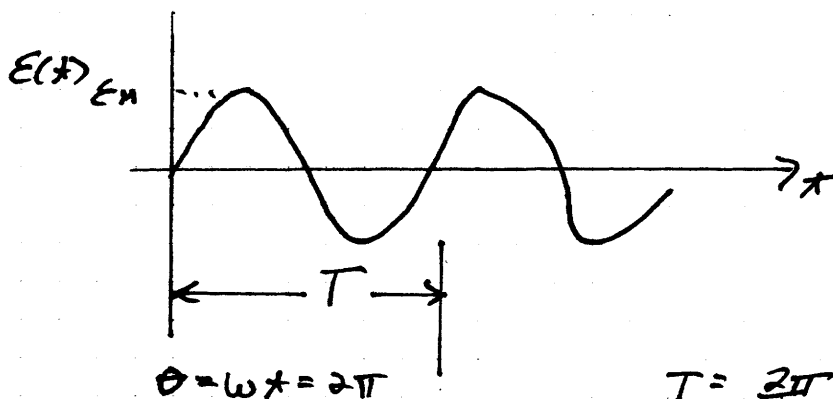

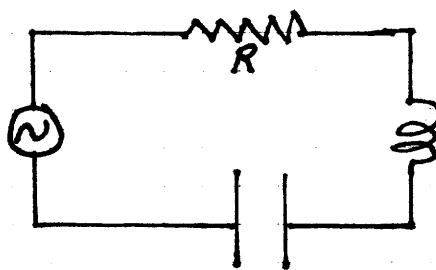
$$T = \frac{2\pi}{\omega} = \frac{1}{f}$$



GEN'L  $i(t) = I_{\max} \sin(\omega t - \phi)$   $\phi \neq \phi'$   
 $v(t) = V_{\max} \sin(\omega t - \phi')$


RESISTIVE LOAD

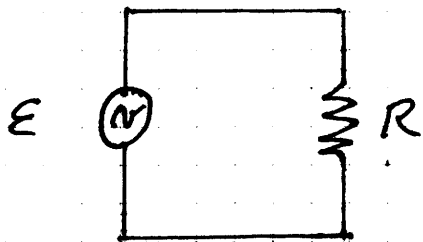

$$v_R = E_m \sin \omega t$$


$$i = \frac{v_R}{R} = \frac{E_m}{R} \sin \omega t$$

$$V_R = IR$$

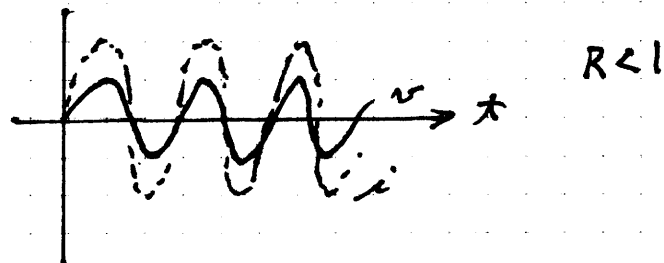

$v_R$  &  $i$  ARE IN PHASE I.E. THE MAX & MIN VALUES <sup>occur</sup> AT THE SAME TIME

PHASOR DIAGRAMS

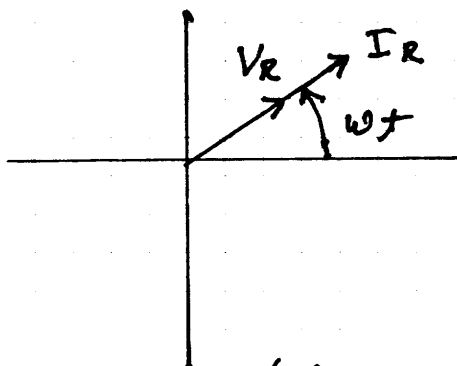


EXAMPLE II FOR  $E_m = 10\text{ V}$  ( $f = 60\text{ Hz}$ ) WHICH IS APPLIED TO A  $20\ \Omega$  RESISTIVE CIRCUIT FIND  $i$  AT  $1/240\text{ Sec}$

$$i = I_{\max} \sin \omega t = \frac{E_m}{R} \sin \omega t$$

$$\omega = 2\pi f = 6.28(\text{low}) = 377\text{ rad/sec}$$

CAPACITIVE LOAD

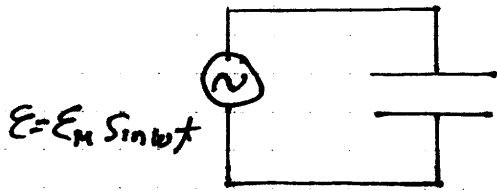

$$E - V_c = 0$$

$$V_c = V_c \sin \omega t$$

$$q_c = C V_c = C V_c \sin \omega t$$

$$i_c = \frac{dq_c}{dt} = \omega C V_c \cos \omega t$$

BUT SINCE  $\cos(\omega t) = \sin(\omega t + \pi/2)$

NOW DEFINE  
CAPACITIVE REACTANCE

$$X_c = \frac{1}{\omega C} \quad [\Omega]$$


$$i_c = \frac{V_c}{X_c} \sin(\omega t + \pi/2) = I_c \sin(\omega t + \pi/2)$$

$$V_c = V_c \sin(\omega t)$$


$$i_c = I_c \sin(\omega t + \pi/2)$$

$i_c$  LEADS  $V_c$

i.e. CURRENT REACHES  
A MAXIMUM VALUE  
BEFORE THE VOLT  
(i.e. TIMEWISE)

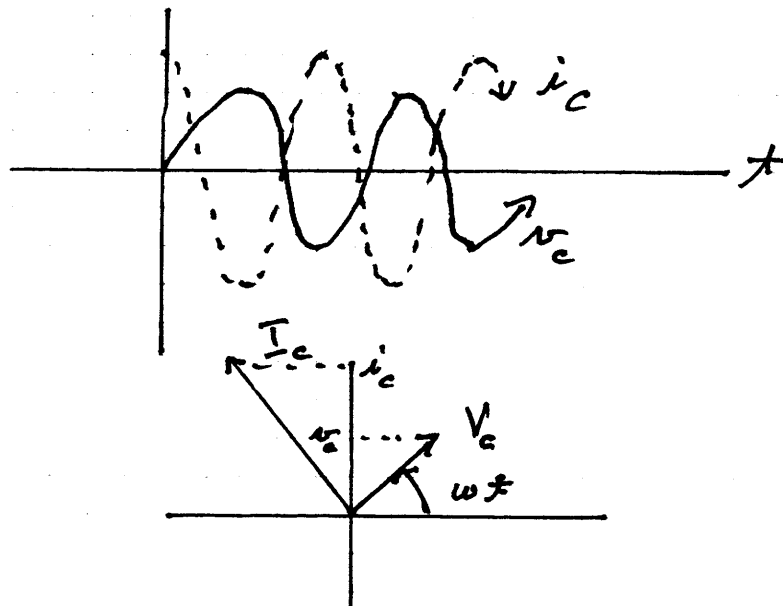

EXAMPLE III

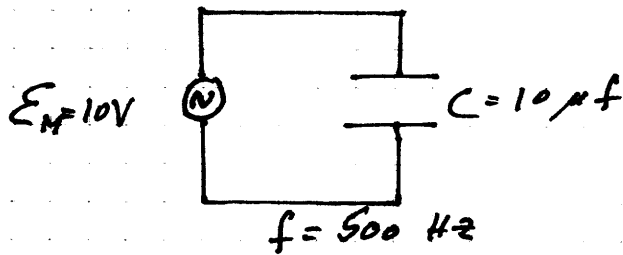

$$\omega = 2\pi f$$

a) FIND THE CAPACITIVE REACTANCE


$$X_C = \frac{1}{\omega C} = \frac{1}{2\pi f C} = \frac{1}{6.28(500)(10 \times 10^{-6})} = 3.2 \times 10^{-2} = 32 \Omega$$

b) DETERMINE THE MAX CURRENT


$$I_C = \frac{V_C}{X_C} = \frac{10}{32} = 0.313 \text{ A}$$

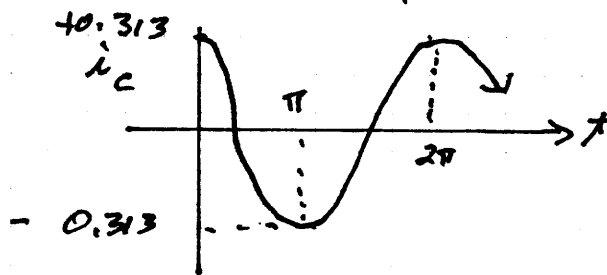c) DETERMINE THE CURRENT AT  $t = 1 \text{ ms}$

$$\begin{aligned} i_c &= I_C \sin(\omega t + \pi/2) \\ &= 0.313 \sin(2\pi f t + \pi/2) \\ &= 0.313 \sin(2\pi(500)(1 \times 10^{-3}) + \pi/2) \\ &\quad (3.14 \text{ RADIANS} = 180^\circ + 90^\circ) \\ &= 0.313 \underbrace{\sin(270^\circ)}_{-1} = -0.313 \text{ Amps} \end{aligned}$$



w/o THE PHASE ANGLE

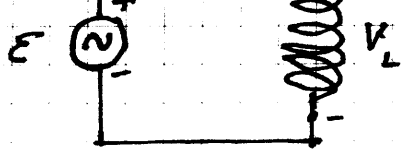

$$+E - V_L = 0$$

$$V_L = V_L \sin \omega t$$

BUT  $V_L = -L \frac{di}{dt}$

$$\int di = -\int \frac{V_L}{L} dt = -\frac{1}{L} \int V_L \sin \omega t dt = -\frac{V_L}{L} \int \sin \omega t dt$$

$$i_L = \frac{V_L}{L\omega} \underbrace{(-\cos \omega t)}_{= \sin(\omega t - \phi) = \sin(\omega t - \frac{\pi}{2})}$$

$$i_L = \frac{V_L}{L\omega} \sin(\omega t - \frac{\pi}{2})$$

$\phi$  IS THE ANGLE

BETWEEN  $i$  &  $V$   
 $\phi = \frac{\pi}{2}$



INDUCTIVE REACTANCE  $X_L = \omega L$

$$i_L = \frac{V_L}{X_L} \sin(\omega t - \frac{\pi}{2})$$


$$V_L = V_L \sin \omega t$$

$i_L$  LAGS  $V_L$

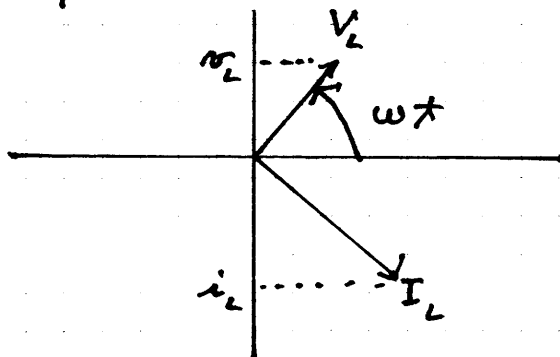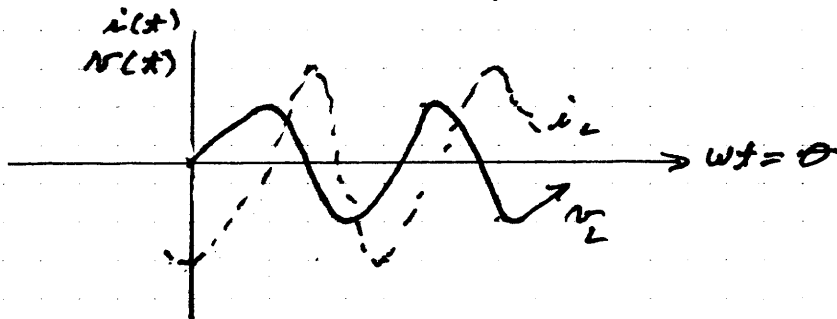i.e. VOLTAGE REACHES MAXIMUM BEFORE THE CURRENT (i.e. TIME)



## EXAMPLE IV

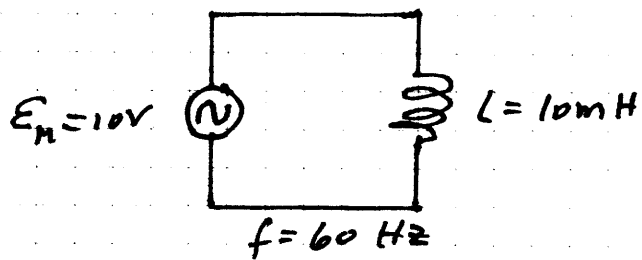

a) find  $X_L = \omega L = 2\pi fL = 2\pi(60)(10 \times 10^{-3}) = 3.77 \Omega$

b) calculate  $I_L$   $I_L = \frac{E_m}{X_L} = \frac{10}{3.77} = 2.65 A$

c) find  $i$  for  $t = \frac{1}{120}$  sec  $\omega t = 2\pi f t = 6.28(60)(\frac{1}{120}) = \pi$

$$i_L = \frac{V_L}{X_L} \sin(\omega t - \pi/2)$$

$$= \frac{10}{3.77} \sin(\underbrace{\pi - \pi/2}_{\pi/2}) = \frac{10}{3.77} \sin(\pi/2) = 2.65 A$$

THE MAX VALUE