

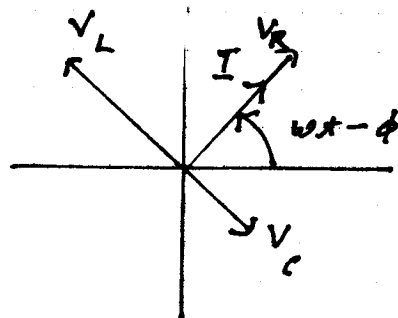
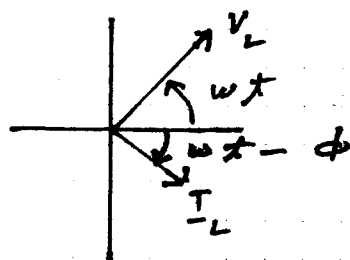
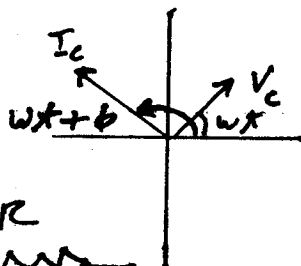


# AC CIRCUITS

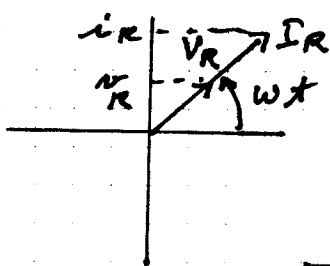

$$E = E_m \sin \omega t$$

$$i = I_m \sin(\omega t - \phi)$$

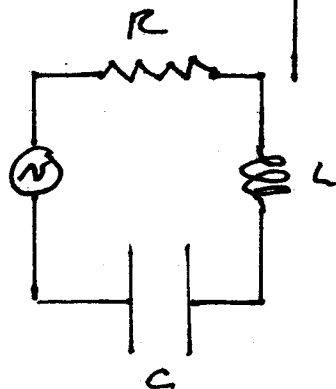

Loop Rule

$$E = V_R + V_L - V_C$$

$$\vec{E}_m = \vec{V}_R + \vec{V}_L - \vec{V}_C$$

OR USING THE PYTHAGOREAN THM

$$E_m^2 = V_R^2 + (V_L - V_C)^2$$

∵ SINCE  $V_R = IR$   $V_L = IX_L$   $V_C = IX_C$

$$E_m^2 = (IR)^2 + (IX_L - IX_C)^2$$


$$I = \frac{E_m}{\sqrt{R^2 + (X_L - X_C)^2}} = \frac{E_m}{Z}$$

IMPEDENCE

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$


INDUCTIVE CIRCUIT

$E_m$  LEADS  $I_{MAX}$

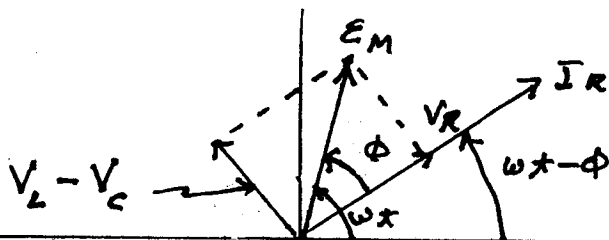

CAPACITIVE CIRCUIT

$I_{MAX}$  LEADS  $E_{MAX}$

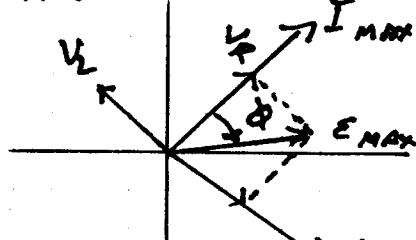


$$\tan \phi = \frac{V_L - V_C}{R} = \frac{IX_L - IX_C}{R} = \frac{X_L - X_C}{R}$$


$$E_{RMS} = \frac{E_{MAX}}{\sqrt{2}}$$

$$I_{RMS} = \frac{I_{MAX}}{\sqrt{2}}$$


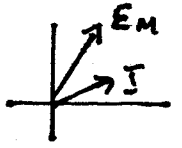
$X_L > X_C$   $\phi > 0$  INDUCTANCE DOMINATES  
 $E_M$  IS AHEAD OF  $I$



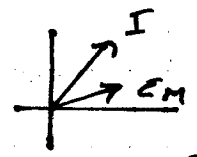$X_C > X_L$   $\phi < 0$  CAPACITANCE DOMINATES  
 $E_M$  IS BEHIND  $I$




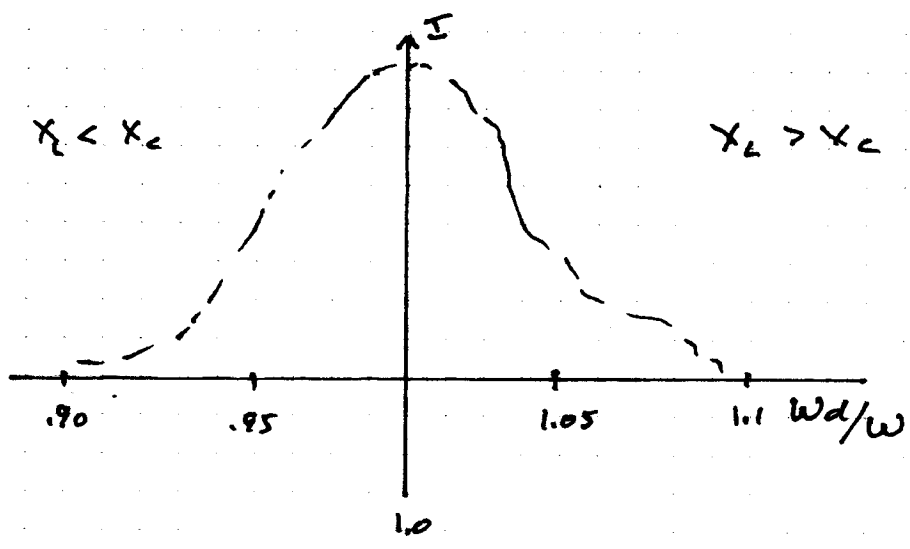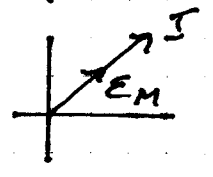$X_L = X_C$   $\phi = 0$  RESONANCE WHICH MEANS  
 MAXIMUM CURRENT



$$\omega = \frac{1}{\sqrt{LC}}$$

TRANSFORMER

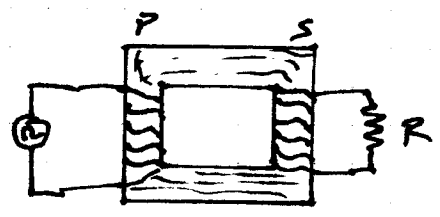

$$V_P = N_P \frac{d\phi}{dt} \quad V_S = N_S \frac{d\phi}{dt}$$

$$\left(\frac{d\phi}{dt}\right)_P = \left(\frac{d\phi}{dt}\right)_S$$

$$\frac{V_P}{N_P} = \frac{V_S}{N_S}$$

$$V_S = V_P \left(\frac{N_S}{N_P}\right)$$

EXAMPLE I  $V_P = 10$   $V_S = 100$   $N_P = 20$   $N_S = \left(\frac{V_S}{V_P}\right) N_P = \frac{100}{10} (20) = 200$

FURTHERMORE IN A TRANSFORMER ENERGY IS CONSERVED

$$\text{POWER}_{\text{IN}} = \text{POWER}_{\text{OUT}}$$

$$V_p I_p = V_s I_s$$

XIV

GIVEN  $I_p = 15 \text{ AMPS}$

$$I_s = \frac{V_p}{V_s} I_p = \frac{10}{100} (15) = 1.5 \text{ AMPS}$$