

PHYS121H + PHYS122-Lecture 12:


Inductance and RLC Circuits

- Final Exam Date/Logistics
- Today: Chap 30:
 - a) Mutual Induction
 - b) Self Induction
 - c). RC circuit
 - d). LC circuit
 - e). RLC circuit

Mutual inductance

- *Mutual inductance:* A changing current in one coil induces a current in a neighboring coil. See Figure 30.1 at the right.
- Follow the discussion of mutual inductance in the text.

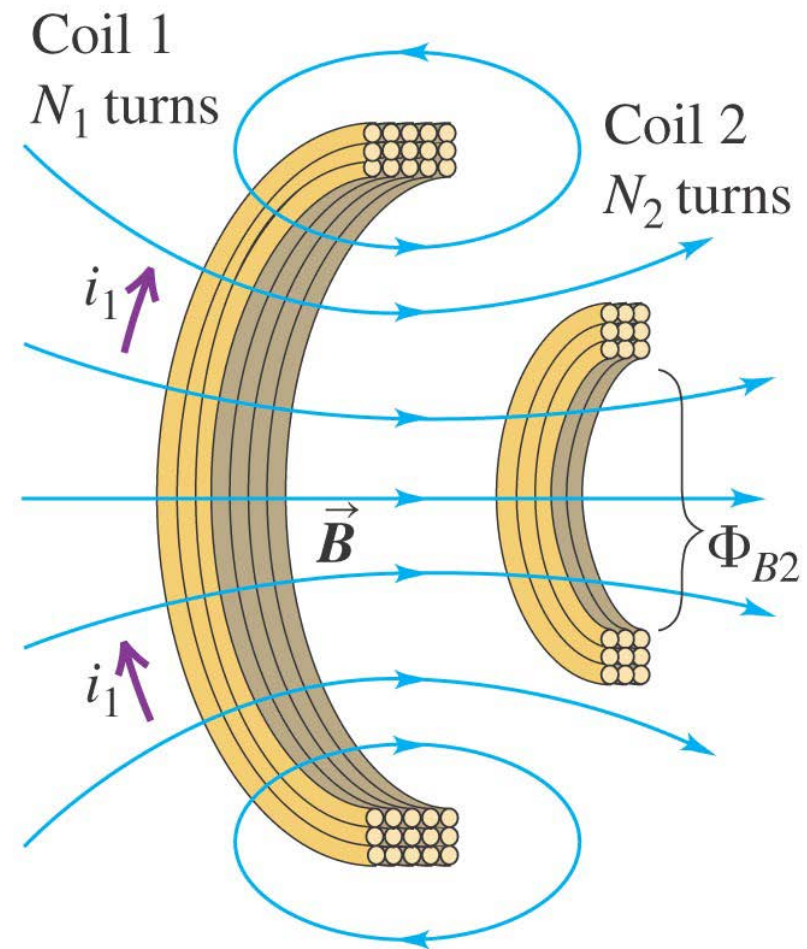
Mutual inductance: If the current in coil 1 is changing, the changing flux through coil 2 induces an emf in coil 2.





Mutual inductance examples

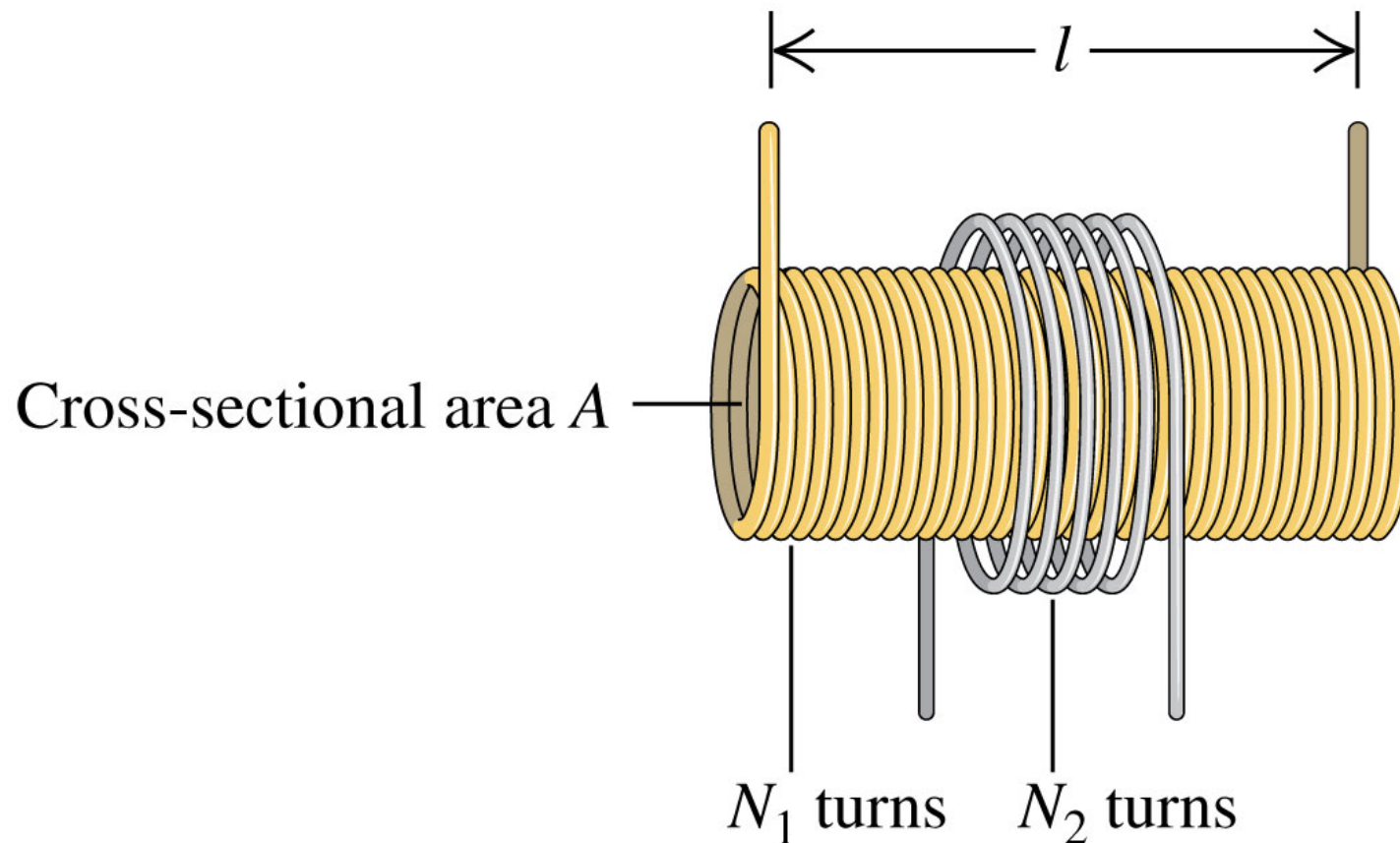- Follow Example 30.1, which shows how to calculate mutual inductance. See Figure 30.3 below.
- Follow Example 30.2, which looks at the induced emf.






Self-inductance

- *Self-inductance*: A varying current in a circuit induces an emf in that same circuit. See Figure 30.4 below.
- Follow the text discussion of self-inductance and inductors.

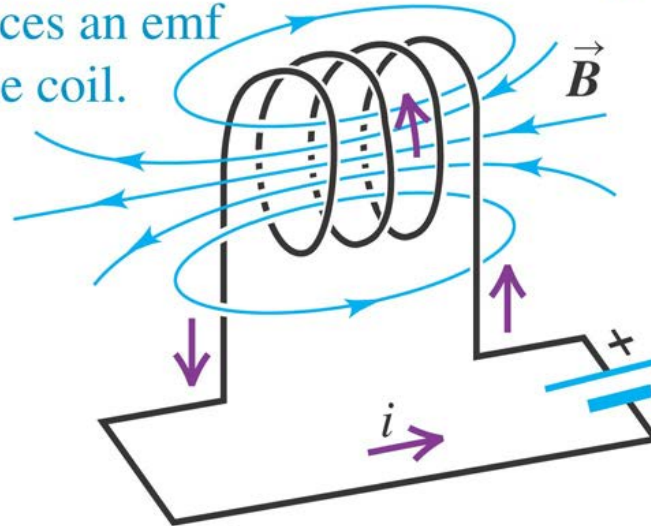
Self-inductance: If the current i in the coil is changing, the changing flux through the coil induces an emf in the coil.





Calculating self-inductance and self-induced emf

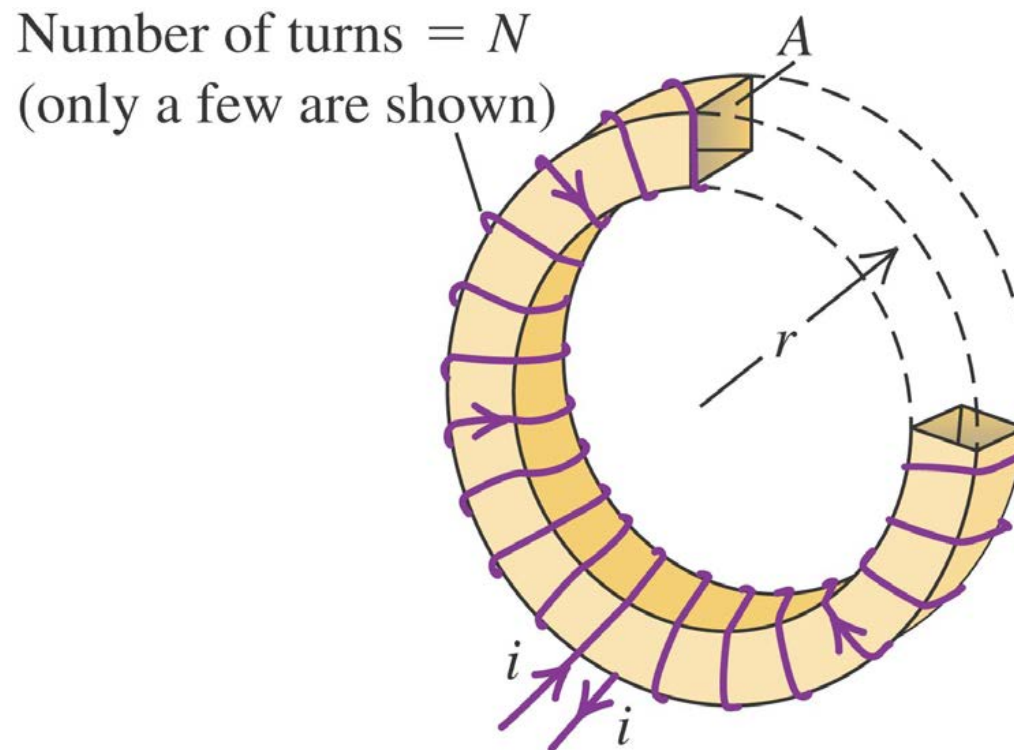- Follow Example 30.3 using Figure 30.8 below.
- Follow Example 30.4.







Potential across an inductor

- The potential across an inductor depends on the rate of change of the current through it.
- Figure 30.6 at the right compares the behavior of the potential across a resistor and an inductor.
- The self-induced emf does *not* oppose current, but opposes a *change* in the current.

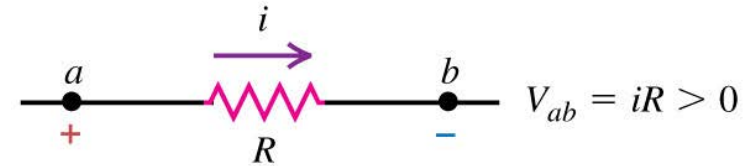
(a) Resistor with current i flowing from a to b : potential drops from a to b .



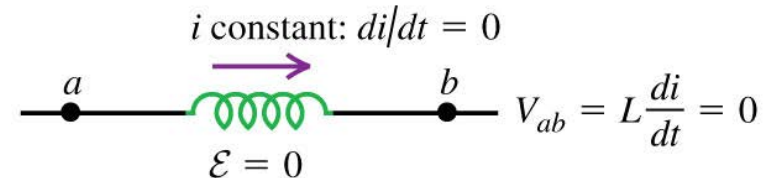
(b) Inductor with *constant* current i flowing from a to b : no potential difference.



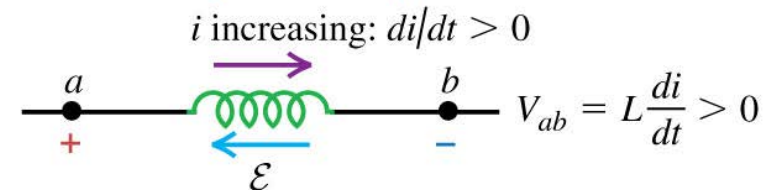(c) Inductor with *increasing* current i flowing from a to b : potential drops from a to b .



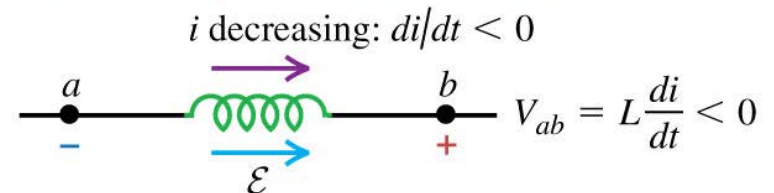(d) Inductor with *decreasing* current i flowing from a to b : potential increases from a to b .







Charging a capacitor

- Read the discussion of charging a capacitor in the text, using Figures 26.20 and 26.21 below.
- The *time constant* is $\tau = RC$.


(a) Capacitor initially uncharged

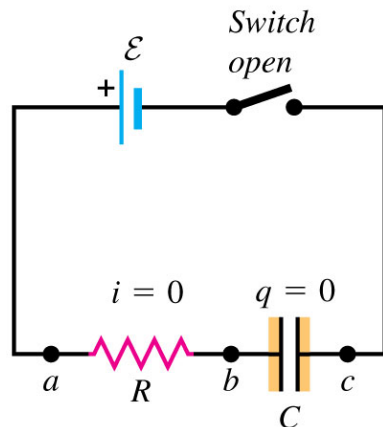


(b) Charging the capacitor

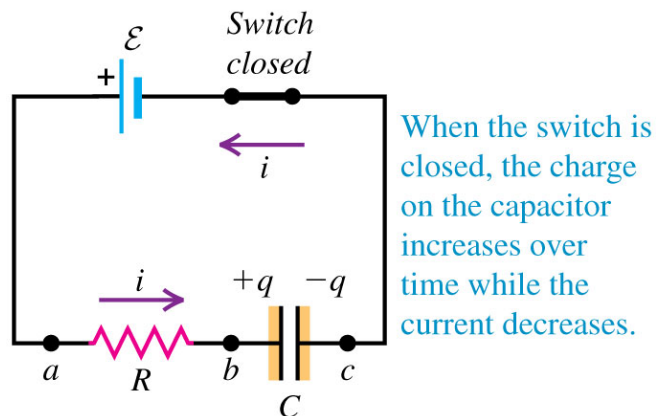

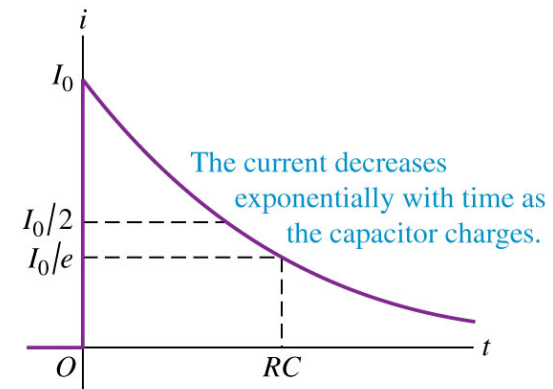(a) Graph of current versus time for a charging capacitor



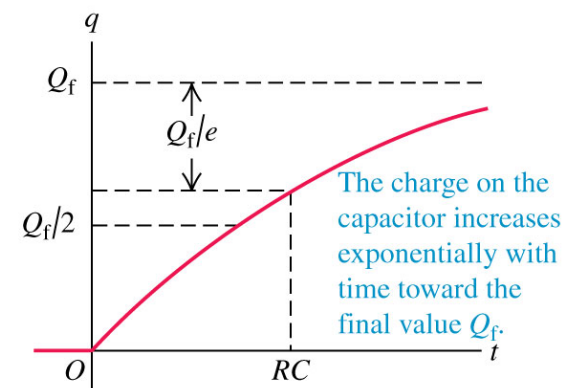
(b) Graph of capacitor charge versus time for a charging capacitor




Discharging a capacitor

- Read the discussion of discharging a capacitor in the text, using Figures 26.22 and 26.23 below.
- Follow Examples 26.12 and 26.13.


(a) Capacitor initially charged

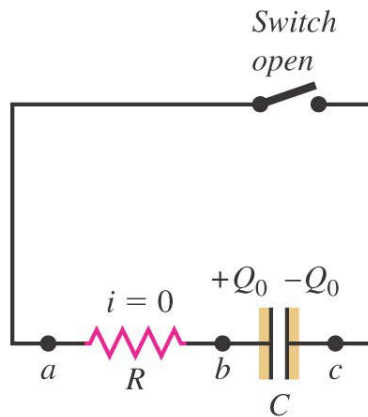


(b) Discharging the capacitor

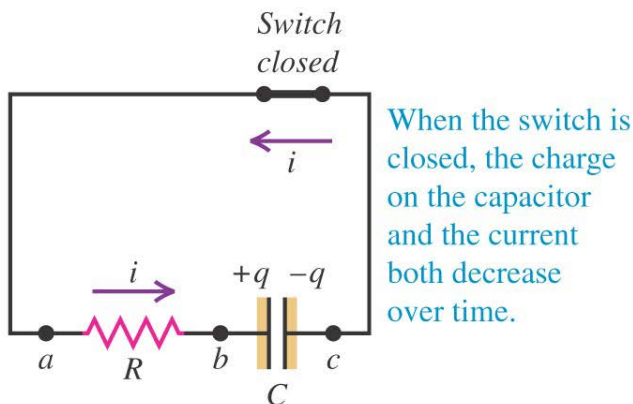

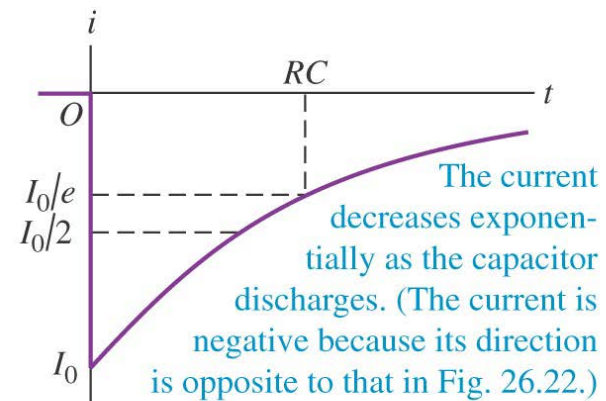(a) Graph of current versus time for a discharging capacitor



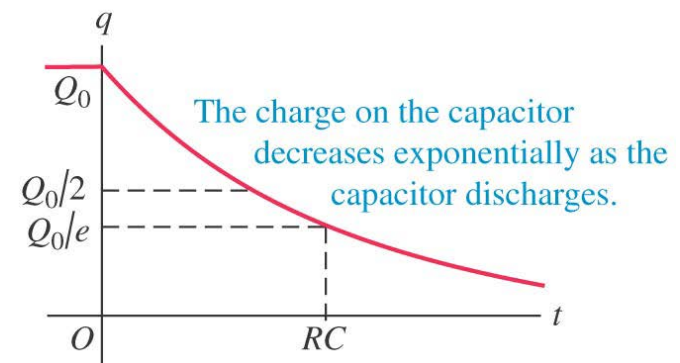(b) Graph of capacitor charge versus time for a discharging capacitor






The R - L circuit

- An R - L circuit contains a resistor and inductor and possibly an emf source.
- Figure 30.11 at the right shows a typical R - L circuit.
- Follow Problem-Solving Strategy 30.1.

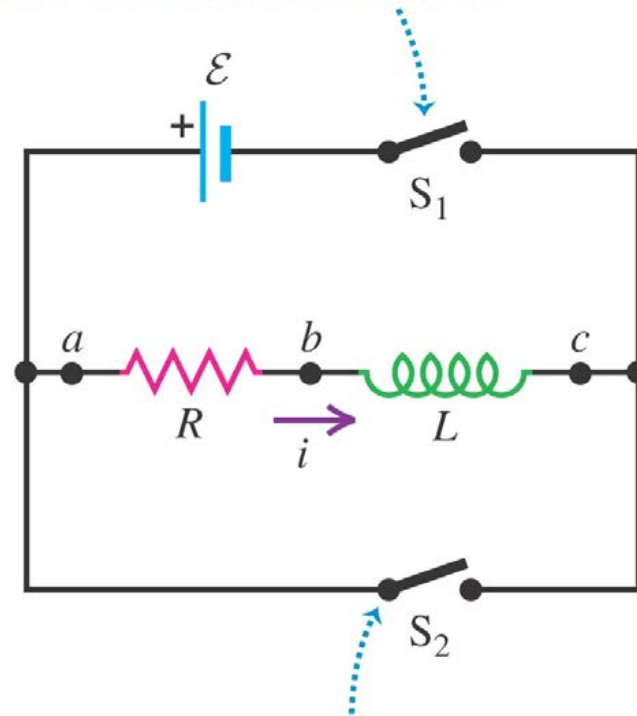
Closing switch S_1 connects the R - L combination in series with a source of emf \mathcal{E} .



Closing switch S_2 while opening switch S_1 disconnects the combination from the source.


Current growth in an R - L circuit

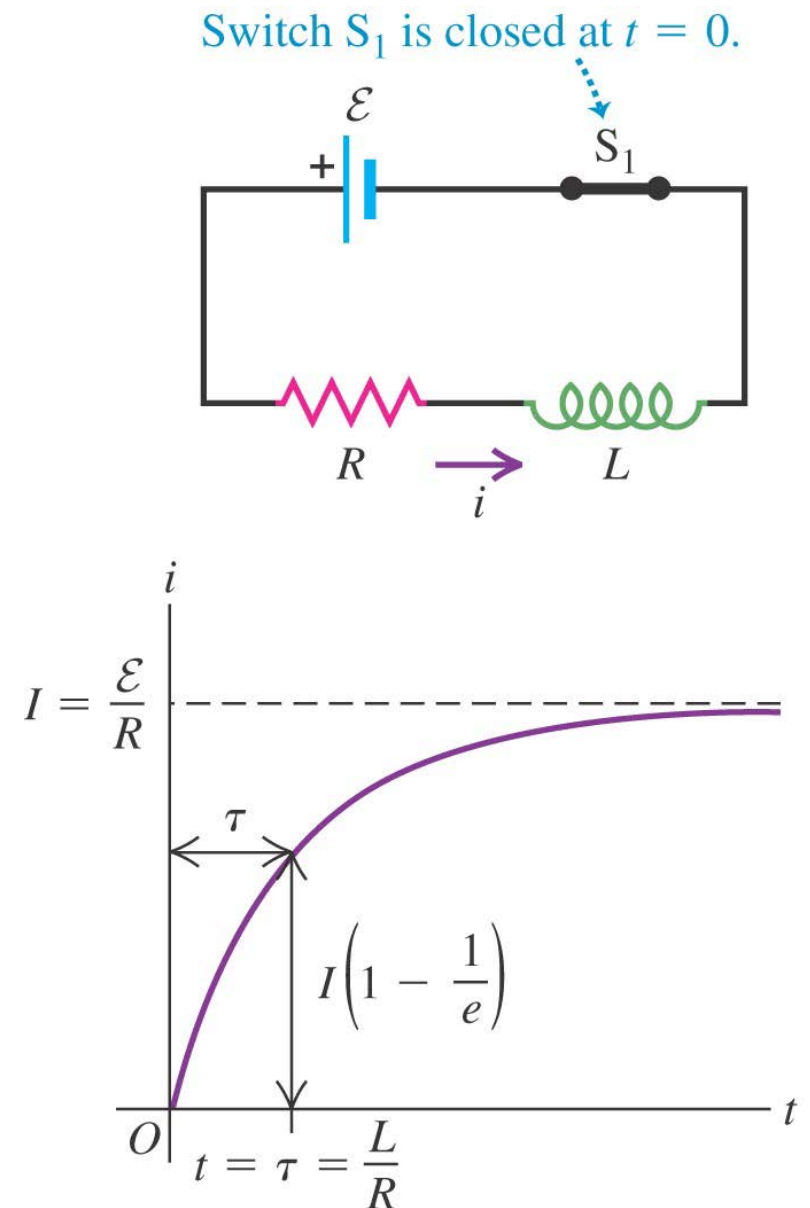- Follow the text analysis of current growth in an R - L circuit.
- The *time constant* for an R - L circuit is $\tau = L/R$.
- Figure 30.12 at the right shows a graph of the current as a function of time in an R - L circuit containing an emf source.
- Follow Example 30.6.




Current decay in an R - L circuit

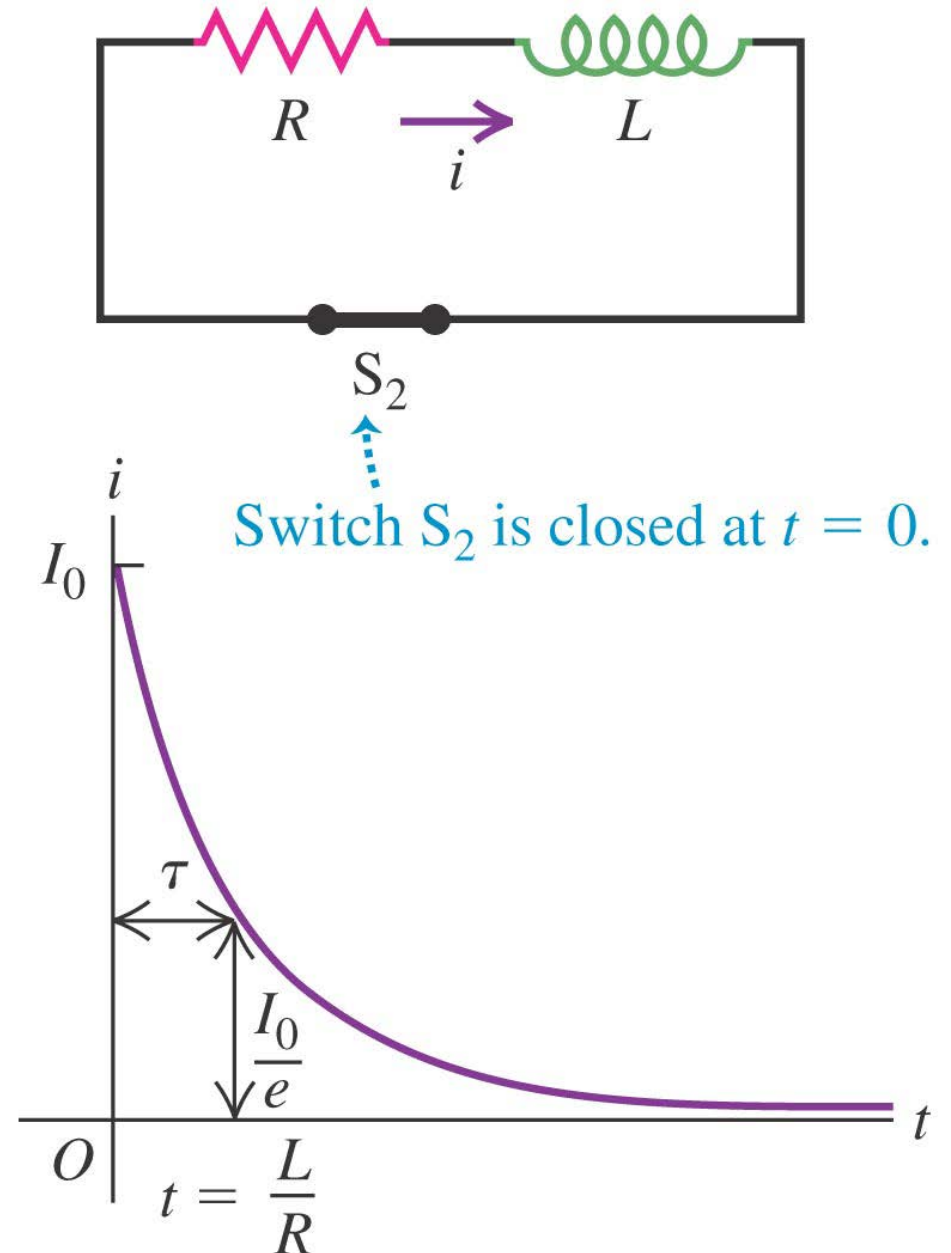- Read the text discussion of current decay in an R - L circuit.
- Figure 30.13 at the right shows a graph of the current versus time.
- Follow Example 30.7.




The *L-C* circuit

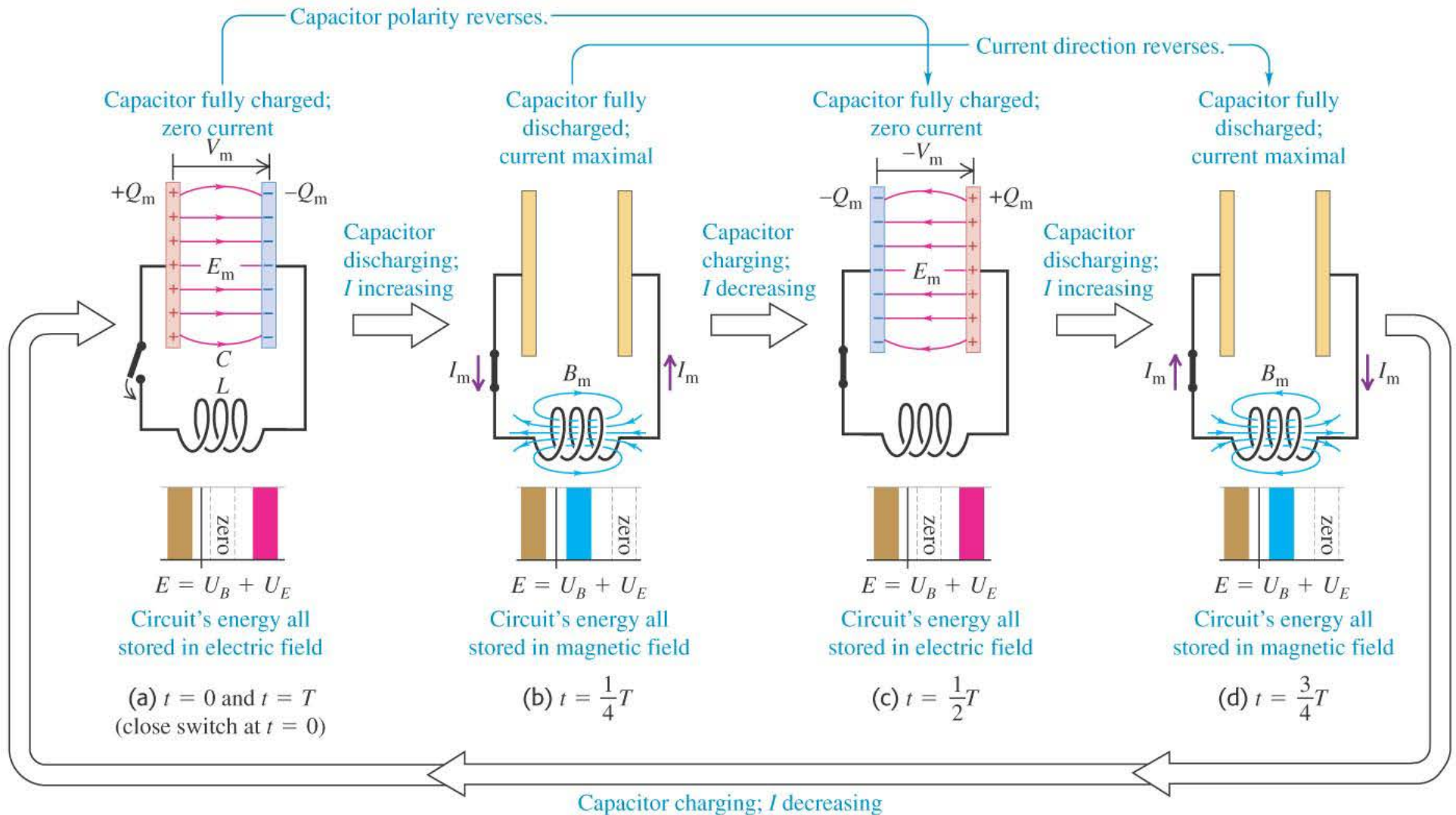- An *L-C circuit* contains an inductor and a capacitor and is an *oscillating circuit*. See Figure 30.14 below.



Electrical oscillations in an L - C circuit

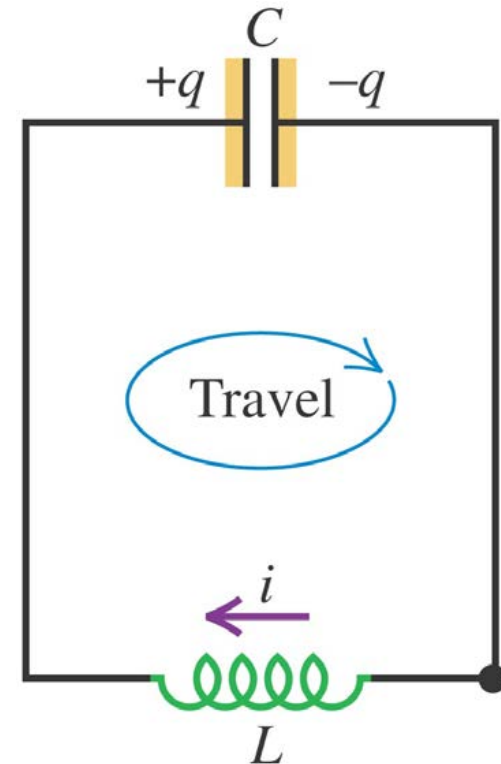- Follow the text analysis of electrical oscillations and energy in an L - C circuit using Figure 30.15 at the right.



Electrical and mechanical oscillations

- Table 30.1 summarizes the analogies between SHM and L - C circuit oscillations.
- Follow Example 30.8.
- Follow Example 30.9.

Table 30.1 Oscillation of a Mass-Spring System Compared with Electrical Oscillation in an L - C Circuit

Mass-Spring System

$$\text{Kinetic energy} = \frac{1}{2}mv_x^2$$

$$\text{Potential energy} = \frac{1}{2}kx^2$$

$$\frac{1}{2}mv_x^2 + \frac{1}{2}kx^2 = \frac{1}{2}kA^2$$

$$v_x = \pm \sqrt{k/m} \sqrt{A^2 - x^2}$$

$$v_x = dx/dt$$

$$\omega = \sqrt{\frac{k}{m}}$$

$$x = A \cos(\omega t + \phi)$$

Inductor-Capacitor Circuit

$$\text{Magnetic energy} = \frac{1}{2}Li^2$$

$$\text{Electric energy} = q^2/2C$$

$$\frac{1}{2}Li^2 + q^2/2C = Q^2/2C$$

$$i = \pm \sqrt{1/LC} \sqrt{Q^2 - q^2}$$

$$i = dq/dt$$


$$\omega = \sqrt{\frac{1}{LC}}$$

$$q = Q \cos(\omega t + \phi)$$


The L - R - C series circuit

- Follow the text analysis of an L - R - C circuit.
- An L - R - C circuit exhibits *damped harmonic motion* if the resistance is not too large. (See graphs in Figure 30.16 at the right.)
- Follow Example 30.10.

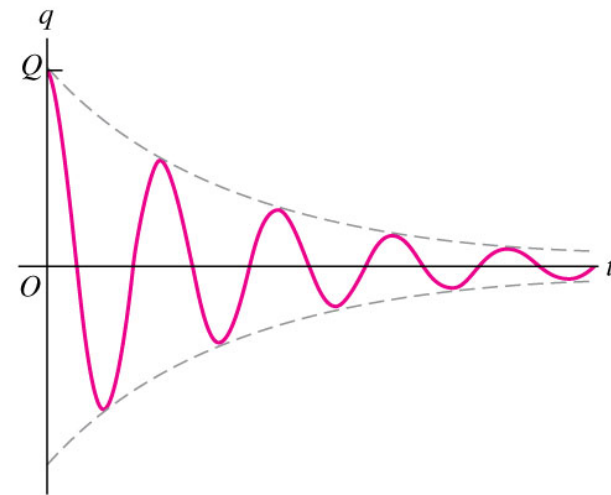
(a) Underdamped circuit (small resistance R)



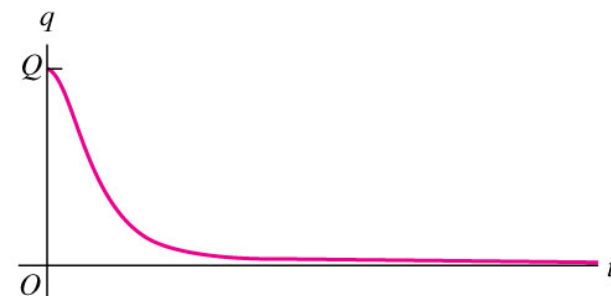(b) Critically damped circuit (larger resistance R)



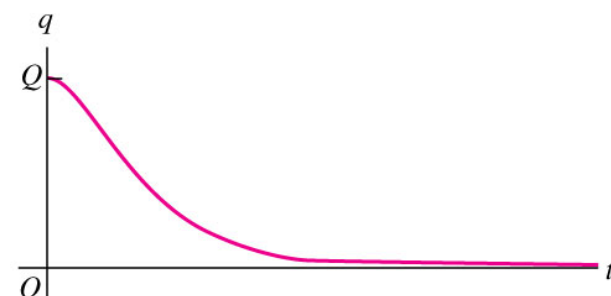(c) Overdamped circuit (very large resistance R)





Maxwell's Equations To Date

$$\oint \vec{E} \cdot d\vec{A} = \frac{Q_{e_enc}}{\epsilon_o}$$

Gauss' Law

$$\oint \vec{B} \cdot d\vec{A} = 0$$

"No Name Law"

$$\oint \vec{B} \cdot d\vec{\ell} = \mu_o I_{e_enc} - \epsilon_o \mu_o \frac{\delta}{\delta t} \int \vec{E} \cdot d\vec{A}$$

Ampere's Law
w/ Maxwell's Correction

$$\oint \vec{E} \cdot d\vec{\ell} = -\frac{\delta}{\delta t} \int \vec{B} \cdot d\vec{A}$$

Faraday's Law

But no magnetic monopoles have been found!
So no magnetic current!