


# BME 301

## 10 - Amplifiers and Feedback

# Basic Amplifier Types

- An amplifier produces an output signal with the same wave shape as the input signal but usually with a larger amplitude.


$$v_o(t) = A_v v_i(t)$$

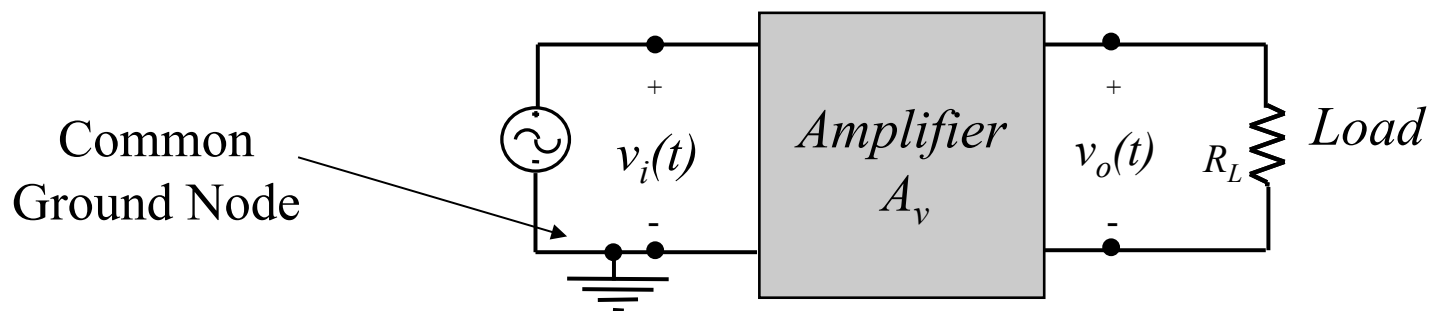

- $A_v$  is called the voltage gain and if  $< 0$  then the amplifier is inverting; otherwise non-inverting.

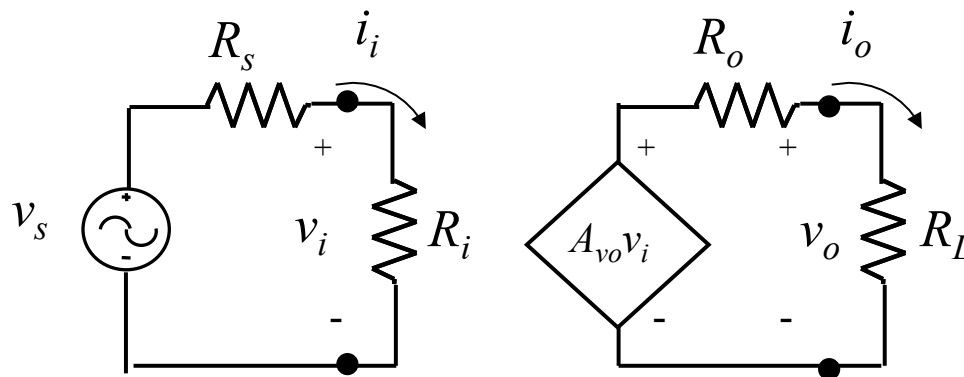
# Voltage-Amplifier Model

- Circuit Parameters:
  - Starting from the left
    - $v_s$  is the source input voltage and represents a microphone of an audio amplifier or the action potential of a muscle.
    - $R_s$  is the resistance of the source voltage device
    - $v_i$  is the voltage to the input of the amplifier
    - $i_i$  is the current flowing in the input of the amplifier
    - $R_i = v_i / i_i$  is the resistance at the input to the amplifier



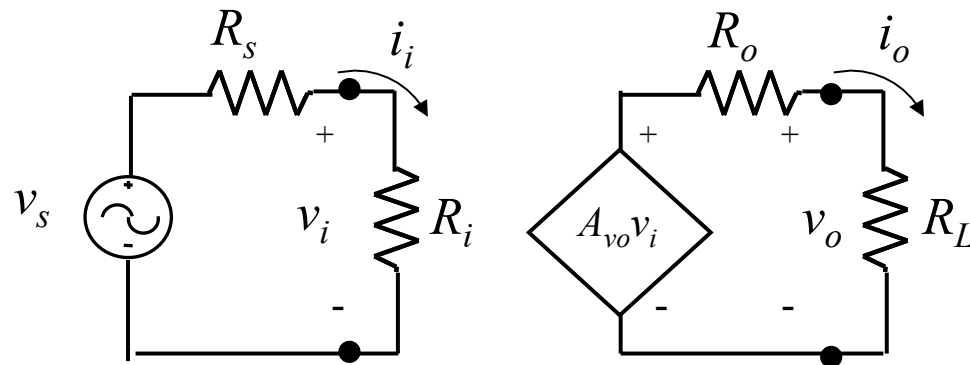
# Voltage-Amplifier Model

- Circuit Parameters:
  - Moving to the right side of the model
    - We see on the right part of the model a new icon called dependent voltage source.
      - It's voltage which depends on a voltage at left side of the model, the input voltage at the amplifier
      - In particular, it's the voltage across the input resistor  $R_i$ .
      - And the gain of the amplifier when nothing is connected to it's output
    - Open Circuit Voltage Gain  $A_{vo}$
    - $R_o$  is the resistance at output of the amplifier
    - $V_o$  is the voltage at the output of the ampilier
    - $i_o$  is the current flowing in the output of the amplifier
    - $R_L = v_o / i_o$  represents the device connect to the output of the amplifier.


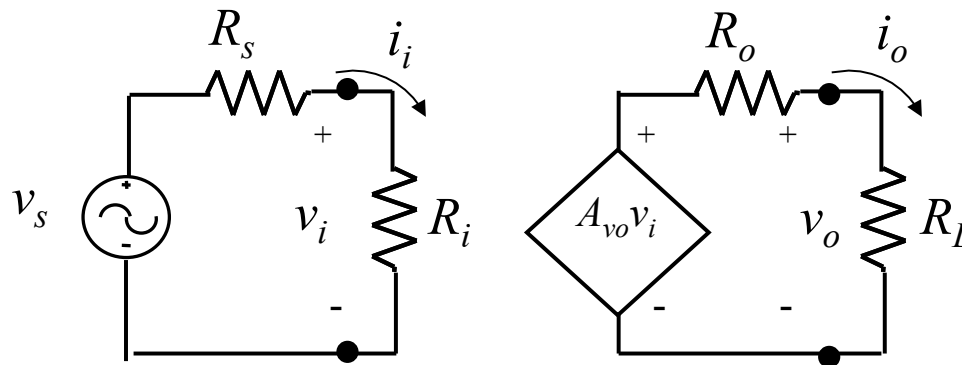
# Voltage-Amplifier Model

- Performance parameters:
  - Voltage Gain  $A_v = v_o / v_i$  from the input of the amplifier to the output of the circuit
  - Voltage Gain  $A_{v_s} = v_o / v_s$  from the source of the amplifier model to the output of the circuit
  - Current Gain  $A_i = i_o / i_i$
  - Power Gain  $G = P_o / P_i$  from the input of the amplifier to the output of the circuit
  - Power Gain  $G_s = P_o / P_s$  from the source of the amplifier model to the output of the circuit




# Power Supply Efficiency

- In addition to the DC power, there is power from the source which is delivered to the input of the amplifier,  $P_i$ .
- Therefore, the total input power is  $P_{DC} + P_i$
- A portion of this power is used to provide the gain and is delivered to the output load,  $P_L$
- The remainder of this power is dissipated by the components of the amplifier,  $P_d$

$$P_{DC} + P_i = P_d + P_L$$

- The amount of power from the DC source delivered to the load is called the power efficiency,  $\eta$


$$\eta = P_L / P_{DC}$$

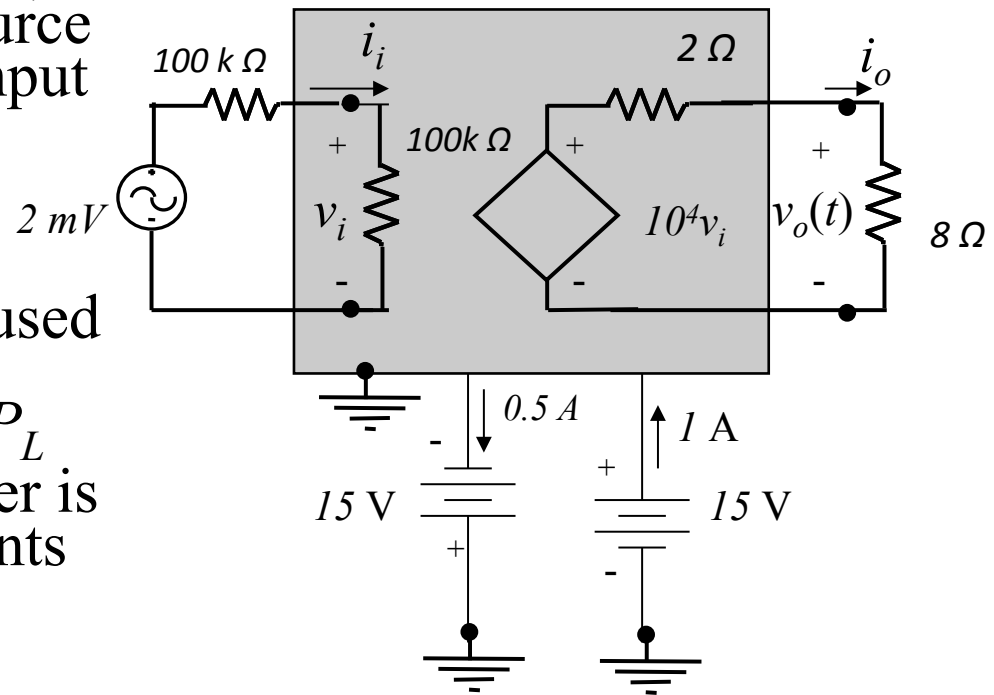

# Feedback

- Types of Feedback
  - Positive: aids the input signal
  - Negative: reduces the input signal
- Positive Feedback Benefits
  - Oscillators
- Negative Feedback Benefits
  - Stabilization of Gain
  - Reduction of Nonlinear Distortion
  - Reduction of noise
  - Control of input and output impedances
  - Extension of Bandwidth
- Design of feedback amplifier to avoid unwanted oscillations

# Closed-Loop Gain

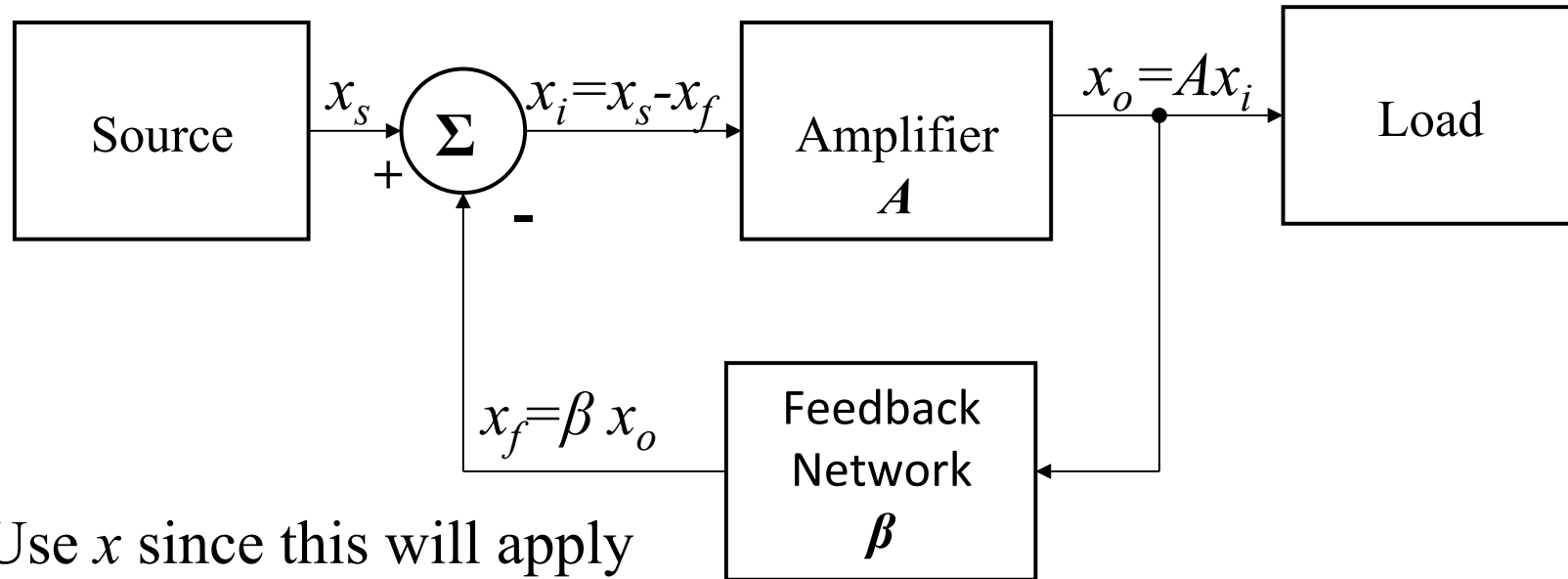

Use  $x$  since this will apply  
equally to voltages and currents

$$x_i = x_s - x_f = x_s - \beta x_o \quad \Rightarrow$$

$$x_o = Ax_i$$

$$x_o = A(x_s - \beta x_o)$$

$$A_f = \frac{x_o}{x_s} = \frac{A}{1 + A\beta}$$

$$\text{Closed - Loop Gain} = A_f$$

$$\text{Open - Loop Gain} = A$$

$$\text{Loop Gain} = A\beta$$



# Problems With Positive Feedback

- If  $|A\beta| \leq 1$  and  $A\beta$  is negative:
  - then  $1+A\beta \leq 1$ ; and  $A_f$  (closed-loop gain)  $> A$  (open-loop gain)
  - if  $A\beta = -1$ , then oscillations occur
  - POSITIVE FEEDBACK
- Example:
  - $A = -10, \beta = 0.0999 \Rightarrow A\beta = -0.999; 1+ A\beta = 0.001; A_f = -10^4$
  - Here is a problem using POSITIVE FEEDBACK
    - $A: -10 \rightarrow -9.9 \Rightarrow A\beta = -0.989; 1+ A\beta = 0.011; \text{then } A_f: -10^4 \rightarrow -901$
    - For a 1% reduction in  $A$  there was a 91% reduction of  $A_f$
  - POOR GAIN STABILITY: worse than the original amplifier

# Problems (Continued)

- Another Example:
  - As  $A\beta \rightarrow -1$ ,  $A_f \rightarrow \infty$  and this implies for a zero input signal an output signal can be generated and a signal will flow around the loop w/o an input  $\Rightarrow$  oscillations. This is ok if an oscillator design is desired.
  - Clearly, a high gain amplifier can be designed with positive feedback; however, care must be taken because any change in the design (temperature shifts increase the power supply voltages) may cause  $A\beta \rightarrow -1$  and oscillations result

# Gain Stabilization Using Negative Feedback

- For Negative Feedback Amplifiers are designed with  $A\beta \gg 1$  and  $A_f \approx 1/\beta$
- This is desirable since the value of  $\beta$  can be designed using solely stable passive components (e.g., resistors and capacitors)
  - This occurs for op amps

# Gain Stabilization Using Negative Feedback

## Continued

- *Example:*  $A = 10^4$  and  $\beta = 0.01 \Rightarrow A_f = 99$ 
  - If  $A \rightarrow 9000$ , then  $A_f \rightarrow 98.9$
  - For a 10% reduction in  $A$  there was only a 0.1% reduction of  $A_f$
- Therefore, we can design precision amplifiers using Negative Feedback

$$\frac{dA_f}{dA} = \frac{1 + A\beta - A\beta}{(1 + A\beta)^2} = \frac{1}{(1 + A\beta)^2}$$


$$dA_f = \frac{dA}{A} \frac{A}{(1 + A\beta)^2} = \frac{dA}{A} \frac{A_f}{1 + A\beta}$$

$$\frac{dA_f}{A_f} = \frac{dA}{A} \frac{1}{1 + A\beta}$$

- This states that for small fractional changes of  $A_f$  is the fractional change in  $A$  divided by  $1 + \beta$
- Clearly, if the loop gain  $A\beta \gg 1$  changes of  $A_f$  are less than  $A$

# Homework

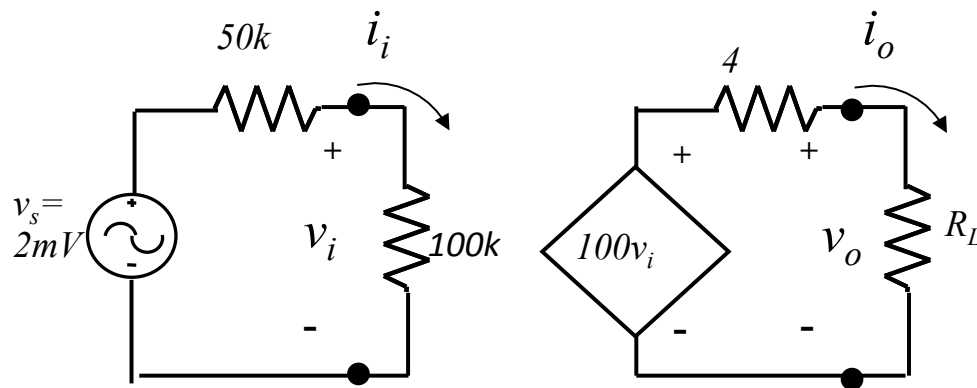1. For the following circuit, determine the value of  $R_L$  to maximize the power gain for this circuit. Provide a proof. Which value of  $R_L$  makes the better design and why?



# Homework

2. What are the benefits of negative feedback?
3. What are the problems with positive feedback?
4. HONORS STUDENTS ADD THE FOLLOWING  
Name 3 types of negative feedback applications.