

# BME 301

## 8-Filters

# What is a filter

- A filter is a system
- A filter can separate unwanted information from a signal
- Like any system a filter has at least one output and at least one input
- A filter manipulates the signal
- Some filters operate on the frequencies of the input signal.

# Filter Basics


- Allows certain frequencies of a signal to pass through the filter; this is called the pass band
- Other frequencies do not get through the filters; this is called the stop band
- Some filters have multiple pass and stop bands
- These bands are defined by certain frequencies; these frequencies are called break frequencies or cutoff frequencies.

# Examples of Filters

- Low Pass Filter (LP) : allows signal frequencies below a defined cutoff frequency to pass through the filter
- High Pass Filter (HP): allows signal frequencies above a defined cutoff frequency to pass through the filter
- Band Pass Filter (BP): allows signal frequencies between a range of a defined cutoff frequencies to pass through the filter
 
# Typical Filter

- This is a typical electric circuit filter
- It has an input and an output (across the capacitor)
- The relationship of the output to the input as a function of frequency, called the transfer function,  $V_{out}(t)/V_{in}(t)$ , is calculated
- Once the transfer function is calculation, a plot of the magnitude and phase as a function of frequency is made. This is called Bode plot.
- This transfer function and it's Bode will demonstrate the operation of the filter; e.g., HP or LP.





# Transfer function Calculation

- In order to determine the Transfer Function of this circuit, we need to learn some circuit analysis techniques.
- Examples of circuit analysis techniques:
  - KVL & KCL
  - Circuit Reduction
  - Voltage Division
  - Current Division
  - Nodal and Mesh Analysis
  - Superposition
  
# Voltage Division

- The voltage across impedances in series divides in proportion to the impedances.



$$\mathbf{V}_{ac} = \mathbf{V}_{ab} + \mathbf{V}_{bc} = \mathbf{I}(Z_1 + Z_2); \text{KVL} + \text{Ohm's Law}$$


$$\mathbf{V}_{bc} = \mathbf{I}Z_2$$

$$\frac{\mathbf{V}_{bc}}{\mathbf{V}_{ac}} = \frac{Z_2}{Z_1 + Z_2}$$

$$\frac{\mathbf{V}_i}{\mathbf{V}_{ac}} = \frac{Z_i}{Z_1 + Z_2 + \dots + Z_n}$$
 
# Current Division

- The current into impedances in parallel divides in proportion to the inverse of the impedances.



$$\mathbf{I}_{ac} = \mathbf{I}_1 + \mathbf{I}_2 = \mathbf{V} \left( \frac{1}{Z_1} + \frac{1}{Z_2} \right); \text{KCL + Ohm's Law}$$

$$\mathbf{I}_1 = \frac{\mathbf{V}}{Z_1}$$


$$\frac{\mathbf{I}_1}{\mathbf{I}_{ac}} = \frac{1/Z_1}{(1/Z_1) + (1/Z_2)} = \frac{Z_2}{Z_1 + Z_2}$$

$$\frac{\mathbf{I}_i}{\mathbf{I}_{ac}} = \frac{(1/Z_i)}{(1/Z_1) + (1/Z_2) + \dots + (1/Z_n)}$$


 
# Let's try Voltage division on this circuit

- Since the capacitor and the resistor are in series and since the voltage across the capacitor is the output, we can use voltage division.
- An easy way to plot the transfer function using Matlab or Excel or one can sketch it by finding 3 points and generate a sketch. Two of the points are when the frequency is zero and when the frequency approaches infinity. The third can be any convenient point in between.



# Let's try Voltage division on this circuit

Using Voltage division

$$\frac{V_{out}}{V_{in}} = \frac{Z_2}{Z_1 + Z_2}; \text{ where } Z_1 \text{ is the resistor which is } R \text{ and } Z_2 \text{ is the capacitor which is } \frac{1}{j\omega C}$$

$$\frac{V_{out}}{V_{in}} = \frac{\frac{1}{j\omega C}}{R + \frac{1}{j\omega C}} = \frac{1}{1 + j\omega RC} = \frac{1}{\sqrt{1 + (\omega RC)^2}} \angle -\tan^{-1}(\omega RC)$$

An easy way to plot the transfer function is determine 3 or more points and sketch its shape.


Two of these points are usually taken at  $\omega=0$  and  $\omega \rightarrow \infty$ . The third can be somewhere in between at any easy point to calculate.

$$\frac{V_{out}}{V_{in}} \Big|_{\omega=0} = \frac{1}{1 + j\omega RC} \Big|_{\omega=0} = 1 = 1 \angle 0$$


$$\frac{V_{out}}{V_{in}} \Big|_{\omega \rightarrow \infty} = \frac{1}{1 + j\omega RC} \Big|_{\omega \rightarrow \infty} \rightarrow \frac{1}{j\omega RC} \Big|_{\omega \rightarrow \infty} = \frac{1}{\omega RC} \angle -\frac{\pi}{2} \Big|_{\omega \rightarrow \infty} \rightarrow 0 \angle -\frac{\pi}{2}$$

A convenient midway point is a  $\omega = \frac{1}{RC}$



$$\frac{V_{out}}{V_{in}} \Big|_{\omega = \frac{1}{RC}} = \frac{1}{1 + j\omega RC} \Big|_{\omega = \frac{1}{RC}} = \frac{1}{1 + j} = \frac{1}{\sqrt{2}} \angle -\frac{\pi}{4}$$

 
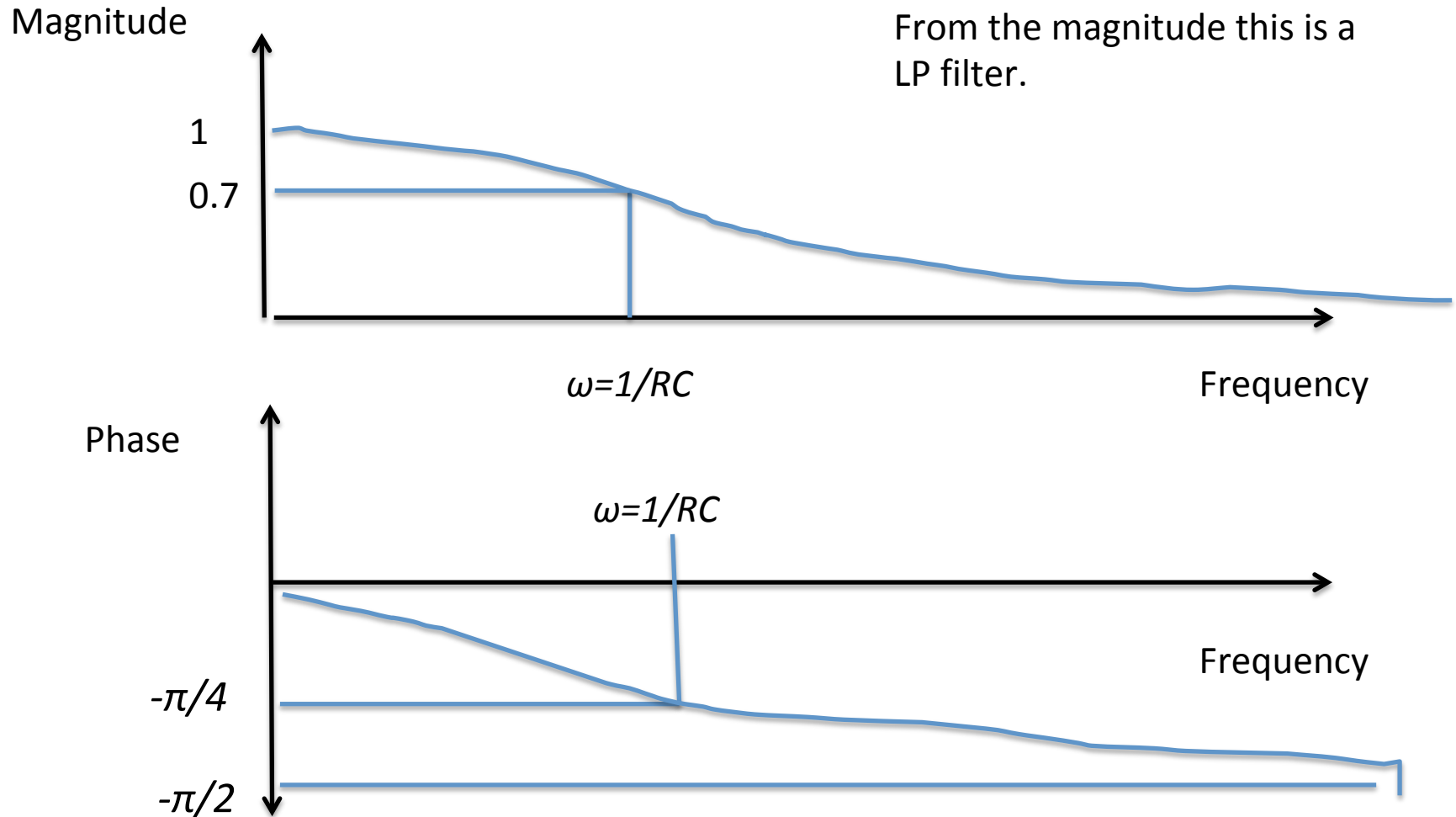
# Sketching the Bode plot of the transfer function




# Excel Bode Plot

 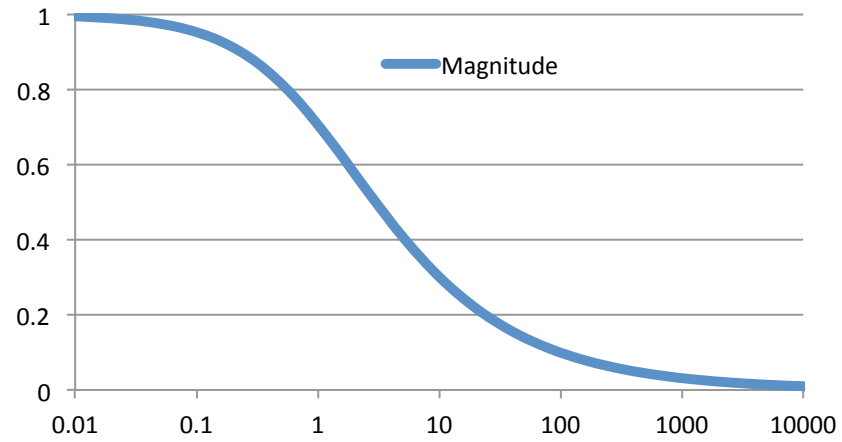

# Homework

 1. Find the transfer function of this circuit as function of  $\omega$ . Plot using Matlab the magnitude and phase as a function of  $\omega$ .



# Homework

## 2. HONORS STUDENTS ADD THE FOLLOWING

An electrode is connected to an oscilloscope which has a purely capacitance input impedance,  $C_{IN}$ . Find and plot using Matlab the transfer function of this circuit as function of  $\omega$ .

