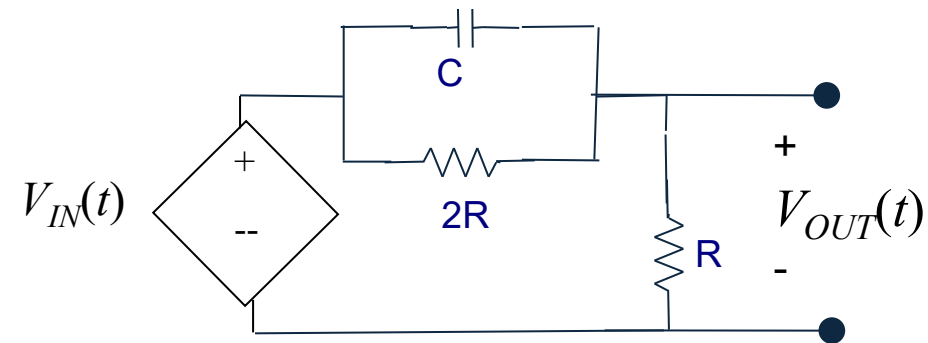


# Special Homework

For the following circuit:

- Determine and sketch the transfer function in ***polar form***.
- Assume that  $R=1$  and  $C=2$ , sketch the transfer function versus the ***frequency,  $f$*** ; i.e. ***in Hertz***.
- What sort of circuit is this?
- What is its cutoff frequency?



# Exam 2

5. For the following circuit:

- Determine the transfer function in **polar form**
- Assume that  $R=1$  and  $C=2$ , sketch the transfer function versus the **frequency,  $f$** ; i.e. **in Hertz**.
- What sort of circuit is this?
- What is its cutoff frequency?


$$a) \frac{V_{out}}{V_{in}} = \frac{R}{Z_{ab}}$$

$$Z_{ab} = \frac{3R + j\omega 2R^2C}{1 + j\omega 2RC}$$

$$\frac{V_{out}}{V_{in}} = \frac{R}{3R + j\omega 2R^2C} = \frac{R(1 + j\omega 2RC)}{3R + j\omega 2R^2C} = \frac{(1 + j\omega 2RC)}{3 + j\omega 2RC}$$

$$\text{Let } \omega = 2\pi f \text{ and } f_o = \frac{1}{2\pi 2RC} = 0.039$$


$$= \frac{1 + j \frac{f}{f_o}}{3 + j \frac{f}{f_o}} = \frac{\sqrt{1 + \left(\frac{f}{f_o}\right)^2} \angle \tan^{-1}\left(\frac{f}{f_o}\right)}{\sqrt{3^2 + \left(\frac{f}{f_o}\right)^2} \angle \tan^{-1}\left(\frac{f}{3f_o}\right)} = \frac{\sqrt{1 + \left(\frac{f}{f_o}\right)^2}}{\sqrt{3^2 + \left(\frac{f}{f_o}\right)^2}} \angle \tan^{-1}\left(\frac{f}{f_o}\right) - \angle \tan^{-1}\left(\frac{f}{3f_o}\right)$$

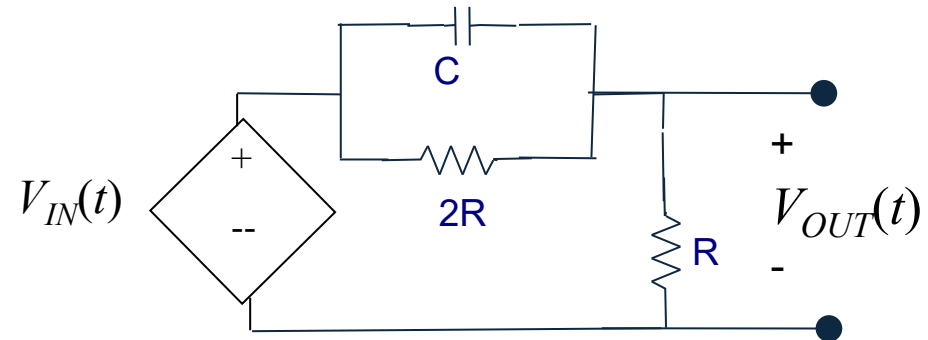

# Exam 2

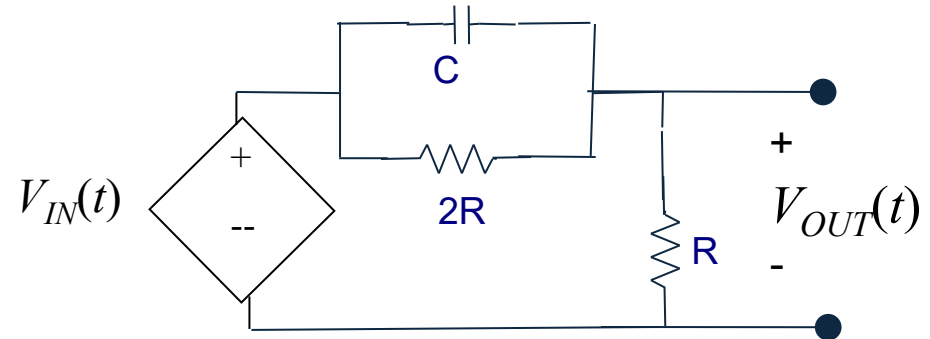5. For the following circuit:

- Determine the transfer function in **polar form**
- Assume that  $R=1$  and  $C=2$ , sketch the transfer function versus the **frequency,  $f$** ; i.e. **in Hertz**.
- What sort of circuit is this?
- What is its cutoff frequency?



c) HPF  
 d) from the graph the cutoff frequency is around  $f = .1$  Hz; Note that  $f_o$  is not the

cutoff frequency since the value of  $\frac{V_{out}}{V_{in}}$  is not equal  $\frac{1}{\sqrt{2}} \times \frac{V_{out}}{V_{in}}|_{\max} = \frac{1}{\sqrt{2}} = 0.707$  but equal to 0.45.

$$b) \frac{V_{out}}{V_{in}} = \frac{1 + j \frac{f}{f_o}}{3 + j \frac{f}{f_o}}$$

$$\frac{V_{out}}{V_{in}}|_{f=0} = \frac{1 + j \frac{0}{f_o}}{3 + j \frac{0}{f_o}} = \frac{1}{3} \angle 0$$

$$\frac{V_{out}}{V_{in}}|_{f \rightarrow \infty} \rightarrow \frac{1 + j \frac{f}{f_o}}{3 + j \frac{f}{f_o}}|_{f \rightarrow \infty} \rightarrow \frac{j \frac{f}{f_o}}{j \frac{f}{f_o}} = 1 \angle 0$$

$$\frac{V_{out}}{V_{in}}|_{f=f_o=0.039} = \frac{1 + j \frac{f_o}{f_o}}{3 + j \frac{f_o}{f_o}} = \frac{1 + j1}{3 + j1} = \frac{\sqrt{2} \angle \frac{\pi}{4}}{\sqrt{10} \angle \tan^{-1}(\frac{1}{3})} = \frac{1}{\sqrt{5}} \angle \frac{\pi}{4} - \tan^{-1}(\frac{1}{3}) = 0.447 \angle 0.46$$

