

# BME 301

## 4-Simple Circuits


# Homework

1. Find the total resistance  $R_{ab}$  where


$$R_1 = 10\Omega, R_2 = 15\Omega, R_3 = 15\Omega,$$

$$R_4 = 15\Omega, R_5 = 10\Omega, R_6 = 10\Omega,$$

$$R_7 = 10\Omega, R_8 = 10\Omega$$

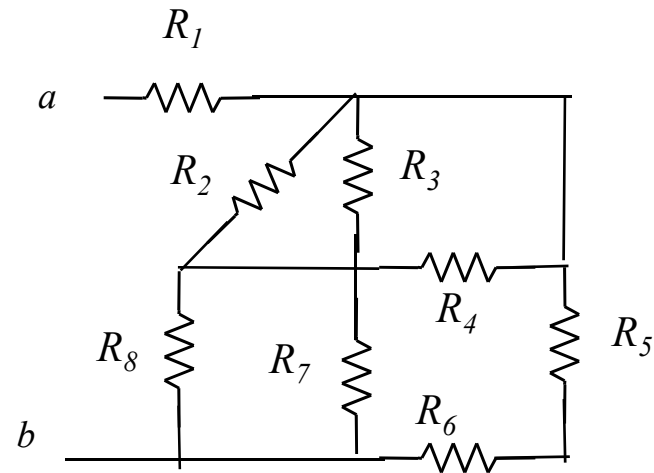

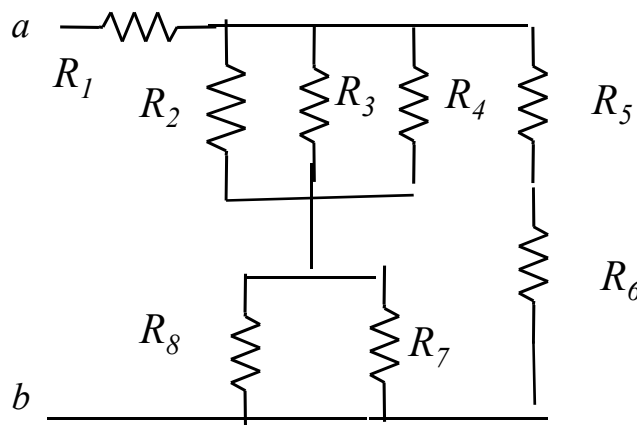In this circuit  $R_5$  and  $R_6$  are in series. In addition,  $R_4$ ,  $R_3$ , and  $R_2$  are in parallel. Finally  $R_7$  and  $R_8$  are in parallel. These two parallel combinations are in series. This series combination is in series with the series combination of  $R_5$  and  $R_6$ .  $R_1$  is in series with this parallel combinations. This is the circuit redrawn. See the follow




# Homework

1. Find the total resistance  $R_{ab}$  where

$$R_1 = 10\Omega, R_2 = 15\Omega, R_3 = 15\Omega,$$

$$R_4 = 15\Omega, R_5 = 10\Omega, R_6 = 10\Omega,$$

$$R_7 = 10\Omega, R_8 = 10\Omega$$

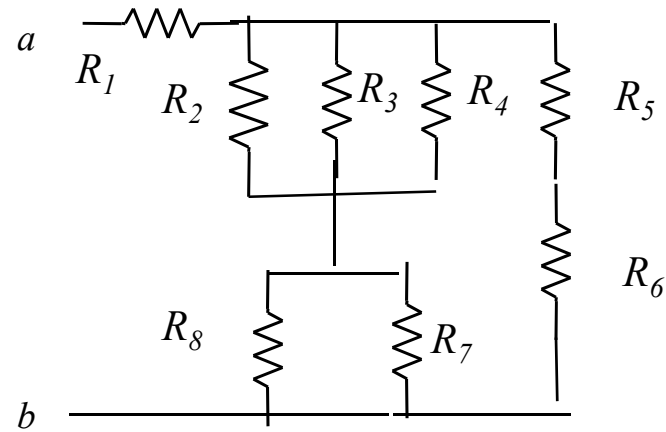

$$R_A = R_5 \text{ in series with } R_6 = 10 + 10 = 20 \Omega$$

$$R_B = R_4, R_3 \text{ and } R_2 \text{ in parallel} = \frac{1}{\frac{1}{15} + \frac{1}{15} + \frac{1}{15}} = \frac{1}{\frac{3}{15}} = \frac{15}{3} = 5\Omega$$

$$R_C = R_7 \text{ in parallel with } R_8 = \frac{1}{\frac{1}{10} + \frac{1}{10}} = \frac{1}{\frac{2}{10}} = 5\Omega$$

$$R_D = R_B \text{ in series with } R_C = 5 + 5 = 10\Omega$$

$$R_E = R_D \text{ in parallel with } R_A = \frac{1}{\frac{1}{10} + \frac{1}{20}} = \frac{20}{3} = 6.67\Omega$$

$$R_1 \text{ in series with } R_E = 10 + 6.67 = 16.67\Omega$$


# Homework

2. Calculate the current labeled,  $i$ .

$$R_1 = 2.5\Omega, R_2 = 5\Omega, R_3 = 2.5\Omega, R_4 = 2.5\Omega, R_5 = 5\Omega,$$

$$R_6 = 5\Omega, R_7 = 5\Omega, V_{cc} = 5$$

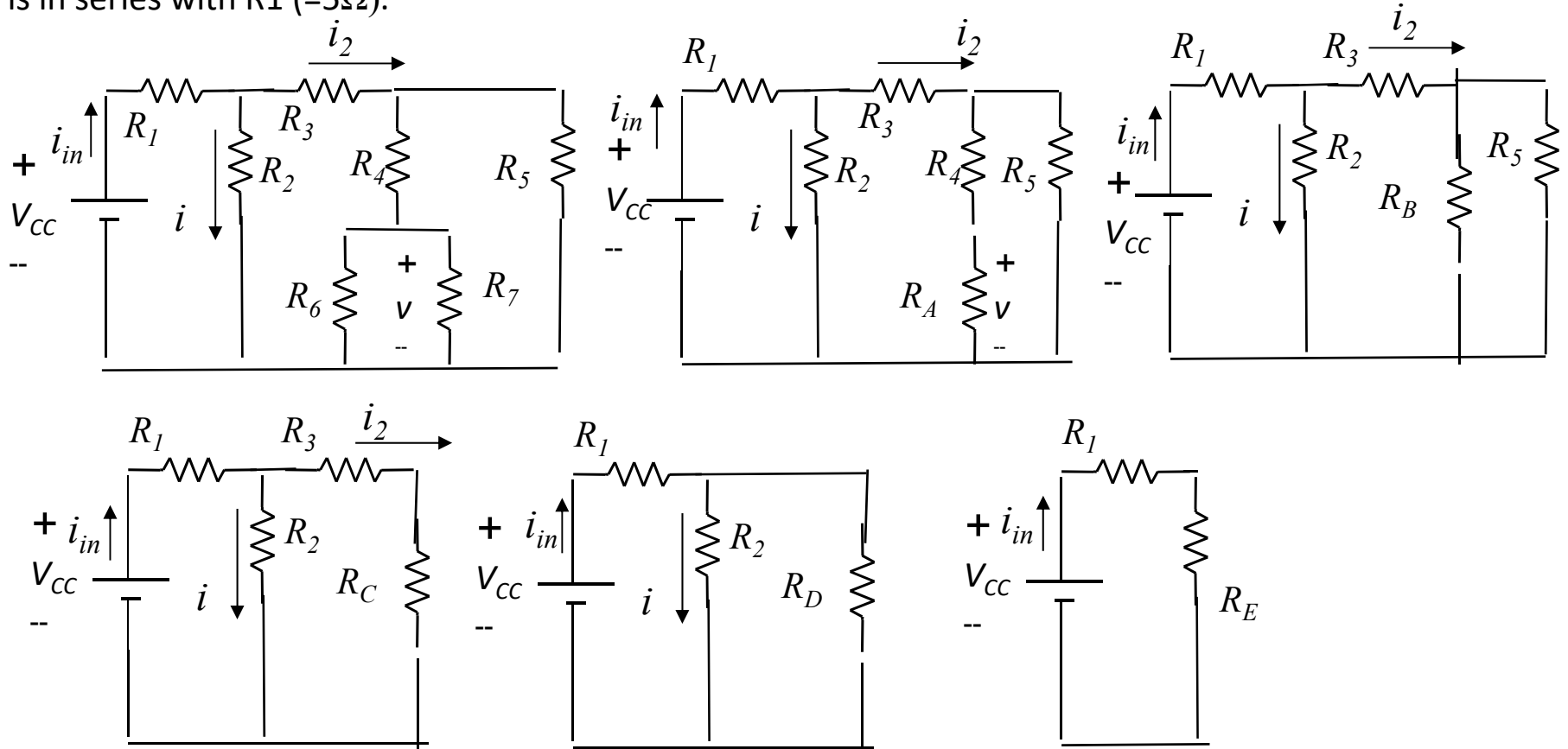$R_6$  and  $R_7$  are in parallel (Call it  $R_A=2.5\Omega$ ).  $R_A$  is in series with  $R_4$  (call is  $R_B=5\Omega$ ).  $R_B$  is in parallel with  $R_5$  (Call it  $R_C=2.5\Omega$ ).  $R_C$  is in series with  $R_3$  (Call it  $R_D=5\Omega$ ).  $R_D$  is in parallel with  $R_2$  (Call it  $R_E=2.5\Omega$ ).  $R_E$  is in series with  $R_1$  ( $=5\Omega$ ).




# Homework

2. Calculate the current labeled,  $i$ .

$$R_1 = 2.5\Omega, R_2 = 5\Omega, R_3 = 2.5\Omega, R_4 = 2.5\Omega, R_5 = 5\Omega,$$

$$R_6 = 5\Omega, R_7 = 5\Omega, V_{cc} = 5$$

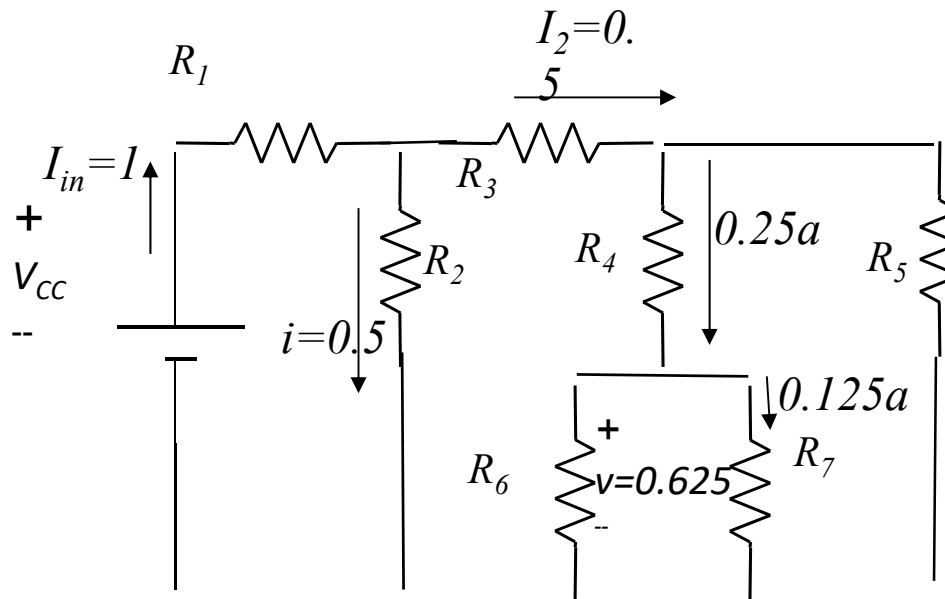
Now  $i_{in} = 5/5 = 1$ . Then using current division  $i = 1/2 = 0.5$  since  $R_D = R_2$ . And therefore,  $i_2 = 0.5$ . Then the current flowing into  $R_B = 0.25$  since  $R_B = R_5$ . Since  $R_6 = R_7$ , Then the current  $R_7 = 0.125$  and the voltage labeled  $v = 0.125 \times 5 = 0.625$  volt or  $v = 0.5 \times 1.5 = 0.625$ .



# Homework


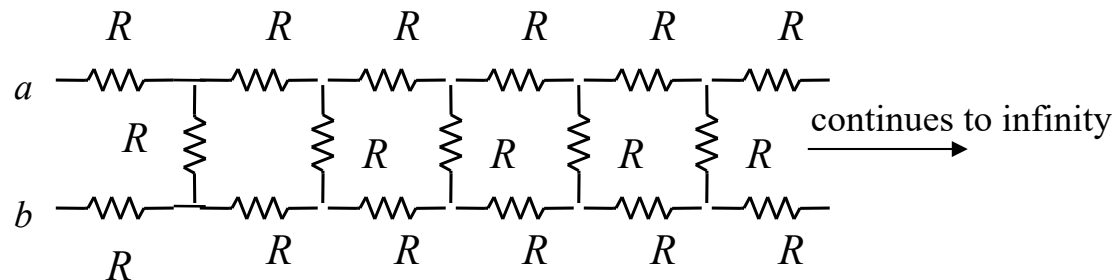
## 3. HONORS STUDENTS ADD THE FOLLOWING

Find the total resistance  $R_{ab}$  for this infinite resistive network.


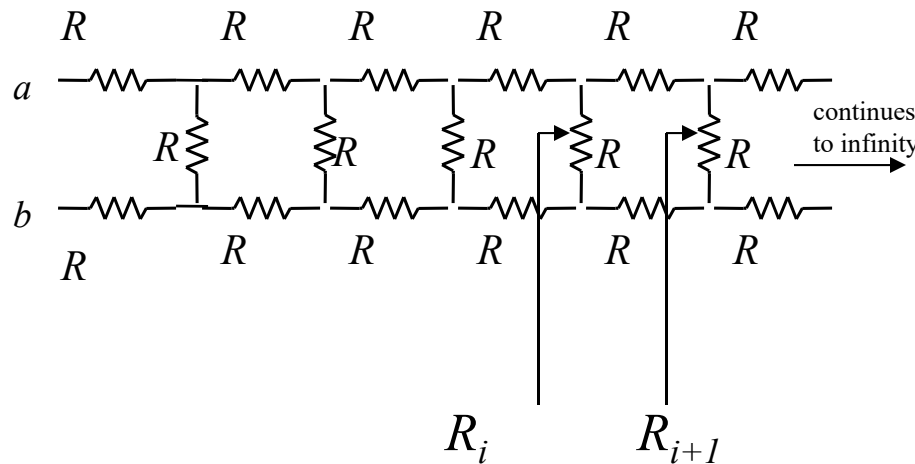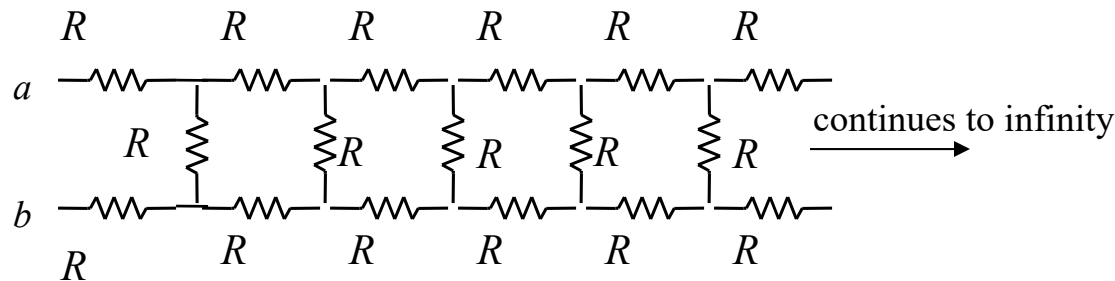
# Homework

Find the total resistance  $R_{ab}$  for this infinite resistive network



METHOD #1 Theoretical

$$R_i = (R_{i+1} + 2R) \parallel R = \frac{(R_{i+1} + 2R)R}{R_{i+1} + 3R}$$

But since the chain is infinite, shouldn't  $R_i = R_{i+1} = r$

$$r = \frac{(r + 2R)R}{r + 3R} \Rightarrow r^2 + 3Rr = Rr + 2R^2 \Rightarrow r^2 + 2Rr - 2R^2 = 0$$



$$r = \frac{-2R \pm \sqrt{(2R)^2 - 4(-2R^2)}}{2} = \frac{-2R \pm R\sqrt{4+8}}{2} = \frac{-2R \pm R2\sqrt{3}}{2}$$

$$r = R(\sqrt{3} - 1)$$

$$R_{ab} = 2R + r = (1 + \sqrt{3})R = 2.732R$$
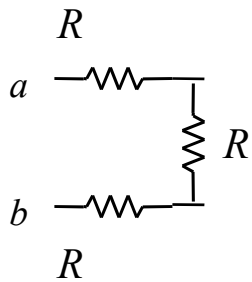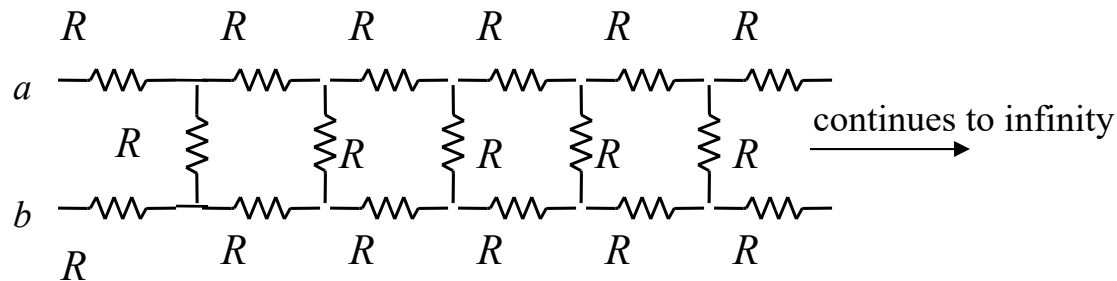
# Homework

Find the total resistance  $R_{ab}$  for this infinite resistive network




METHOD #2

Numerical Iteration

Iteration 1


$$R_{ab}^1 = 3R$$

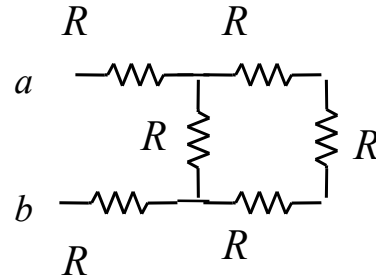

Iteration 2

$$R_{ab}^2 = 2R + R \parallel 3R = 2R + R \parallel R_{ab}^1$$

$$R_{ab}^2 = 2R + \frac{R(3R)}{4R} = 2R + .75R = 2.75R$$

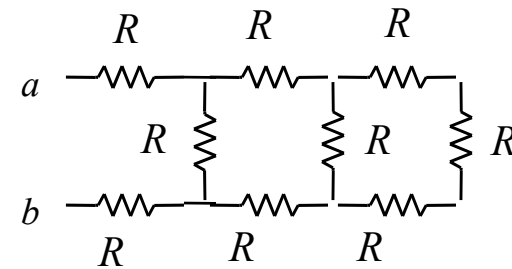

Iteration 3


$$R_{ab}^3 = 2R + R \parallel (2R + R \parallel 3R) = 2R + R \parallel (R_{ab}^2)$$

$$R_{ab}^3 = 2R + \frac{R(2.75R)}{R + (2.75R)} = 2R + \frac{2.75R}{3.75} = 2R + .733R = 2.733R$$


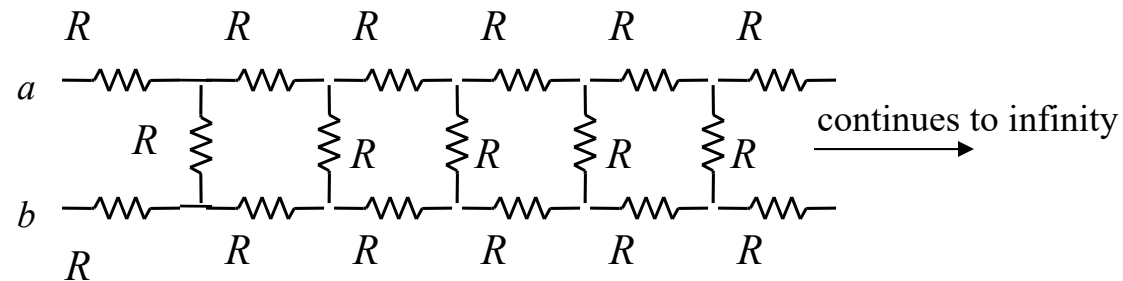
# Homework

Find the total resistance  $R_{ab}$  for this infinite resistive network



Iteration  $N$

$$R_{ab}^N = 2R + R \parallel R_{ab}^{N-1}$$

Continuing this way we see that  $R_{ab}$  approaches  $2.732R$  where  $2.732$  is the  $\sqrt{3}+1$

| Iteration | Rab      |
|-----------|----------|
| 1         | 3        |
| 2         | 2.75     |
| 3         | 2.733333 |
| 4         | 2.732143 |
| 5         | 2.732057 |
| 6         | 2.732051 |
| 7         | 2.732051 |
| 8         | 2.732051 |
| 9         | 2.732051 |
| 10        | 2.732051 |
| 11        | 2.732051 |
| 12        | 2.732051 |
| 13        | 2.732051 |
| 14        | 2.732051 |
| 15        | 2.732051 |
| 16        | 2.732051 |
| 17        | 2.732051 |
| 18        | 2.732051 |
| 19        | 2.732051 |
| 20        | 2.732051 |

