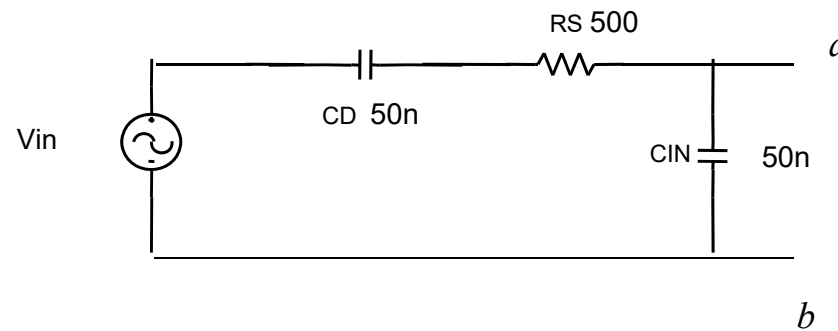


BME 301

8-Filters


Homework

1. If the circuit in problem 1 was too challenging, try this circuit, first. Find the transfer function of this circuit as function of ω .



Homework

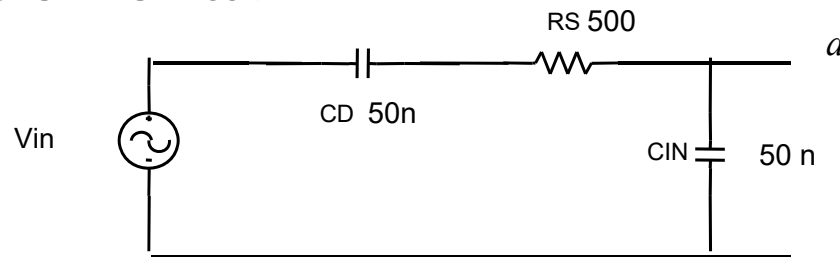
1. If the circuit in problem 1 was too challenging, try this circuit. Find the transfer function of this circuit as function of ω .



$$\begin{aligned}
 \frac{V_{ab}}{V_{in}} &= \frac{\frac{1}{j\omega C_{IN}}}{\frac{1}{j\omega C_{IN}} + R_S + \frac{1}{j\omega C_D}} = \frac{j\omega C_D}{j\omega C_D + j\omega C_{IN} j\omega C_D R_S + j\omega C_{IN}} = \frac{j\omega C_D}{-\omega^2 C_{IN} C_D R_S + j\omega(C_{IN} + C_D)} \\
 &= \frac{\omega C_D \angle \frac{\pi}{2}}{\sqrt{(\omega^2 C_{IN} C_D R_S)^2 + (\omega(C_{IN} + C_D))^2} \angle \tan^{-1}\left(\frac{\omega(C_{IN} + C_D)}{-\omega^2 C_{IN} C_D R_S}\right)} \\
 &= \frac{\omega C_D}{\sqrt{(\omega^2 C_{IN} C_D R_S)^2 + (\omega(C_{IN} + C_D))^2}} \angle \left[\frac{\pi}{2} - \tan^{-1}\left(\frac{\omega(C_{IN} + C_D)}{-\omega^2 C_{IN} C_D R_S}\right) \right]
 \end{aligned}$$

Homework (Extra Credit if done)

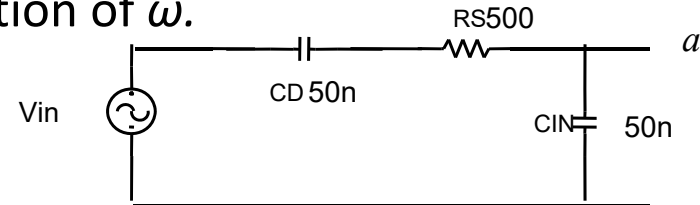1. If the circuit in problem 1 was too challenging, try this circuit. Find the transfer function of this circuit as function of ω .



$$\frac{V_{ab}}{V_{in}} = \frac{j\omega C_D}{-\omega^2 C_{IN} C_D R_S + j\omega(C_{IN} + C_D)} = \frac{\omega C_D}{\sqrt{(\omega^2 C_{IN} C_D R_S)^2 + (\omega(C_{IN} + C_D))^2}} \angle \left[\frac{\pi}{2} - \tan^{-1} \left(\frac{\omega(C_{IN} + C_D)}{-\omega^2 C_{IN} C_D R_S} \right) \right]$$

$$\frac{V_{ab}}{V_{in}} \Big|_{\omega \rightarrow 0} = \frac{j\omega C_D}{-\omega^2 C_{IN} C_D R_S + j\omega(C_{IN} + C_D)} \Big|_{\omega \rightarrow 0} \rightarrow \frac{j\omega C_D}{j\omega(C_{IN} + C_D)} = \frac{C_D}{(C_{IN} + C_D)} \angle 0$$

$$= \frac{1/C_{IN}}{(1/C_{IN} + 1/C_D)} \angle 0 = 0.5 \angle 0 \text{ voltage divides according to the capacitor impedances.}$$

$$\frac{V_{ab}}{V_{in}} \Big|_{\omega \rightarrow \infty} = \frac{j\omega C_D}{-\omega^2 C_{IN} C_D R_S + j\omega(C_{IN} + C_D)} \Big|_{\omega \rightarrow \infty} \rightarrow \frac{j\omega C_D}{-\omega^2 C_{IN} C_D R_S} = \frac{j}{-\omega C_{IN} R_S} = \frac{-j}{\omega C_{IN} R_S} \Big|_{\omega \rightarrow \infty}$$

$\rightarrow 0 \angle -\frac{\pi}{2}$ output capacitor is a short circuit.




$$\omega = \frac{1}{C_{IN} R_S} = 4 \times 10^4$$

$$\frac{V_{ab}}{V_{in}} \Big|_{\omega = \frac{1}{C_{IN} R_S}} = \frac{j\omega C_D}{-\omega^2 C_{IN} C_D R_S + j\omega(C_{IN} + C_D)} \Big|_{\omega = \frac{1}{C_{IN} R_S}} = \frac{j}{-\omega C_{IN} R_S + j \left(\frac{C_{IN} + C_D}{C_D} \right)} \Big|_{\omega = \frac{1}{C_{IN} R_S}} = \frac{j}{-1 + j \left(\frac{C_{IN} + C_D}{C_D} \right)}$$

$$= \frac{1}{\sqrt{1 + \left(\frac{C_{IN} + C_D}{C_D} \right)^2}} \angle \left[\frac{\pi}{2} - \tan^{-1} \left(\frac{C_{IN} + C_D}{-C_D} \right) \right] = 0.45 \angle -0.46$$

Homework (Extra Credit if done)

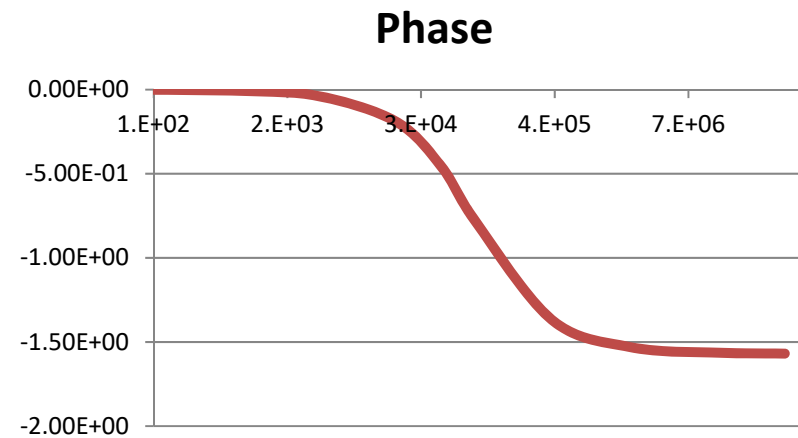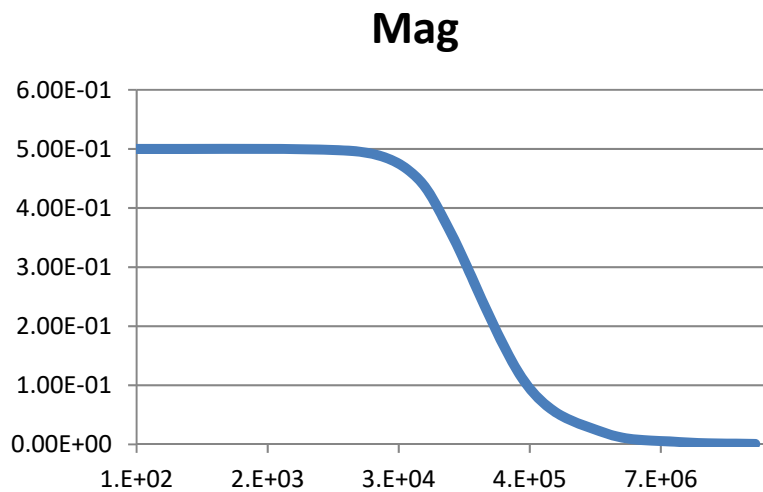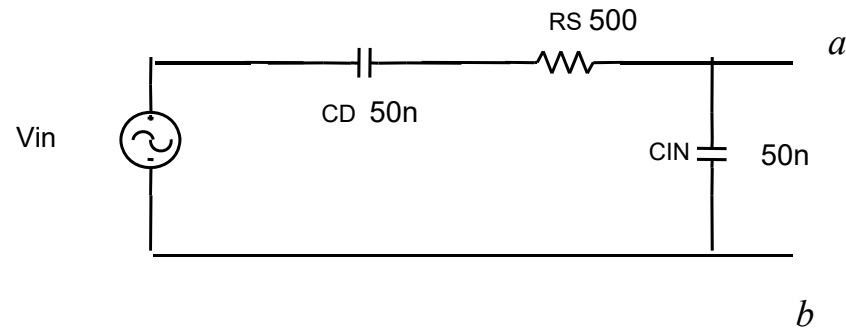
1. If the circuit in problem 1 was too challenging, try this circuit. Find the transfer function of this circuit as function of ω .



Homework

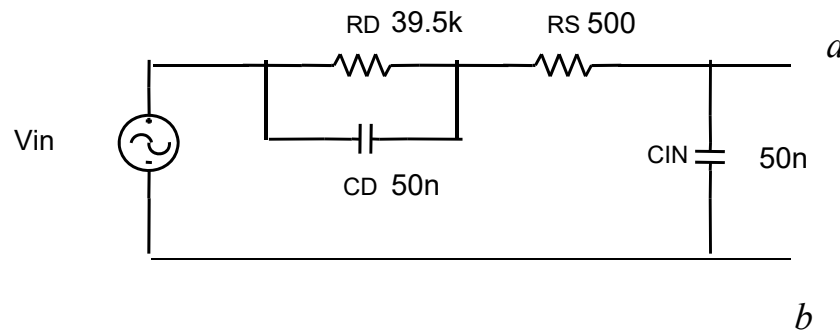2. HONORS STUDENTS ADD THE FOLLOWING

An electrode is connected to an oscilloscope which has a purely capacitance input impedance, C_{IN} . Find the transfer function of this circuit as function of ω .



Homework

2. An electrode is connected to an oscilloscope which has a purely capacitance input impedance, C_{IN} . Find the transfer function of this circuit as function of ω .

Using voltage division:

$$\frac{V_{ab}}{V_{in}} = \frac{Z_{out}}{Z_{out} + Z_{series}}$$


$$\text{where } Z_{out} = \frac{1}{j\omega C_{IN}}$$

$$\text{and } Z_{series} = R_S + R_D // C_D = R_S + \frac{1}{\frac{1}{R_D} + \frac{1}{j\omega C_D}} = R_S + \frac{1}{\frac{1}{R_D} + j\omega C_D}$$

$$= R_S + \frac{R_D}{1 + j\omega R_D C_D} = \frac{R_S(1 + j\omega R_D C_D) + R_D}{1 + j\omega R_D C_D} = \frac{R_S + R_D + j\omega R_D R_S C_D}{1 + j\omega R_D C_D}$$


$$Z_{out} + Z_{series} = \frac{1}{j\omega C_{IN}} + \frac{R_S + R_D + j\omega R_D R_S C_D}{1 + j\omega R_D C_D} = \frac{1 + j\omega R_D C_D + j\omega C_{IN}(R_S + R_D + j\omega R_D R_S C_D)}{j\omega C_{IN}(1 + j\omega R_D C_D)} = \frac{1 - \omega^2 R_D C_{IN} R_S C_D + j\omega[C_{IN}(R_S + R_D) + R_D C_D]}{j\omega C_{IN}(1 + j\omega R_D C_D)}$$
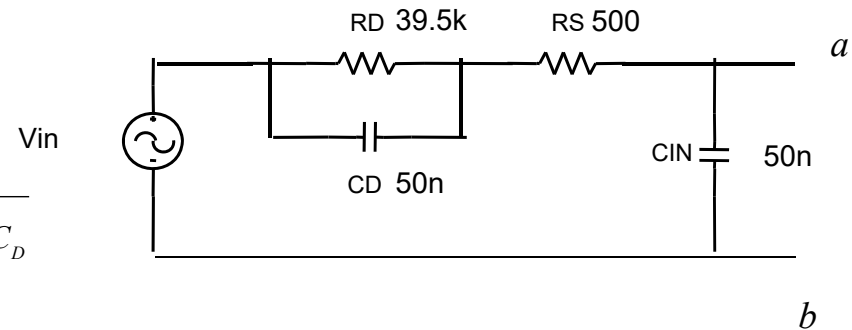
$$\frac{V_{ab}}{V_{in}} = \frac{Z_{out}}{Z_{out} + Z_{series}} = \frac{\frac{1}{j\omega C_{IN}}}{\frac{1 - \omega^2 R_D C_{IN} R_S C_D + j\omega[C_{IN}(R_S + R_D) + R_D C_D]}{j\omega C_{IN}(1 + j\omega R_D C_D)}} = \frac{1 + j\omega R_D C_D}{1 - \omega^2 R_D C_{IN} R_S C_D + j\omega[C_{IN}(R_S + R_D) + R_D C_D]}$$



Homework

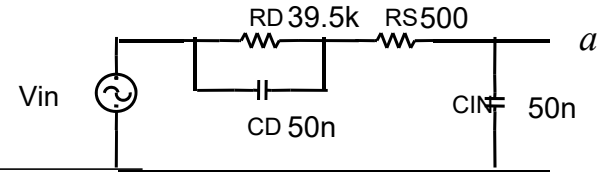2. An electrode is connected to an oscilloscope which has a purely capacitance input impedance, C_{IN} . Find the transfer function of this circuit as function of ω .



$$\frac{V_{ab}}{V_{in}} = \frac{1 + j\omega R_D C_D}{1 - \omega^2 R_D C_{IN} R_S C_D + j\omega [C_{IN} (R_S + R_D) + R_D C_D]} = \frac{\sqrt{1 + (\omega R_D C_D)^2} \angle \tan^{-1}(\omega R_D C_D)}{\sqrt{(1 - \omega^2 R_D C_{IN} R_S C_D)^2 + (\omega [C_{IN} (R_S + R_D) + R_D C_D])^2} \angle \tan^{-1}\left(\frac{\omega [C_{IN} (R_S + R_D) + R_D C_D]}{1 - \omega^2 R_D C_{IN} R_S C_D}\right)}$$

$$= \frac{\sqrt{1 + (\omega R_D C_D)^2}}{\sqrt{(1 - \omega^2 R_D C_{IN} R_S C_D)^2 + (\omega [C_{IN} (R_S + R_D) + R_D C_D])^2}} \angle [\tan^{-1}(\omega R_D C_D) - \tan^{-1}\left(\frac{\omega [C_{IN} (R_S + R_D) + R_D C_D]}{1 - \omega^2 R_D C_{IN} R_S C_D}\right)]$$

$$\frac{V_{ab}}{V_{in}} \Big|_{\omega=0} = \frac{1}{1} = 1 \angle 0$$

$$\frac{V_{ab}}{V_{in}} \Big|_{\omega \rightarrow \infty} \rightarrow \frac{j\omega R_D C_D}{-\omega^2 R_D C_{IN} R_S C_D} = \frac{j}{-\omega C_{IN} R_S} = 0 \angle -\frac{\pi}{2}$$


$$\omega = \frac{1}{\sqrt{R_D C_{IN} R_S C_D}} = 1.69 \times 10^4$$

$$\frac{V_{ab}}{V_{in}} \Big|_{\omega = \frac{1}{\sqrt{R_D C_{IN} R_S C_D}}} = \frac{1 + j \frac{1}{\sqrt{R_D C_{IN} R_S C_D}} R_D C_D}{j \frac{1}{\sqrt{R_D C_{IN} R_S C_D}} [C_{IN} (R_S + R_D) + R_D C_D]} = \frac{\sqrt{1 + \left(\frac{1}{\sqrt{R_D C_{IN} R_S C_D}} R_D C_D\right)^2}}{\frac{1}{\sqrt{R_D C_{IN} R_S C_D}} [C_{IN} (R_S + R_D) + R_D C_D]} \angle \left[\tan^{-1}\left(\frac{1}{\sqrt{R_D C_{IN} R_S C_D}} R_D C_D\right) - \frac{\pi}{2} \right]$$


$$= 2.2 \times 10^{-2} \angle -1.18$$

Homework

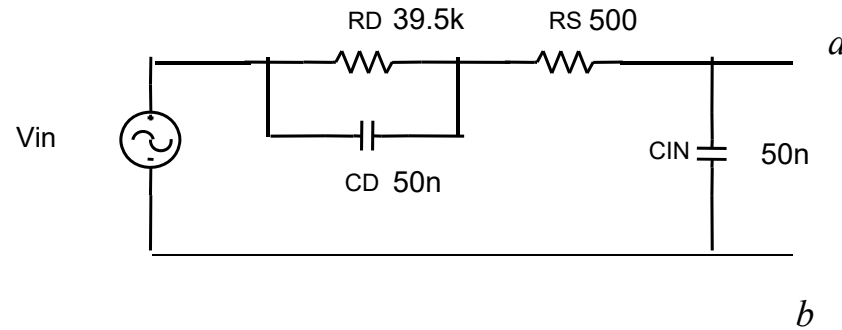2. An electrode is connected to an oscilloscope which has a purely capacitance input impedance, C_{IN} . Find the transfer function of this circuit as function of ω .



Mag

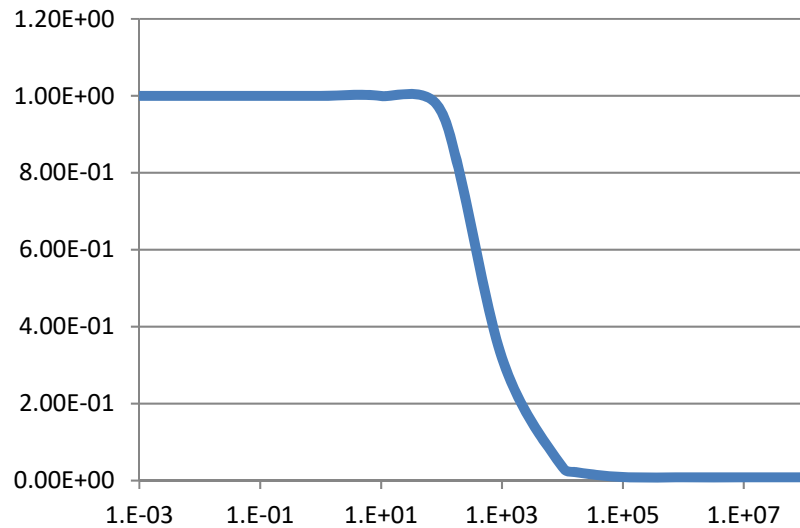

Phase

