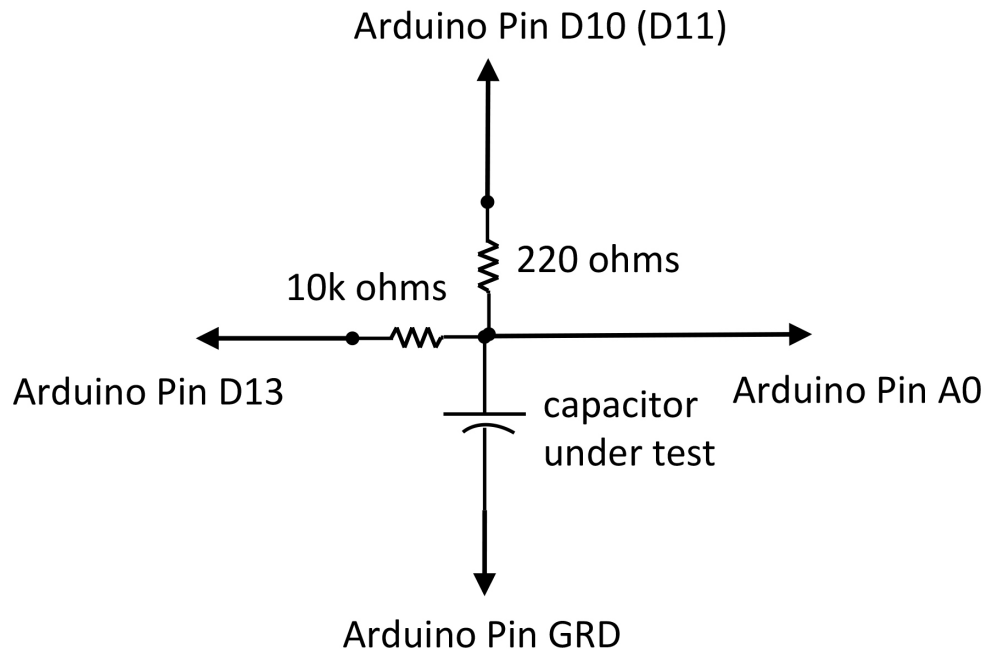


Lab 4 Determining the value of a Capacitor

1. Connect two known resistors (10k and 220) with a capacitor in the following fashion. If you use an electrolytic capacitor that the polarization of voltage applied matches the polarization of the capacitor terminals. **Make sure you connect the 220 ohm resistor to digital pin D11.**



2. Run the sketch from at the end of this document.
3. The way this sketch works
 - a. The Arduino reads the voltage across the capacitor from the Analog pin A0
 - b. The Arduino sets Digital Pin D13 to high to charge the capacitor
 - c. The Arduino reads the voltage of the capacitor to see when 1 time constant has elapsed.
 - d. When 1 time constant has elapsed, knowing that the charging resistor is 10k ohms it calculates the value of the capacitance by dividing the time for 1 time constant.
 - e. It then determines if the capacitor it's units are microfarads or nanofarads.
 - f. It then discharges the capacitor through digital pin 11.

4. Does the Capacitance reading from the sketch the same as the manufacturers designation.
5. Repeat the experiment with 2 different capacitors

Some background

The basic equation of a charging (discharging) capacitor is:

$$v_c(t) = V - Ve^{-\left(\frac{t}{RC}\right)}$$

where V is the voltage it charges to, R is the resistance through which it charges, C is its Capacitance and RC is called it's time constant.

It takes an infinite amount of time to truly charge up

$$v_c(t \rightarrow \infty)|_{\max} = V - Ve^{-\left(\frac{t \rightarrow \infty}{RC}\right)} = V$$

however after a time equivalent to 1 time constant. it reaches 63% of it's final charge.

$$\frac{v_c(t = RC)}{V} = 1 - e^{-1} = 0.63$$

On the Arduino analog inputs range from

0-1023


Therefore, $0.63 \times 1023 =$

646.7 = 647

Elapsed time, $t_{elapsed}$, to reach 648 or 63.2% of 5volts equals the time constant, RC seconds.

$$C = \frac{t_{elapsed}}{R}$$

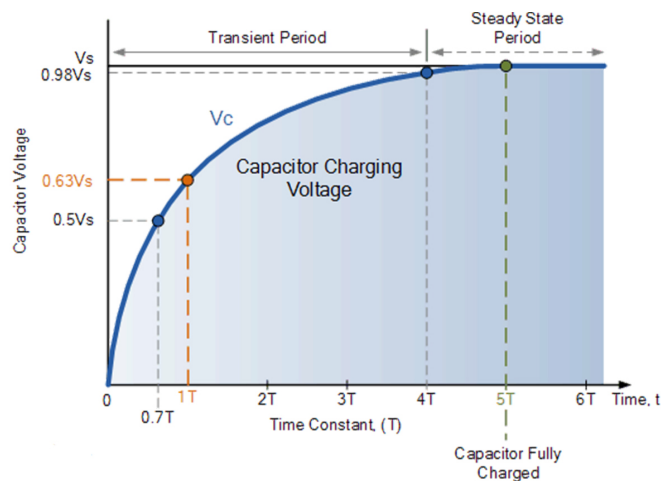That is, when the analog input reaches to 648 one time constant has elapsed.



https://www.electronics-tutorials.ws/rc/rc_1.html

Arduino Sketch

```
/* RCTiming_capacitance_meter
 * Paul Badger 2008
 * Demonstrates use of RC time constants to measure the value of a capacitor
 *
 * Theory A capacitor will charge, through a resistor, in one time constant, defined as T
 seconds where
 *  $TC = R * C$ 
 *
 * TC = time constant period in seconds
 * R = resistance in ohms
 * C = capacitance in farads (1 microfarad (ufd) = .0000001 farad =  $10^{-6}$  farads )
 *
 * The capacitor's voltage at one time constant is defined as 63.2% of the charging
 voltage.
 *
 * Hardware setup:
 * Test Capacitor between common point and ground (positive side of an electrolytic
 capacitor to common)
 * Test Resistor between chargePin and common point
 * 220 ohm resistor between dischargePin and common point
 * Wire between common point and analogPin (A/D input)
 */

#define analogPin 0 // analog pin for measuring capacitor voltage
#define chargePin 13 // pin to charge the capacitor - connected to one end of
the charging resistor
#define dischargePin 11 // pin to discharge the capacitor
#define resistorValue 10000.0F // change this to whatever resistor value you are
using
// F formatter tells compliler it's a floating point value

unsigned long startTime;
unsigned long elapsedTime;
float microFarads; // floating point variable to preserve precision, make
calculations
float nanoFarads;

void setup(){
  pinMode(chargePin, OUTPUT); // set chargePin to output
  digitalWrite(chargePin, LOW);

  Serial.begin(9600); // initialize serial transmission for debugging
}

void loop(){
```

```

digitalWrite(chargePin, HIGH); // set chargePin HIGH and capacitor charging
startTime = millis();

while(analogRead(analogPin) < 648){ // 647 is 63.2% of 1023, which
corresponds to full-scale voltage
}

elapsedTime= millis() - startTime;
// convert milliseconds to seconds ( 10^-3 ) and Farads to microFarads ( 10^-6 ), net
10^3 (1000)
microFarads = ((float)elapsedTime / resistorValue) * 1000;
Serial.print(elapsedTime); // print the value to serial port
Serial.print(" mS "); // print units and carriage return

if (microFarads > 1){
Serial.print((long)microFarads); // print the value to serial port
Serial.println(" microFarads"); // print units and carriage return
}
else
{
// if value is smaller than one microFarad, convert to nanoFarads (10^-9 Farad).
// This is a workaround because Serial.print will not print floats

nanoFarads = microFarads * 1000.0; // multiply by 1000 to convert to
nanoFarads (10^-9 Farads)
Serial.print((long)nanoFarads); // print the value to serial port
Serial.println(" nanoFarads"); // print units and carriage return
}

/* discharge the capacitor */
digitalWrite(chargePin, LOW); // set charge pin to LOW
pinMode(dischargePin, OUTPUT); // set discharge pin to output
digitalWrite(dischargePin, LOW); // set discharge pin LOW
while(analogRead(analogPin) > 0){ // wait until capacitor is completely
discharged
}

pinMode(dischargePin, INPUT); // set discharge pin back to input
}

```