

BME 301

- There are 5 questions to be answered.
- There is a 6th question for extra credit.
- Write neatly and clearly.

Exam 1

1. Action Potential

- a) Simply describe action potential in terms of electrical activity.
- b) What initiates Action Potential?
- c) Describe the 3 main states in terms of electrical activity that occurs for an action potential to be generated.
- d) What effects does Action Potential have on muscles and on nerves.
- e) Sketch the Action Potential, show where the electrical states occur, and what happens to muscles during these states.

2. ECG

- a) How are heart rhythms and blood flow related to action potential? What initiates this?
- b) Discuss the key phases of the heart and how action potential causes these phases to occur.

Exam 1


3. Electrical Basics

- a) Describe the electrical parameters that are required to create a working electrical system.
- b) Describe the rules for these electrical parameters adhere to.
- c) What are the key electrical circuit elements and describe how they function in a circuit. How many of these elements are needed for an electrical circuit to operate.
- d) How must these these elements be connected to support an electrical circuit? What must not be the connection method?

Exam 1

4. Simple Circuitry


- a) In the circuit in part b) what elements are in series and what elements are in parallel with respect to terminals a and b.
- b) Calculate the resistance of the following circuit with respect to terminals a-b where $R_1=10$ ohms; $R_2=R_5=4$ ohms; $R_3=R_4=6$ ohms; $R_6=R_9=2$; $R_7=R_8=6$ ohms and $R_{11}=R_{12}=R_{10}=2$ ohms.

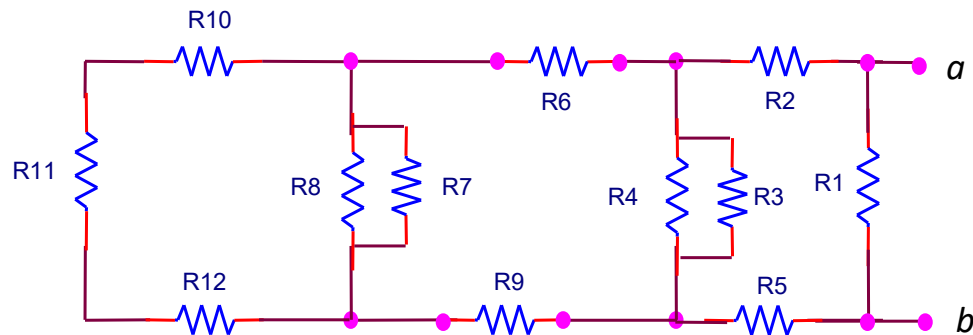

Exam 1

4. Simple Circuitry




- c) Determine the capacitance of the following circuit with respect to terminals a-b.

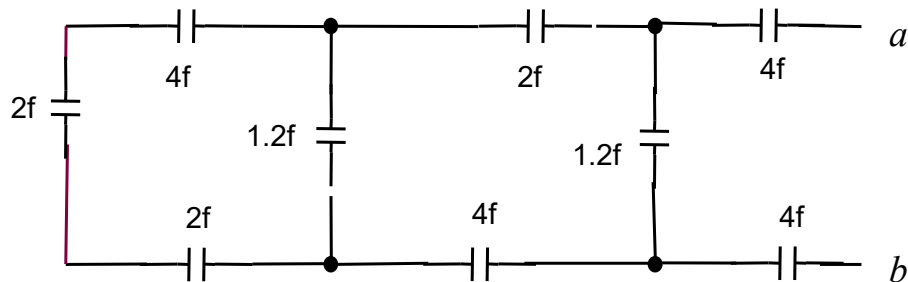

Exam 1

5. Complex circuits


Find the impedance in the simplest polar form of the following circuits with respect to terminals a-b.

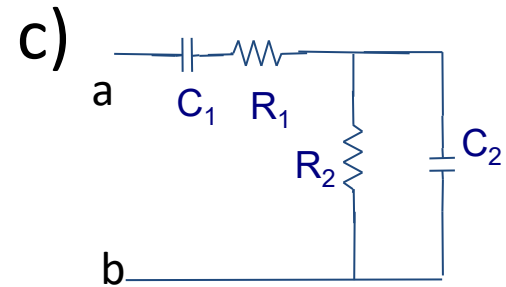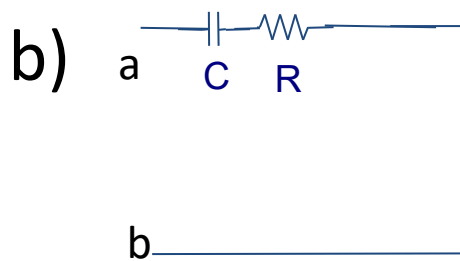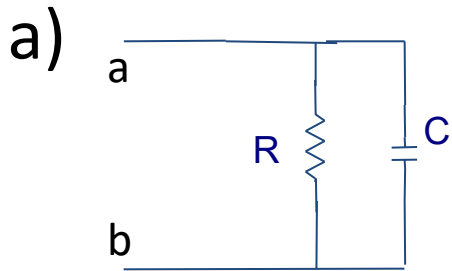

Exam 1

6. Extra Credit

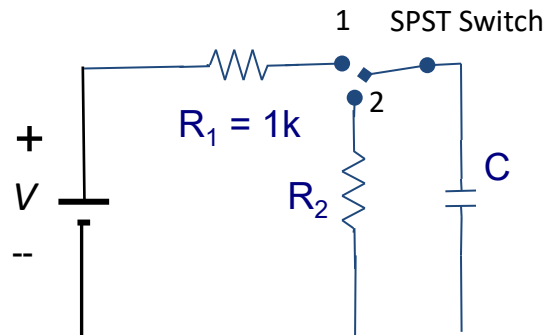- a) Describe what happens when the switch is in position 1
- b) Describe what happens when the switch is in position 2
- c) The switch is in position 1 for 10msec and it is determined that the voltage across the capacitor reaches approximately 63% of its final value. What is the value of the capacitor?
- d) The switch is moved to position 2. What should the value of R_2 be for the capacitor to discharge its voltage 1000 times slower than when it charges?



Exam 1 Answers

1. Action Potential

a) Simply describe action potential in terms of electrical activity.

A change in voltage across a Cell membrane.

b) What initiates Action Potential?

A stimulating voltage such as the action potential of an adjunct cell.

c) Describe the 3 main states in terms of electrical activity that occurs for an action potential to be generated.

Rest state where the voltage across the membrane measured from outside of the cell to the inside of the cell is around -70mv.

Depolarization where the voltage across the cell membrane rises to +30mv due to Na ions flowing into the cell.

Repolarization where the voltage across the cell membrane returns to the Rest State by lowering the voltage across the membrane to -70mv due to K ions flowing out of the cell.


d) What affects does Action Potential have on muscles and on nerves.

For muscles, a contraction of the muscle occurs during Depolarization, and a relaxation of the muscle occurs during Repolarization. For nerve cells, AP causes an electrical signal to be transmitted down the axon.

Exam 1 Answers

1. Action Potential

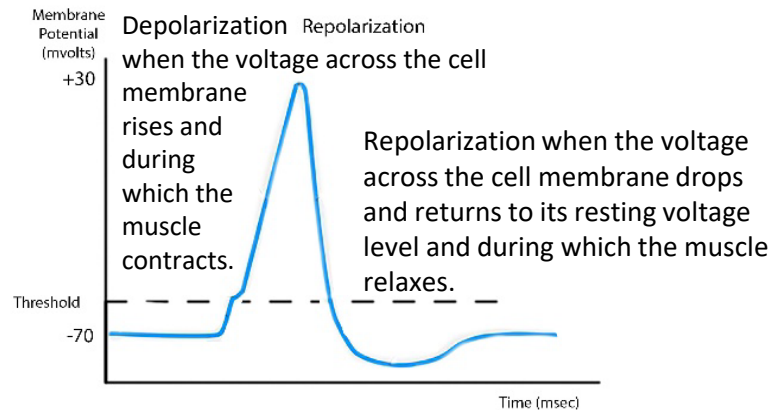- e) Sketch the Action Potential, show where the electrical states occur, and what happens to muscles during these states.



Exam 1 Answers

2. ECG

- a) How are heart rhythms and blood flow related to action potential? What initiates these phases?

The Action Potential causes the chambers to contract and relax causing oxygenated blood to flow into the body and deoxygenated blood to flow into the lungs to receive oxygen.

First the Sinoatrial (SA) node initiates the atria to contract and also sends a signal to the AV node to cause the ventricles to contract. IT then sends a delayed signal to Atrioventricular (AV) node which causes an Action Potential at the muscles of the ventricles to contract (the stimulus to depolarize).

Exam 1 Answers


2. ECG

- b) Discuss the key phases of the heart and how action potential causes these phases to occur.

During the P wave the atria contract (during AP depolarization of the cells in the atria) sending blood to the ventricles. The right atrium receives deoxygenated blood and then sends it to the right ventricle. The left atrium receives oxygenated blood to be sent to the left ventricle.

During the QRS complex the right ventricle contracts (during AP depolarization of the cells in the ventricles) and sends deoxygenated blood to the lungs to obtain oxygen. The left ventricle contracts (during AP depolarization of the cells in the ventricles) and sends oxygenated blood to the body. During this time the atria relax (during AP repolarization of the cells in the atria) but since the signal from the ventricles is large the atria's depolarization signal is not visible.

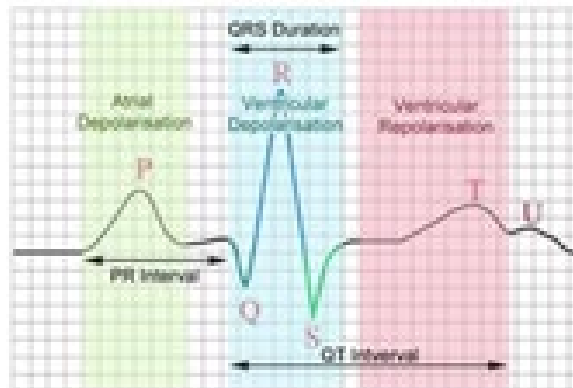During the T wave, the ventricles relax (during AP repolarization of the cells in the ventricles).



Exam 1 Answers

3. Electrical Basics

- a) Describe the electrical parameters that are required to create a working electrical system.

The key electrical parameters are current, the movement or flow of charges and voltage, the force needs to move these charges.

- b) Describe the rules for these electrical parameters adhere to.

Kirchhoff's voltage law (sum of the voltages around a loop must be equal to zero) and Kirchhoff's current law (sum of the currents entering or leaving a node must be equal to zero) .

Exam 1 Answers

3. Electrical Basics

- c) What are the key electrical circuit elements and describe how they function in a circuit. How many of these elements are needed for an electrical circuit to operate.

The 5 linear electrical circuit elements are grouped into active and passive elements.

The active elements are voltage sources and current sources which provides the energy/power to the passive elements.

The passive elements are the resistor which dissipates the energy into heat, the inductor which stores the energy as a magnetic field and the capacitor which stores the energy as an electric field.

There needs to be at least one active element and one passive element.

Exam 1 Answers

3. Electrical Basics

- d) How must these elements be connected to support an electrical circuit? What must not be the connection method?

The active and passive elements must be connected to allow for a closed path for current to flow from the active element, through the passive elements and return to active elements. This is called a closed circuit.


An open circuit where there is no closed path and can not support current flow.

Exam 1 Answers

4. Simple Circuitry

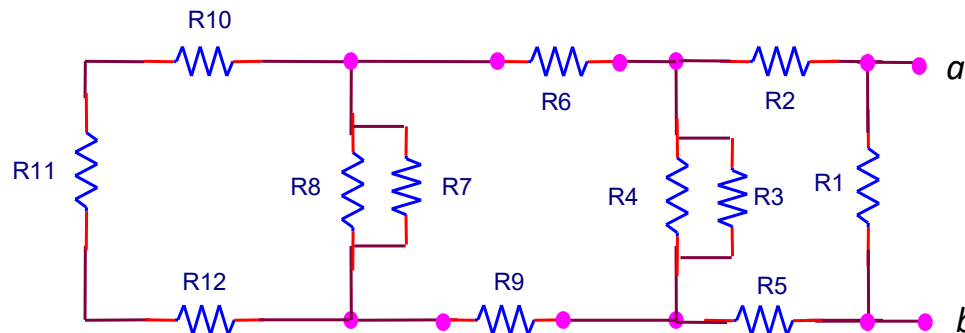- a) In the circuit in part b) what elements are in series and what elements are in parallel with respect to terminals a and b.


STEP 1: R_{10} , R_{11} , and R_{12} are all in series. Call this R_A . STEP 2: R_A is in parallel with R_7 and R_8 . Call this R_B . STEP 3: R_B , R_6 and R_9 are in series; call this R_C . STEP 4: R_C is in parallel with R_4 and R_3 . Call this R_D . STEP 5: R_D is in series with R_2 and R_5 . Call this R_E . Finally STEP 6: R_E is in parallel with R_1 ; call this R_F . R_F is R_{ab} .



Exam 1 Answers

4. Simple Circuitry

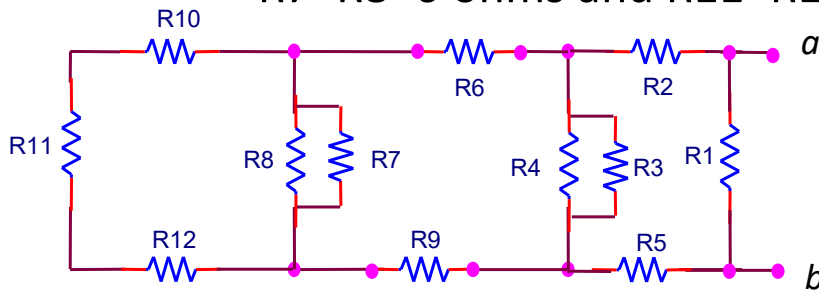
- b) Calculate the resistance of the following circuit with respect to terminals a-b where $R_1=10$ ohms; $R_2=R_5=4$ ohms; $R_3=R_4=6$ ohms, $R_6=R_9=2$; $R_7=R_8=6$ ohms and $R_{11}=R_{12}=R_{10}=2$ ohms.



Step 1

$$R_A = R_{10} + R_{11} + R_{12}$$


$$R_A = 2 + 2 + 2 = 6$$

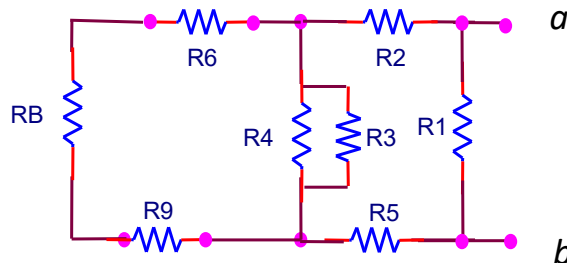

Step 3

$$R_C = R_B + R_6 + R_9$$


$$R_C = 2 + 2 + 2 = 6$$

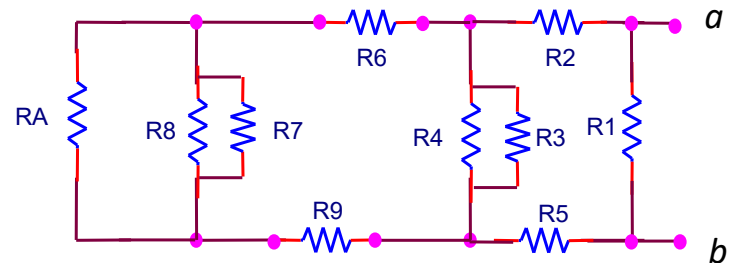

Step 2

$$R_B = R_A \parallel R_7 \parallel R_8$$

$$R_B = 6 \parallel 6 \parallel 6 = 2$$

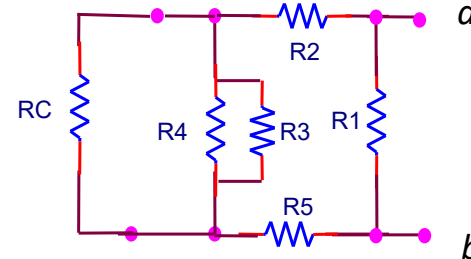

Step 4


$$R_D = R_C \parallel R_4 \parallel R_3$$

$$R_D = 6 \parallel 6 \parallel 6 = 2$$

Exam 1 Answers

4. Simple Circuitry

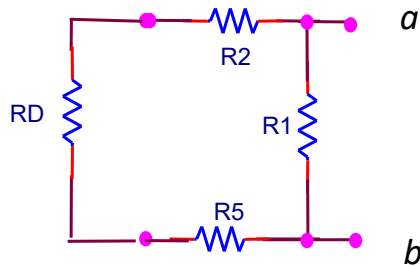
- b) Calculate the resistance of the following circuit with respect to terminals a-b where $R_1=10$ ohms; $R_2=R_5=4$ ohms; $R_3=R_4=6$ ohms, $R_6=R_9=2$; $R_7=R_8=6$ ohms and $R_{11}=R_{12}=R_{10}=2$ ohms.



Step 5

$$R_E = R_D + R_5 + R_2$$

$$R_E = 2 + 4 + 4 = 10$$

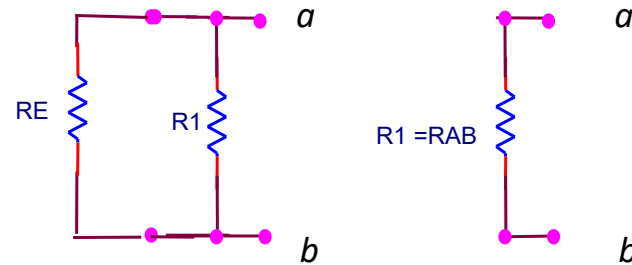

Step 6

$$R_F = R_E \parallel R_1$$


$$R_F = 10 \parallel 10 = 5$$

$$R_{AB} = R_F = 5$$

Exam 1 Answers

4. Simple Circuitry

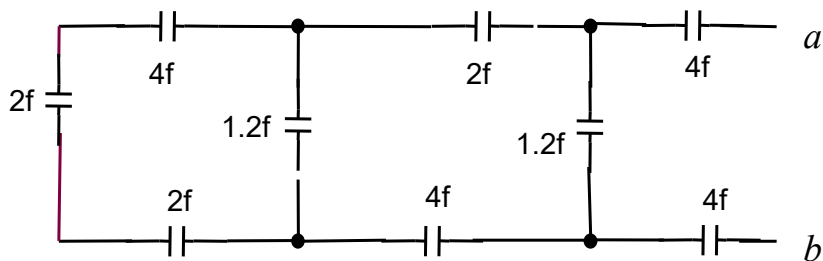c) Determine the capacitance of the following circuit with respect to terminals a-b.



$$CA = 4 \text{ in series } 2 \text{ in series } 2 = \frac{1}{\frac{1}{4} + \frac{1}{2} + \frac{1}{2}} = \frac{4}{5}$$

$$CB = CA \text{ in parallel with } \frac{6}{5} = CA \parallel \frac{6}{5} = \frac{4}{5} \parallel \frac{6}{5} = 2$$

$$CC = CB \text{ in series } 4 \text{ in series } 2 = \frac{1}{\frac{1}{4} + \frac{1}{2} + \frac{1}{2}} = \frac{4}{5}$$




$$CD = CC \text{ in parallel with } \frac{6}{5} = CC \parallel \frac{6}{5} = \frac{4}{5} \parallel \frac{6}{5} = 2$$

$$Cab = CD \text{ in series } 4 \text{ in series } 4 = \frac{1}{\frac{1}{2} + \frac{1}{4} + \frac{1}{4}} = 1$$

Exam 1 Answers

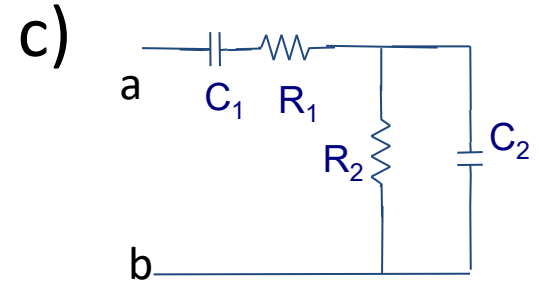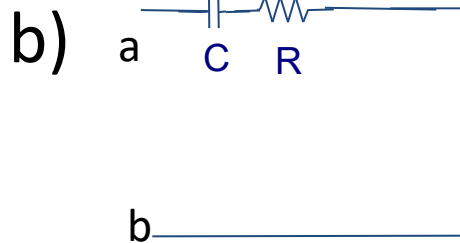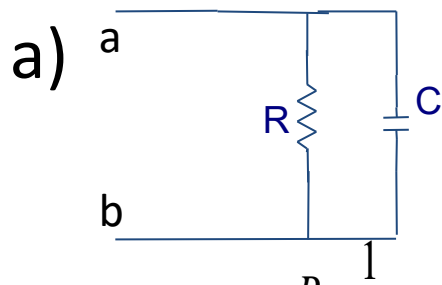5. Complex circuits

Find the impedance in the simplest polar form of the following circuits with respect to terminals a-




$$a) R \parallel \frac{1}{j\omega C} = \frac{R \frac{1}{j\omega C}}{R + \frac{1}{j\omega C}} = \frac{R}{1 + j\omega RC} = \frac{R}{\sqrt{1 + (\omega RC)^2} \angle \tan^{-1}(\omega RC)} = \frac{R}{\sqrt{1 + (\omega RC)^2}} \angle -\tan^{-1}(\omega RC)$$

$$b) R + \frac{1}{j\omega C} = \frac{1 + j\omega RC}{j\omega C} = \frac{\sqrt{1 + (\omega RC)^2} \angle \tan^{-1}(\omega RC)}{\omega C \angle \frac{\pi}{2}} = \frac{\sqrt{1 + (\omega RC)^2}}{\omega C} \angle [\tan^{-1}(\omega RC) - \frac{\pi}{2}]$$

Exam 1 Answers

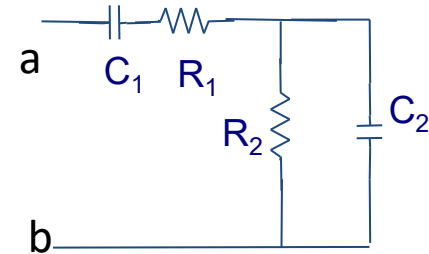5. Complex circuits

Find the impedance in the simplest polar form of the following circuits with respect to terminals a-b.



$$\begin{aligned}
 c) \quad R_1 + \frac{1}{j\omega C_1} + R_2 \parallel \frac{1}{j\omega C_2} &= \frac{1+j\omega R_1 C_1}{j\omega C_1} + \frac{R_2}{1+j\omega R_2 C_2} = \frac{(1+j\omega R_1 C_1)(1+j\omega R_2 C_2) + j\omega R_2 C_1}{j\omega C_1(1+j\omega R_2 C_2)} \\
 &= \frac{1-\omega^2 R_1 C_1 R_2 C_2 + j\omega(R_2 C_2 + R_1 C_1 + R_2 C_1)}{-\omega^2 C_1 R_2 C_2 + j\omega C_1} \\
 &= \frac{\sqrt{(1-\omega^2 R_1 C_1 R_2 C_2)^2 + (\omega(R_2 C_2 + R_1 C_1 + R_2 C_1))^2} \angle \tan^{-1}\left(\frac{\omega(R_2 C_2 + R_1 C_1 + R_2 C_1)}{1-\omega^2 R_1 C_1 R_2 C_2}\right)}{\sqrt{(\omega^2 C_1 R_2 C_2)^2 + (\omega C_1)^2} \angle \tan^{-1}\left(\frac{\omega C_1}{-\omega^2 C_1 R_2 C_2}\right)} \\
 &= \frac{\sqrt{(1-\omega^2 R_1 C_1 R_2 C_2)^2 + (\omega(R_2 C_2 + R_1 C_1 + R_2 C_1))^2}}{\sqrt{(\omega^2 C_1 R_2 C_2)^2 + (\omega C_1)^2}} \angle \tan^{-1}\left(\frac{\omega(R_2 C_2 + R_1 C_1 + R_2 C_1)}{1-\omega^2 R_1 C_1 R_2 C_2}\right) - \angle \tan^{-1}\left(\frac{\omega C_1}{-\omega^2 C_1 R_2 C_2}\right)
 \end{aligned}$$

Exam 1 Answers


6. Extra Credit/Honors

a) Describe what happens when the switch is in position 1

The capacitor charges through R_1 .

b) Describe what happens when the switch is in position 2

The capacitor discharges through R_2 .

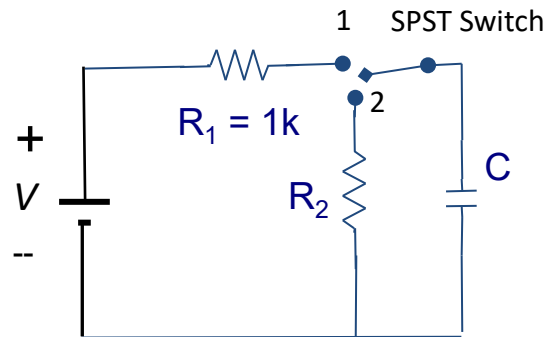

Exam 1 Answers

6. Extra Credit

- c) The switch is in position 1 for 10msec and it is determined that the voltage across the capacitor reaches approximately 63% of its final value. What is the value of the capacitor?

The voltage for a charging capacitor is

$$V_c(t) = V(1 - e^{-\frac{t}{RC}}) = V(1 - e^{-\frac{t}{\tau}}) \text{ where } \tau \text{ is the time constant } RC$$

And 63 percent is when $t_{63\%}$ is:


$$\frac{V(t_{63\%})}{V} = 0.63 = (1 - e^{-\frac{t_{63\%}}{\tau}})$$

$$0.37 = e^{-\frac{t_{63\%}}{\tau}} \Rightarrow \ln 0.37 \cong -1 = -\frac{t_{63\%}}{\tau} \text{ Therefore 63\% is one time constant.}$$

$$t_{63\%} = \tau \text{ or 1 time constant}$$

$$\therefore \tau = RC = 10\text{msec} = 0.010$$
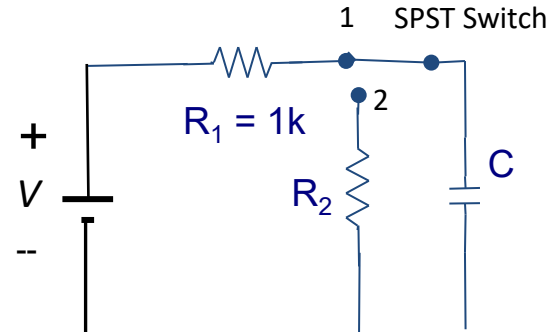
$$\therefore C = \frac{0.01}{1000} = 1 \times 10^{-5} = 10\mu f$$



Exam 1 Answers

6. Extra Credit/Honors

- d) The switch is moved to position 2. What should the value of R_2 be for the capacitor to discharge its voltage 1000 times slower than when it charges?

1000 times slower would make the time constant $= 0.01 \times 1000 = 1 \times 10^{-2} \times 1 \times 10^3 = 10 \text{ sec}$

$$\therefore R_2 C = 10 \Rightarrow R_2 = \frac{10}{1 \times 10^{-5}} = 10^6 = 1 \text{ M}\Omega$$

