

BME 372 New

Lecture #1 Electrical Basics

Circuit Analysis

- Circuit Elements
 - Passive Devices
 - Active Devices
- Circuit Analysis Tools
 - Ohms Law
 - Kirchhoff's Law
 - Impedances
 - Mesh and Nodal Analysis
 - Superposition
- Examples

Characterize Circuit Elements

- **Passive Devices:** dissipates or stores energy
 - Linear
 - Non-linear
- **Active Devices:** Provider of energy or supports power gain
 - Linear
 - Non-linear

Circuit Elements – Linear Passive Devices


- **Linear:** supports a linear relationship between the voltage across the device and the current through it.
 - **Resistor:** supports a voltage and current which are proportional, device dissipates heat, and is governed by Ohm's Law, units: resistance or ohms Ω



$V_R(t) = I_R(t)R$ where R is the value of the resistance associated with the resistor

Circuit Elements – Linear Passive Devices

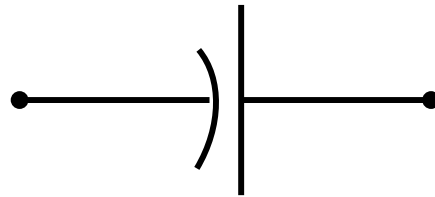- **Capacitor:** supports a current which is proportional to its changing voltage, device stores an electric field between its plates, and is governed by Gauss' Law, units: capacitance or farads, f



$$I_C(t) = C \frac{dV_C(t)}{dt} \text{ where } C \text{ is the value of the capacitance associated with the capacitor}$$

Circuit Elements – Linear Passive Devices

- **Inductor:** supports a voltage which is proportional to its changing current, device stores a magnetic field through its coils and is governed by Faraday's Law, units: inductance or henries, h



$$V_L(t) = L \frac{dI_L(t)}{dt} \text{ where } L \text{ is the value of the inductance associated with the inductor}$$

Circuit Elements - Passive Devices

Continued


- **Non-linear:** supports a non-linear relationship among the currents and voltages associated with it
 - **Diodes:** supports current flowing through it in only one direction

Circuit Elements - Active Devices

- **Linear**


- **Sources**

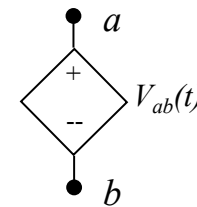- **Voltage Source:** a device which supplies a voltage as a function of time at its terminals which is independent of the current flowing through it, units: Volts



- DC, AC, Pulse Trains, Square Waves, Triangular Waves

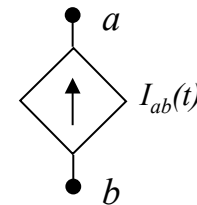- **Current Source:** a device which supplies a current as a function of time out of its terminals which is independent of the voltage across it, units: Amperes
- DC, AC, Pulse Trains, Square Waves, Triangular Waves





Circuit Elements - Active Devices

Continued

– Ideal Sources vs Practical Sources


- An ideal source is one which only depends on the type of source (i.e., current or voltage)
- A practical source is one where other circuit elements are associated with it (e.g., resistance, inductance, etc.)
 - A practical voltage source consists of an ideal voltage source connected in series with passive circuit elements such as a resistor
 - A practical current source consists of an ideal current source connected in parallel with passive circuit elements such as a resistor

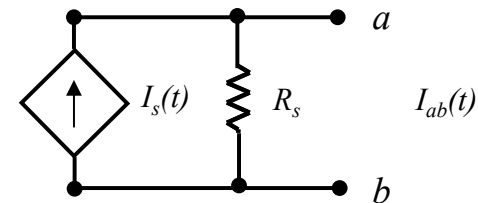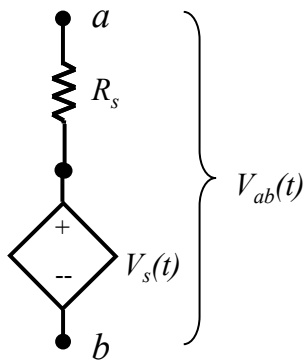


Circuit Elements - Active Devices

Continued

– Independent vs Dependent Sources

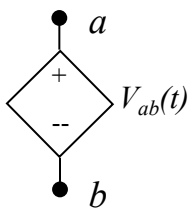

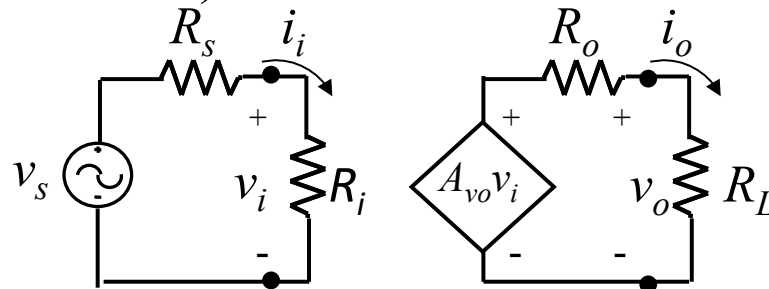- An independent source is one where the output voltage or current is not dependent on other voltages or currents in the device
- A dependent source is one where the output voltage or current is a function of another voltage or current in the device (e.g., a BJT transistor may be viewed as having an output current source which is dependent on the input current)



Circuit Elements - Active Devices Continued

- **Non-Linear**
 - **Transistors:** three or more terminal devices where its output voltage and current characteristics are a function on its input voltage and/or current characteristics, several types BJT, FETs, etc.

Circuits


- A circuit is a grouping of passive and active elements
- Elements may be connecting is series, parallel or combinations of both

Circuits Continued

- Series Connection: Same current through the devices
 - The resultant resistance of two or more Resistors connected in series is the sum of the resistance
 - The resultant inductance of two or more Inductors connected in series is the sum of the inductances
 - The resultant capacitance of two or more Capacitors connected in series is the inverse of the sum of the inverse capacitances
 - The resultant voltage of two or more Ideal Voltage Sources connected in series is the sum of the voltages
 - Two or more Ideal Current sources can not be connected in series

Series Circuits


- Resistors

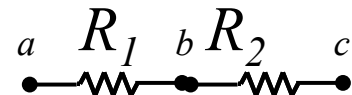

$$V_{ac} = V_{ab} + V_{bc} = IR_1 + IR_2$$

$$R_T = R_1 + R_2 = I(R_1 + R_2) = IR_T$$


- Inductors

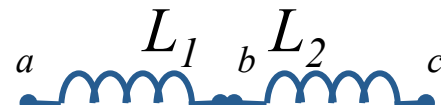

$$V_{ac} = V_{ab} + V_{bc} = L_1 \frac{dI}{dt} + L_2 \frac{dI}{dt}$$

$$L_T = L_1 + L_2 = (L_1 + L_2) \frac{dI}{dt} = L_T \frac{dI}{dt}$$

- Capacitors

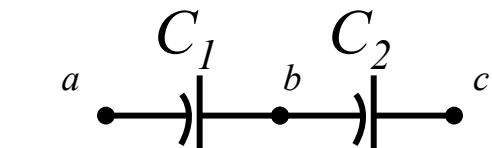


$$V_{ac} = V_{ab} + V_{bc} = \frac{1}{C_1} \int Idt + \frac{1}{C_2} \int Idt$$

$$C_T = \frac{1}{\frac{1}{C_1} + \frac{1}{C_2}} = \frac{C_1 C_2}{C_1 + C_2} = \left(\frac{1}{C_1} + \frac{1}{C_2}\right) \int Idt = \frac{1}{C_T} \int Idt$$

Series Circuits

- Resistors

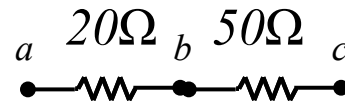


$$R_T = 20 + 50 = 70\Omega$$

$$\begin{aligned} V_{ac} &= V_{ab} + V_{bc} = I20 + I50 \\ &= I(20 + 50) = I70 \end{aligned}$$

Series Circuits

- Inductors

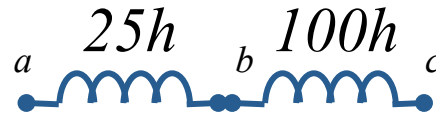


$$L_T = 25 + 100 = 125h$$

$$\begin{aligned} V_{ac} &= V_{ab} + V_{bc} = 25 \frac{dI}{dt} + 100 \frac{dI}{dt} \\ &= (25 + 100) \frac{dI}{dt} = 125 \frac{dI}{dt} \end{aligned}$$

Series Circuits

- Capacitors

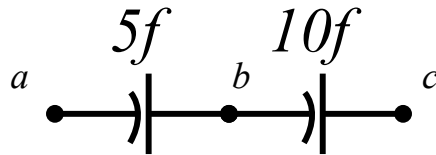


$$C_T = \frac{1}{\frac{1}{5} + \frac{1}{10}} = \frac{5 \times 10}{5 + 10} = \frac{50}{15} = \frac{10}{3} = 3.33 f$$

$$\begin{aligned} V_{ac} &= V_{ab} + V_{bc} = \frac{1}{5} \int Idt + \frac{1}{10} \int Idt \\ &= \left(\frac{1}{5} + \frac{1}{10} \right) \int Idt = \frac{3}{10} \int Idt \end{aligned}$$

Series Circuits

- Capacitors

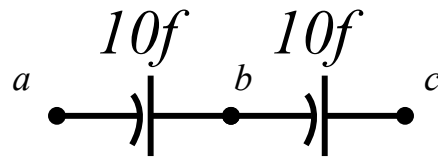

$$C_T = \frac{1}{\frac{1}{10} + \frac{1}{10}} = \frac{10 \times 10}{10 + 10} = \frac{100}{20} = \frac{10}{2} = 5f$$

$$\begin{aligned} V_{ac} &= V_{ab} + V_{bc} = \frac{1}{10} \int Idt + \frac{1}{10} \int Idt \\ &= \left(\frac{1}{10} + \frac{1}{10} \right) \int Idt = \frac{2}{10} \int Idt = \frac{1}{5} \int Idt \end{aligned}$$


Circuits Continued

- Parallel Connection: Same Voltage across the devices
 - The resultant resistance of two or more Resistors connected in parallel is the inverse of the sum of the inverse resistances
 - The resultant inductance of two or more Inductors connected in parallel is the inverse of the sum of the inverse inductances
 - The resultant capacitance of two or more Capacitors connected in parallel is the sum of the capacitances
 - The resultant current of two or more Ideal Current Sources connected in parallel is the sum of the currents
 - Two or more Ideal Voltage sources can not be connected in parallel

Parallel Circuits

- Resistors
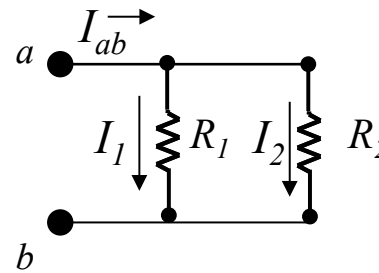
$$R_T = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2}} = \frac{R_1 R_2}{R_1 + R_2}$$




$$I_{ab} = I_1 + I_2 = \frac{V}{R_1} + \frac{V}{R_2}$$

$$= \left(\frac{1}{R_1} + \frac{1}{R_2}\right)V = \frac{V}{R_T}$$

- Inductors
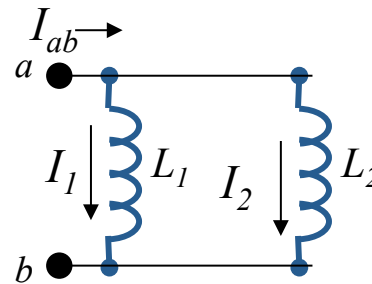
$$L_T = \frac{1}{\frac{1}{L_1} + \frac{1}{L_2}} = \frac{L_1 L_2}{L_1 + L_2}$$




$$I_{ab} = I_1 + I_2 = \frac{1}{L_1} \int V dt + \frac{1}{L_2} \int V dt$$

$$= \left(\frac{1}{L_1} + \frac{1}{L_2}\right) \int V dt = \frac{1}{L_T} \int V dt$$

- Capacitors

$$C_T = C_1 + C_2$$

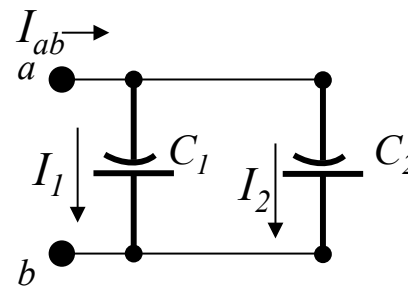

$$I_{ab} = I_1 + I_2 = C_1 \frac{dV}{dt} + C_2 \frac{dV}{dt}$$

$$= (C_1 + C_2) \frac{dV}{dt} = C_T \frac{dV}{dt}$$

Combining Circuit Elements

Kirchhoff's Laws

- Kirchhoff Voltage Law: The sum of the voltages around a loop must equal zero
- Kirchhoff Current Law: The sum of the currents leaving (entering) a node must equal zero


Combining Rs, Ls and Cs

- We can use KVL or KCL to write and solve an equation associated with the circuit.
 - Example: a series Resistive Circuit

Using KVL

$$V(t) = I(t)R_1 + I(t)R_2$$

$$V(t) = I(t)(R_1 + R_2)$$

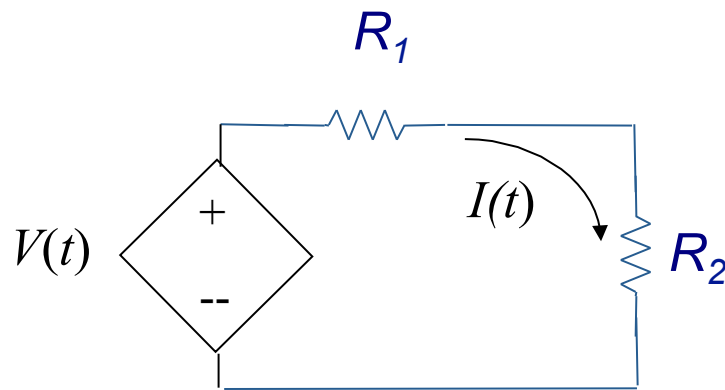

Combining Rs, Ls, and Cs

- We can use KVL or KCL to write and solve an equation associated with the circuit.
 - Example: a series Resistive Circuit

Using KCL:


$$I_1 + I_2 + I_3 = 0 \Rightarrow I_1 = -I_2 - I_3$$

But

$$I_2 = -\frac{V(t)}{R_1}; I_3 = -\frac{V(t)}{R_2}$$

Therefore,
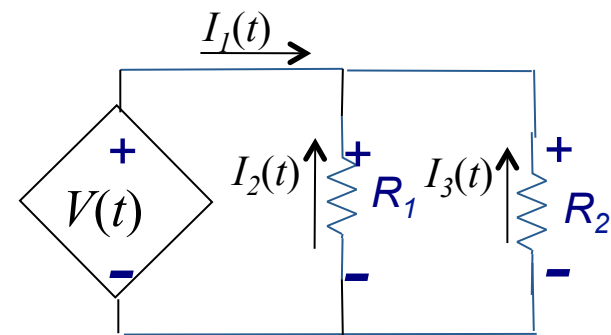
$$I_1 = -I_2 - I_3 = \frac{V(t)}{R_1} + \frac{V(t)}{R_2} = \left[\frac{1}{R_1} + \frac{1}{R_2} \right] V(t)$$



Impedances

- Our special case, signals of the form: $V(t)$ or $I(t) = Ae^{st}$ where s can be a real or complex number


$$V(t) = I(t)R_1 + L_1 \frac{dI(t)}{dt} + \frac{1}{C_1} \int I(t) dt$$

Let's assume:

$$V(t) = 10e^{5t}; R_1 = 10\Omega; L_1 = 5h; C_1 = .2f$$

Let's try:

$$I(t) = Ae^{5t}$$

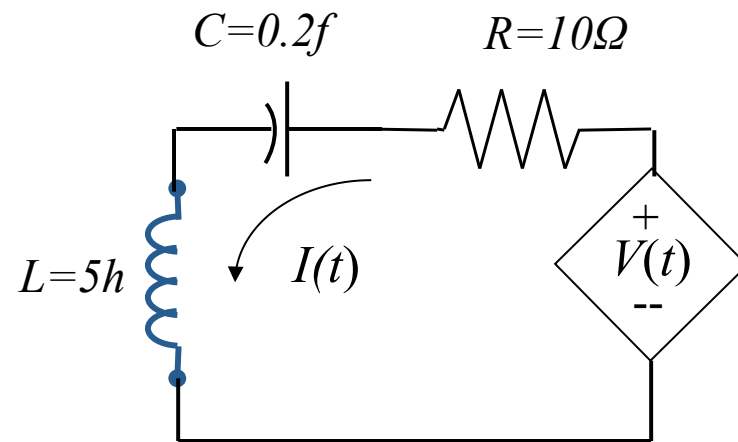

- This is only one portion of the solution and does not include the transient response.

Impedances


- Our special case, signals of the form: $V(t)$ or $I(t) = Ae^{st}$ where s can be a real or complex number

$$10e^{5t} = I(t)10 + 5\frac{dI(t)}{dt} + \frac{1}{.2}\int I(t)dt$$

$$10e^{5t} = Ae^{5t}10 + 5\frac{dAe^{5t}}{dt} + 5\int Ae^{5t}dt$$

$$10e^{5t} = A(e^{5t}10 + 5 \times 5e^{5t} + \frac{5e^{5t}}{5})$$
$$= A(e^{5t}36)$$

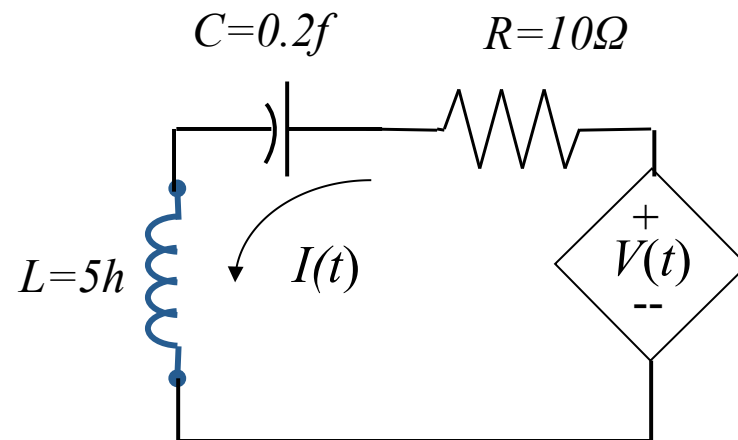
$$A = \frac{10}{36}; I(t) = \frac{10}{36}e^{5t}$$



- This is only one portion of the solution and does not include the transient response.

Impedances

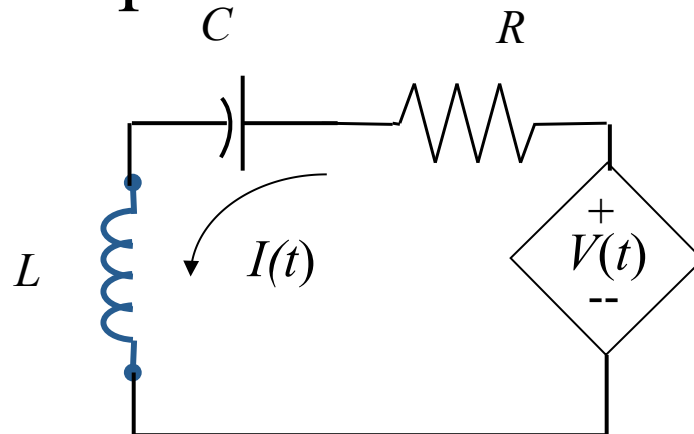- Since the derivative [and integral] of $Ae^{st} = sAe^{st}$ [$= (1/s)Ae^{st}$], we can define the impedance of a circuit element as $Z(s) = V/I$ where Z is only a function of s since the time dependency drops out.



Impedances

For an inductor, let's assume $I(t) = Ae^{st}$;

$$\text{then } V_L(t) = L \frac{dI(t)}{dt} = LsAe^{st};$$

$$Z(s) = \frac{V_L}{I} = \frac{sLAe^{st}}{Ae^{st}} = sL$$

For a capacitor, let's assume $V(t) = Ae^{st}$;



$$\text{then } I(t) = C \frac{dV_C(t)}{dt} = CsAe^{st};$$

$$Z(s) = \frac{V_C}{I} = \frac{Ae^{st}}{sCAe^{st}} = \frac{1}{sC}$$

For a resistor, let's assume $I(t) = Ae^{st}$;

$$\text{then } V_R(t) = RI(t) = RAe^{st};$$
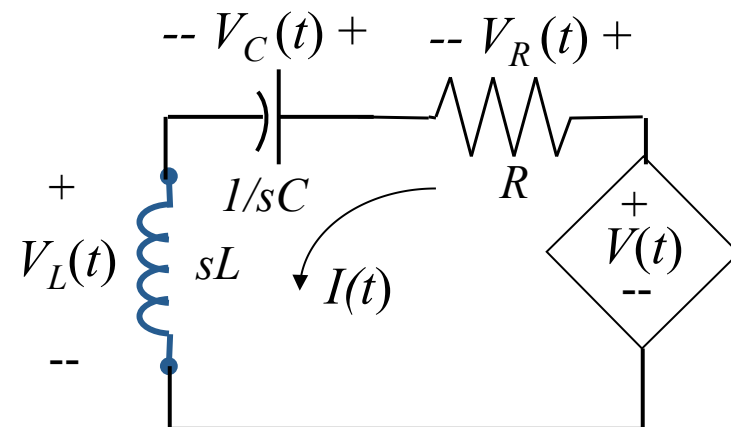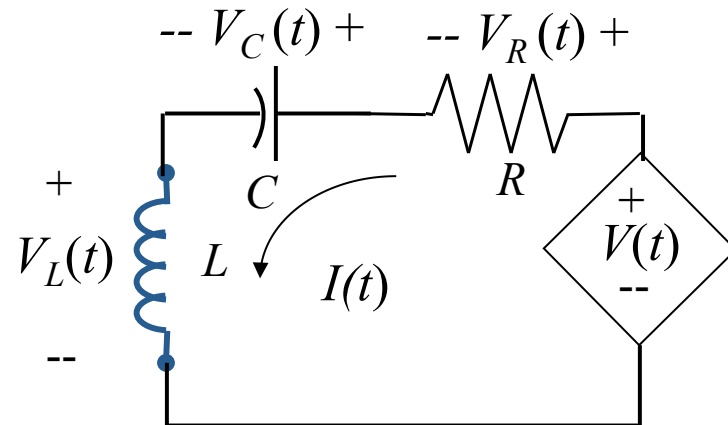
$$Z(s) = \frac{V_R}{I} = \frac{RAe^{st}}{Ae^{st}} = R$$






Impedances

- What about signals of the type: $\cos(\omega t + \theta)$;
- Recall Euler's formula $e^{j\theta} = \cos \theta + j \sin \theta$
where j is the imaginary number $= \sqrt{-1}$
- A special case of our special case is for sinusoidal inputs, where $s = j\omega$

Sinusoidal Steady State Continued

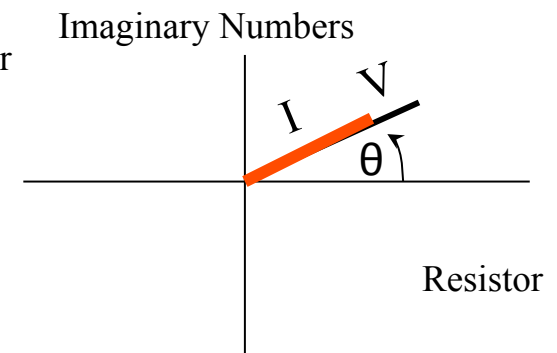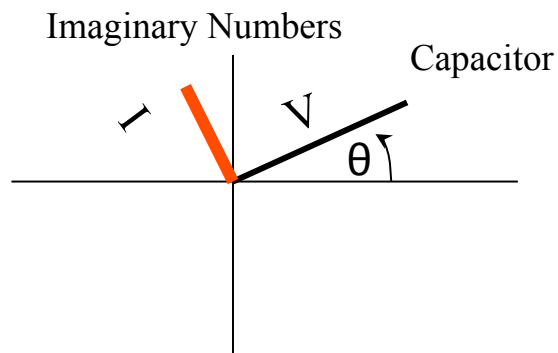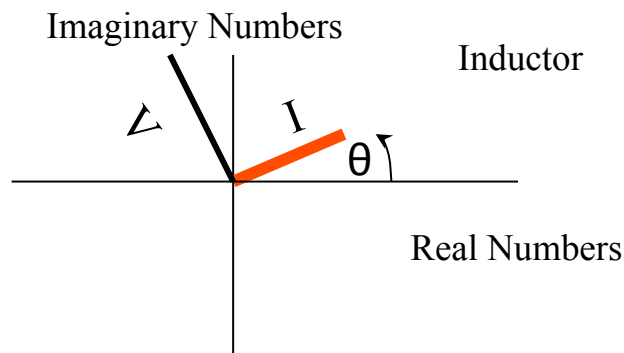- For an inductor, $Z_L = j\omega L \Rightarrow \omega L \angle \frac{\pi}{2}$
- For a capacitor, $Z_C = \frac{1}{j\omega C} \Rightarrow \frac{1}{\omega C} \angle -\frac{\pi}{2}$.
- For a resistor, $Z_R = R \Rightarrow R \angle 0$




Sinusoidal Steady State Continued

For $V(t) = A \cos \omega t$, using phasor notation for $V(t) \rightarrow \mathbf{V} = A \angle 0$ and $I(t) \rightarrow \mathbf{I}$, our equation can be re-written:

$$V(t) = I(t)R_1 + L_1 \frac{dI(t)}{dt} + \frac{1}{C_1} \int I(t) dt$$

Converting to Phasor representation
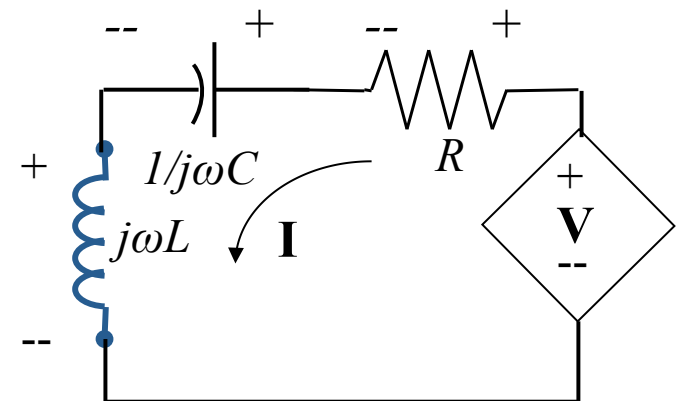
$$\mathbf{V} = A \angle 0 = \mathbf{I}R_1 + j\omega L_1 \mathbf{I} + \frac{1}{j\omega C_1} \mathbf{I}$$



Sinusoidal Steady State Continued

$$\mathbf{I} = \frac{A\angle 0}{R_1 + j\omega L_1 + \frac{1}{j\omega C_1}} = \frac{A\angle 0}{R_1 + j(\omega L_1 - \frac{1}{\omega C_1})} = \frac{A}{\sqrt{R_1^2 + (\omega L_1 - \frac{1}{\omega C_1})^2}} \angle -\tan^{-1}\left[\frac{(\omega L_1 - \frac{1}{\omega C_1})}{R_1}\right]$$

Converting back to the time representation,

$$I(t) = \frac{A}{\sqrt{R_1^2 + (\omega L_1 - \frac{1}{\omega C_1})^2}} \cos(\omega t - \tan^{-1}\left[\frac{(\omega L_1 - \frac{1}{\omega C_1})}{R_1}\right])$$



Bode Plots

- Plotting the magnitude and phase versus frequency.

$$\mathbf{I} = \frac{A}{\sqrt{R_1^2 + (\omega L_1 - \frac{1}{\omega C_1})^2}} \angle -\tan^{-1}\left[\frac{(\omega L_1 - \frac{1}{\omega C_1})}{R_1}\right]$$

$$\text{Magnitude of I} \Rightarrow |\mathbf{I}| = \frac{A}{\sqrt{R_1^2 + (\omega L_1 - \frac{1}{\omega C_1})^2}}$$
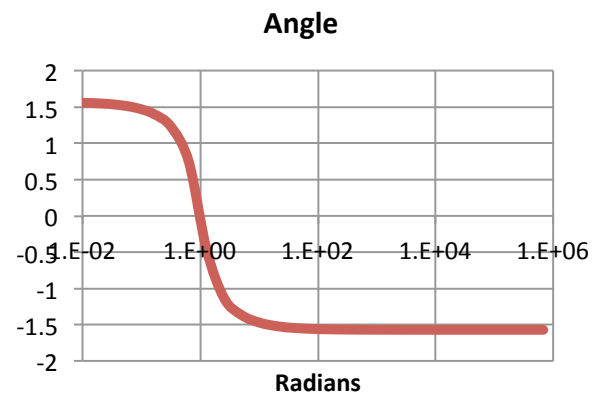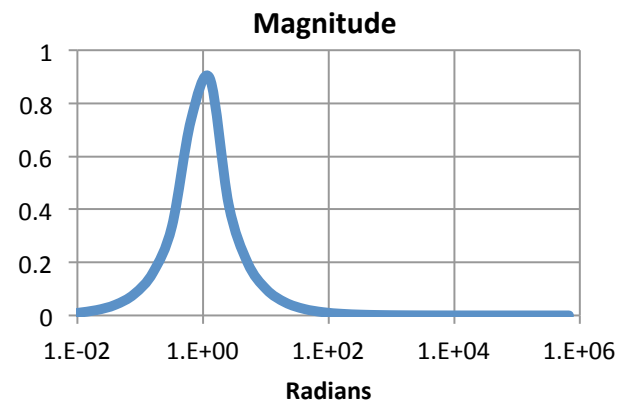
$$\text{Angle of I} \Rightarrow \angle \mathbf{I} = \angle -\tan^{-1}\left[\frac{(\omega L_1 - \frac{1}{\omega C_1})}{R_1}\right]$$



Bode Plots

- Easy way to plot the magnitude.

$$\mathbf{I} = \frac{A}{R_1 + j\omega L_1 + \frac{1}{j\omega C_1}}$$

First evaluate at the initial condition $\omega=0$

$$\mathbf{I}|_{\omega=0} = \frac{A}{R_1 + j\omega L_1 + \frac{1}{j\omega C_1}} \Big|_{\omega=0} \rightarrow \frac{A}{R_1 + j0L_1 + \frac{1}{j0C_1}} \xrightarrow{\text{Determine the dominate terms}} \frac{A}{\frac{1}{j0C_1}} \rightarrow j\frac{A}{\infty} \rightarrow 0 \angle \frac{\pi}{2}$$

Next evaluate at the final condition $\omega \rightarrow \infty$


$$\mathbf{I}|_{\omega \rightarrow \infty} = \frac{A}{R_1 + j\omega L_1 + \frac{1}{j\omega C_1}} \Big|_{\omega \rightarrow \infty} \rightarrow \frac{A}{R_1 + j\infty L_1 + \frac{1}{j\infty C_1}} \xrightarrow{\text{Determine the dominate terms}} \frac{A}{j\infty L_1} \rightarrow -j\frac{A}{\infty} \rightarrow 0 \angle -\frac{\pi}{2}$$

Find an interesting point; for this example choose $\omega = \omega_0 = \frac{1}{\sqrt{LC}}$ since this is when the imaginary part of the denominator is zero.


$$\mathbf{I}|_{\omega_0 = \frac{1}{\sqrt{LC}}} = \frac{A}{R_1 + j\omega L_1 + \frac{1}{j\omega C_1}} \Big|_{\omega_0 = \frac{1}{\sqrt{LC}}} = \frac{A}{R_1 + j\left(\frac{1}{\sqrt{LC}}L_1 - \frac{1}{\frac{1}{\sqrt{LC}}C_1}\right)} = \frac{A}{R_1 + j\left(\sqrt{\frac{L_1}{C_1}} - \frac{1}{\sqrt{\frac{C_1}{L_1}}}\right)} = \frac{A}{R_1} = \frac{A}{R_1} \angle 0$$

Bode Plots

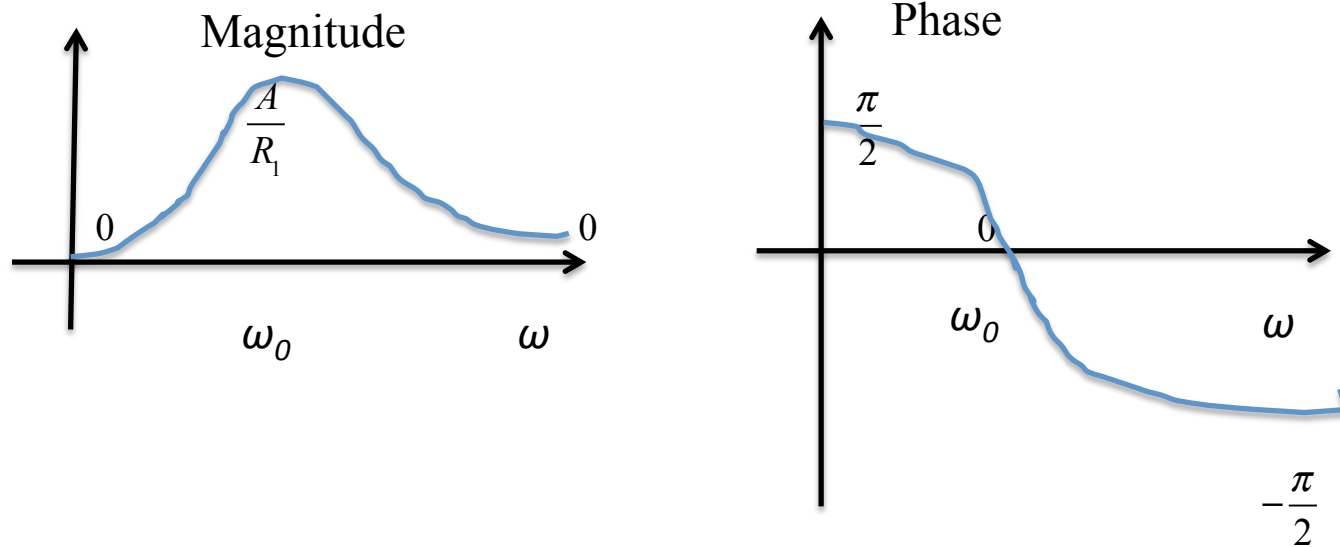- With the three point, plots can be made



Homework

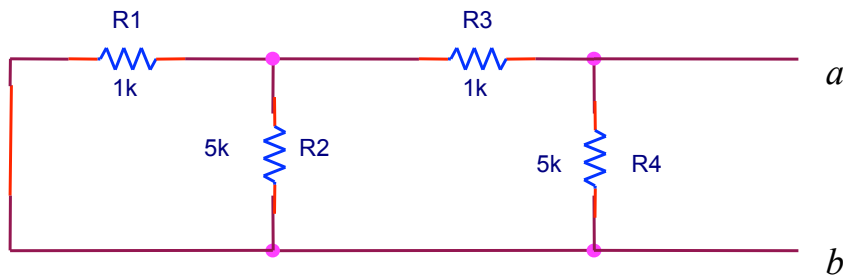


Find the total resistance

Homework

Find the total resistance R_{ab} where

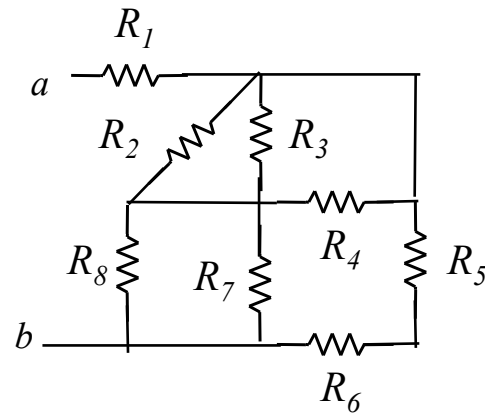
$$R_1 = 3\Omega, R_2 = 6\Omega, R_3 = 12\Omega, R_4 = 4\Omega, R_5 = 2\Omega, R_6 = 2\Omega, R_7 = 4\Omega, R_8 = 4\Omega$$



Homework


Find the total resistance R_{ab} where
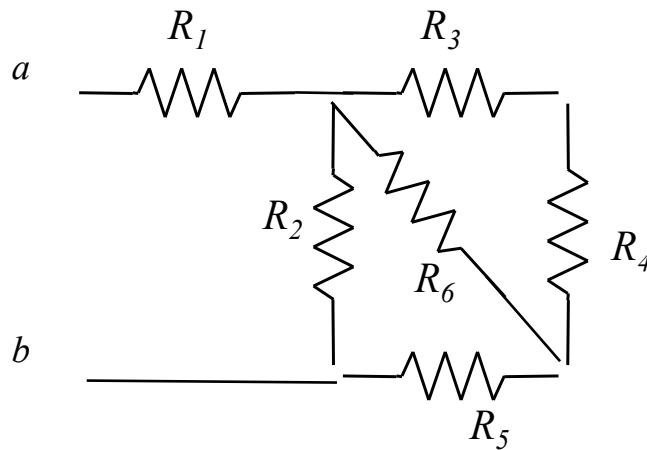
$$R_1 = 2\Omega, R_2 = 4\Omega, R_3 = 2\Omega, R_4 = 2\Omega, R_5 = 2\Omega, R_6 = 4\Omega,$$




Homework

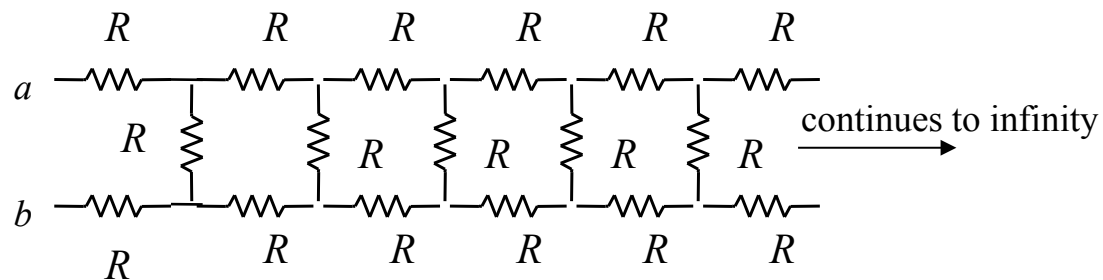Find the total resistance R_{ab} for this infinite resistive network




Homework

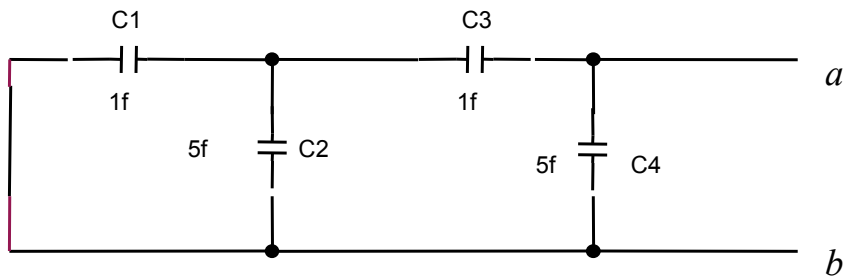

Find the total capacitance


Homework

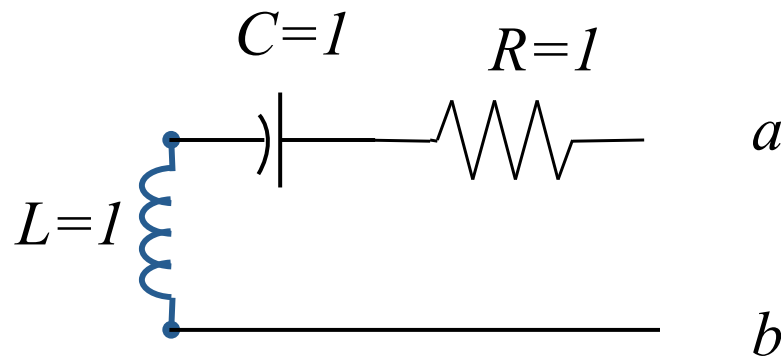Find and plot the impedance $Z_{ab}(j\omega)$ as a function of frequency. Use Matlab to calculate the Bode plot.




Homework

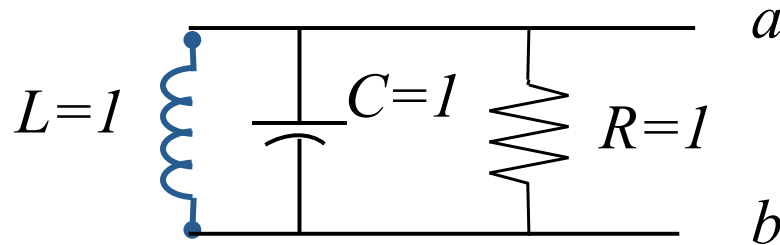Find and plot the impedance $Z_{ab}(j\omega)$ as a function of frequency. Use Matlab to calculate the Bode plot.



Homework

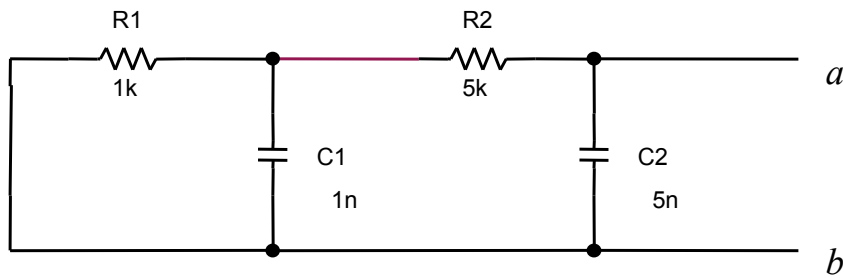

Find and plot the impedance $Z_{ab}(j\omega)$ as function of ω .
Use Matlab to calculate the Bode plot.