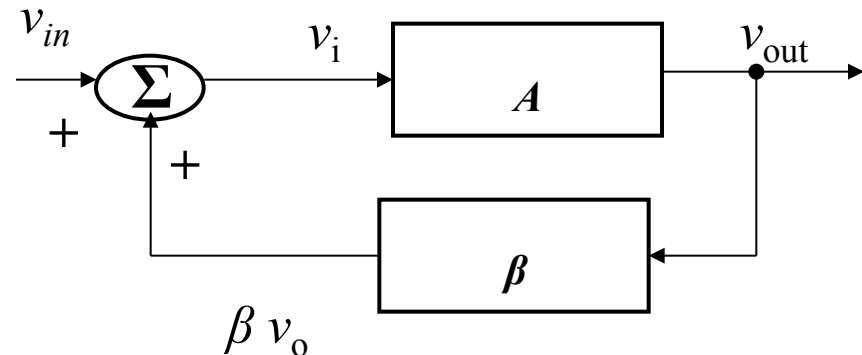


Schmitt Triggers Circuits

Lecture 12

Effects of Positive Feedback


- From this circuit: $v_o = Av_i$ and $v_i = v_f - v_{in} = \beta v_o - v_{in}$
- Because of the positive feedback v_i is no longer equal to zero (not a virtual ground)
- So as v_i increases in the positive (negative) direction, increases in the positive (negative) direction.
- Because of the positive feedback, this will increase v_i in the positive direction (negative) which will further increase v_o which further increase v_i and so on.
- When will this stop?



- If we had infinite power, then never.
- However, we have limited power which is given by the amplifier's DC voltage supplies: $+A$, $-A$.
- If v_i goes positive, then v_o “instantaneously” grows to $+A$ volts
- And if v_i goes negative, then v_o “instantaneously” grows to $-A$ volts

Hysteresis

- Assume that $\beta = R_2 / (R_1 + R_2) = 0.1$ and v_o levels are $+10$ (for $v_i > 0$) and -10 V (for $v_i < 0$).
- First, note that $v_i = v_f - v_{in}$. Now, let's assume $v_o = +10$ V and therefore $v_f = 1$ V then as long as v_{in} is less than 1 V, then $v_o = +10$ V (it's high state) since v_i , the input to the comparator, will be > 0 . Once v_{in} surpasses 1 , $v_i < 0$, and the output will switch to -10 V.
- At this point, $v_f = -1$ V and as long as the $v_{in} > -1$ V, the output will stay in its low state, -10 V.
- Note that has the characteristic of being a flip-flop. If one pulses it with high (> 1), then the output switches to a low and visa versa.

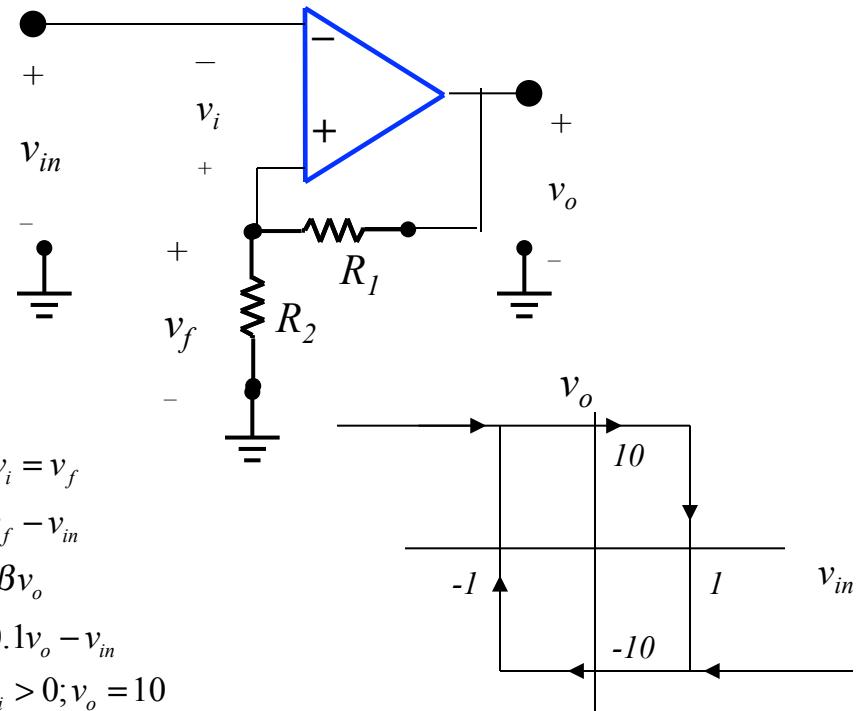

$$v_{in} + v_i = v_f$$

$$v_i = v_f - v_{in}$$

$$v_f = \beta v_o$$

$$v_i = 0.1v_o - v_{in}$$

$$\text{For } v_i > 0; v_o = 10$$

$$v_i = 0.1 \times 10 - v_{in} > 0 \Rightarrow 1 - v_{in} > 0 \Rightarrow 1 > v_{in}$$

$$v_{in} < 1$$

$$\text{For } v_i < 0; v_o = -10$$

$$v_i = 0.1v_o - v_{in} < 0 \Rightarrow -0.1 \times 10 - v_{in} < 0 \Rightarrow -1 < v_{in}$$

$$v_{in} > -1$$

This is characteristic is called **hysteresis**

Inverter

$$v_{in} + v_i = v_f$$

$$v_i = v_f - v_{in}$$

$$v_f = \beta v_o$$

$$v_i = \beta v_o - v_{in}$$

For $v_i > 0; v_o = A$

$$v_i = \beta v_o - v_{in} > 0 \Rightarrow \beta A - v_{in} > 0 \Rightarrow \beta A > v_{in}$$



$$v_{in} < \beta A$$

For $v_i < 0; v_o = -A$

$$v_i = \beta v_o - v_{in} < 0 \Rightarrow -\beta A - v_{in} < 0 \Rightarrow -\beta A < v_{in}$$


$$v_{in} > -\beta A$$

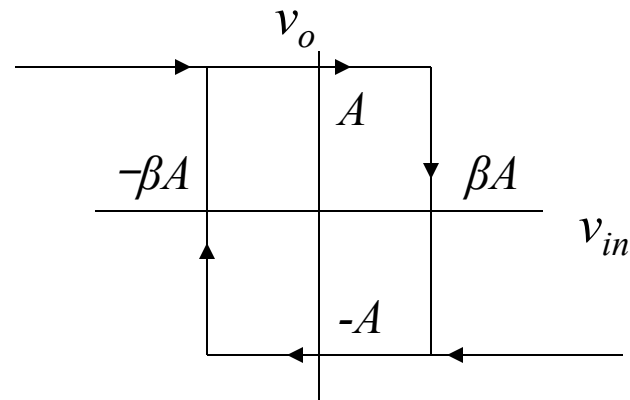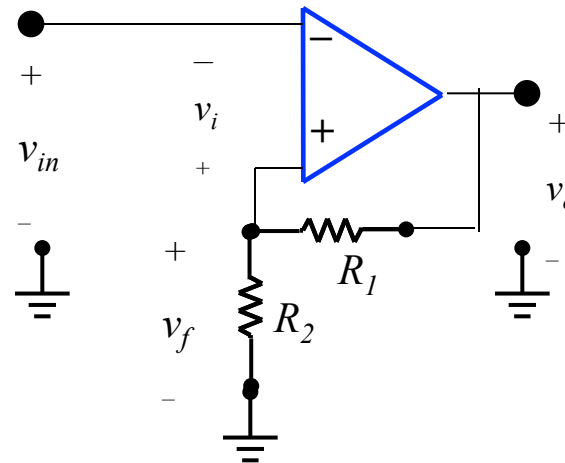Note that $\pm \beta A$ volts are the thresholds for when the circuit switches states.




Other Forms of Schmitt Triggers

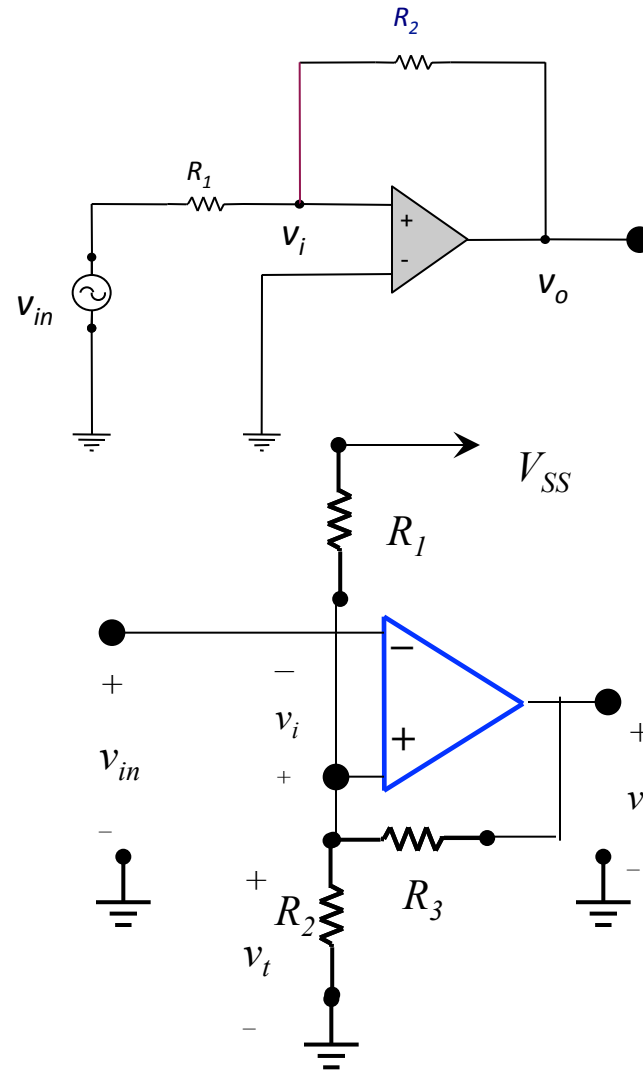- Non-inverting types
- Specified Thresholds



Specific Thresholds

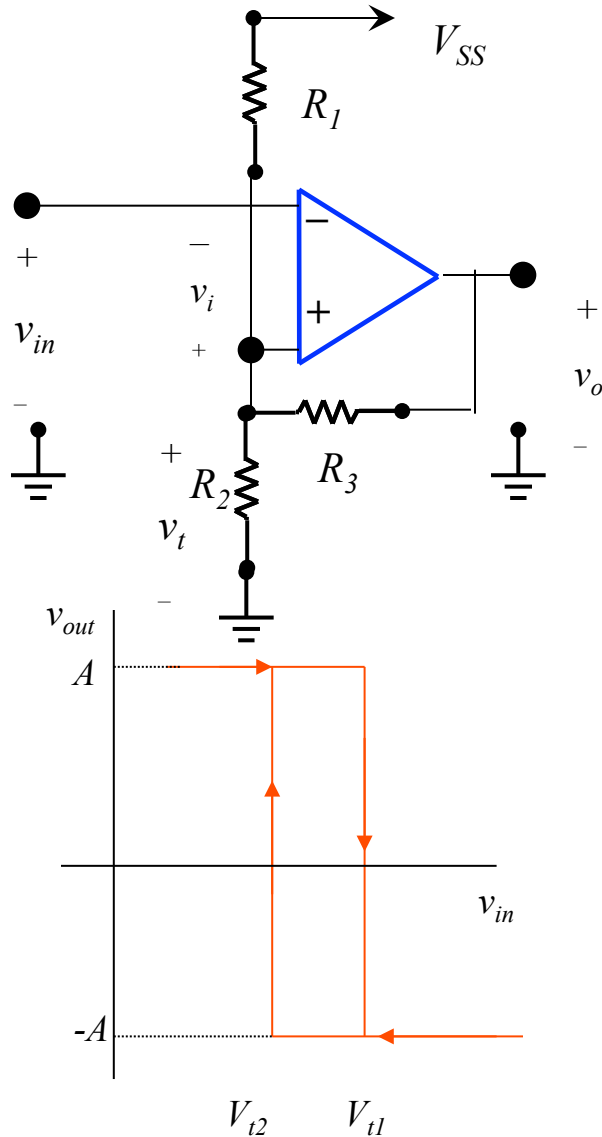

$$v_i = v_t - v_{in}$$

$$v_i > 0; v_o = +A$$

$$v_i < 0; v_o = -A$$

From node at noninverting input:

$$\frac{v_t}{R_2} + \frac{v_t - v_o}{R_3} + \frac{v_t - V_{SS}}{R_1} = 0$$

$$v_t = \frac{\frac{v_o}{R_3} + \frac{V_{SS}}{R_1}}{\frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_1}} = \frac{\frac{v_o}{R_3} + \frac{V_{SS}}{R_1}}{G_T} = \frac{v_o}{G_T R_3} + \frac{V_{SS}}{G_T R_1}$$


$$v_i = \frac{v_o}{G_T R_3} + \frac{V_{SS}}{G_T R_1} - v_{in}$$

$$v_i = \frac{A}{G_T R_3} + \frac{V_{SS}}{G_T R_1} - v_{in} > 0; v_{in} < V_{t1} = \frac{A}{G_T R_3} + \frac{V_{SS}}{G_T R_1}$$

$$v_i = \frac{-A}{G_T R_3} + \frac{V_{SS}}{G_T R_1} - v_{in} < 0; v_{in} > V_{t2} = \frac{-A}{G_T R_3} + \frac{V_{SS}}{G_T R_1}$$

An Example

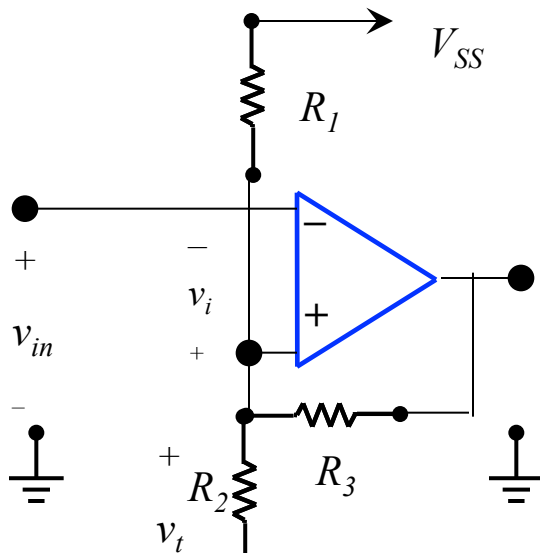- Choose the 3 resistors to provide thresholds of 5 ± 0.1 V for output levels of ± 14.6 V.



At the non - inverting mode, we have :

$$\frac{V_t}{R_2} + \frac{V_t - V_{SS}}{R_1} + \frac{V_t - v_o}{R_3} = 0$$

Using 15 V for V_{SS} and $V_t = 5.1$ for $v_o = +14.6$, we have

$$\frac{5.1}{R_2} + \frac{5.1 - 15}{R_1} + \frac{5.1 - 14.6}{R_3} = \frac{5.1}{R_2} + \frac{9.9}{R_1} + \frac{9.5}{R_3} = 0$$

Using $V_t = 4.9$ for $v_o = -14.6$, we have

$$\frac{4.9}{R_2} + \frac{4.9 - 15}{R_1} + \frac{4.9 + 14.6}{R_3} = \frac{4.9}{R_2} + \frac{10.1}{R_1} + \frac{19.5}{R_3} = 0$$

- We need to choose one of the 3 resistors. If we choose $R_3 = 1$ M, then $R_1 = 20.55$ k and $R_2 = 10.38$ k. If we chose resistors too small then may draw excessive amounts of current from our 15 V supply and create a large power drain on the circuit.

Example contintued

$$v_i = v_t - v_{in}$$

when $v_i > 0$; $v_o = +14.6v$

therefore,

$$v_i = v_t - v_{in} > 0$$

$$v_t > v_{in}; \text{ or } v_{in} < 5.1$$


$$v_i = v_t - v_{in}$$

when $v_i < 0$; $v_o = -14.6v$

therefore,

$$v_i = v_t - v_{in} < 0$$
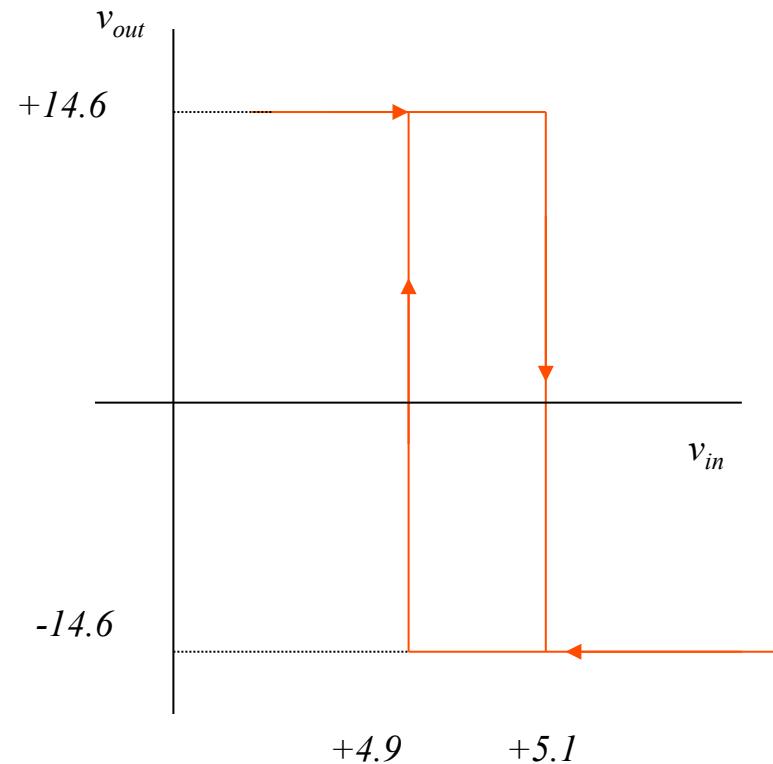
$$v_t < v_{in}; \text{ or } v_{in} > 4.9$$



Another Example

- What are the transfer characteristics for this circuit if $R_1=1k$ and $R_2=2k$ and the thresholds levels are ± 10 V.

$$V_{in} = i(R_1 + R_2) + v_o$$

$$V_t = iR_1 = \frac{V_{in} - v_o}{R_1 + R_2} R_1$$

$$v_i = V_{in} - V_t = V_{in} - \frac{V_{in} - v_o}{R_1 + R_2} R_1$$


$$v_i = V_{in} - \frac{V_{in} - v_o}{3} = \frac{2}{3}V_{in} + \frac{v_o}{3}$$

For $v_o = +10$ V, $v_i > 0$

$$v_i = \frac{2}{3}V_{in} + \frac{v_o}{3} > 0; \frac{2}{3}V_{in} > -\frac{v_o}{3}; V_{in} > -5$$

For $v_o = -10$ V, $v_i < 0$
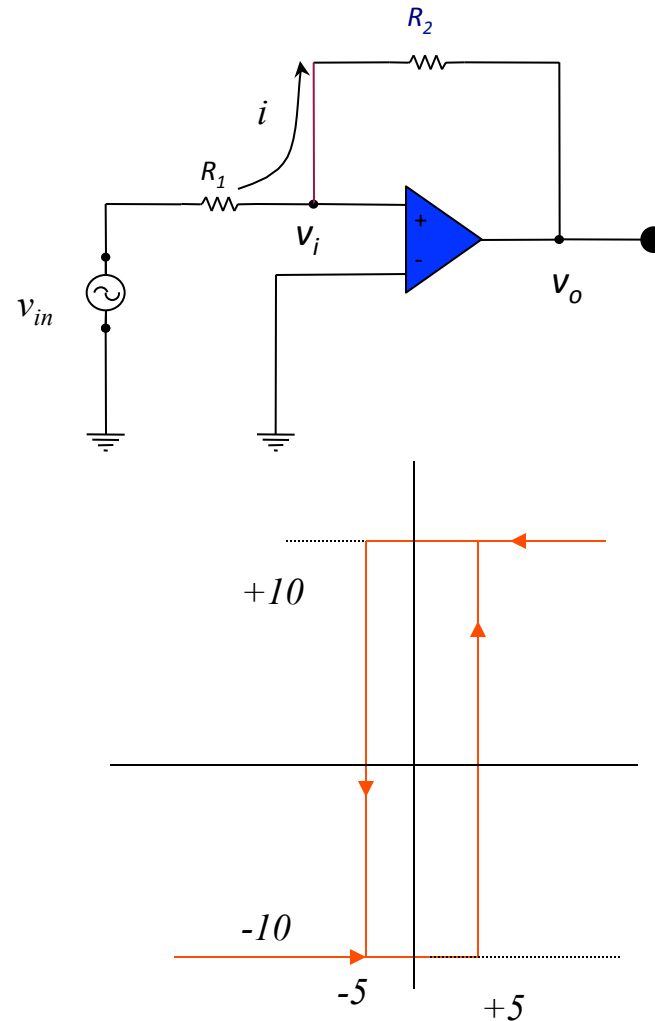
$$v_i = \frac{2}{3}V_{in} + \frac{v_o}{3} < 0; \frac{2}{3}V_{in} < -\frac{v_o}{3}; V_{in} < 5$$



Astable Multivibrators

- A switching oscillator or Astable Multivibrator can be formed from a Schmitt trigger as follows:
- Assume that output levels are $\pm A$ and the thresholds are $\pm A/2$ since the feedback voltage = $\frac{1}{2} v_o$.

$$v_i = v_t - v_{in}$$

when $v_i > 0$; $v_o = A$; therefore,

$$v_i = v_t - v_{in} > 0$$



$$v_t > v_{in}; \text{ or } v_{in} < \frac{A}{2}$$

$$v_i = v_t - v_{in}$$

when $v_i < 0$; $v_o = -A$; therefore,




$$v_i = v_t - v_{in} < 0$$
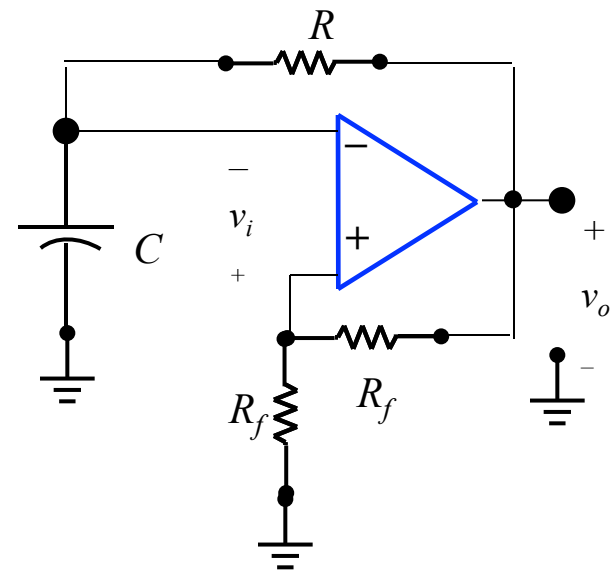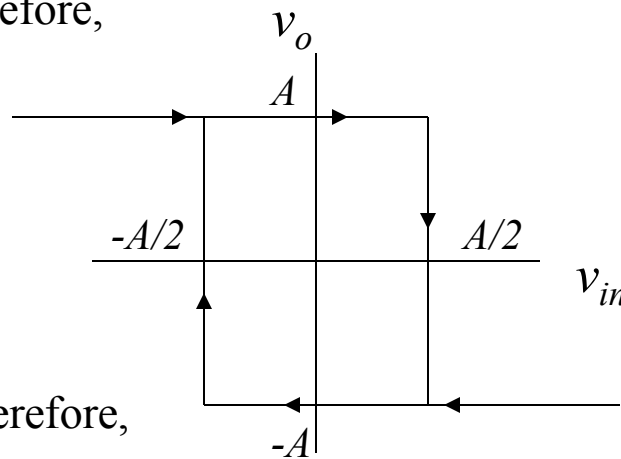
$$v_t < v_{in}; \text{ or } v_{in} > -\frac{A}{2}$$




Astable Multivibrators

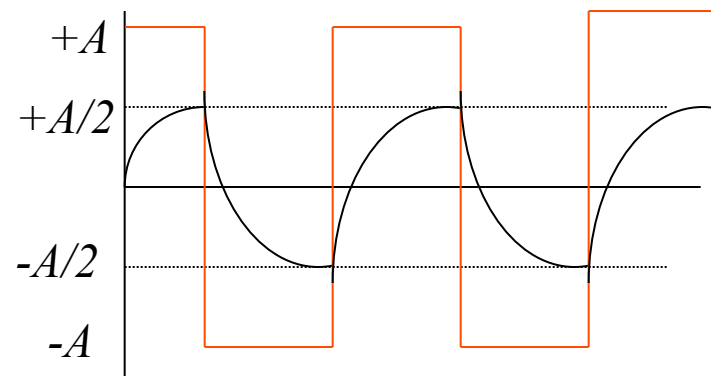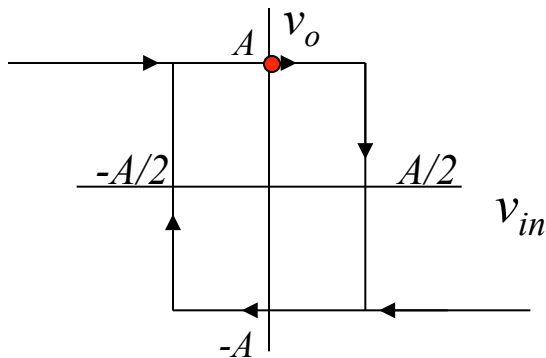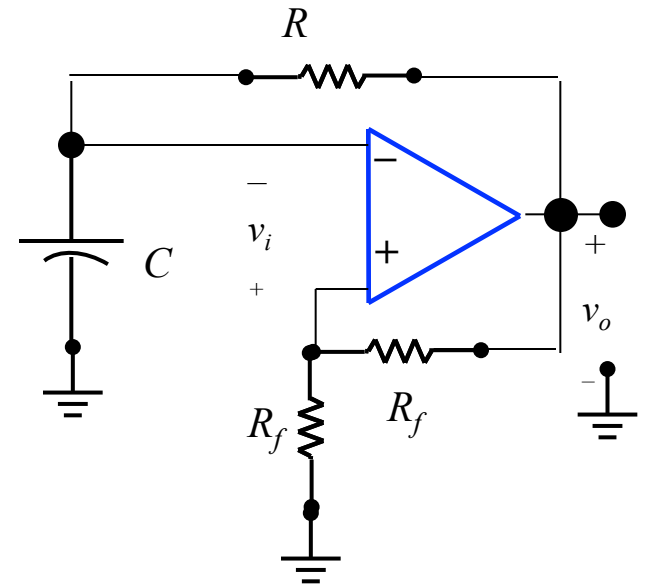- Assume that the output starts off at $+A$.
- The capacitor starts to charge to $+A$
- However, when it reaches $+A/2$, $v_i = 0$ and the output switches to $-A$.
- The capacitor then charges to $-A$.
- However, when it reaches $-A/2$, $v_i = 0$ and the output switches to $+A$
- And the capacitor charges to $+A$
- This process continues.



Timing Calculation

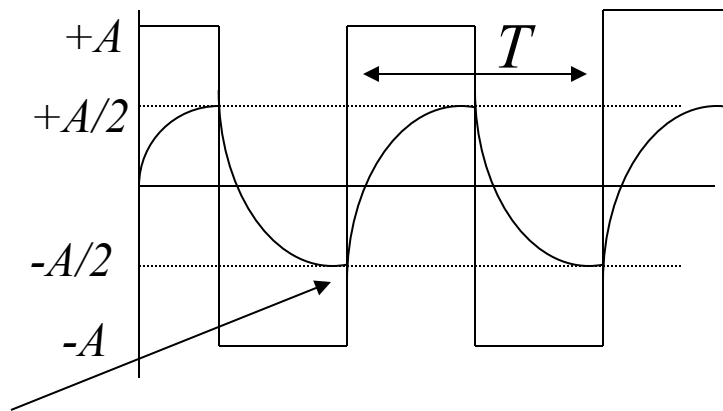

Start the timing calculation here

$$v_c(t) = K_1 + K_2 e^{-t/RC}$$

Initial Condition :

$$v_c(0) = -\frac{A}{2} = K_1 + K_2 e^{-0/RC} = K_1 + K_2 \text{ (eqn. 1)}$$

Final Condition :

$$v_c(\infty) = +A = K_1 + K_2 e^{-\infty/RC} = K_1 \text{ (eqn. 2)}$$

From eqns (1) and (2)

$$K_1 = A$$

$$K_2 = -\frac{A}{2} - K_1 = -\frac{3}{2}A$$

$$v_c(t) = A\left(1 - \frac{3}{2}e^{-t/RC}\right)$$

But

$$v_c\left(\frac{T}{2}\right) = \frac{A}{2} = A\left(1 - \frac{3}{2}e^{-T/2RC}\right)$$

$$\therefore e^{-T/2RC} = \frac{1}{3}$$

$$T = 2RC \ln(3)$$

Homework

- Comparators and Schmitt Trigger Circuits
 - Problems: 12.8-9
- Astable Multivibrators
 - Problems: 12.14