



Electronic Systems

Lesson #4

Chapter 1

Homework

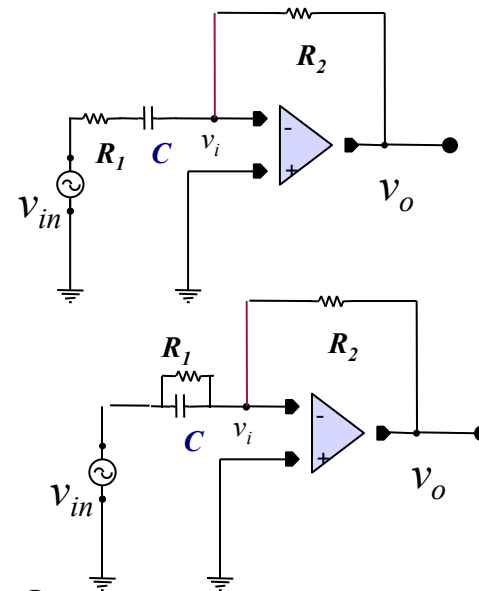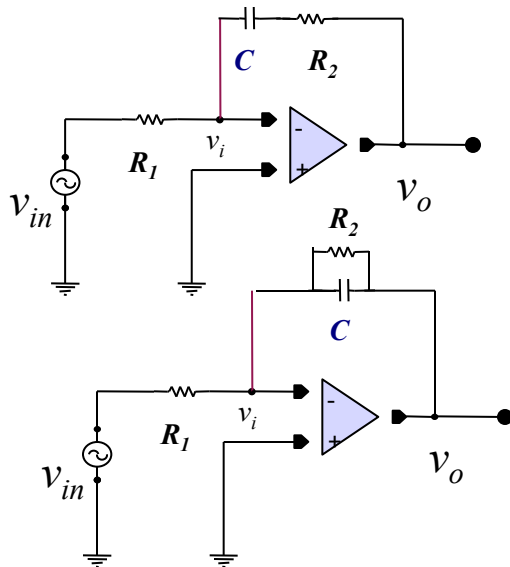- Probs 2.2, 2.5, 2.6, 2.10, 2.22, 2.24, 2.25, 2.28
- Calculate and plot the output vs frequency for these circuits. $R_1=1\text{k}$, $R_2=3\text{k}$, $C=1\text{mf}$




Homework Answers #10


- Probs 2.2
$$v_1(t) = 0.1 \cos(20\pi t) + 20 \sin(120\pi t)$$
$$v_2(t) = -0.1 \cos(20\pi t) + 20 \sin(120\pi t)$$
$$v_{cm}(t) = \frac{v_1(t) + v_2(t)}{2} = 20 \sin(120\pi t)$$
$$v_d(t) = v_1(t) - v_2(t) = 0.2 \cos(20\pi t)$$
- Probs 2.5
 - The summing point constraint only applies to negative feedback
- Probs 2.6
 - Verify that negative feedback is present
 - Assume that the differential input voltage and input current of the op amp forced to zero
 - Apply standard circuit analysis principles such as Kirchhoff's laws and Ohm's law to solve for quantities of interest.

Homework Answers #11


- Probs 2.10

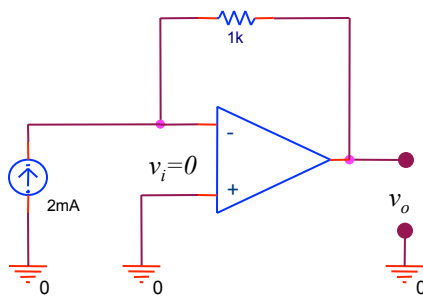


$$v_o = -2mA \times 1k + v_i = -2V$$

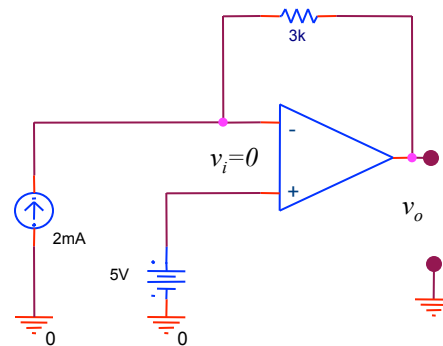

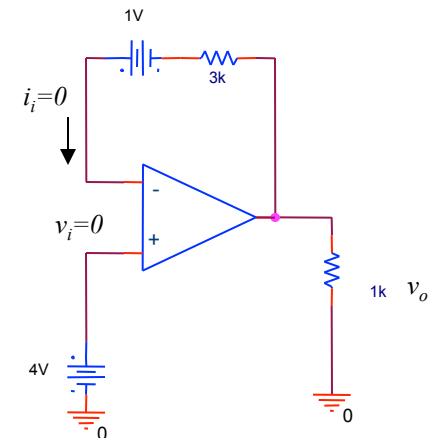
$$v_o = -2mA \times 3k + v_i + 5V = -1V$$



$$v_o = 4V + v_i - 1V + 0 = 3V$$

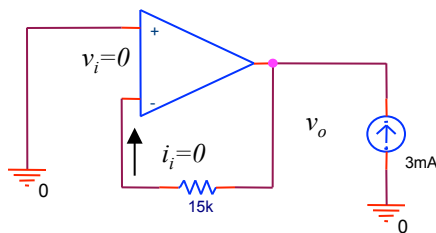


$$v_o = 0 + v_i = 0V$$

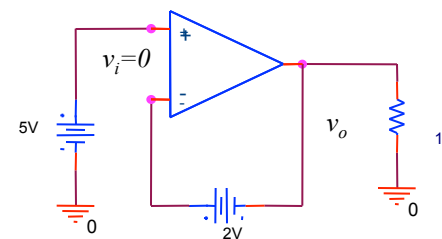

$$v_o = -2V + v_i + 5V = 3V$$

Homework Answers #12

- Probs 2.22

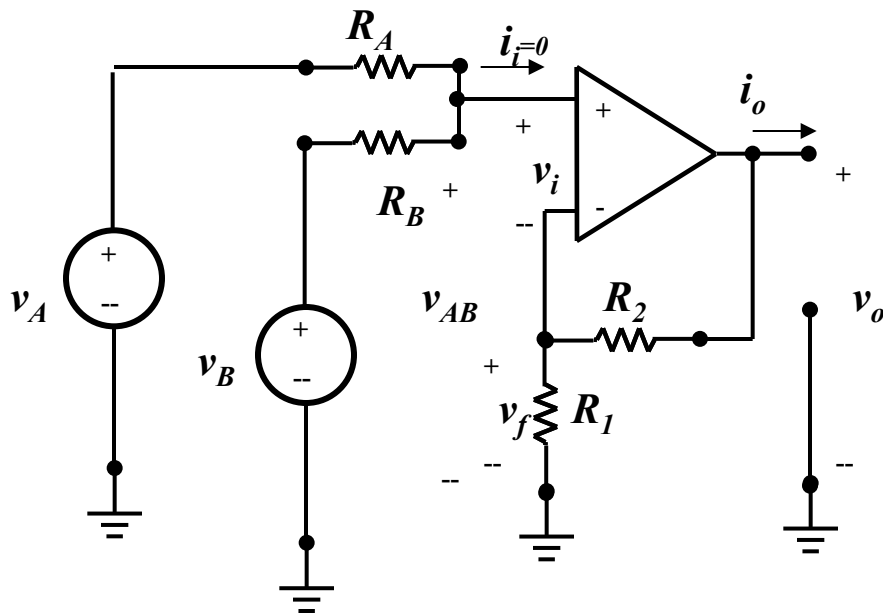

$$v_{AB} = v_i + v_f = v_f$$

$$v_f = \frac{R_1}{R_1 + R_2} v_o$$

$$i_i = i_A + i_B = 0$$

$$0 = \frac{v_A - v_{AB}}{R_A} + \frac{v_B - v_{AB}}{R_B}$$

$$\frac{v_A}{R_A} + \frac{v_B}{R_B} = \left(\frac{1}{R_A} + \frac{1}{R_B} \right) v_{AB}$$

$$v_{AB} = \frac{v_A R_B + v_B R_A}{R_A R_B} \left(\frac{R_A R_B}{R_B + R_A} \right)$$

$$= \frac{v_A R_B + v_B R_A}{R_B + R_A}$$

$$v_o = \frac{v_A R_B + v_B R_A}{R_B + R_A} \times \frac{R_1 + R_2}{R_1}$$

Homework Answers #13


- Probs 2.24

INVERTING AMP

$$v_o = -i_f R_2; i_f = \frac{v_s}{R_1}; \frac{v_o}{v_s} = -\frac{R_2}{R_1}$$

$$P_{in} = \frac{v_s^2}{R_1}; P_{out} = \frac{v_o^2}{R_L} = \frac{v_s^2}{R_L} \left(\frac{R_2}{R_1}\right)^2$$
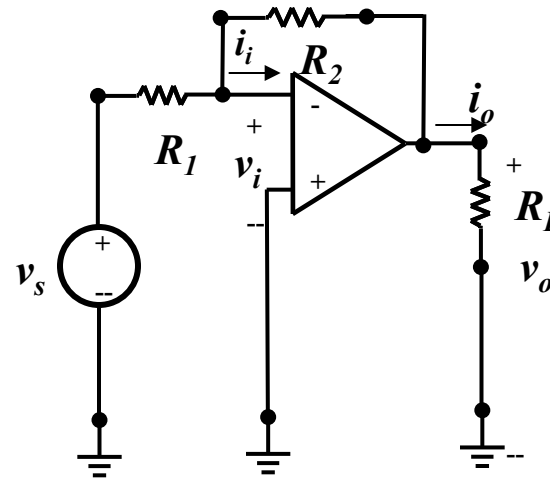
$$G = \frac{P_{out}}{P_{in}} = \frac{R_2^2}{R_L R_1}$$




NON INVERTING AMP

$$v_s = \frac{R_2}{R_1 + R_2} v_o; \frac{v_o}{v_s} = \frac{R_1 + R_2}{R_1}$$

$$P_{in} = 0; i_i = 0$$


$$P_{out} = \frac{v_o^2}{R_L}$$

$$G = \frac{P_{out}}{P_{in}} = \infty$$

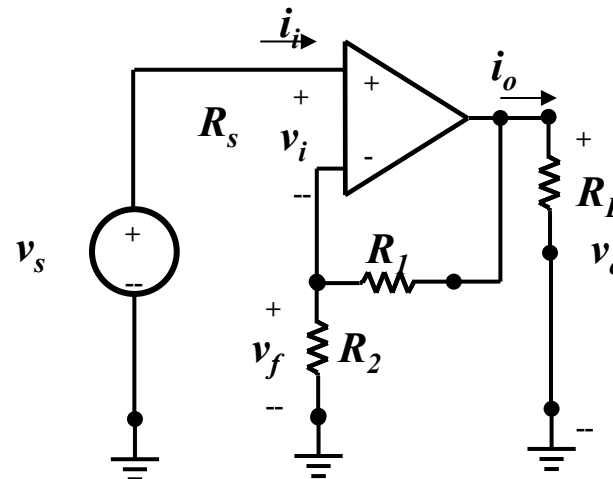

Homework Answers #14


- Probs 2.25

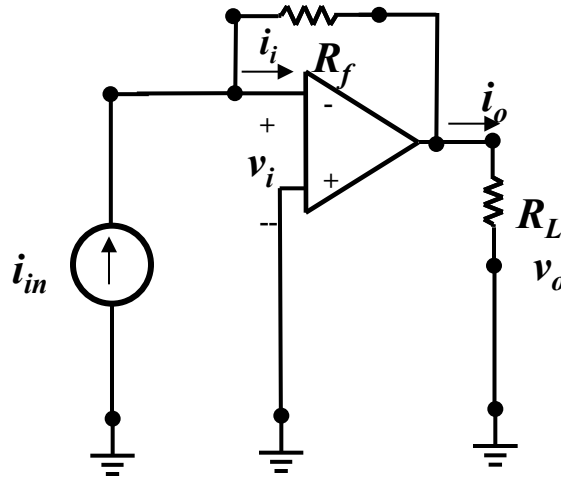

- a) $v_o = -i_{in}R_f$
- b) Since v_o is independent of R_L , then we have an ideal voltage source and $R_{out} = 0$
- c) $R_{in} = \frac{v_i}{i_{in}} = \frac{0}{i_{in}} = 0$
- d) Since the output voltage is proportional to the input current, it is an ideal transresistance amplifier


Homework Answers #15

- Probs 2.28

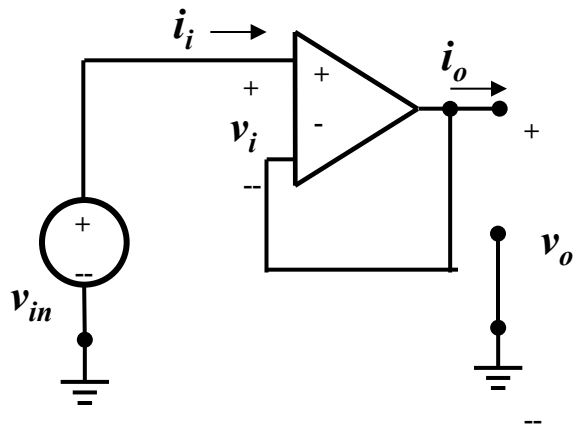



Negative Feedback

$$v_{in} = v_i + v_o = v_o$$

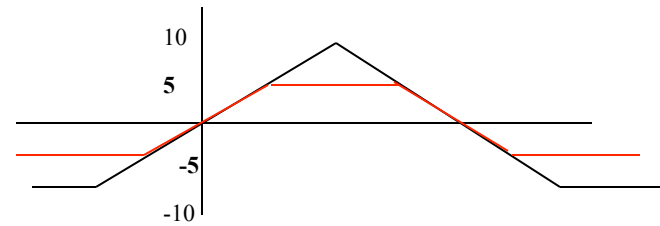

Homework Answers #16

- Probs 2.28

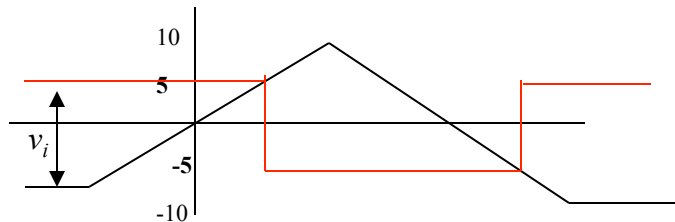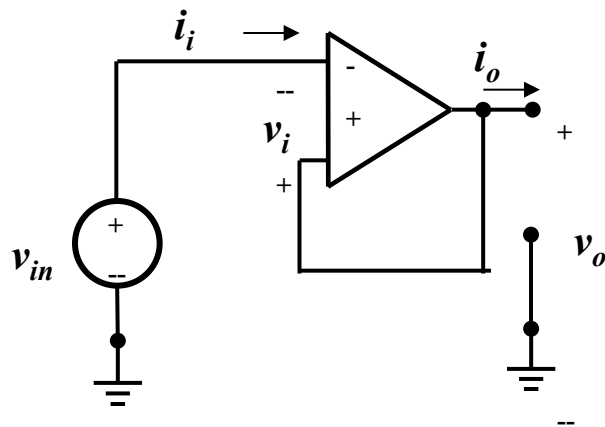

Positive Feedback and $v_i \neq 0$

1) When $v_i > 0$, v_o is $+5$, then :

$$v_i = v_o - v_{in} = +5 - v_{in} > 0; \text{ or when } 5 > v_{in}$$

So v_o switches to -5 when $v_{in} \geq 5$ since

$$v_i = +5 - v_{in} \leq 0 \text{ for } v_{in} > 5$$

(e.g., if $v_{in} = 5.001$, then $v_i = +5 - 5.001 = -.001$)

2) When $v_i < 0$, v_o is -5 , then :

$$v_i = v_o - v_{in} = -5 - v_{in} < 0; \text{ or when } -5 < v_{in}$$


So v_o switches to $+5$ when $v_{in} \leq -5$ since

$$v_i = -5 - v_{in} \geq 0 \text{ for } v_{in} < -5$$

(e.g., if $v_{in} = -5.001$, then $v_i = -5 - (-5.001) = .001$)

Homework Answers

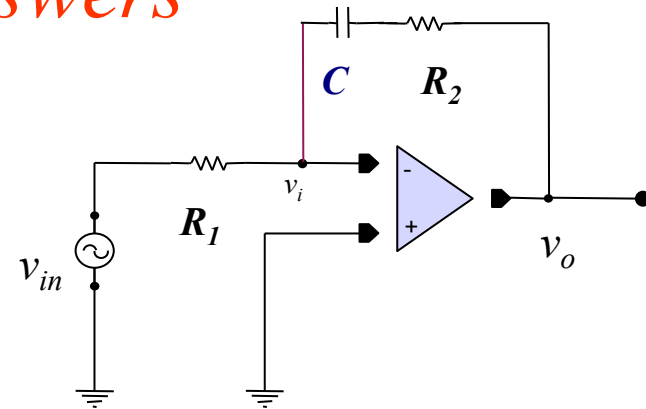- Calculate and plot the output vs frequency for these circuits.



$$\frac{v_o}{v_{in}} = -\frac{Z_2}{Z_1}$$

$$Z_2 = R_2 + \frac{1}{j\omega C} = \frac{1 + j\omega CR_2}{j\omega C}$$


$$Z_1 = R_1$$

$$\begin{aligned} \frac{v_o}{v_{in}} &= -\frac{Z_2}{Z_1} = -\frac{\frac{1 + j\omega CR_2}{j\omega C}}{R_1} = -\frac{1 + j\omega CR_2}{j\omega CR_1} = \frac{\sqrt{1 + (\omega CR_2)^2}}{\omega CR_1} \angle (\pi + \tan^{-1}(\omega CR_2) - \frac{\pi}{2}) \\ &= \frac{\sqrt{1 + (\omega CR_2)^2}}{\omega CR_1} \angle (\frac{\pi}{2} + \tan^{-1}(\omega CR_2)) \end{aligned}$$

$$\left. \frac{v_o}{v_{in}} \right|_{\omega \rightarrow 0} = -\frac{1 + j\omega CR_2}{j\omega CR_1} \Big|_{\omega \rightarrow 0} \rightarrow -\frac{1}{j\omega CR_1} \Big|_{\omega \rightarrow 0} \rightarrow \infty \angle \frac{\pi}{2}$$


$$\left. \frac{v_o}{v_{in}} \right|_{\omega = \frac{1}{CR_2}} = \frac{\sqrt{2}R_2}{R_1} \angle (\frac{\pi}{2} + \frac{\pi}{4}) = \sqrt{2} \frac{R_2}{R_1} \angle \frac{3\pi}{4}$$

$$\left. \frac{v_o}{v_{in}} \right|_{\omega \rightarrow \infty} = -\frac{1 + j\omega CR_2}{j\omega CR_1} \Big|_{\omega \rightarrow \infty} \rightarrow -\frac{\omega CR_2}{\omega CR_1} \angle \pi = \frac{R_2}{R_1} \angle \pi = -\frac{R_2}{R_1}$$

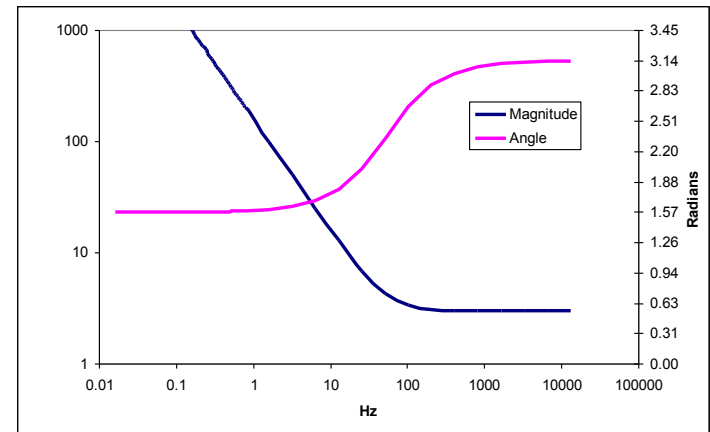


Matlab Code

```
clear all;
R1=1e3;R2=3e3;C=1e-6;
omega=(10:10:10000);maxomega=length(omega);
for i=1:maxomega
    ZC=1/complex(0,(omega(i)*C));
    z1=R1;
    z2=R2+ZC;
    VOUT(i)=-z2/z1;
end
f=omega/(2*pi);
subplot(2,1,1);
loglog(f,abs(VOUT));
title('OpAmp Low Pass Magnitude');
xlabel('Hz');
axis([f(1) f(maxomega) .1 1000]);
subplot(2,1,2);
semilogx(f,atan2(imag(VOUT),real(VOUT)));
title('OpAmp Low Pass Phase Angle');
xlabel('Hz');
axis([f(1) f(maxomega) pi/2 1.1*pi]);
```

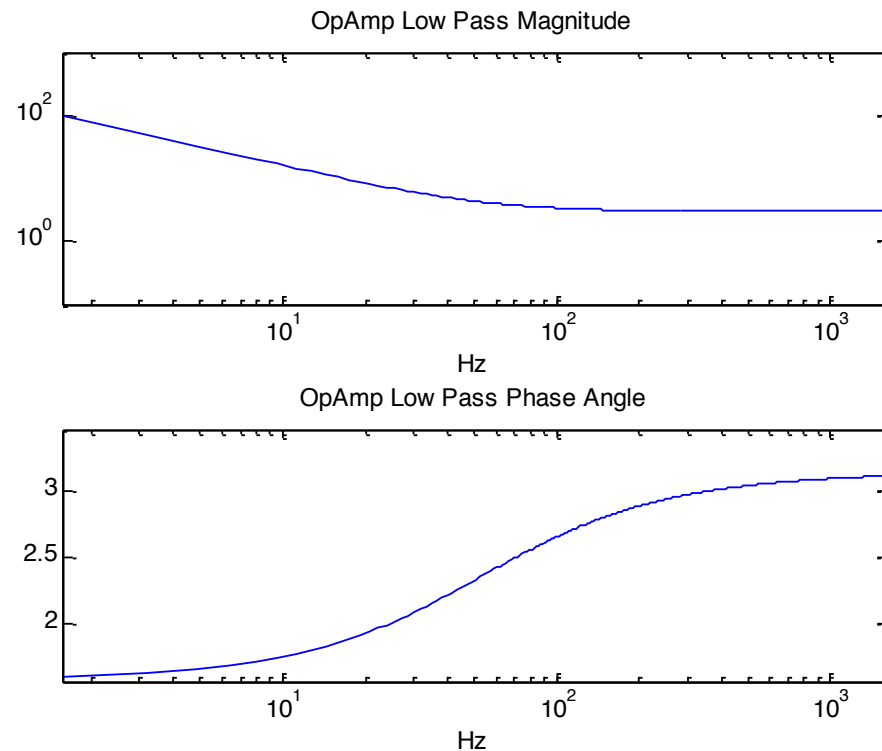

Homework Answers

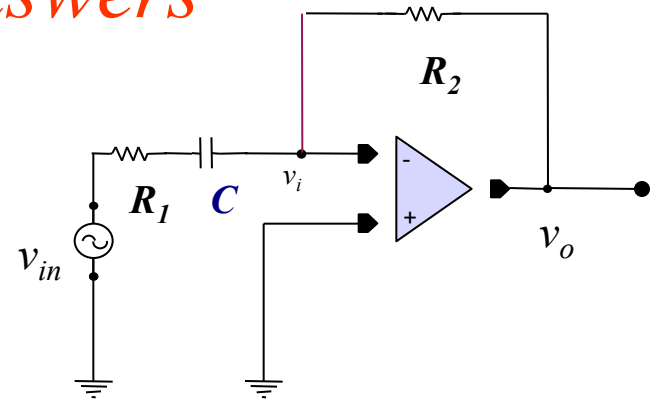- Calculate and plot the output vs frequency for these circuits.



$$\frac{v_o}{v_{in}} = -\frac{Z_2}{Z_1}$$

$$Z_2 = R_2$$

$$Z_1 = R_1 + \frac{1}{j\omega C} = \frac{1 + j\omega CR_1}{j\omega C}$$


$$\frac{v_o}{v_{in}} = -\frac{Z_2}{Z_1} = -\frac{R_2}{\frac{1 + j\omega CR_1}{j\omega C}} = -\frac{j\omega CR_2}{1 + j\omega CR_1} = \frac{\omega CR_2}{\sqrt{1 + (\omega CR_1)^2}} \angle(\pi + \frac{\pi}{2} - \tan^{-1}(\omega CR_1))$$

$$= \frac{\omega CR_2}{\sqrt{1 + (\omega CR_1)^2}} \angle(\frac{3\pi}{2} - \tan^{-1}(\omega CR_1)) = \frac{\omega CR_2}{\sqrt{1 + (\omega CR_1)^2}} \angle(-\frac{\pi}{2} - \tan^{-1}(\omega CR_1))$$

$$\frac{v_o}{v_{in}} \Big|_{\omega=0} = -\frac{j\omega CR_2}{1 + j\omega CR_1} = 0 \angle -\frac{\pi}{2}$$


$$\frac{v_o}{v_{in}} \Big|_{\omega=\frac{1}{CR_1}} = -\frac{j\frac{R_2}{R_1}}{1 + j} = \frac{1}{\sqrt{2}} \frac{R_2}{R_1} \angle -\frac{3\pi}{4}$$

$$\frac{v_o}{v_{in}} \Big|_{\omega \rightarrow \infty} = -\frac{j\omega CR_2}{1 + j\omega CR_1} \Big|_{\omega \rightarrow \infty} \rightarrow -\frac{j\omega CR_2}{j\omega CR_1} = \frac{R_2}{R_1} \angle -\pi = -\frac{R_2}{R_1}$$

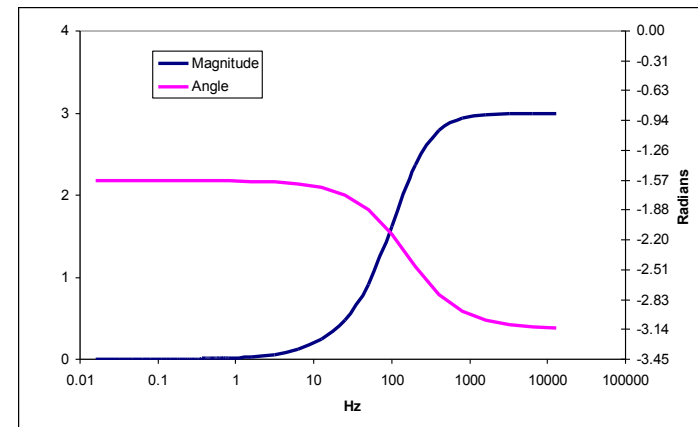


Matlab Code

```
clear all;
R1=1e3;R2=3e3;C=1e-6;
omega=(10:10:10000);maxomega=length(omega);
for i=1:maxomega
    ZC=1/complex(0,(omega(i)*C));
    z2=R2;
    z1=R1+ZC;
    VOUT(i)=-z2/z1;
end
f=omega/(2*pi);
subplot(2,1,1);
loglog(f,abs(VOUT));
title('OpAmp High Pass Magnitude');
xlabel('Hz');
axis([f(1) f(maxomega) .01 10]);
subplot(2,1,2);
semilogx(f,atan2(imag(VOUT),real(VOUT)));
title('OpAmp High Pass Phase Angle');
xlabel('Hz');
axis([f(1) f(maxomega) -1.1*pi -pi/2]);
```

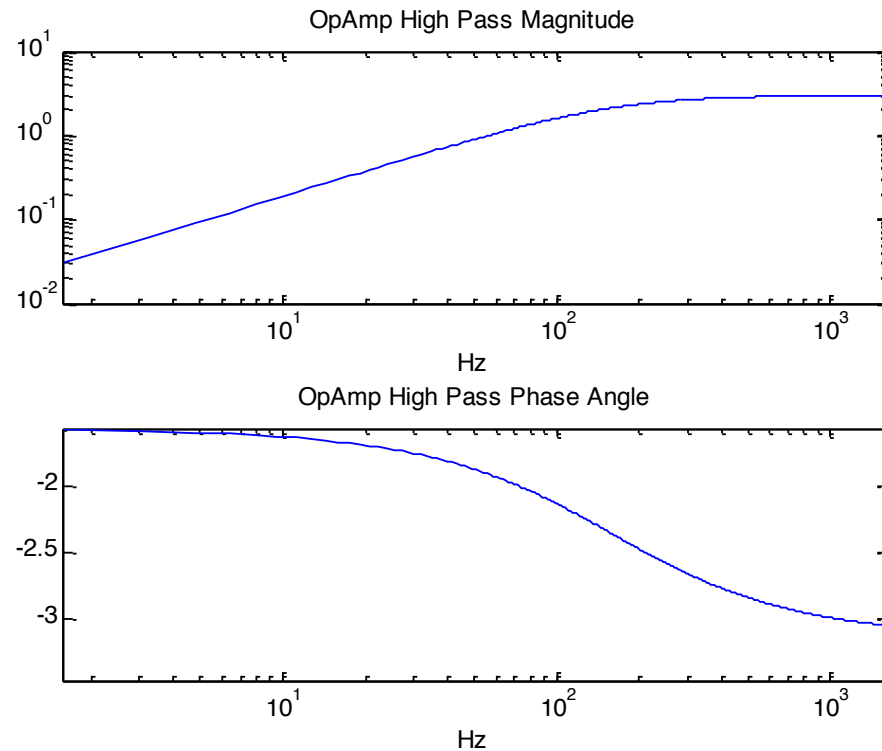

Homework Answers

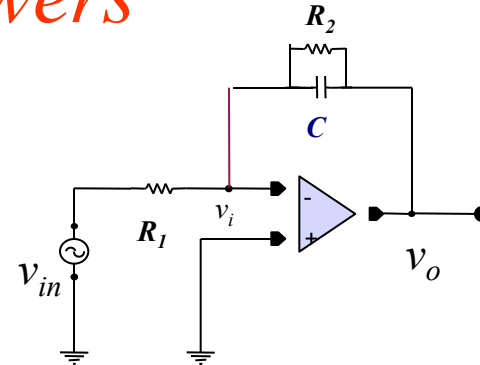- Calculate and plot the output vs frequency for these circuits.



$$\frac{v_o}{v_{in}} = -\frac{Z_2}{Z_1}$$

$$Z_2 = R_2 \parallel \frac{1}{j\omega C} = \frac{R_2 \times \frac{1}{j\omega C}}{R_2 + \frac{1}{j\omega C}} = \frac{R_2}{1 + j\omega CR_2}$$


$$Z_1 = R_1$$

$$\frac{v_o}{v_{in}} = -\frac{Z_2}{Z_1} = -\frac{R_2}{R_1} \times \frac{1}{1 + j\omega CR_2} = \frac{R_2}{R_1} \times \frac{1}{\sqrt{1 + (\omega CR_2)^2}} \angle(\pi - \tan^{-1}(\omega CR_2))$$

$$\left. \frac{v_o}{v_{in}} \right|_{\omega \rightarrow 0} = \frac{R_2}{R_1} \times \frac{1}{1} \angle \pi = -\frac{R_2}{R_1}$$


$$\left. \frac{v_o}{v_{in}} \right|_{\omega = \frac{1}{CR_2}} = \frac{1}{\sqrt{2}} \times \frac{R_2}{R_1} \angle(\pi - \frac{\pi}{4}) = \frac{1}{\sqrt{2}} \frac{R_2}{R_1} \angle \frac{3\pi}{4}$$

$$\left. \frac{v_o}{v_{in}} \right|_{\omega \rightarrow \infty} = -\frac{R_2}{R_1} \times \frac{1}{1 + j\omega CR_2} \Big|_{\omega \rightarrow \infty} \rightarrow -\frac{R_2}{R_1} \times \frac{1}{j\omega CR_2} \rightarrow 0 \angle \frac{\pi}{2}$$

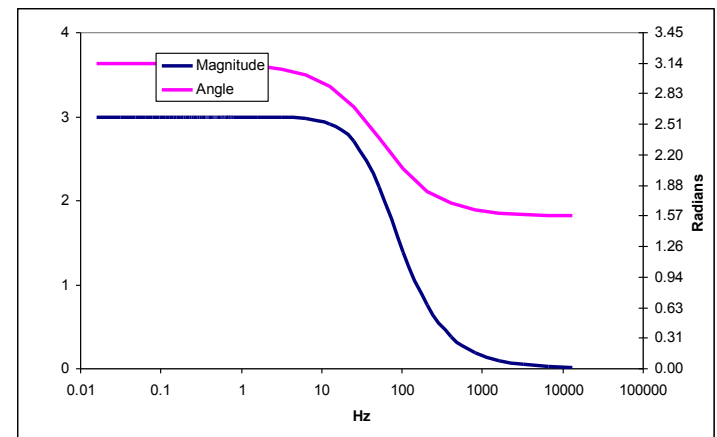


Matlab Code

```
clear all;
R1=1e3;R2=3e3;C=1e-6;
omega=(10:10:10000);maxomega=length(omega);
for i=1:maxomega
    ZC=1/complex(0,(omega(i)*C));
    z1=R1;
    z2=1/(1/R2+1/ZC);
    VOUT(i)=-z2/z1;
end
f=omega/(2*pi);
subplot(2,1,1);
loglog(f,abs(VOUT));
title('OpAmp Low Pass 2 Magnitude');
xlabel('Hz');
axis([f(1) f(maxomega) .01 10]);
subplot(2,1,2);
semilogx(f,atan2(imag(VOUT),real(VOUT)));
title('OpAmp Low Pass 2 Phase Angle');
xlabel('Hz');
axis([f(1) f(maxomega) pi/2 1.1*pi]);
```

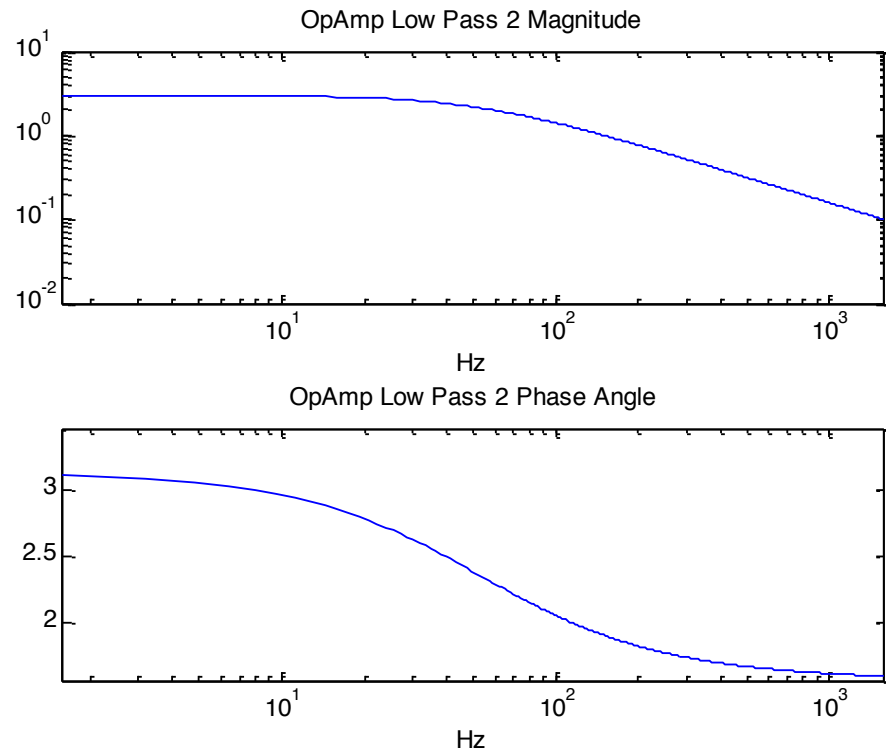

Homework Answers

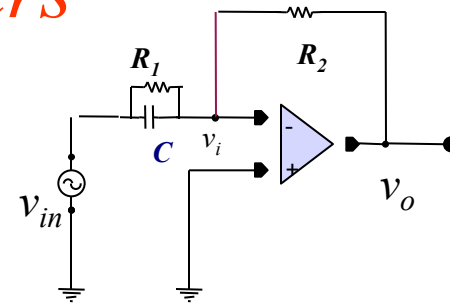- Calculate and plot the output vs frequency for these circuits.



$$\frac{v_o}{v_{in}} = -\frac{Z_2}{Z_1}$$

$$Z_2 = R_2$$


$$Z_1 = R_1 \parallel \frac{1}{j\omega C} = \frac{R_1 \times \frac{1}{j\omega C}}{R_1 + \frac{1}{j\omega C}} = \frac{R_1}{1 + j\omega CR_1}$$

$$\frac{v_o}{v_{in}} = -\frac{Z_2}{Z_1} = -\frac{R_2}{\frac{R_1}{1 + j\omega CR_1}} = -\frac{R_2}{R_1} \times (1 + j\omega CR_1) = \frac{R_2}{R_1} \times \sqrt{1 + (\omega CR_1)^2} \angle(-\pi + \tan^{-1}(\omega CR_1))$$

$$\left. \frac{v_o}{v_{in}} \right|_{\omega=0} = -\frac{R_2}{R_1} \times (1 + j\omega CR_1) = -\frac{R_2}{R_1} = \frac{R_2}{R_1} \angle -\pi$$

$$\left. \frac{v_o}{v_{in}} \right|_{\omega=\frac{1}{CR_1}} = \frac{R_2}{R_1} \times \sqrt{2} \angle(-\pi + \frac{\pi}{4}) = \sqrt{2} \frac{R_2}{R_1} \angle -\frac{3\pi}{4}$$

$$\left. \frac{v_o}{v_{in}} \right|_{\omega \rightarrow \infty} = -\frac{R_2}{R_1} \times (1 + j\omega CR_1) \Big|_{\omega \rightarrow \infty} = -\frac{R_2}{R_1} \times \sqrt{1 + (\omega CR_1)^2} \angle(-\pi + \tan^{-1}(\omega CR_1)) \Big|_{\omega \rightarrow \infty} \rightarrow \infty \angle -\frac{\pi}{2}$$

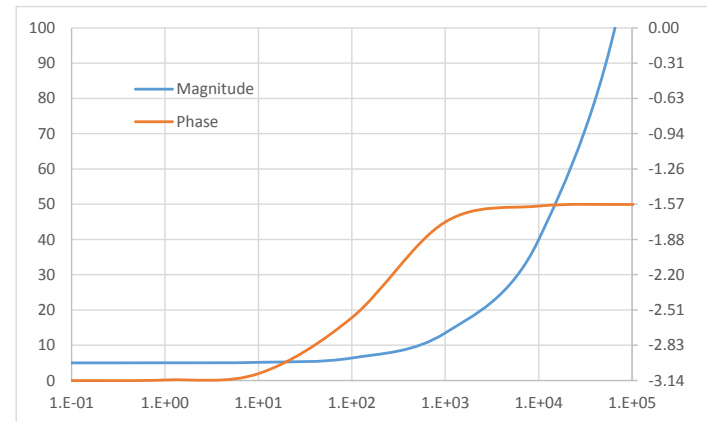

Matlab Code

```
clear all;
R1=1e3;R2=3e3;C=1e-6;
omega=(10:10:10000);maxomega=length(omega);
for i=1:maxomega
    ZC=1/complex(0,(omega(i)*C));
    z2=R2;
    z1=1/(1/R1+1/ZC);
    VOUT(i)=-z2/z1;
end
f=omega/(2*pi);
subplot(2,1,1);
loglog(f,abs(VOUT));
title('OpAmp High Pass 2 Magnitude');
xlabel('Hz');
axis([f(1) f(maxomega) 1 1000]);
subplot(2,1,2);
semilogx(f,atan2(imag(VOUT),real(VOUT)));
title('OpAmp High Pass 2 Phase Angle');
xlabel('Hz');
axis([f(1) f(maxomega) -1.1*pi -pi/2]);
```

