

## Fundamentals of Engineering Design (FED) 101- LC9


### Test 3

Student name:

Student ID number:

Please provide complete and clear answers.

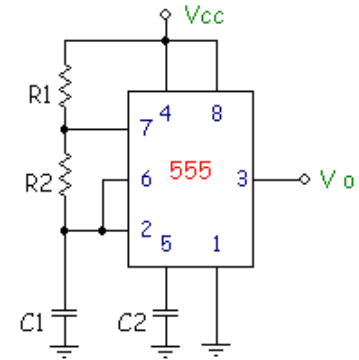1. Given the following 555 timer in Astable mode, where  $R1=50K\Omega$ ,  $R2=10K\Omega$ ,  $C1=0.001\mu F$  and  $C2=1nF$ 
  - a) Calculate the on-time,  $T_{ON}$ . (2 points)
  - b) Calculate the frequency,  $f$ . (2 points)
  - c) Calculate the duty cycle,  $d$ . (2 points)
  - d) How could you change components in the circuit to double the frequency of the output pulses without affecting the duty cycle? Demonstrate mathematically that your component changes have had the desired effect. (4 points)



Solution:

$$a) T_{ON} = 0.693(R1 + R2)C1 = 0.693(50 \times 10^3 + 10 \times 10^3)(1 \times 10^{-9}) = 41.58 \times 10^{-6} =$$

$$T_{ON} = 41.6 \mu s$$

$$b) f = 1.44/((R1 + 2R2)(C1)) = 1.44/((50 \times 10^3 + 20 \times 10^3)(1 \times 10^{-9})) = 0.020571 \times 10^{-6}$$

$$f = 20571 Hz$$

$$c) D = \left(\frac{T_{ON}}{T}\right) \times 100$$

$$T = \frac{1}{f} = 4.86 \times 10^{-5}$$

$$D = (41.6 \times 10^{-6} / 4.86 \times 10^{-5}) \times 100 = 0.856 \times 100$$

$$D = 86\%$$

$$d) f = 20571 Hz \text{ Double that is } 41,143 Hz$$

Half the size of  $C1$  to  $0.5 nF$

$$f = 1.44/((R1 + 2R2)(C1)) = 1.44/((50 \times 10^3 + 20 \times 10^3)(5 \times 10^{-10})) = 41,143 Hz$$