

LC and driven *RLC* circuits

1. Consider an *LC* circuit with $L = 10\text{ mH}$, $C = 0.7\text{ mF}$ and capacitor initially charged to 10 V .
 - (a) find the resonant frequency ω_0 in *rad/s*
 - (b) derive explicit formulas for the charge $q(t)$ and the electric energy $U_C(t)$ in the capacitor
 - (c) derive explicit formulas for the current $I(t)$ and the magnetic energy $U_M(t)$ in the inductor
 - (d) verify $U_M(t) + U_E(t) = \text{const}$ (and determine the *const*)
2. A series *RLC* circuit is driven by an external AC source with $V_{RMS} = 120\text{ volt}$ and variable frequency f . Use $L = 10\text{ mH}$, $C = 0.7\text{ mF}$, $R = 0.1\ \Omega$.
 - (a) Find the resonant frequency f_0 (in *Hz*)
 - (b) Plot I_{RMS} as a function of f . (Select the horizontal scale $f_0 \pm 40\text{ Hz}$ for a good plot).

