

A series RLC circuit is driven by an external AC source with $V_{RMS} = 120 \text{ volt}$ and variable frequency f . Use $L = 10 \text{ mH}$, $C = 0.7 \text{ mF}$, $R = 0.1 \Omega$.

1. Find the resonant frequency f_0 (in Hz)
2. Plot I_{RMS} as a function of f . (Select the horizontal scale $f_0 \pm 40 \text{ Hz}$ for a good plot).
3. plot $V_C - V_L$ and compare with V_R .

