
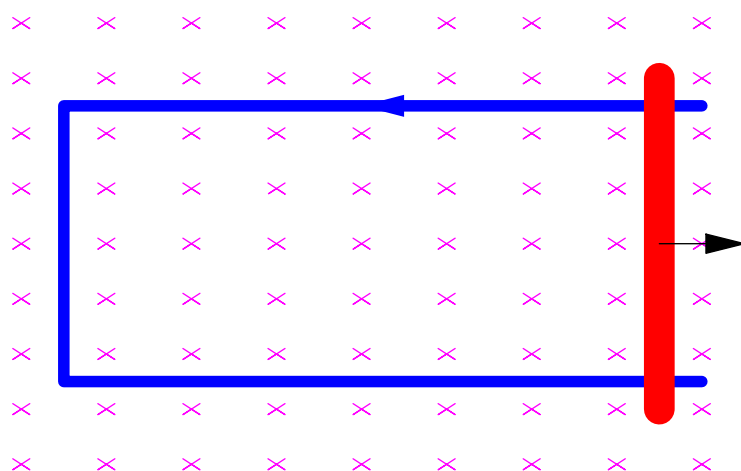


Faraday's Law and inductors

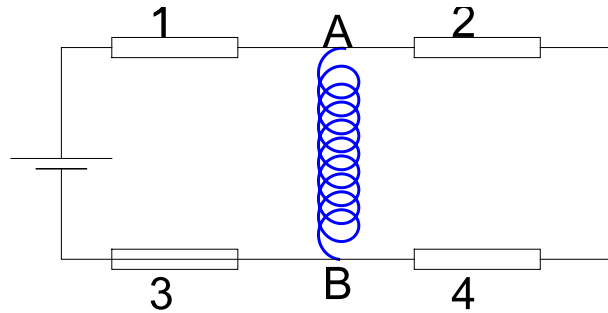


1. A sliding rod and rails make a conducting path with resistance $R = 1\text{ k}\Omega$. The distance between rails (length of the rod) is $l = 10\text{ cm}$, and there is a magnetic field $B = 2\text{ T}$ which points into the page; the rod is moving with speed $v = 10\text{ m/s}$ to the right.
 - (a) find E_{ind}
 - (b) find I_{ind}
 - (c) find the electric power P released in the circuit
 - (d) find \vec{F}_M acting on the rod (direction)
 - (e) find \vec{F}_M acting on the rod (magnitude)
 - (f) find the mechanical power which is required to overcome F_M and compare to P
 - (g) what would be the direction of the induced current and the magnetic force if the rod would slide left?



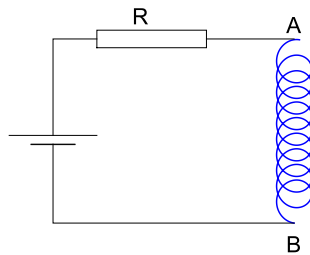2.

In the above circuit $R_1 = 1\ \Omega$, $R_2 = 2\ \Omega$, $R_3 = 3\ \Omega$, $R_4 = 4\ \Omega$ and $E = 12\ V$. The switch (not shown) was closed at $t = 0$.

- redraw the circuit and find all currents as $t \rightarrow 0$
- redraw the circuit and find all currents as $t \rightarrow \infty$
- the same if the inductor is replaced by a capacitor C
- for the original circuit with R_2, R_4 removed and $R = R_1 + R_2$, find the induced emf E_L when the current reaches 20% of its maximum value. (*Note.* The actual value of the inductance L does not matter here; you can get the result from the loop equation, or use any value of L in explicit calculations).



- find the *time* for the current to reach 50% of its maximum value; use $L = 2\ mH$.
- Assume that a long time after the maximum current was reached, the battery is also removed and replaced by a wire. At that instant, time is "restarted", i.e. $t = 0$. Plot $i(t)$ and $U_M(t)$; use the attached graphpaper (select a good scale!).

