
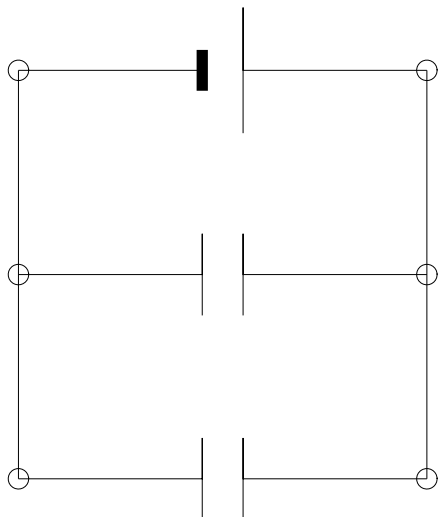


Capacitors

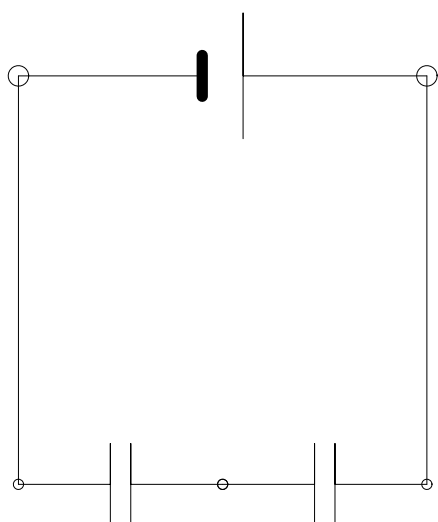- When the electric field in a certain dielectric exceeds $10^6 V/m$ it experiences *dielectric breakdown* (gets destroyed). What is the breakdown voltage of a $10 \times 10 \text{ cm}^2$, $1 \mu F$ capacitor if $\kappa = 3.7$?
- In the circuit below $V = 12 \text{ volt}$, $C_1 = C_2 = 1 \text{ nF}$.




- Find C_{eq} , V_1 , V_2 , q_1 , q_2 and charge taken from the battery
 - the same, if the space between the plates of C_2 (lower) is filled with $\kappa = 2$.
- In the circuit below $V = 12 \text{ volt}$, $C_1 = C_2 = 1 \text{ nF}$.



- Find C_{eq} , V_1 , V_2 , q_1 , q_2 and charge taken from the battery
- the same, if the space between the plates of C_2 (right) is filled with $\kappa = 2$.

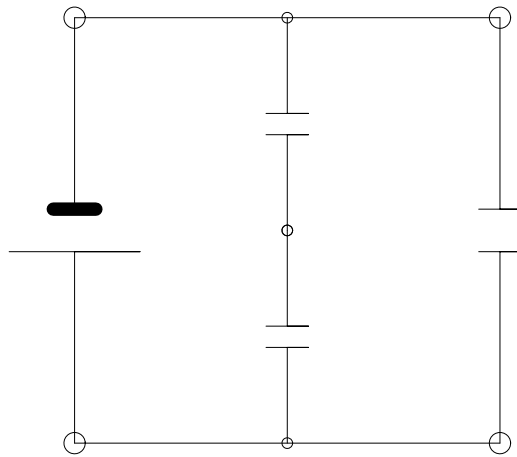
4. In the circuit below $V = 10 \text{ volt}$, $C_1 = C_2 = C_3 = 1 \mu F$.



(a) Find C_{eq} and charge taken from the battery

(b) Find $V_1, V_2, V_3, q_1, q_2, q_3$

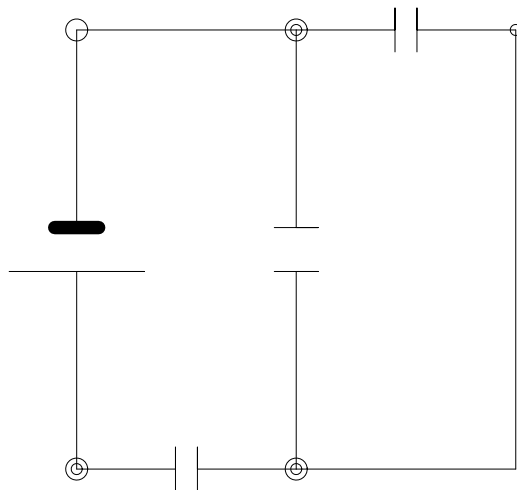5. In the circuit below $V = 10 \text{ volt}$, $C_1 = C_2 = C_3 = 1 \mu F$.



(a) Find C_{eq} and charge taken from the battery

(b) Find $V_1, V_2, V_3, q_1, q_2, q_3$