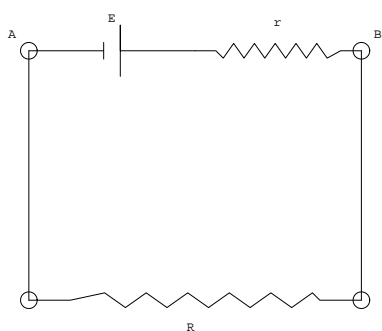


Circuits with  $R$  and  $C$ 

1. For  $R = 10\ \Omega$ ,  $r = 2\ \Omega$ ,  $E = 12\ V$  find


- current  $I$
- $V_{AB}$
- power  $P$  released by the battery
- power  $P_R$  on external load; where does the extra power go?
- (\*) for which  $R$  one gets  $P_R = \max$  ?



2. find


- current  $I$
- power released by each battery (watch for sign !)

(a)

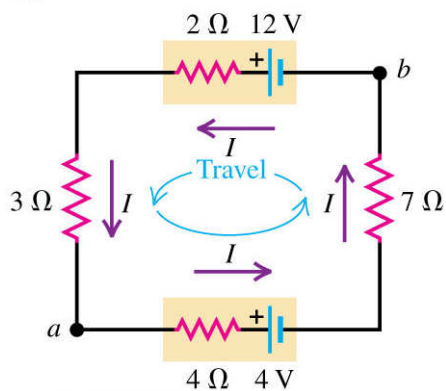


2

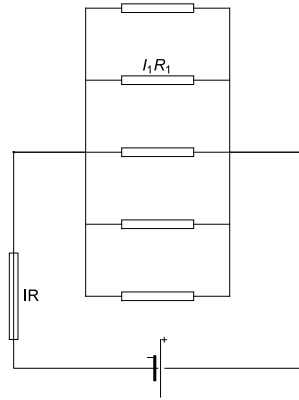3. for  $E = 10\text{ V}$ ,  $I_1 = 1\text{ A}$ ,  $R_1 = R = 2\ \Omega$  find  $I$




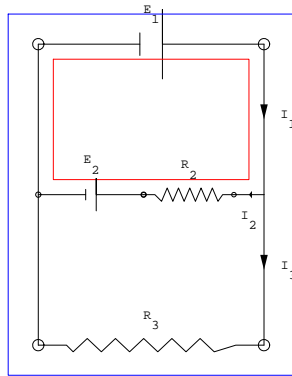4. for  $E_1 = 1\text{ V}$ ,  $E_2 = 2\text{ V}$ ,  $R_2 = R_3 = 2\ \Omega$  find all currents



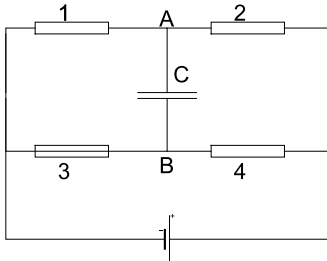
5. for  $E = 12, V, C = 1 \mu F$  and indicated  $R$ 's (in Ohms) find

- all currents at  $t = 0^+$
- all currents at  $t \rightarrow \infty$
- $V_C$  and  $Q_C$  at  $t \rightarrow \infty$



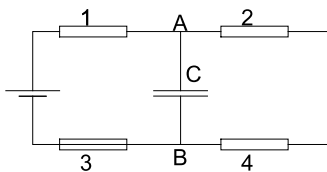
6. for  $E = 12, V, C = 1 \mu F$  and indicated  $R$ 's (in Ohms) find

- all currents at  $t = 0^+$
- all currents at  $t \rightarrow \infty$
- $V_C$  and  $Q_C$  at  $t \rightarrow \infty$




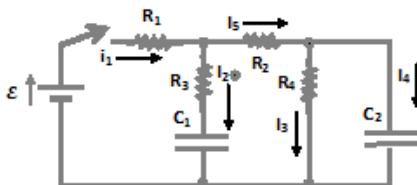7. for  $E = 12, V, C_1 = C_2 = 1 \mu F$  and all  $R$ 's = 1 Ohm find


- currents in  $R_4$  at  $t = 0^+$  and  $t \rightarrow \infty$
- $V_{C_2}$  and  $Q_{C_2}$  at  $t \rightarrow \infty$



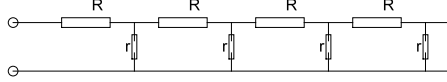8. (\*) for  $R = r = 1 \Omega$  find  $R_{eq}$  for an infinite chain



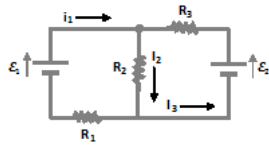9. (\*) Let  $E_1 = E_2 = 1 V$ ,  $R_1 = R_3 = 3 \Omega$  and  $R_2 = 1 \Omega$ ; find the current in resistor  $R_1$ .



10. A  $4 \mu F$  capacitor is discharged through a  $4 k\Omega$  resistor.

- How long does it take for the capacitor to lose half of its initial charge?
- how long does it take for the capacitor to lose half of its initial energy?