

Carry-Select Adder

ECE 658 VLSI-I

Prof: Durgamadhab Misra


Yuvraj Patel || yp239@njit.edu

Vineel Varma || sp2725@njit.edu

Introduction

Design a 32-bit carry-select adder as shown in the figure utilizing the n-well 0.18 μm CMOS (SUBM) process ($\lambda = 0.1 \mu\text{m}$) as described in course. Use your own design approach to satisfy the requirements for the chip, which include:

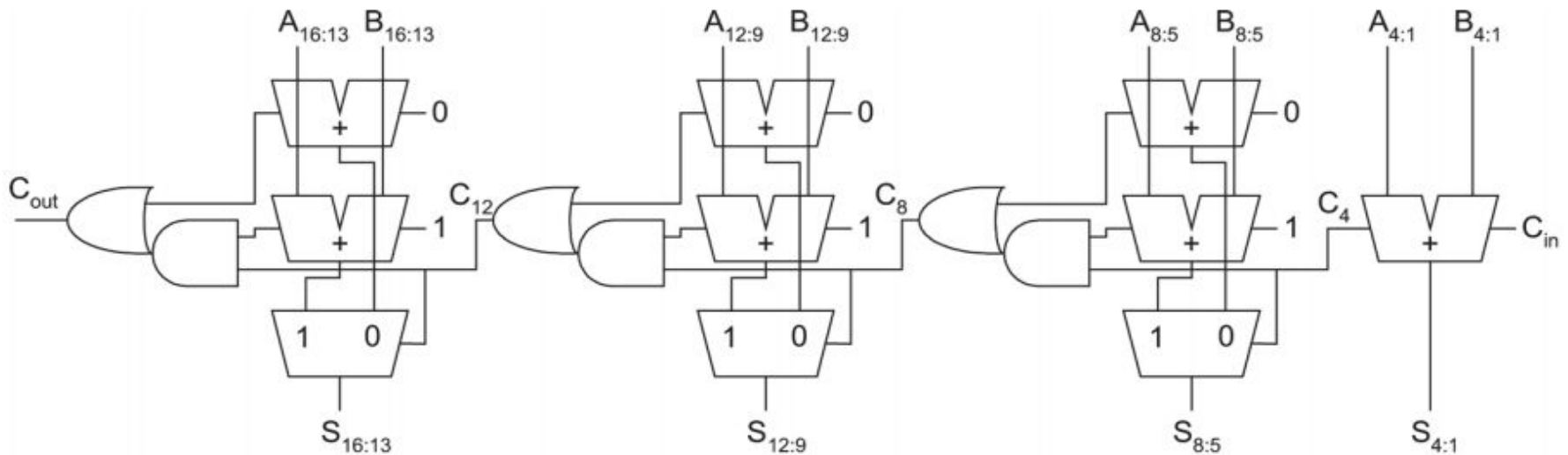- Speed: Data output rate: preferably 900 MHz if possible but definitely not less than 850MHz.
- Logic Reliability: Good Noise Margin
- Less than 40 pin-out count



Design

Advantages of Carry-Select Adder

Performance is better.

Disadvantages

Area is increased because of the extra full adders.

Design Challenges


Carry-Select Adder Design and Challenges

- Due to limitation in input pins on the pad, we had to design Serial In Parallel Out(SIPO).
- Delay in carry propagation. We reduced delay by keeping buffers at carry out of the adders.

Design Challenges

SIPO Design and Challenges

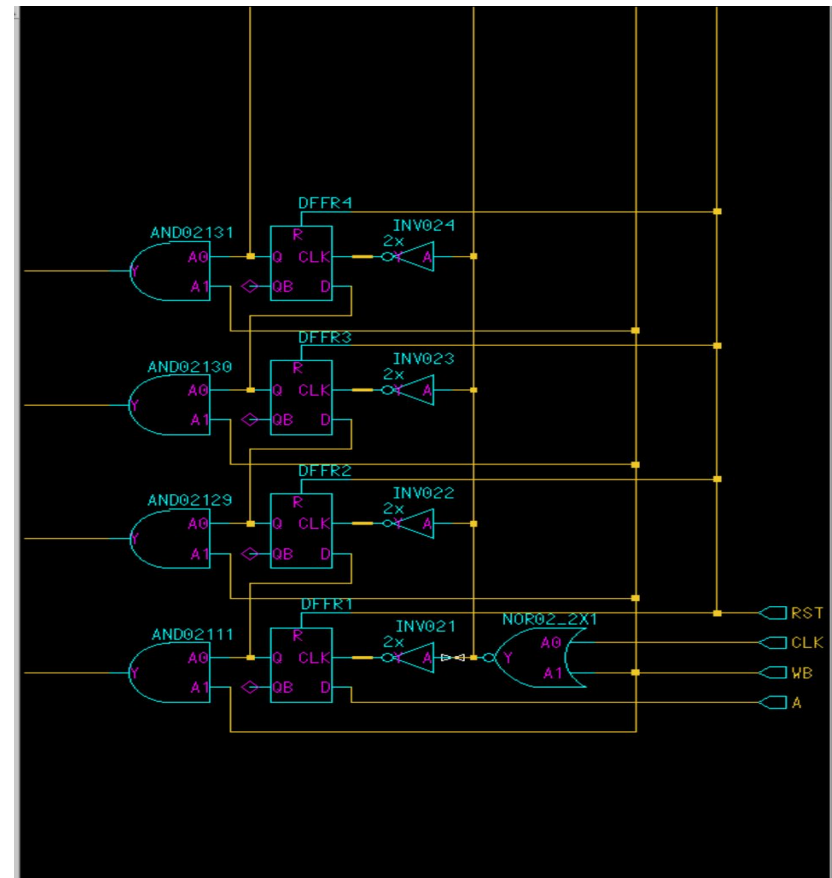
- The output of the NOR gate has a load of 32 flip flops, because of the the clk signal was degraded.
- Buffers were added at the output of the NOR gate, which solved the issue of degraded signal.
- HSpice simulation of the 32 bit SIPO was a challenge due to big waveform file



Design Challenges


Carry-Select adder design

Four-bit adder

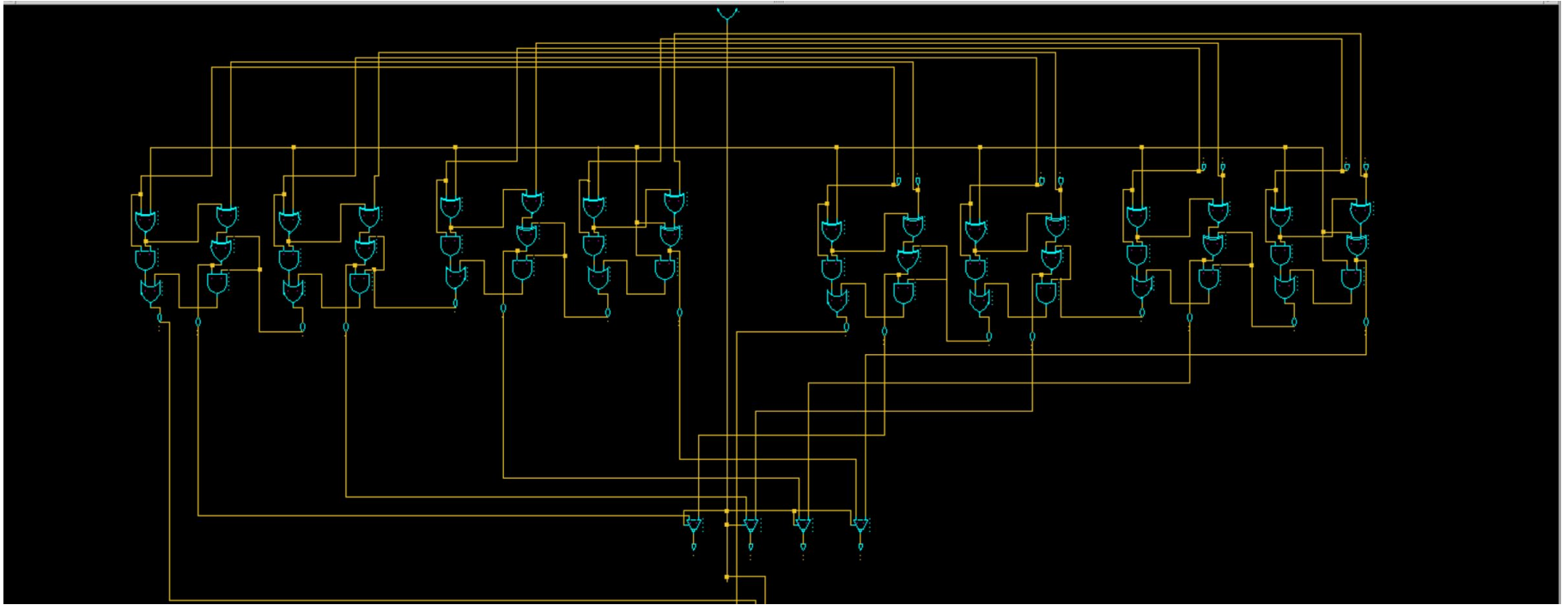


Design Challenges

32 bit Carry-Select adder design

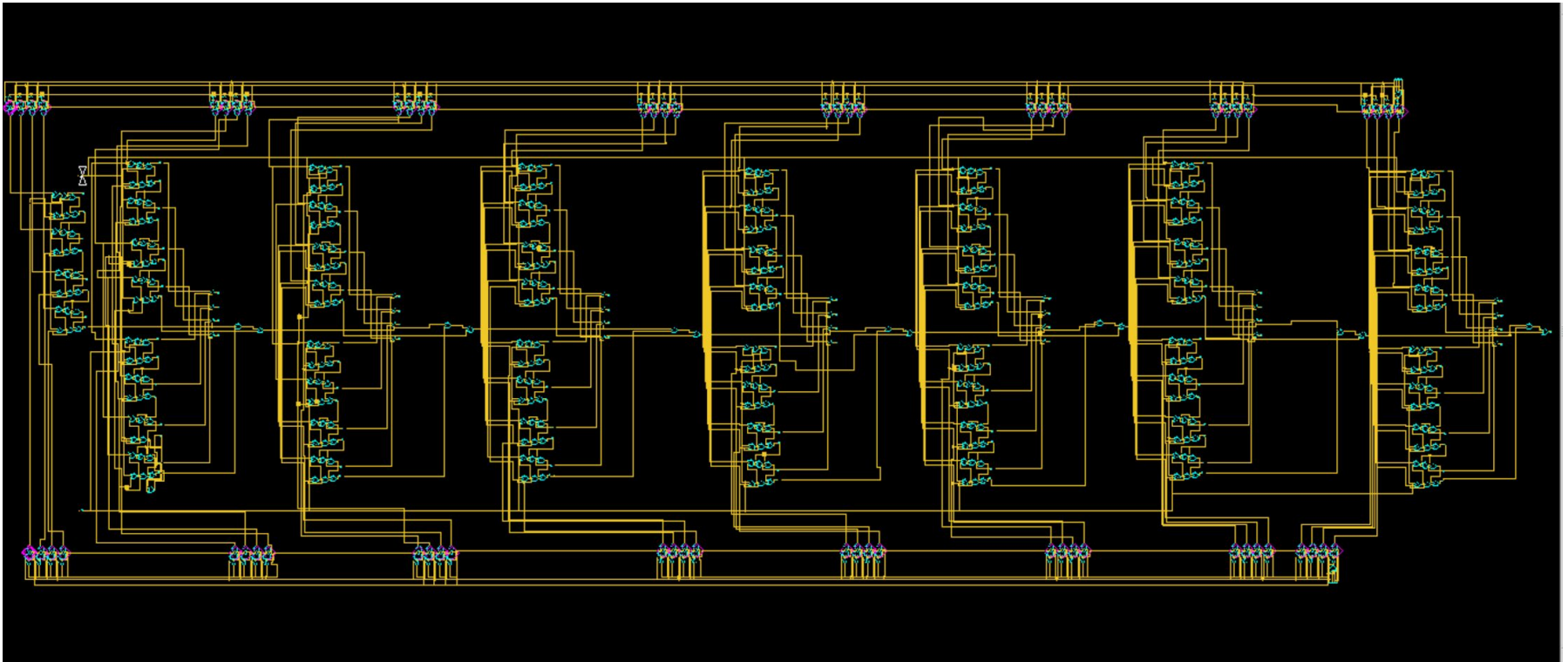

Design Challenges

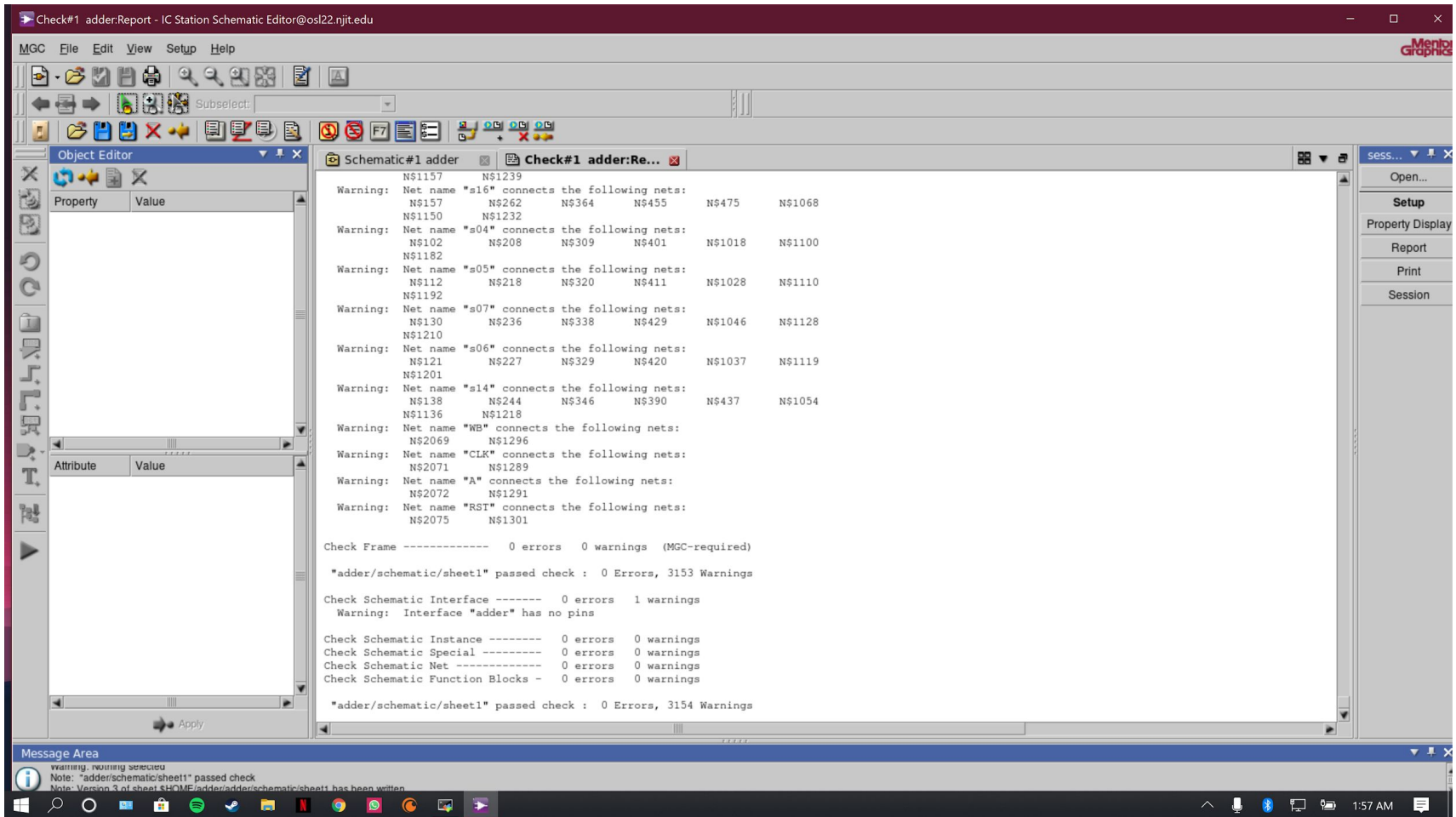

HSpice simulation


32-bit SIPO working



HSpice simulation

Clock delay

 
- Pex extracted gates components were used for simulation.
- Therefore, the layout capacitance were included.
- The clock delay can be reduced further



HSpice simulation

Carry Selecting Adder working(8_bits)

A=00001111 B=11111111 SUM=011100001

 

Applications

Image processing In image processing with interpolation, an output of the gamma circuit and the input data are input to an adder circuit so as to obtain the added and averaged values at a predetermined ratio.

Signal processing Addition is by far the most fundamental arithmetic operation. It has been ranked the most extensively used operation among a set of real-time digital signal processing benchmarks from application specific DSP to general purpose processors.

Arithmetic logic units Carry select adder is used in arithmetic logic units to perform addition and multiplication in a less amount of time.

Advanced microprocessor design In microprocessor design, the adder is used for the conversion mechanism in calculating the physical address using the offset address and segment address.

High speed multiplications In multiplier, each bit of the Product P is obtained by a summation of bits $A_i B_j$ using an array of single bit adders. The bits $A_i B_j$ are formed using AND gates.

Further work

- Layout still needed to be done.
- Further optimisation in reduction of the clock delay for the SIPO is possible
- Optimisation for layout area still needs to be done.

References

A.RAMESH, and B. Siva Nageswara Rao. *EFFICIENT AND ENHANCED CARRY SELECT ADDER FOR MULTIPURPOSE APPLICATIONS*.

www.ijser.org/researchpaper/EFFICIENT-AND-ENHANCED-CARRY-SELECT-ADDER-FOR-MULTIPURPOSE-APPLICATIONS.pdf.

Weste, Neil H.E. CMOS VLSI design:a circuit and system perspective / Neil H.E. Weste, David Harris.--3rd ed.

Thank you!!

Questions are welcomed!